



# Semiconductor Diode


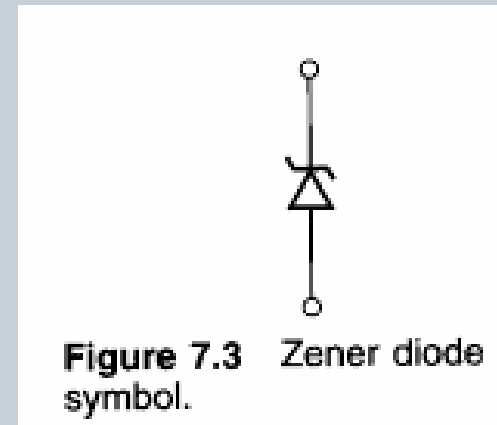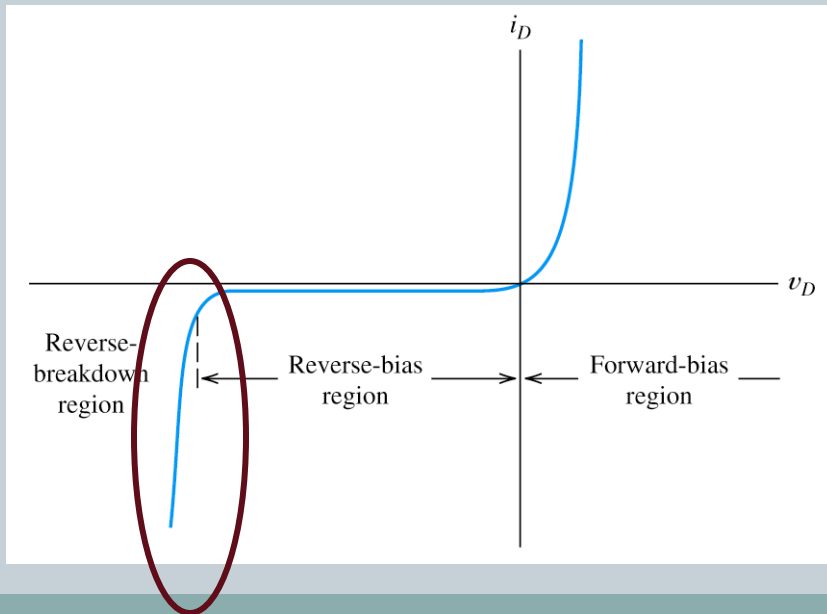
# The Zener Diode

2



- \* *Zener diode* is designed for operation in the reverse-breakdown region.
- \* The *breakdown voltage* is controlled by the doping level ( $-1.8\text{ V}$  to  $-200\text{ V}$ ).
- \* The major application of Zener diode is to provide an output reference that is stable despite changes in input voltage – power supplies, voltmeter,...



# Zener Diode

3

- \* Sometimes, a circuit that produces constant output voltage while operating from a variable supply voltage is needed. Such circuits are called *voltage regulator*.
- \* The Zener diode has a breakdown voltage equal to the desired output voltage.
- \* The resistor limits the diode current to a safe

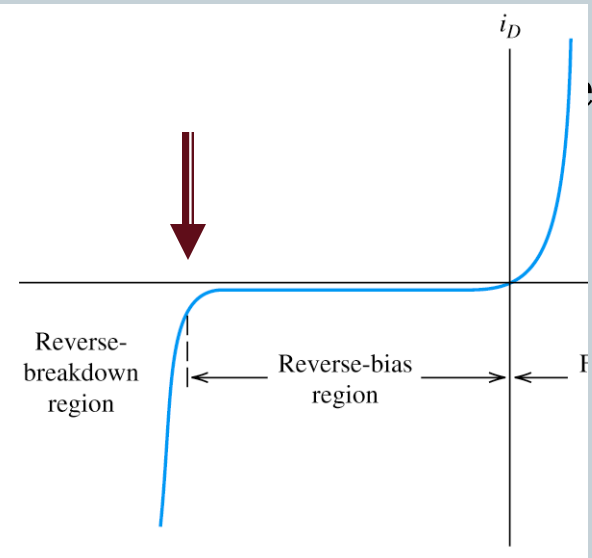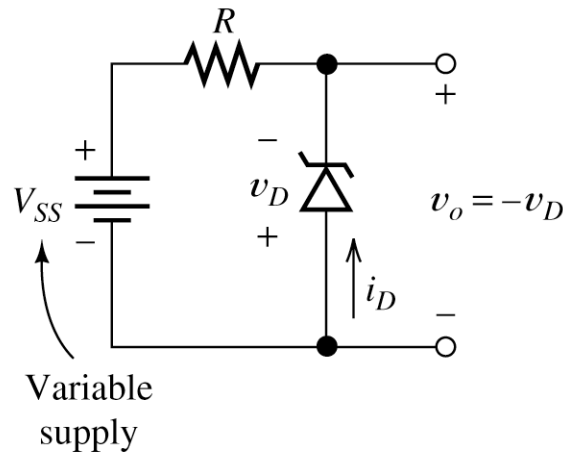


**Figure 10.9** A simple regulator circuit that provides a nearly constant output voltage  $v_o$  from a variable supply voltage.

## Example Zener-Diode Voltage-Regulator Circuits

Given : the Zener diode  $I - V$  curve,  $R = 1k\Omega$

Find : the output voltage for  $V_{SS} = 15V$  and

$$V_{SS} = 20V$$

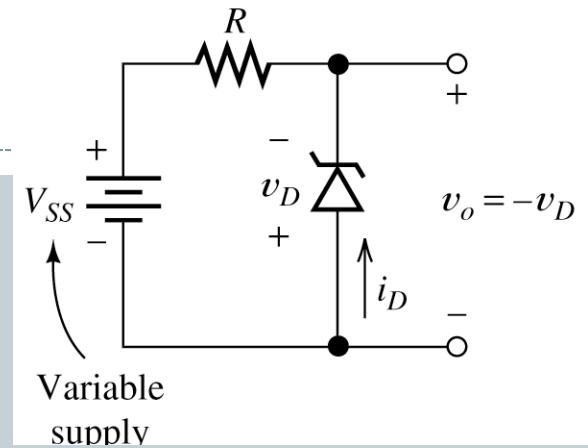

KVL gives the load line :

$$V_{SS} + Ri_D + v_D = 0$$

From the  $Q$  - point we have :


$$v_o = 10.0V \text{ for } V_{SS} = 15V$$

$$v_o = 10.5V \text{ for } V_{SS} = 20V$$

5V change in input

$\Rightarrow$  0.5V change in  $v_o$


Actual Zener diode performs much better!

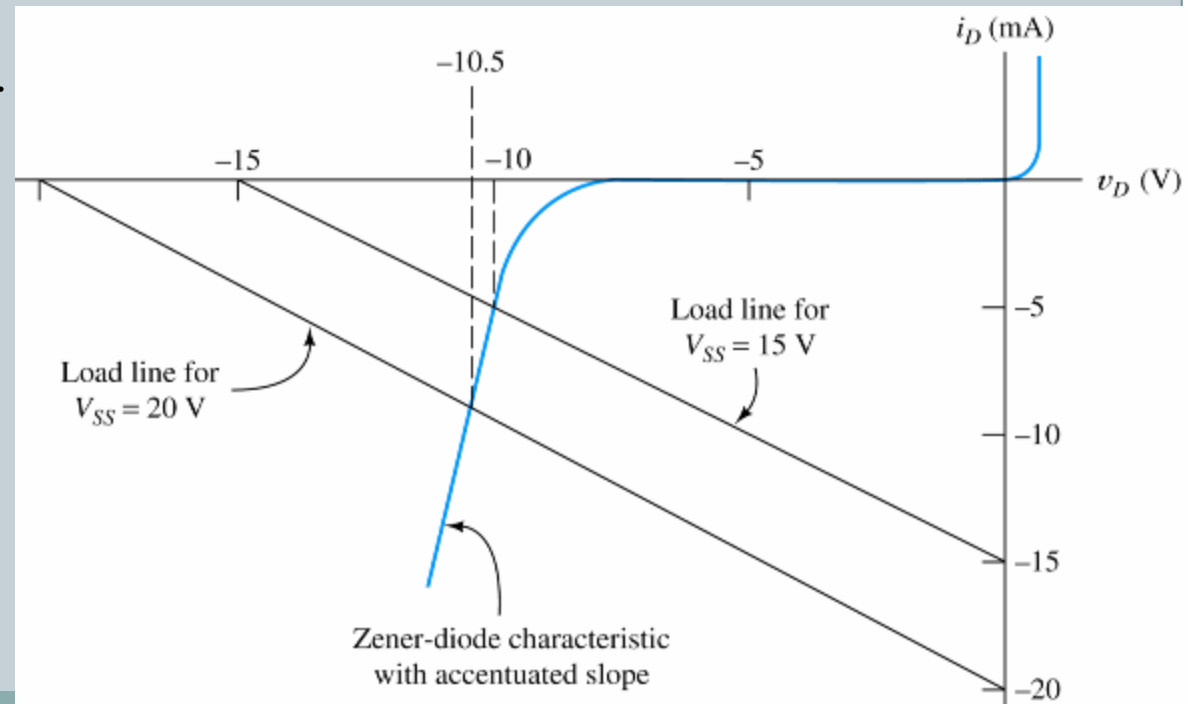


# Load-Line Analysis of Complex Circuits

\* Use the Thevenin Equivalent

5

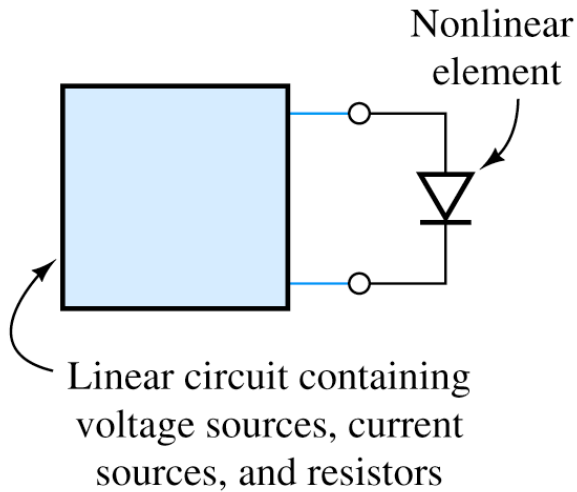

(a) Original circuit

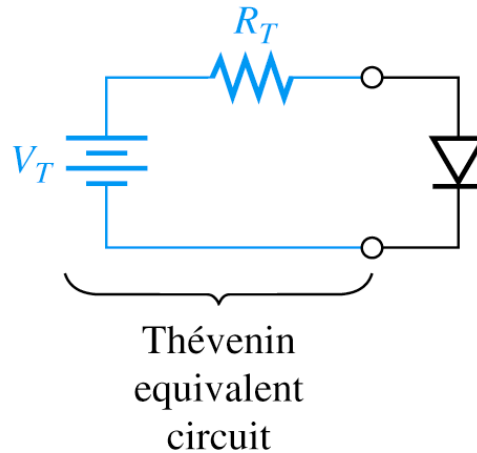

(b) Simplified circuit

**Figure 10.11** Analysis of a circuit containing a single nonlinear element can be accomplished by load-line analysis of a simplified circuit.

## Example – Zener-Diode Voltage-Regulator with a Load

Given : Zener diode  $I - V$  curve,  $V_{SS} = 24V$ ,  $R = 1.2k\Omega$ ,  $R_L = 6k\Omega$

Find : the load voltage  $v_L$  and source currents  $I_S$

Applying Thevenin Equivalent  $\Rightarrow V_T = V_{SS} \frac{R_L}{R + R_L} = 20V$ ,  $R_T = \frac{R R_L}{R + R_L} = 1k\Omega$

$$\Rightarrow V_T + R_T i_D + v_D = 0$$

$$\Rightarrow v_L = -v_D = 10.0V$$

$$I_S = (V_{SS} - v_L) / R = 11.67 mA$$

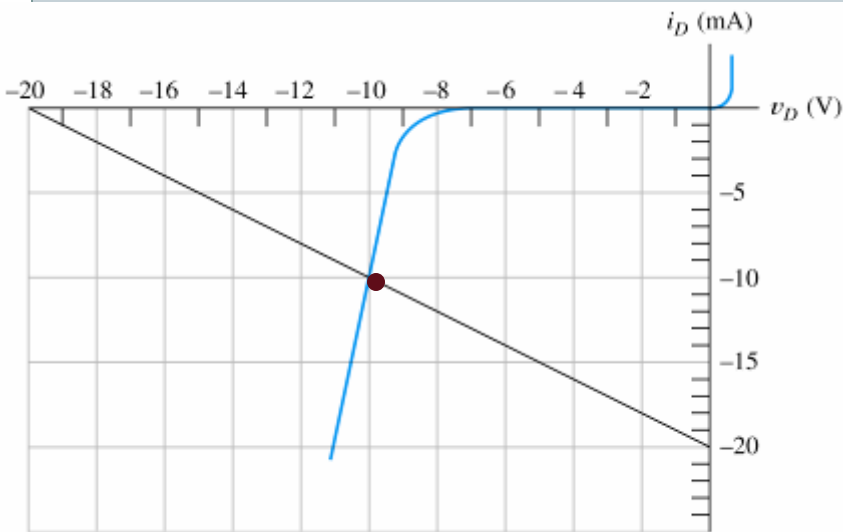


Figure 10.13 Zener-diode characteristic for Example 10.4 and Exercise 10.4.

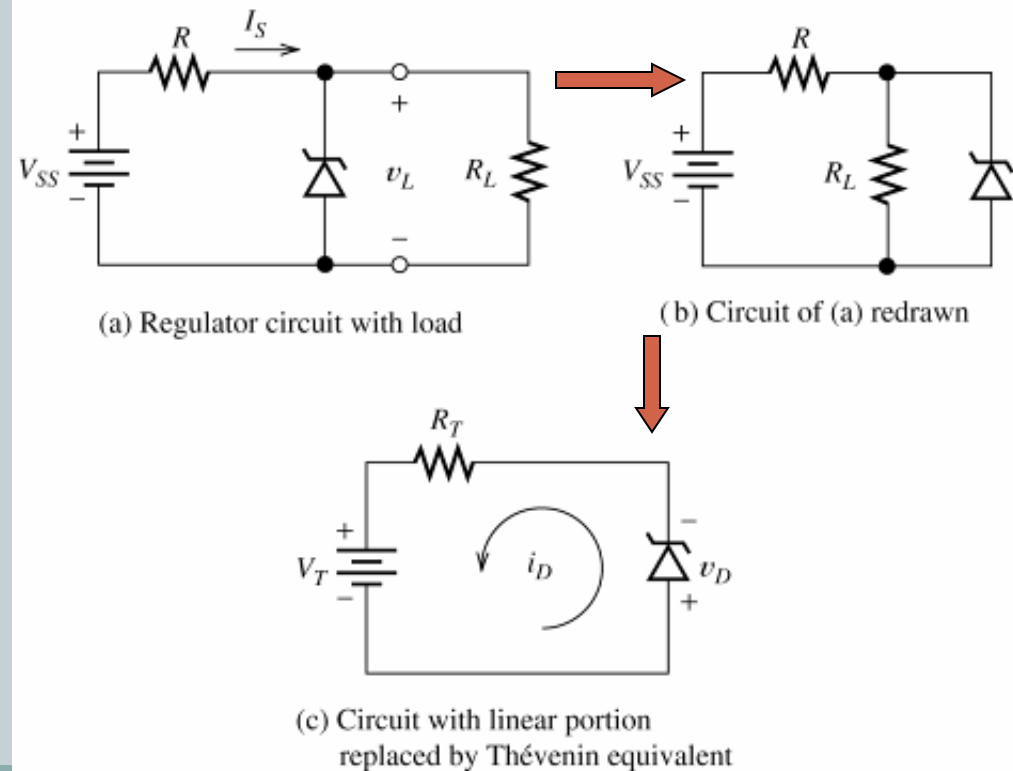
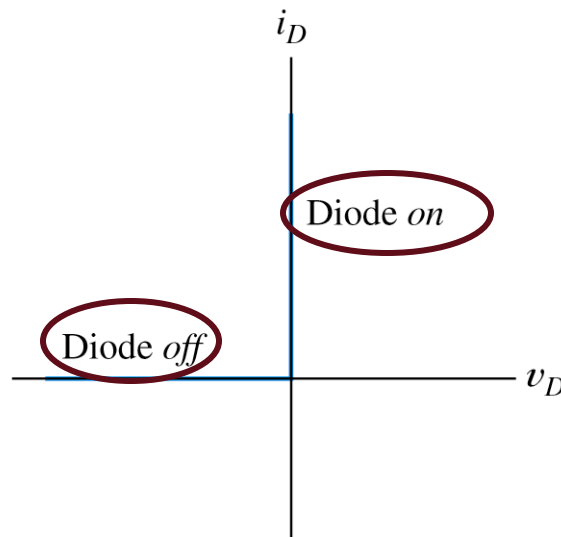


Figure 10.12 See Example 10.4.

## ***Ideal-Diode Model***

- \* Graphical load-line analysis is too cumbersome for complex circuits,
- \* We may apply “*Ideal-Diode Model*” to simplify the analysis:
  - (1) in forward direction: *short-circuit assumption*, zero voltage drop;
  - (2) in reverse direction: *open-circuit assumption*.
- \* The ideal-diode model can be used when the forward voltage drop and reverse currents are negligible.

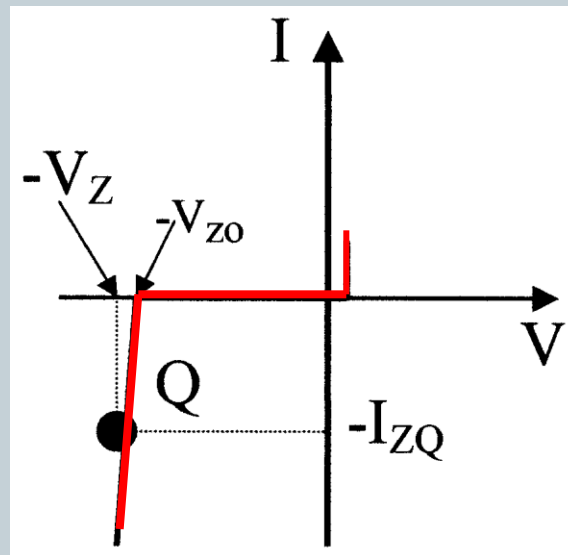


**Figure 10.15** Ideal-diode volt-ampere characteristic.

# Zener Diode



- The linear approximation to the I-V characteristic of a zener diode in the reverse bias and breakdown regions is as follows.





# Zener Diode



- The slope of the line at Q is  $1/r_Z$
- $r_Z$  is called the incremental resistance of the zener diode
- This is exaggerated for clarity in the figure. In practice  $r_Z$  is small (a few ohms) and the breakdown voltage is approximately constant irrespective of the reverse current.

# Zener Diode



- Zener breakdown occurs when the electric field in the depletion layer increases to the point where it can break covalent bonds and generate electron-hole pairs.
- Electrons generated in this way are swept by the electric field into the n side.
- Holes generated in this way are swept by the electric field into the p side.

# Zener Current



- These electrons and holes constitute a reverse current through the junction.
- Once the zener effect starts a large number of carriers can be generated with negligible increase in the junction voltage.
- In the breakdown region the reverse current is thus determined by the external circuit, the reverse voltage across the diode remains close to the rated breakdown voltage.

# Zener Diode



- The other breakdown mechanism is avalanche breakdown.
- This occurs when minority carrier in the depletion layer gain sufficient kinetic energy to break covalent bonds in atoms when they collide.

# Zener Diode



- Avalanche breakdown.
- Carriers liberated may have or gain sufficient energy to cause other carriers to be generated.
- This process continues in the fashion of an ‘avalanche’
- Many carriers can be created to support any reverse current determined by the external current.

# Zener Diode



- The device is operated in reverse bias.
- Thus we reverse the sign notation that we normally use for diode voltages and currents, as shown on the next slide

# Zener Diode



- The device is operated in reverse bias.
- Thus we reverse the sign notation that we normally use for diode voltages and currents, as shown on the next slide

# Zener Diode



- The device is operated in reverse bias.
- Thus we reverse the sign notation that we normally use for diode voltages and currents, as shown on the next slide