

Semiconductor Diode




Clipper and Clamper Circuits



Clippers

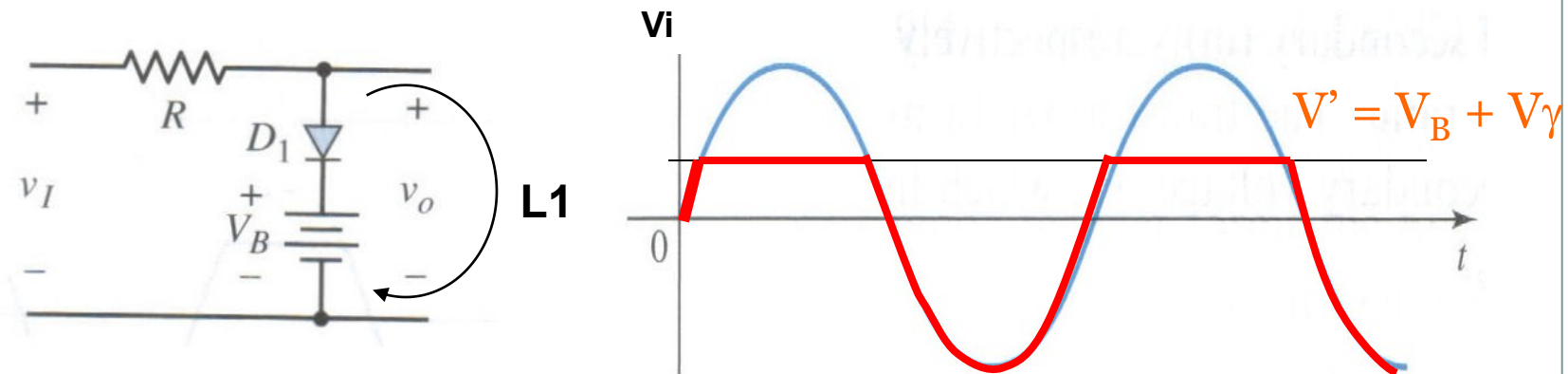- Clipper circuits, also called **limiter circuits**, are used to eliminate portion of a signal that are above or below a specified level – clip value.
- The purpose of the diode is that when it is turn on, it provides the clip value
- Clip value = V' . To find V' , use KVL at L1
- The equation is : $V' - V_B - V_\gamma = 0 \rightarrow V' = V_B + V_\gamma$



➤ Then, set the conditions


➤ If $v_i > V'$, what happens? \rightarrow diode conducts, hence $v_o = V'$

➤ If $v_i < V'$, what happens? \rightarrow diode off, open circuit, no current flow, $v_o = v_i$

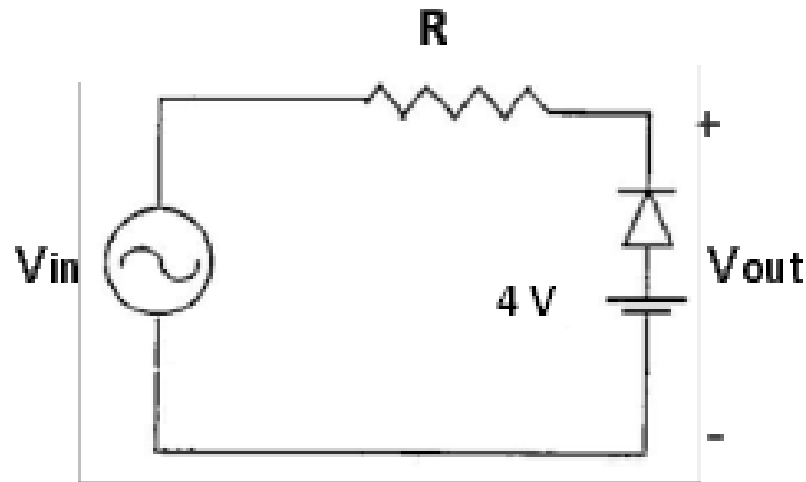EXAMPLE





For the circuit shown below sketch the waveform of the output voltage, V_{out} . The input voltage is a sine wave where $V_{\text{in}} = 10 \sin \omega t$. Assume $V_{\gamma} = 0.7 \text{ V}$



Parallel Based Clippers

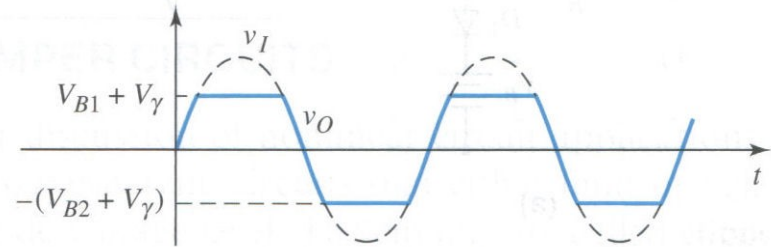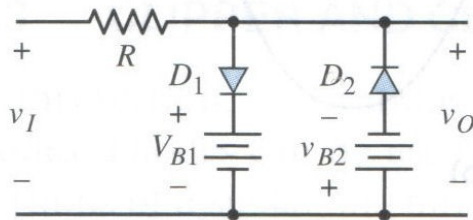- Positive and negative clipping can be performed simultaneously by using a double limiter or a **parallel-based clipper**.




- The parallel-based clipper is designed with two diodes and two voltage sources oriented in opposite directions.
- This circuit is to allow clipping to occur during both cycles; negative and positive


Clipper – Diode in Series

Problem 3.11

Figure P3.11(a) shows the input voltage of the circuit as shown in Figure P3.11(b). Plot the output voltage V_o of these circuits if $V_\gamma = 0.7\text{ V}$

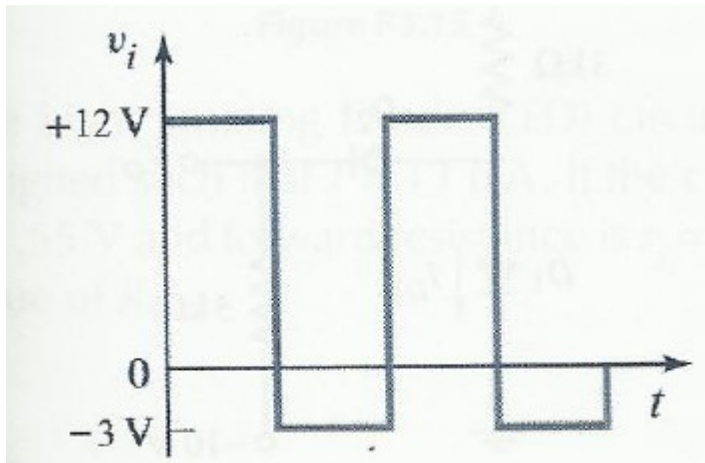

P3.11(a)

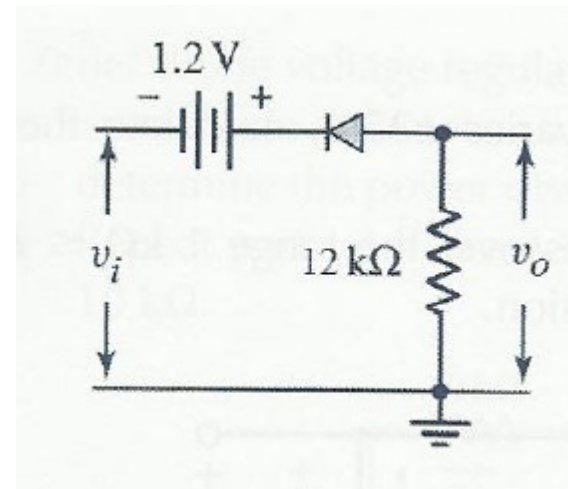

P3.11(b)





Clampers

- Clamping shifts the entire signal voltage by a DC level.

- Consider, the sinusoidal input voltage signal, v_I .
- 1st 90°, the capacitor is charged up to the peak value of V_i which is V_M .
- Then, as V_i moves towards the -ve cycle,
 - the diode is reverse biased.
 - Ideally, capacitor cannot discharge, hence $V_c = V_M$
- By KVL, we get


$$v_O = -v_C + v_I = -V_M + V_M \sin \omega t$$

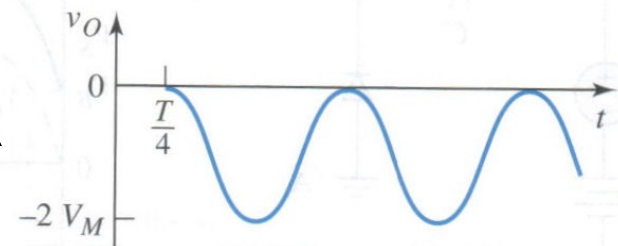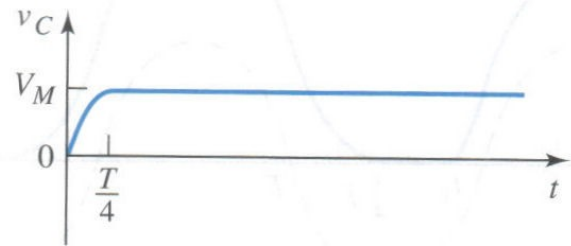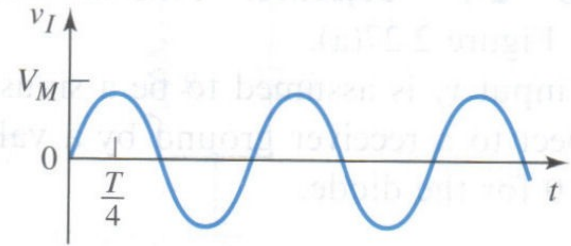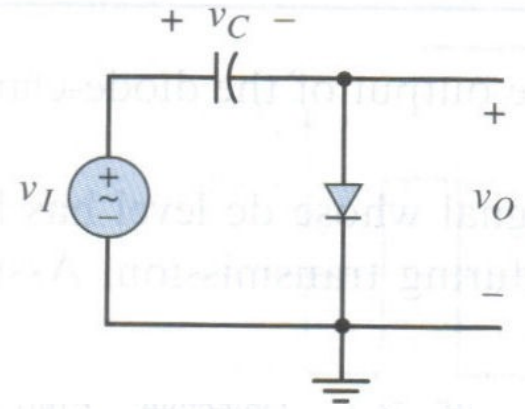NOTE: The input signal is shifted by a dc level; and that the peak-to-peak value is the same



Clampers

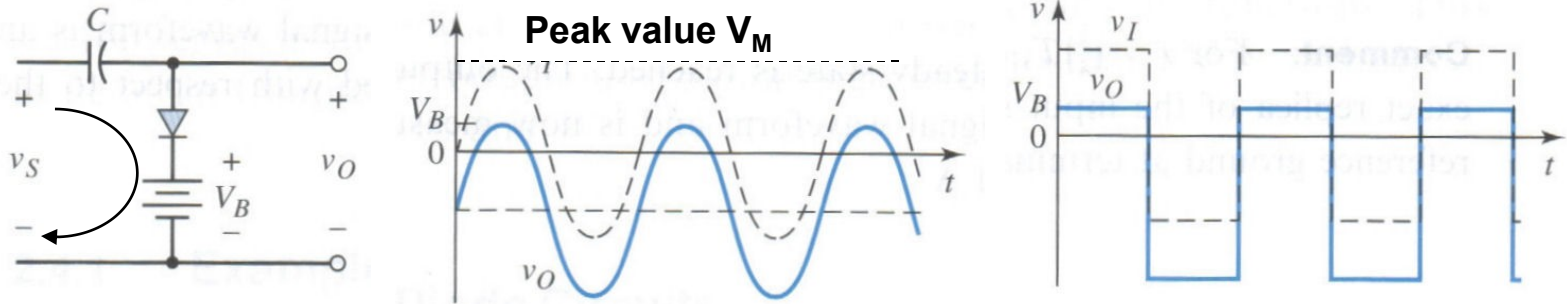- A clamping circuit that includes an independent voltage source V_B .




- **STEP 1:** Knowing what value that the capacitor is charged to. And from the polarity of the diode, we know that it is charged during positive cycle. Using KVL,
 - $V_C + V_B - V_S = 0 \rightarrow V_C = V_M - V_B$
- **STEP 2:** When the diode is reversed biased and V_C is already a constant value
 - $V_O - V_S + V_C = 0 \rightarrow V_O = V_S - V_C.$

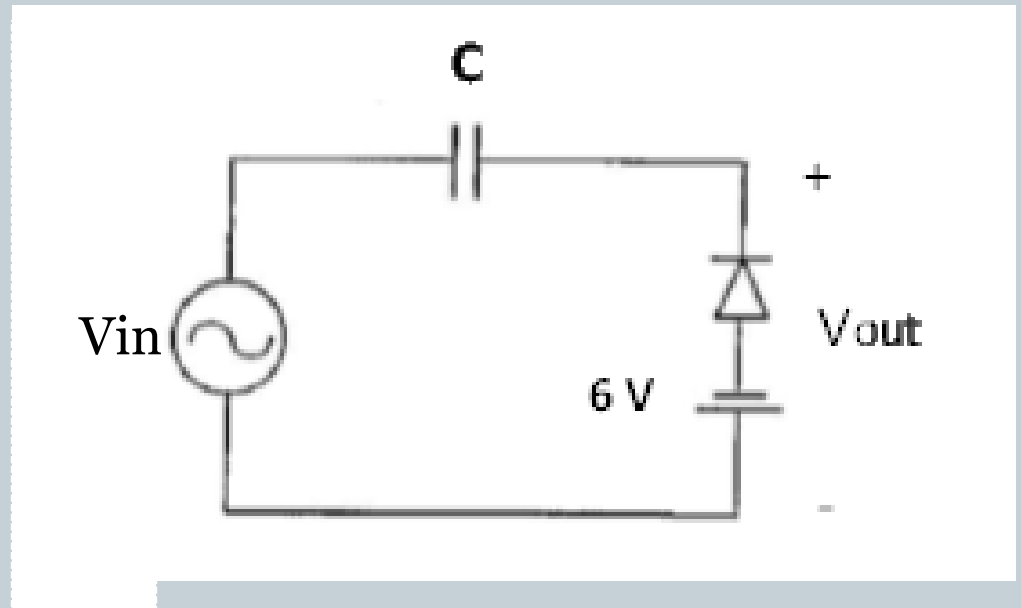
EXAMPLE – clampers with ideal diode



For the circuit shown in figure below, sketch the waveforms of the output voltage, V_{out} . The input voltage is a sine wave where $V_{in} = 20 \sin \omega t$. Assume ideal diodes.



What if the diode is non-ideal?

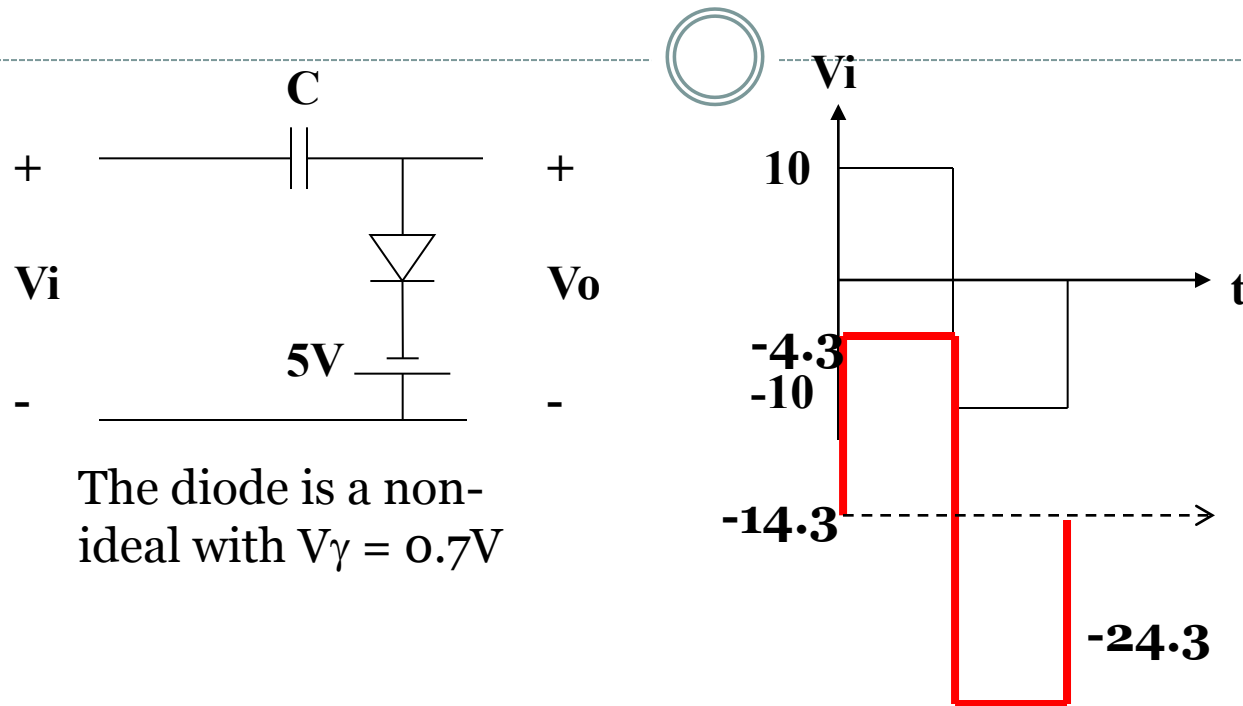


The diode is a non-ideal with $V_\gamma = 0.7V$


- **Step 1:** $V_C + V_\gamma - V_B - V_i = 0 \rightarrow V_C = 10 + 5 - 0.7 = 14.3V$
- **Step 2:** $V_O - V_i + V_C = 0 \rightarrow V_O = V_i - 14.3.$

Diode Clampers

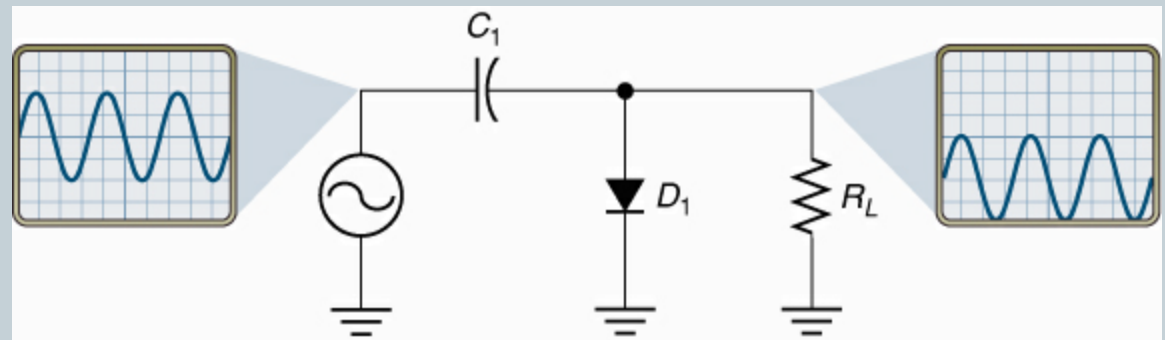A clamper (or dc restorer) sets (or restores) the dc reference of a waveform.



(a) Negative clamper

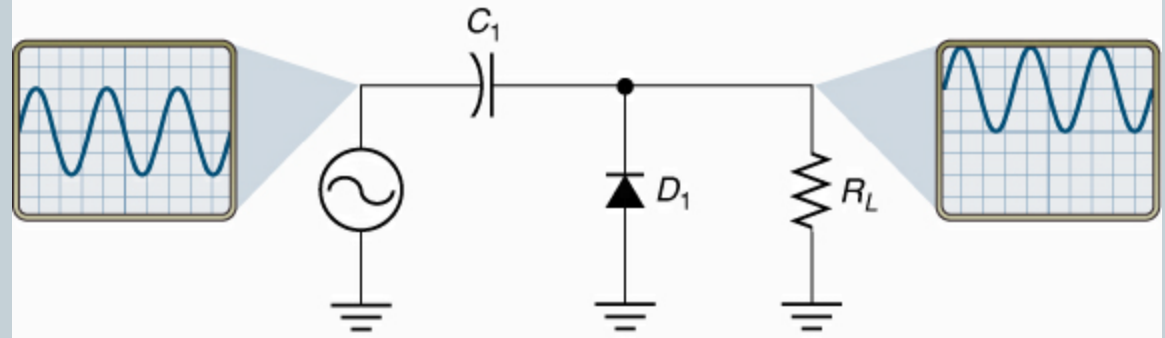


(b) Positive clamper


Clipper Circuit




Clipper circuits have the ability to 'clip' off a portion of the input signal without distorting the remaining part of the alternating waveform.

Single Diode Clipper

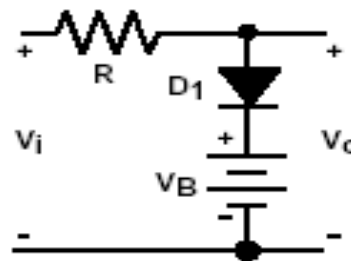


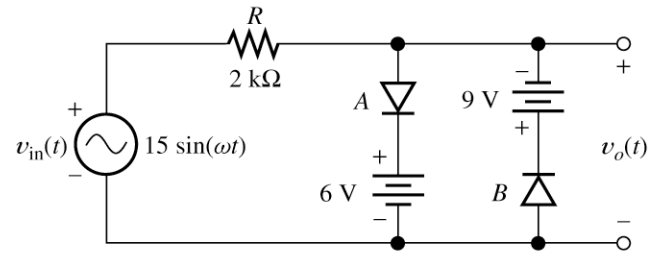

(a) Circuit diagram

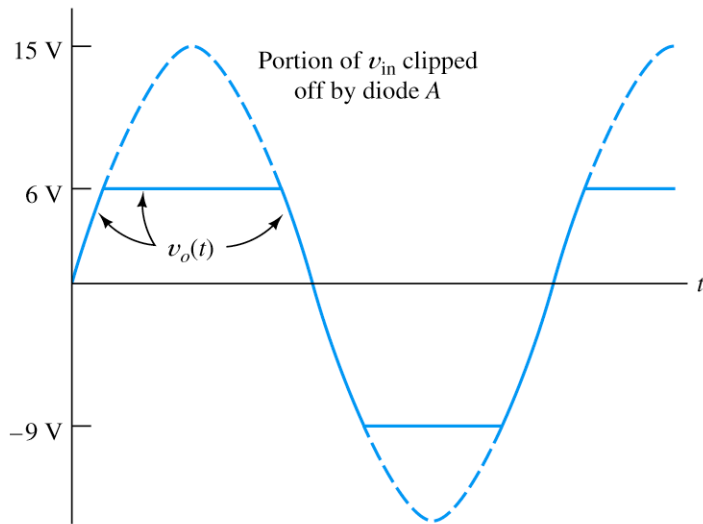

(b) Waveforms

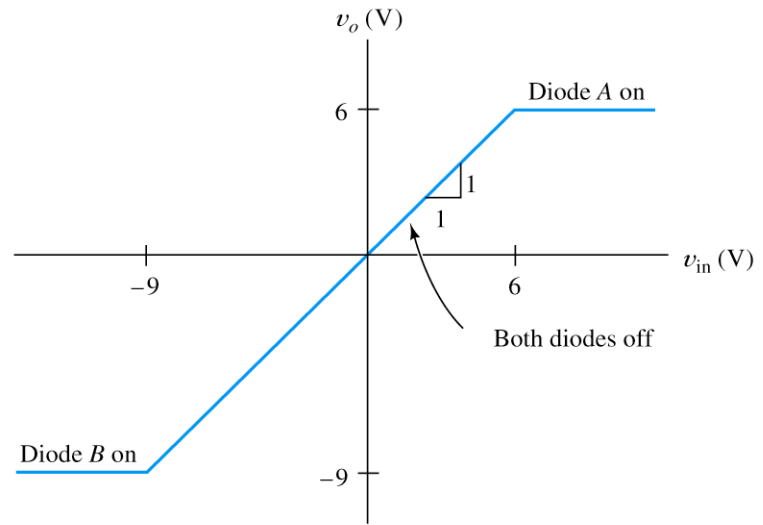

(c) Transfer characteristic

Figure 10.29 Clipper circuit.

Clamper Circuit

Clamper Circuit



The clamping network 'clamp' a signal to different dc level without altering the wave-shape.

The network will have a capacitor, a diode and a resistive element.

The magnitude of R and C must be chosen such that the time constant $t = RC$ is large enough to ensure that the voltage across the capacitor does not discharge significantly during the interval the diode is non-conducting


Used in TV receivers as a DC restorer

Diode :- Clamper

POSITIVE CLAMPER

The circuit for a positive clamper is shown in the figure. During the negative half cycle of the input signal, the diode conducts and acts like a short circuit. The output voltage $V_o \Rightarrow 0$ volts. The capacitor is charged to the peak value of input voltage V_m and it behaves like a battery. During the positive half of the input signal, the diode does not conduct and acts as an open circuit. Hence the output voltage $V_o \Rightarrow V_m + V_m$. This gives a positively clamped voltage.



Positive Clamper

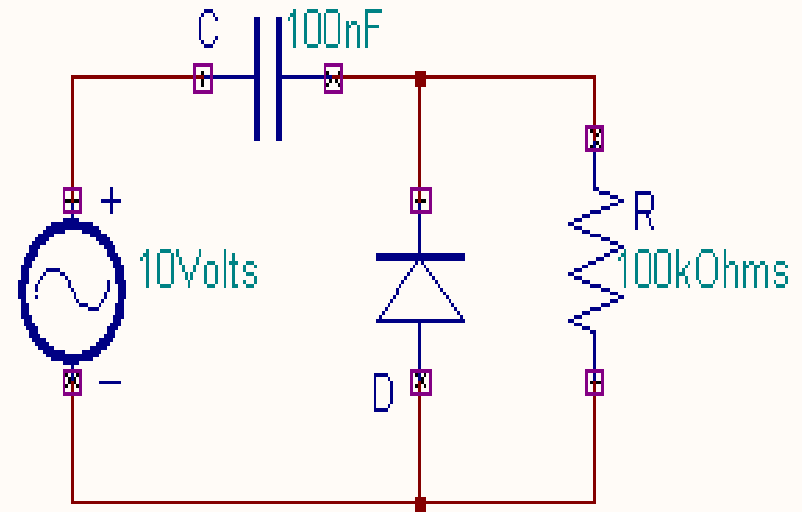

$$V_o \Rightarrow V_m + V_m = 2V_m$$

Diode :- Clamper

Positive Clamper

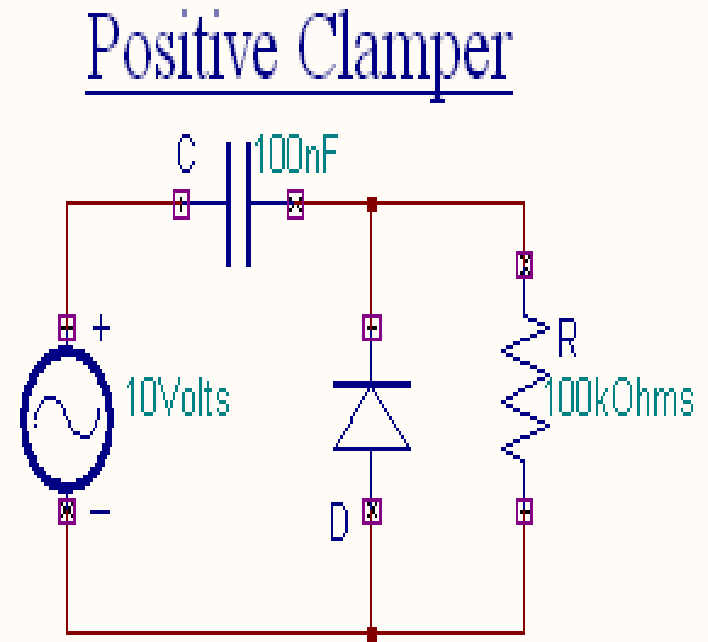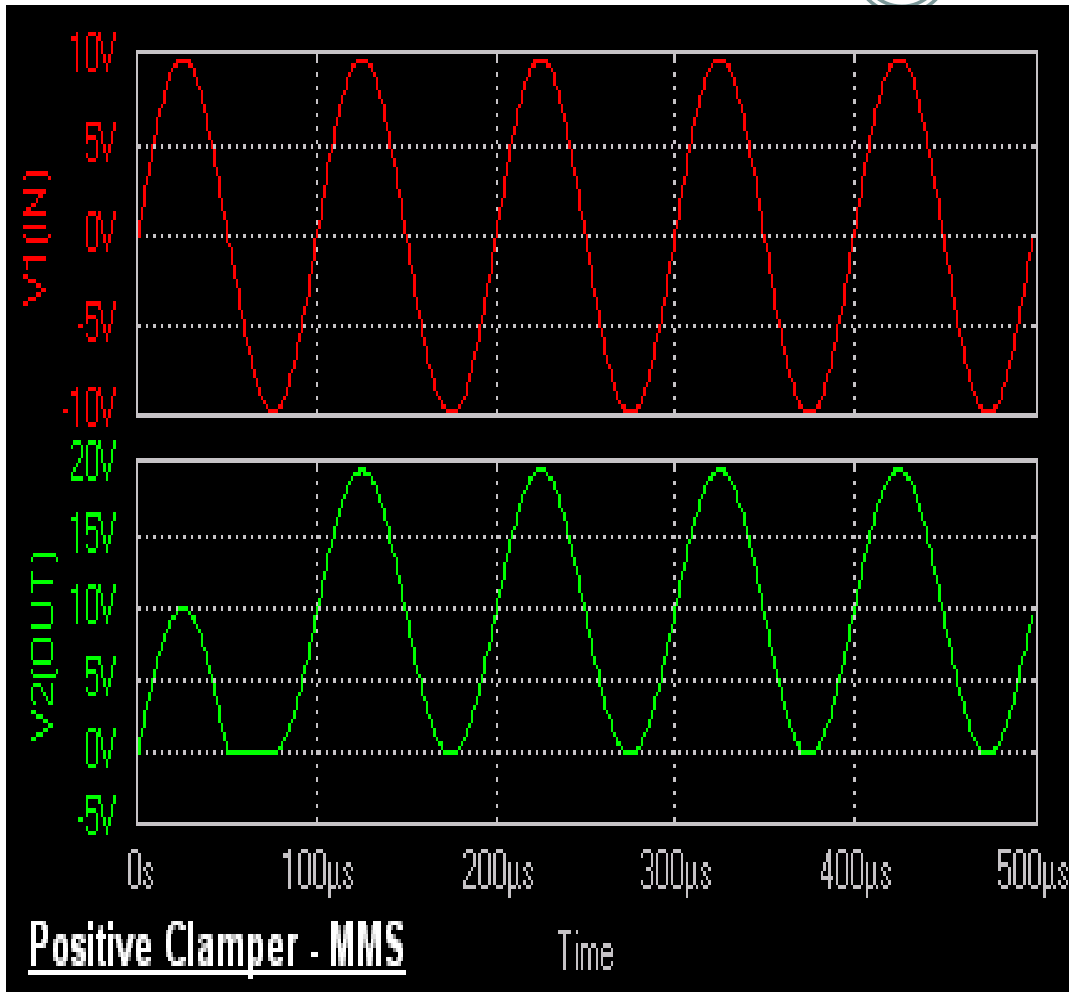


Diode :- Clamper

Negative Clamper

During the positive half cycle the diode conducts and acts like a short circuit. The capacitor charges to peak value of input voltage V_m . During this interval the output V_o which is taken across the short circuit will be zero. During the negative half cycle, the diode is open. The output voltage can be found by applying KVL.

Negative Clamper

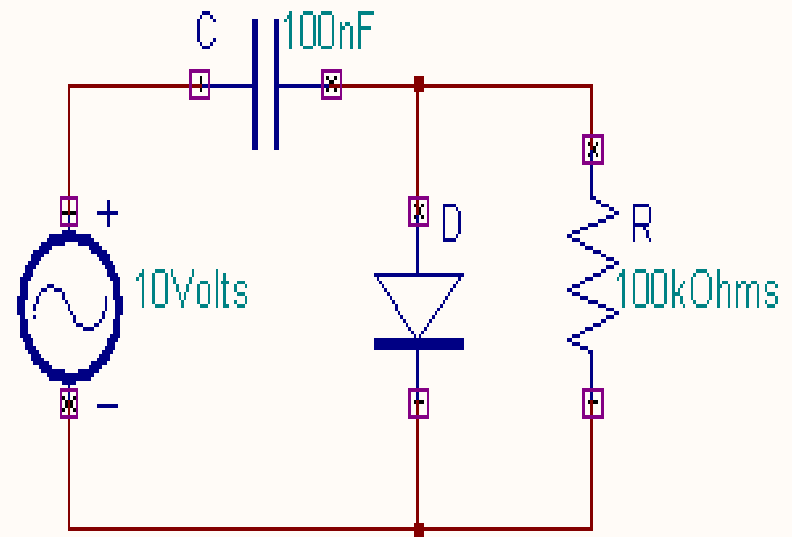


$$-V_m - V_m - V_o = 0$$


$$V_o = -2V_m$$

Diode :- Clamper

Negative Clamper

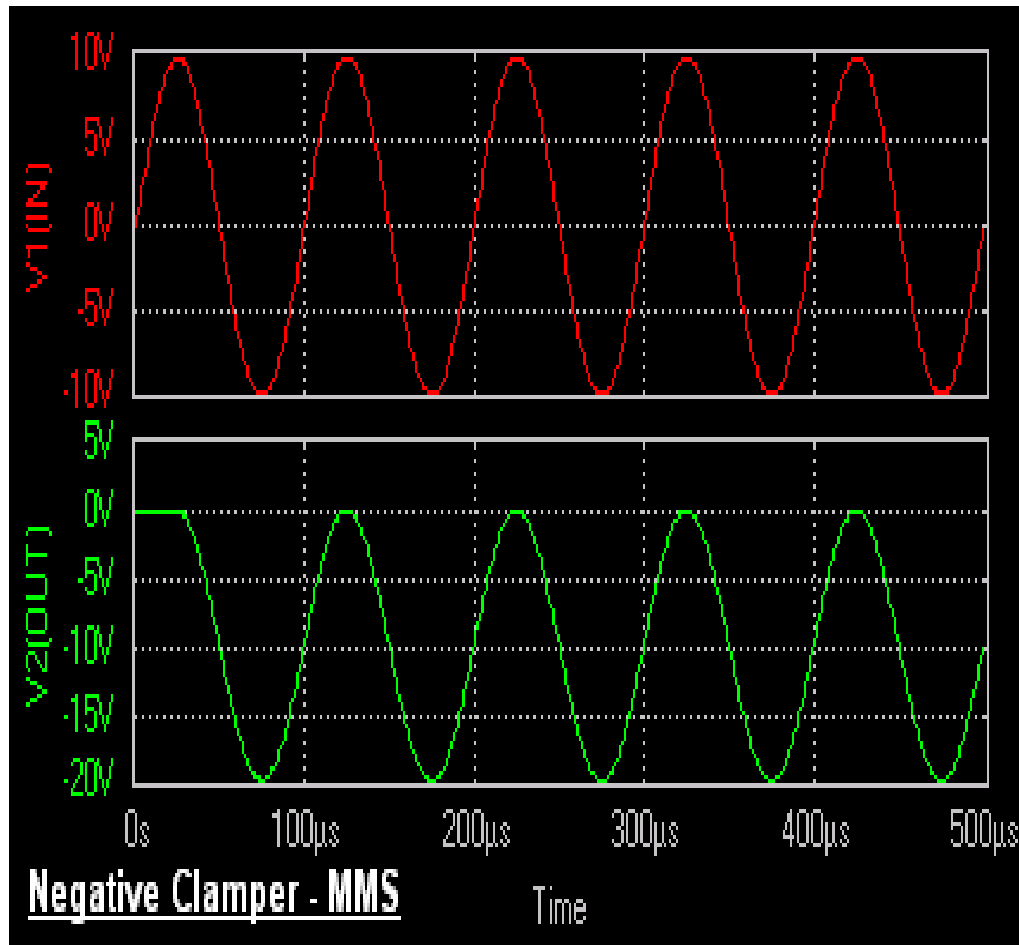


Negative Clamper

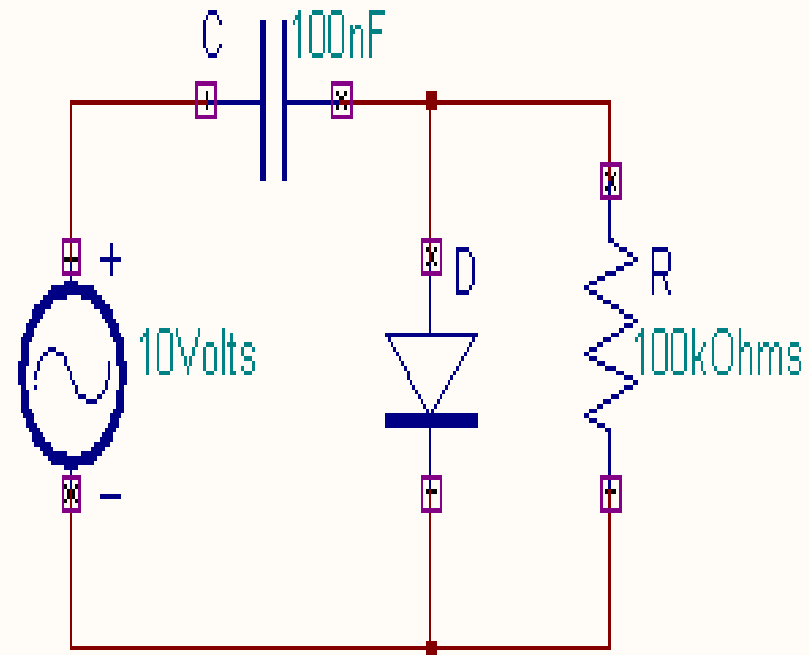


Diode :- Clamper

Biased Clamper

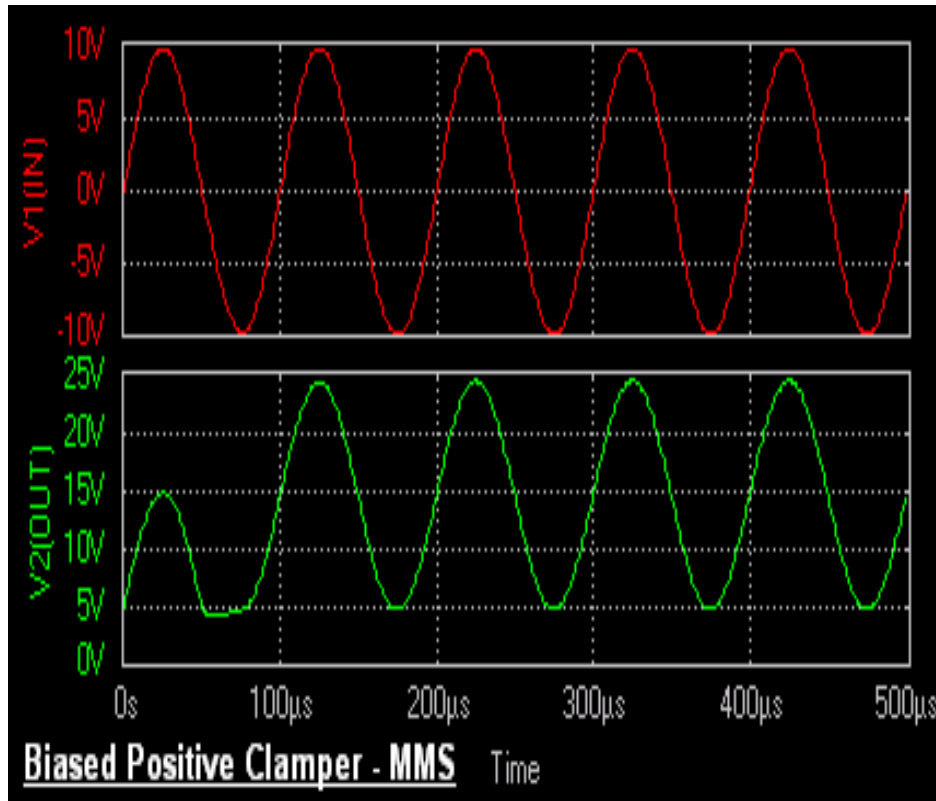

Biased Positive Clamper

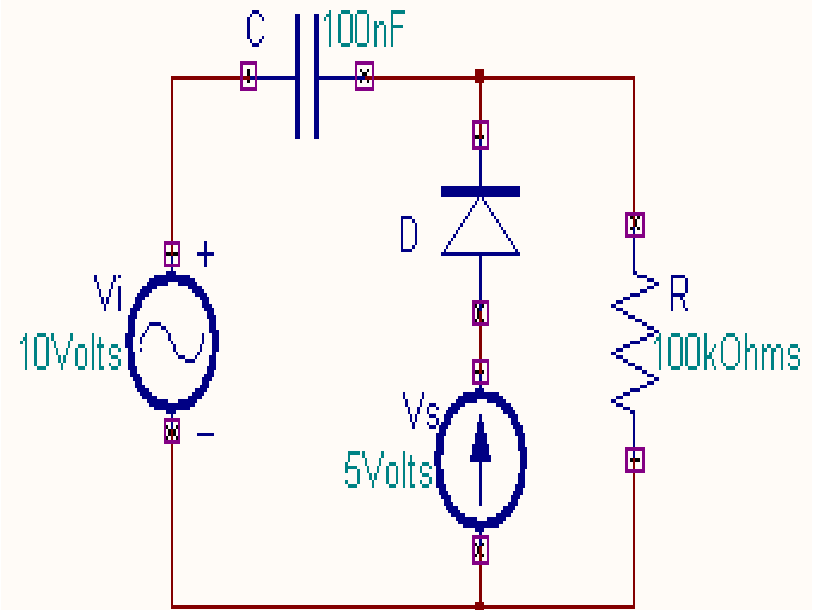

Diode :- Clamper

The circuit of a **positively biased clamper** is shown in the figure. During the negative half cycle of the input signal the diode is forward biased and acts like a short circuit. The capacitor charges to $V_i + V_s$. Applying the KVL to the input side

$$-V_i + V_c - V_s = 0$$

$$V_c = V_s + V_i$$

During the positive half cycle of the input signal, the diode is reverse biased and it acts as an open circuit. Hence V_s has no effect on V_o . Applying KVL around the outside loop.


$$V_i + V_c - V_o = 0$$

$$\therefore V_o = V_i + V_c$$


How Does A Clamp Circuit Work?

• In the positive half cycle C gets charged through D to $10V$ (peak of sine wave + $5V$) with the straight plate of C at a higher potential. D clips the output to a maximum of $-5V$.

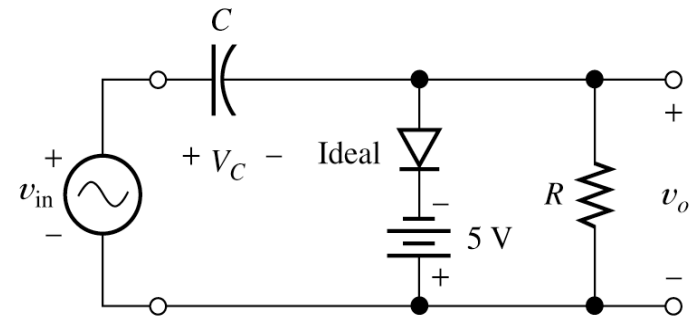• In the negative half cycle D is reverse biased. The output can reach a minimum of $-15V$ ($-V_C +$ negative peak of sine wave).



(a) Circuit diagram

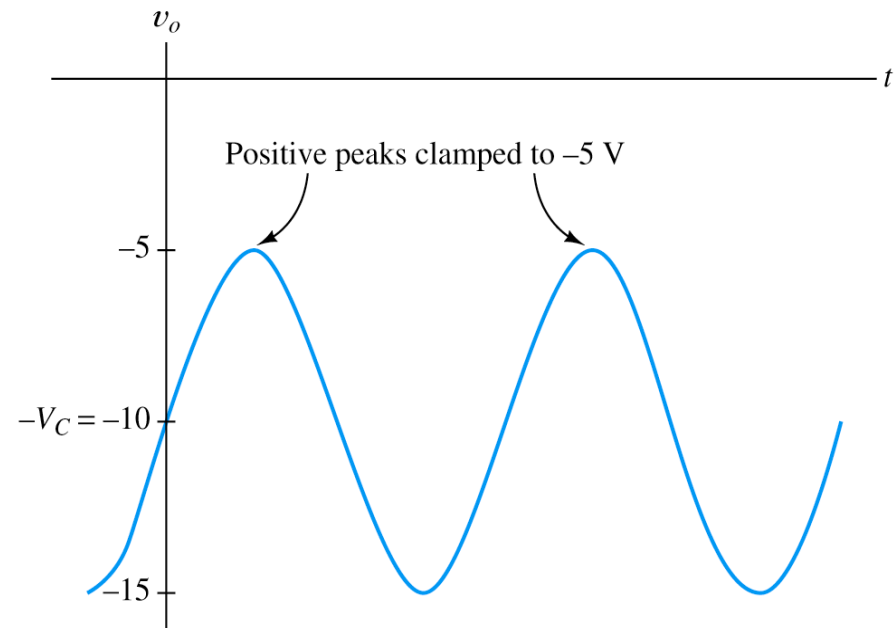


(b) Output waveform for $v_{in} = 5 \sin(\omega t)$

Biased clampers



Biased clampers allow a waveform to be shifted above or below a dc reference other than 0 V.

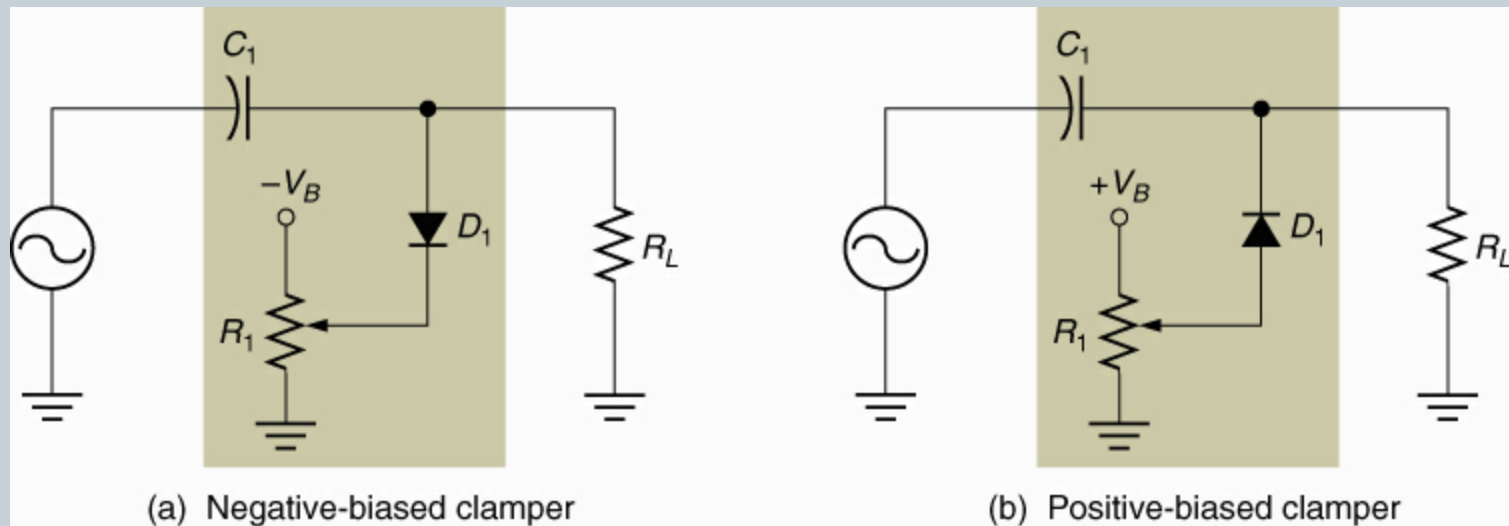
- The dc reference is determined by the biasing voltage (V_B) and the setting of the potentiometer (R_1).




Zener clampers



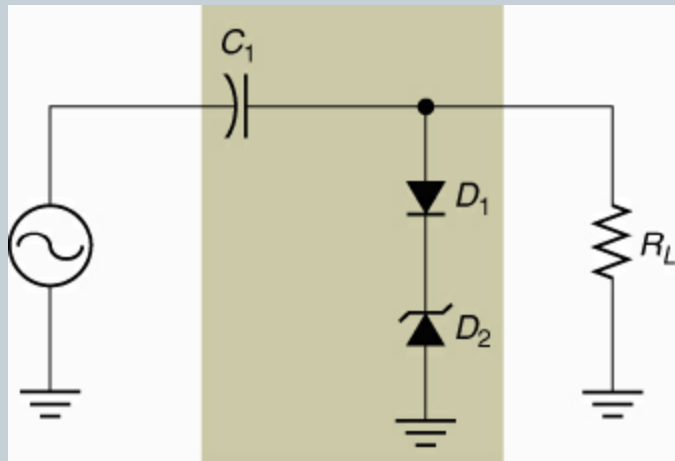The diodes in (a) are in a common-cathode configuration. The diodes in (b) are in a common-anode configuration.



(a) Negative zener clamper

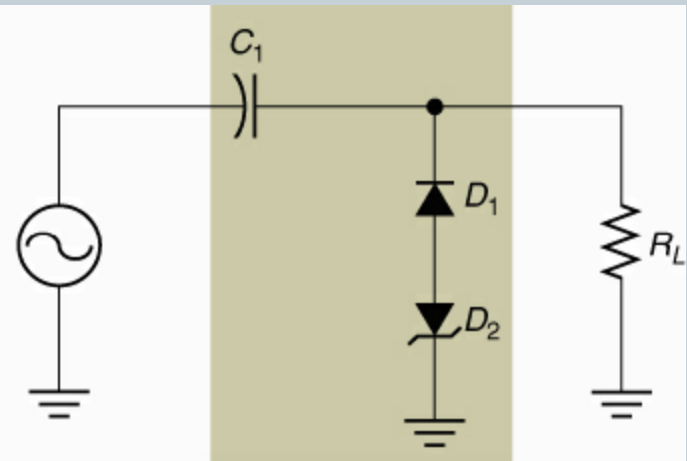

(b) Positive zener clamper



**Thank
You**