




Semiconductor Diode



Applications of Diode




Half-Wave Rectifier

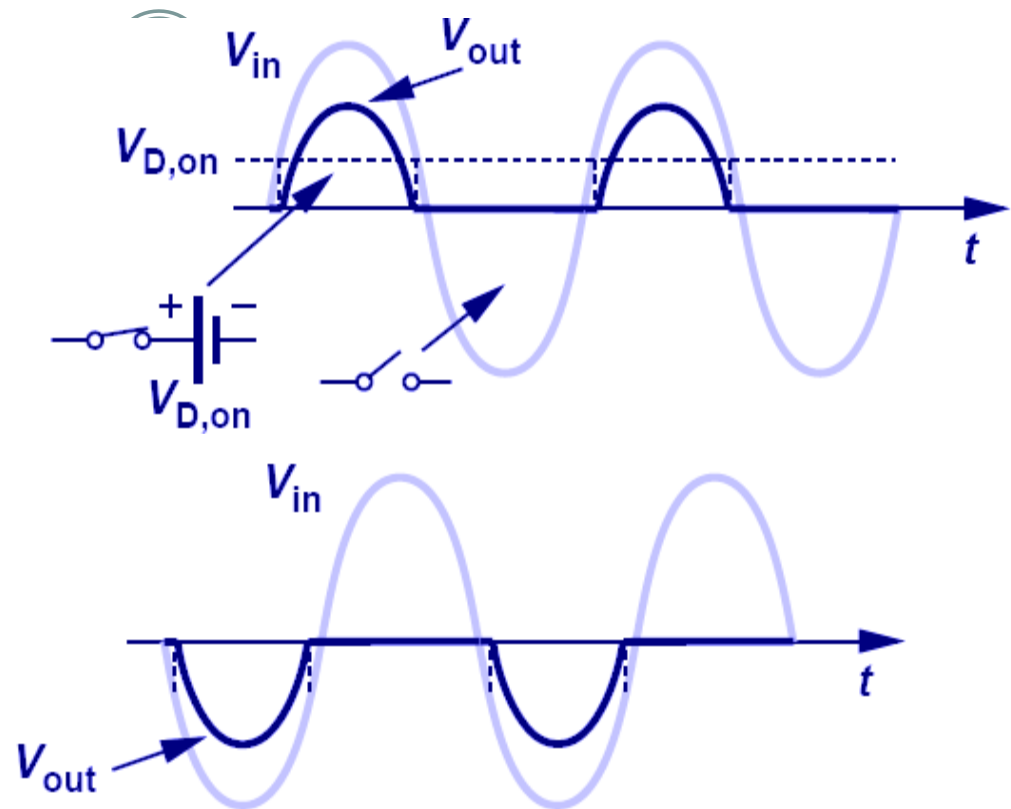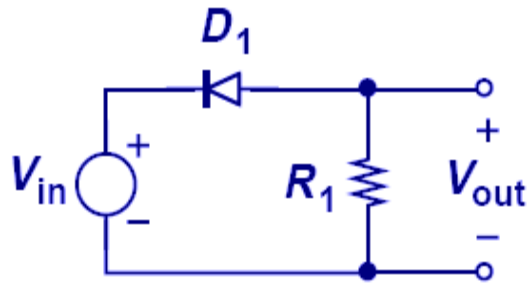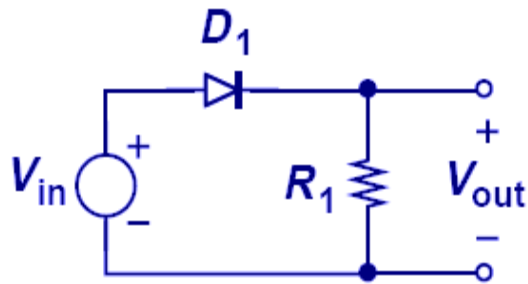


- A very common application of diodes is half-wave rectification, where either the positive or negative half of the input is blocked.
- But, how do we generate a *constant* output?

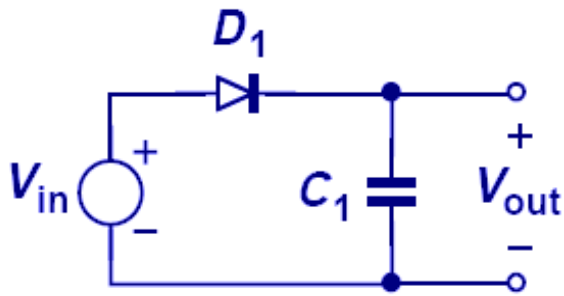Diode-Capacitor Circuit: Constant Voltage Model






(a)

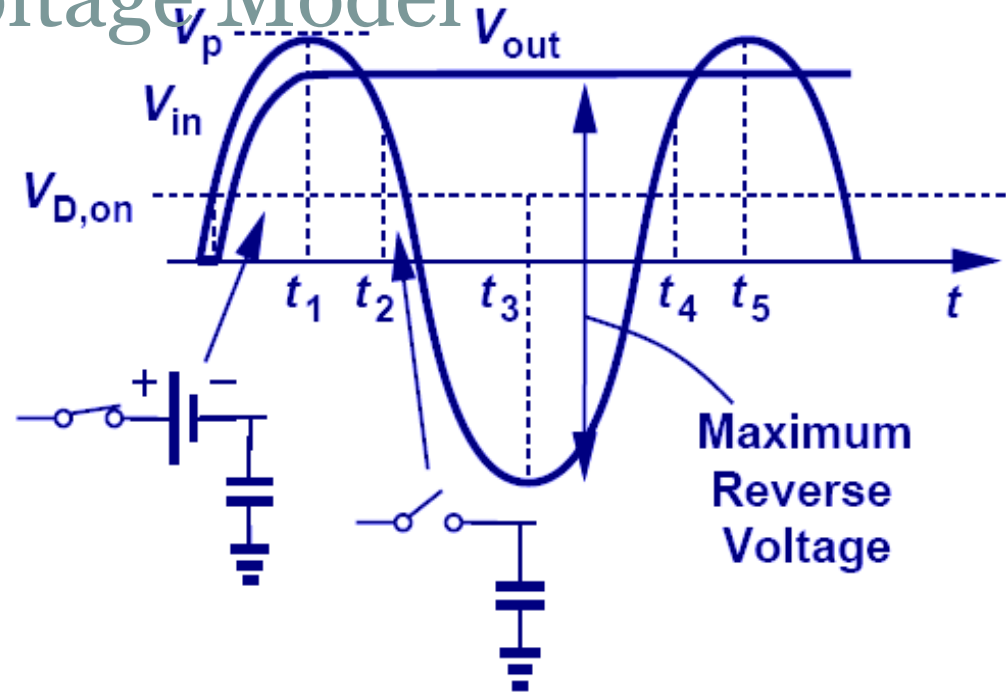

(b)


- If the resistor in half-wave rectifier is replaced by a capacitor, a fixed voltage output is obtained since the capacitor (assumed ideal) has no path to discharge.

Diode-Capacitor Circuit: Ideal Model

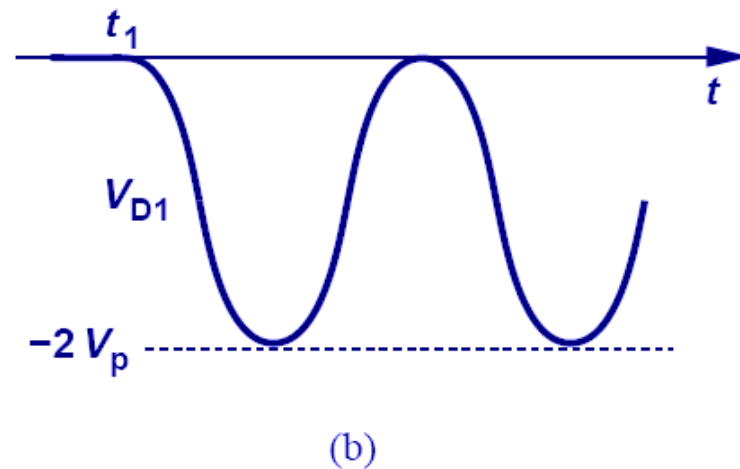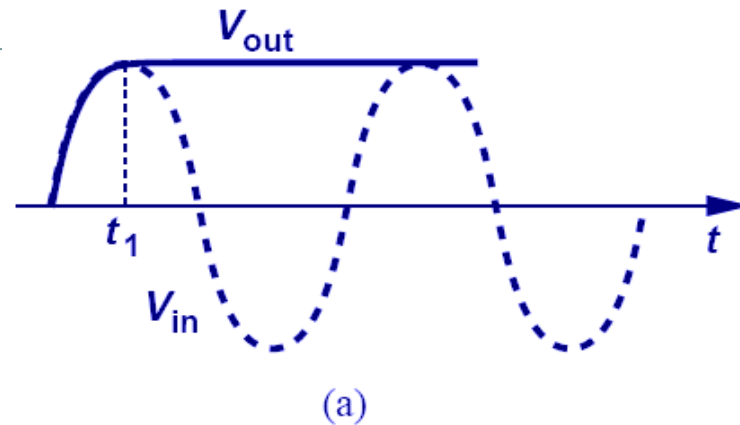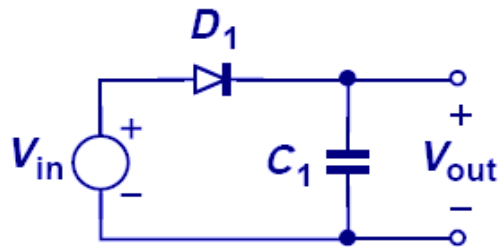



- Note that (b) is just like V_{in} , only shifted down.

Diode-Capacitor With Load Resistor

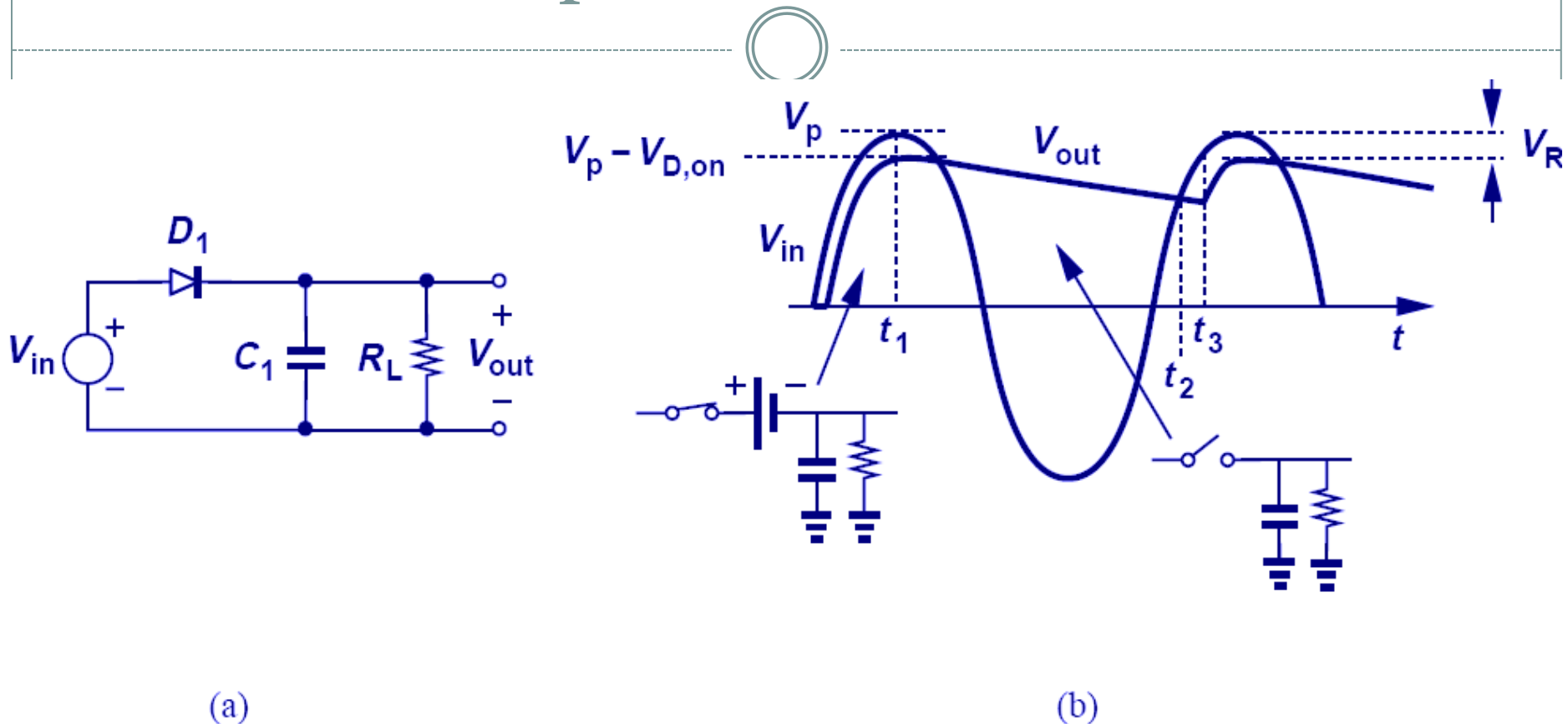

- A path is available for capacitor to discharge. Therefore, V_{out} will not be constant and a ripple exists.

Behavior for Different Capacitor Values

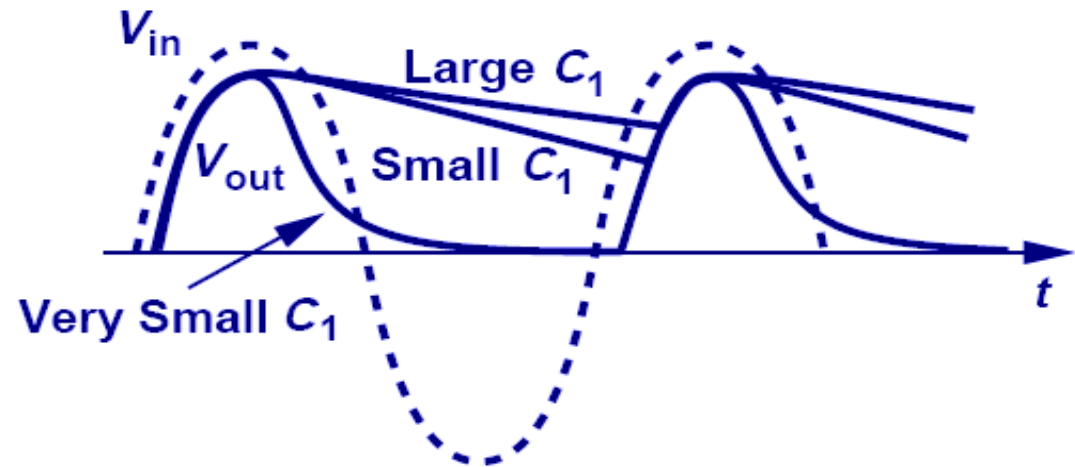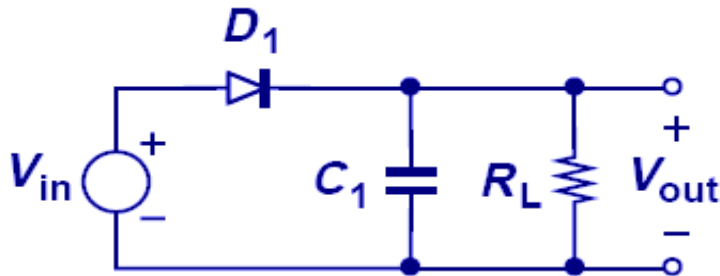

- For large C_1 , V_{out} has small ripple.

Peak to Peak amplitude of Ripple



$$V_{out}(t) = (V_p - V_{D,on}) \exp \frac{-t}{R_L C_1} \quad 0 \leq t \leq T_{in}$$

$$V_{out}(t) \approx (V_p - V_{D,on}) \left(1 - \frac{t}{R_L C_1}\right) \approx (V_p - V_{D,on}) - \frac{V_p - V_{D,on}}{R_L} \frac{t}{C_1}$$

$$V_R \approx \frac{V_p - V_{D,on}}{R_L} \cdot \frac{T_{in}}{C_1} \approx \frac{V_p - V_{D,on}}{R_L C_1 f_{in}}$$

- The ripple amplitude is the decaying part of the exponential.
- Ripple voltage becomes a problem if it goes above 5 to 10% of the output voltage.


Maximum Diode Current

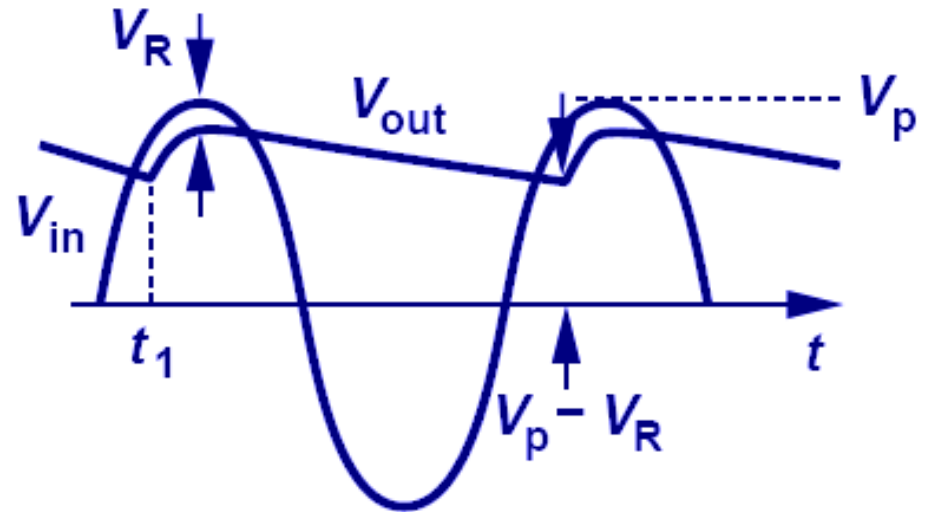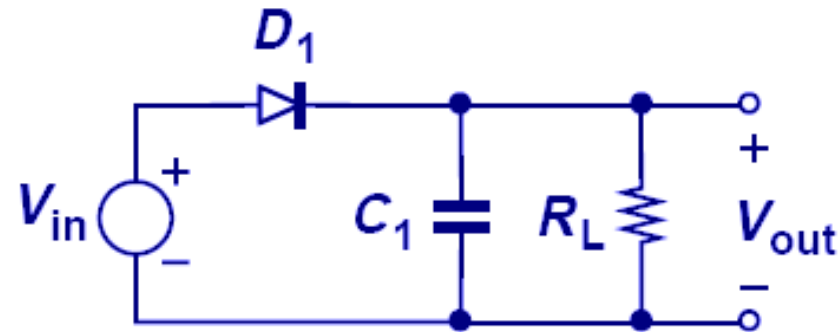


$$I_p \approx C_1 \omega_{in} V_p \sqrt{\frac{2V_R}{V_p} + \frac{V_p}{R_L}} \approx \frac{V_p}{R_L} (R_L C_1 \omega_{in} \sqrt{\frac{2V_R}{V_p} + 1})$$

- The diode has its maximum current at t_1 , since that's when the slope of V_{out} is the greatest.
- This current has to be carefully controlled so it does not damage the device.

Full-Wave Rectifier

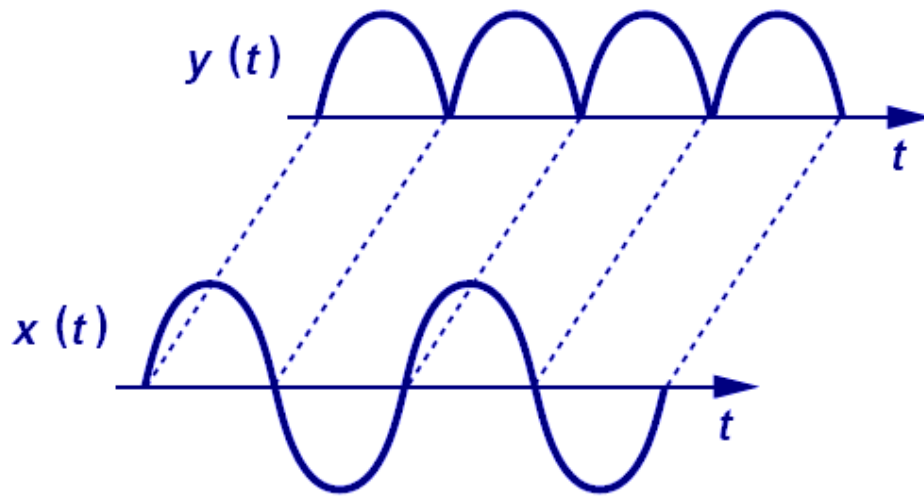


(a)

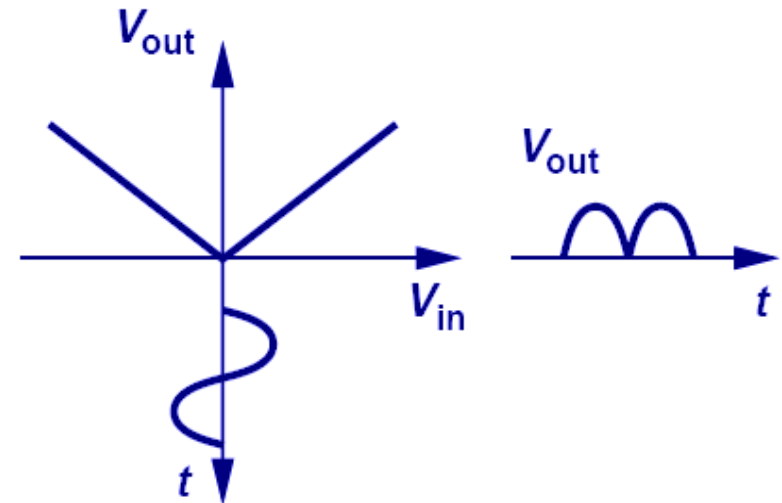


(b)

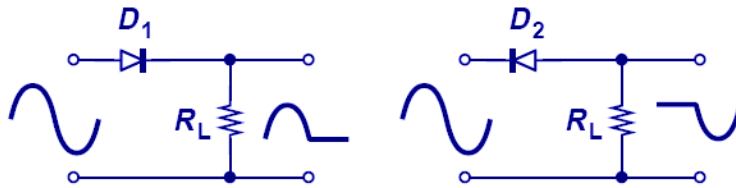
- A full-wave rectifier passes both the negative and positive half cycles of the input, while inverting the negative half of the input.
- As proved later, a full-wave rectifier reduces the ripple by a factor of two.




(a)

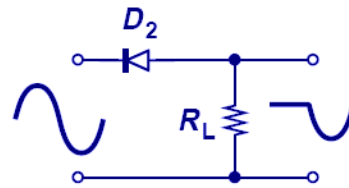


(b)

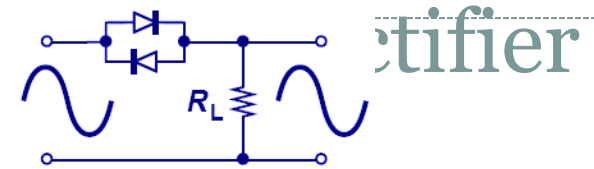


rectifier

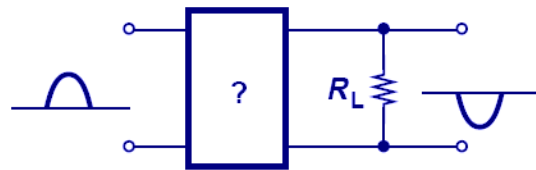


(c)

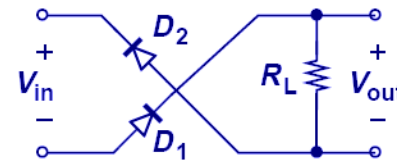

(d)

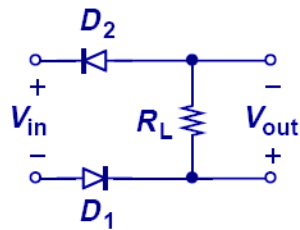





(e)

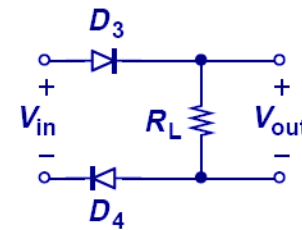

(f)


- Figures (e) and (f) show the topology that inverts the negative half cycle of the input.

Full-Wave Rectifier: Bridge Rectifier

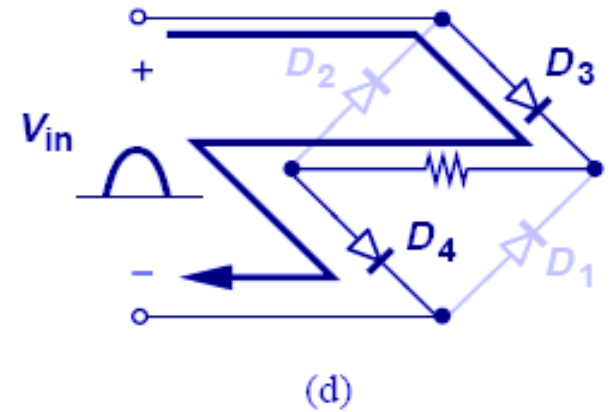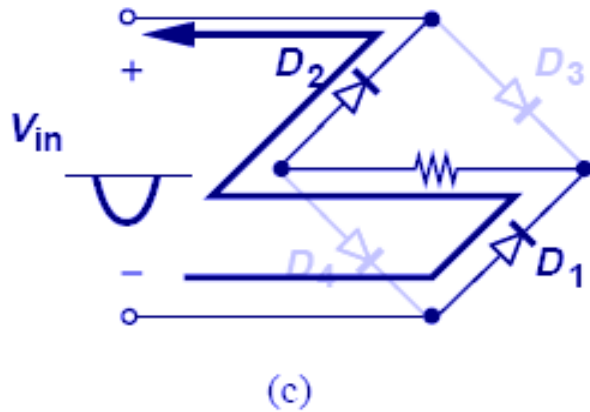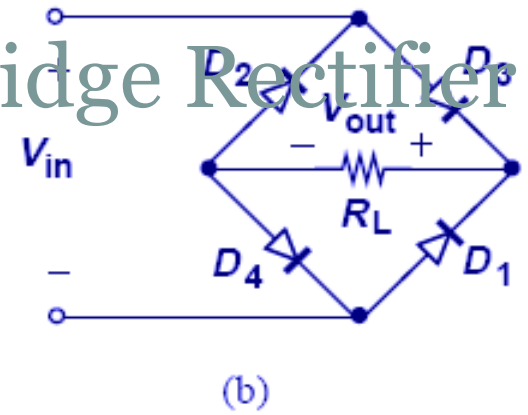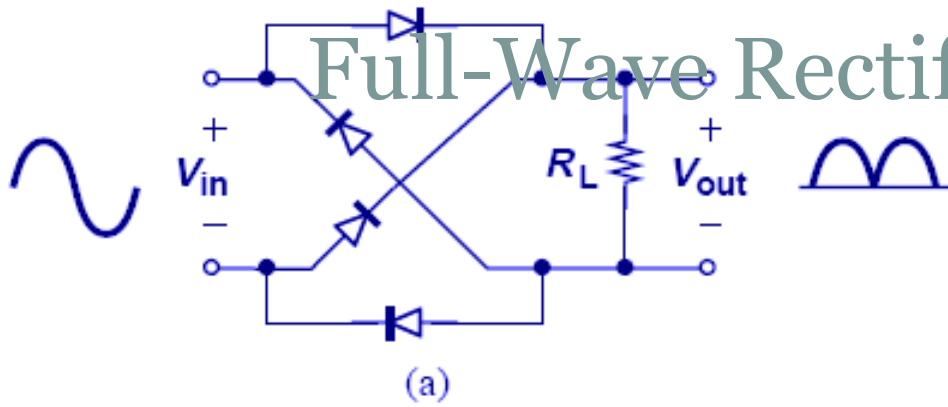

- The figure above shows a full-wave rectifier, where D_1 and D_2 pass/invert the negative half cycle of input and D_3 and D_4 pass the positive half cycle.

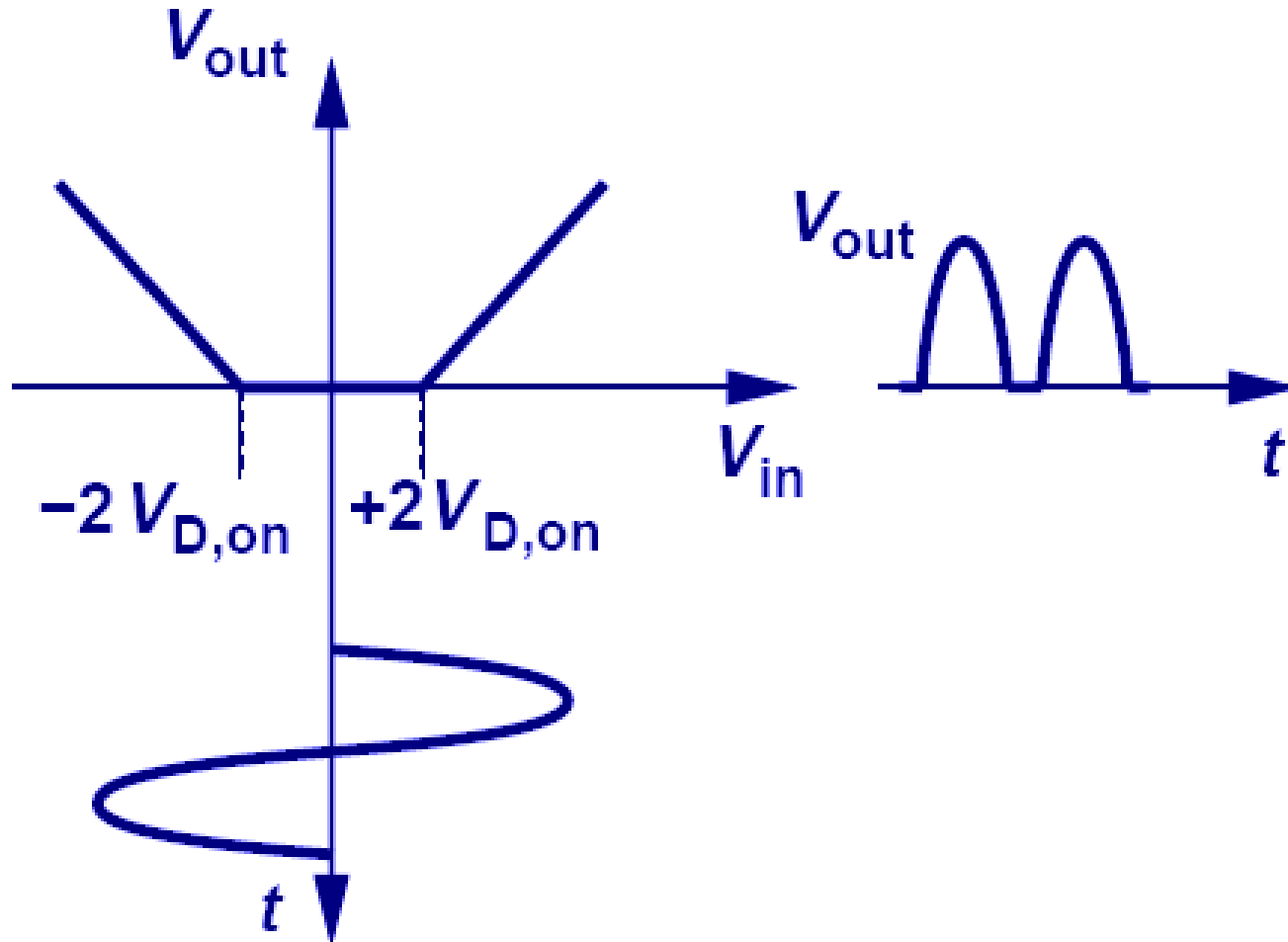
Input/Output Characteristics of a Full Wave





- The dead-zone around V_{in} arises because V_{in} must exceed $2V_{D,ON}$ to turn on the bridge.

Cur

Rectifier


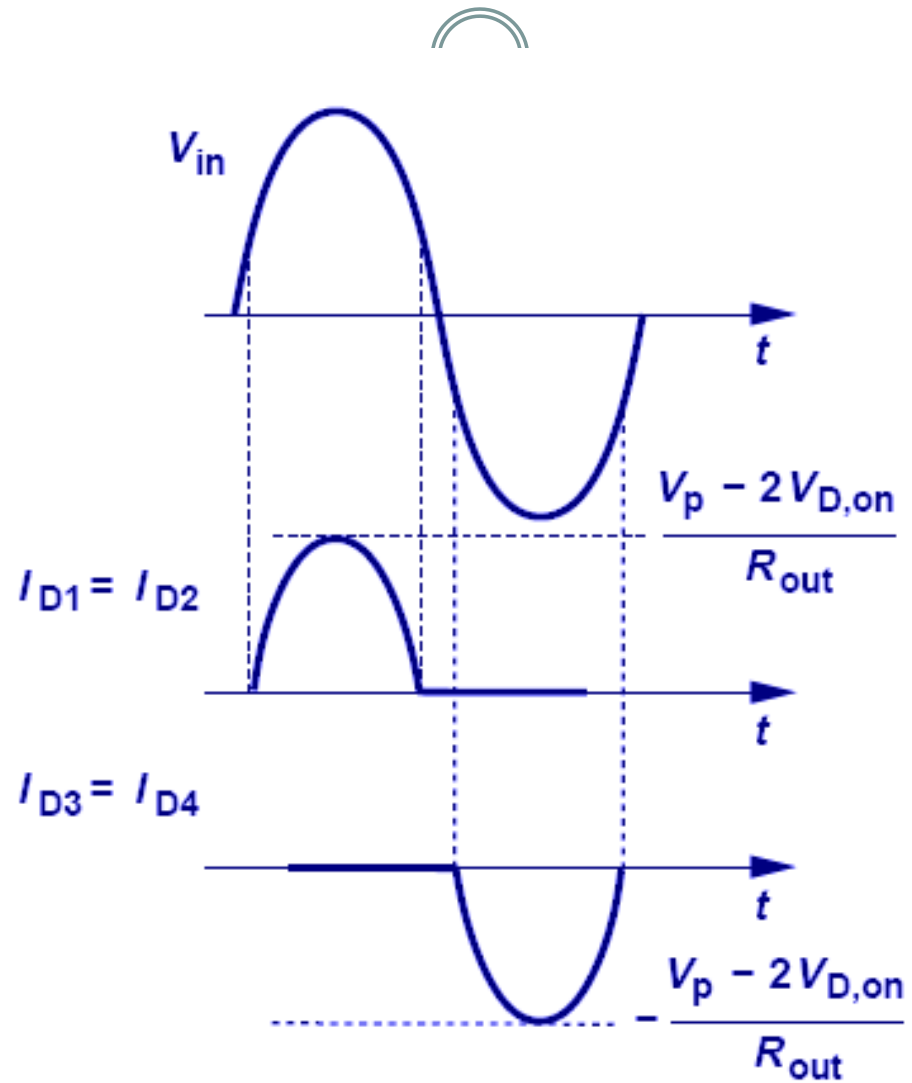


Summary of Half and Full-Wave

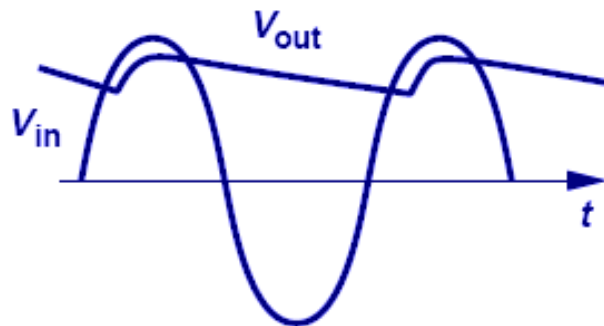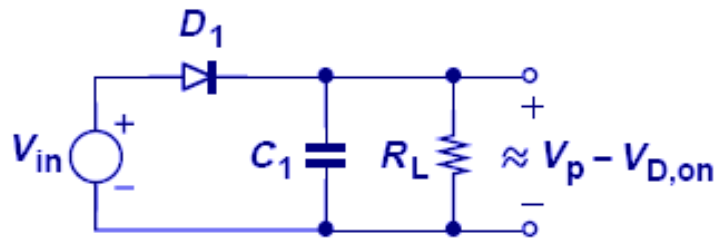

Reverse Bias $\approx 2V_p$

(a)

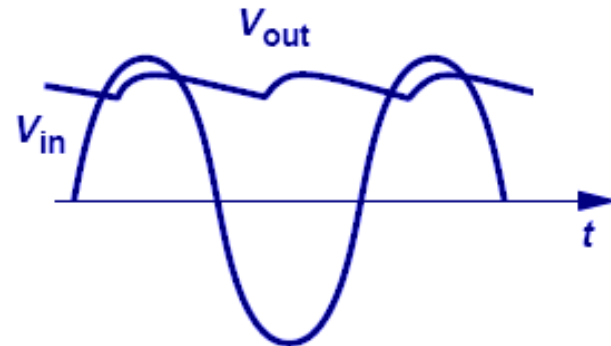
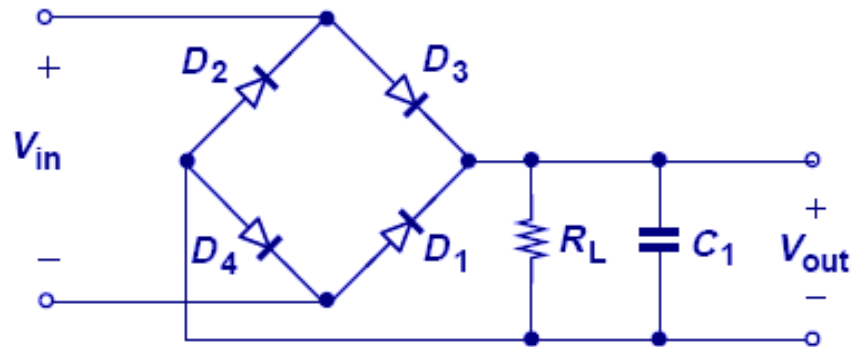


Reverse Bias $\approx V_p$

(b)

- Full-wave rectifier is more suited to adapter and charger applications.

Complete Full-Wave Rectifier

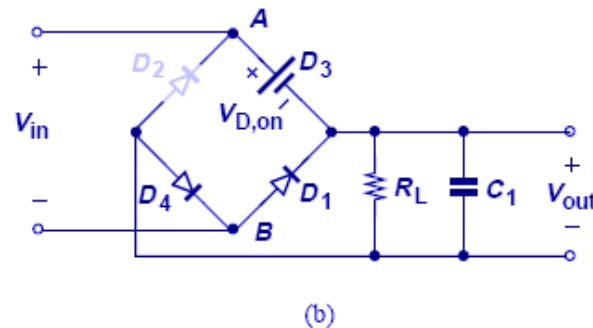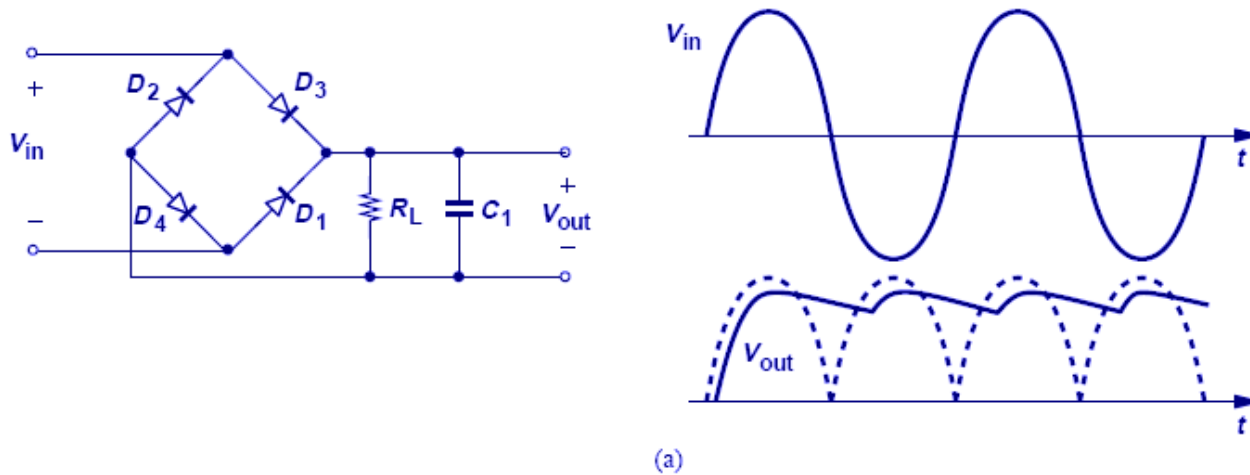


- Since C_1 only gets $1/2$ of period to discharge, ripple voltage is decreased by a factor of 2. Also (b) shows that each diode is subjected to approximately one V_p reverse bias drop (versus $2V_p$ in half-wave rectifier).

Half-wave Rectifiers






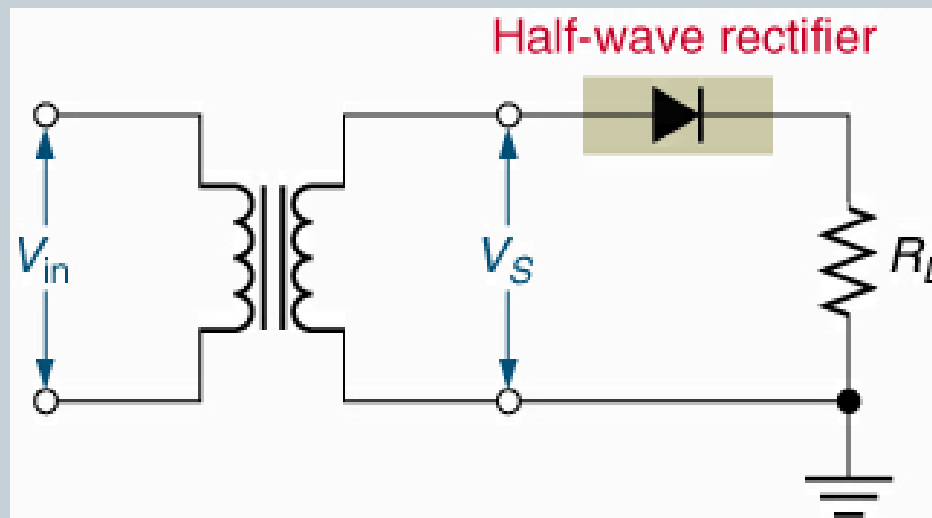- Half-wave rectifier – A diode placed in series between a transformer (or ac line input) and its load.



Positive Half-wave Rectifiers

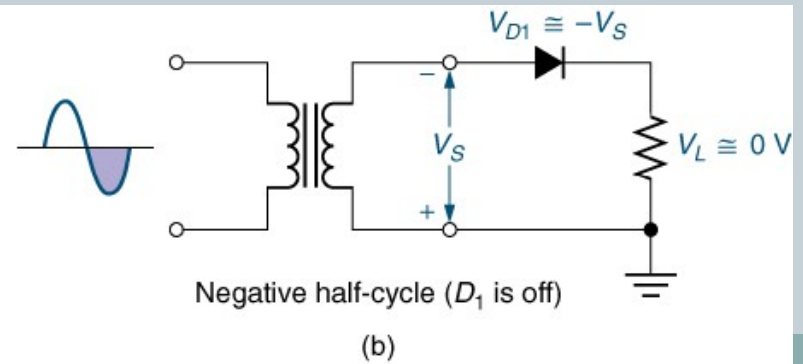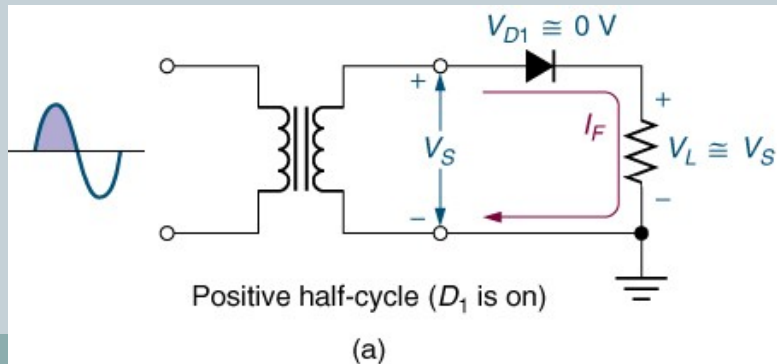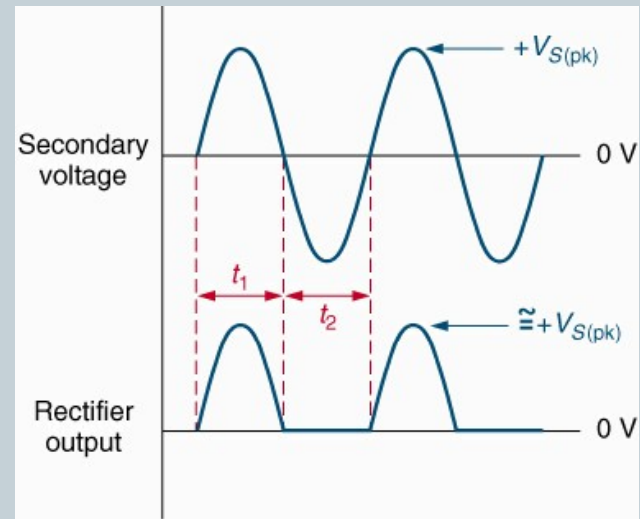This circuit converts an ac input to a series of positive pulses.



Average Load Voltage and Current



- Average voltage (V_{ave}) – The dc equivalent of a voltage waveform.
- Average current (I_{ave}) – The dc equivalent of a current waveform.



For the output from a *half-wave* rectifier:

$$V_{ave} = \frac{V_{pk}}{\pi}$$

$$I_{ave} = \frac{I_{pk}}{\pi}$$


Negative Half-wave Rectifiers

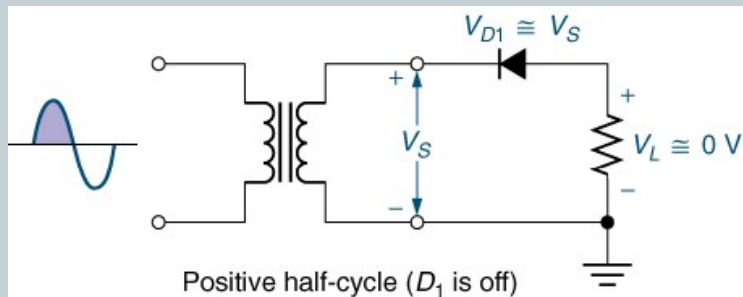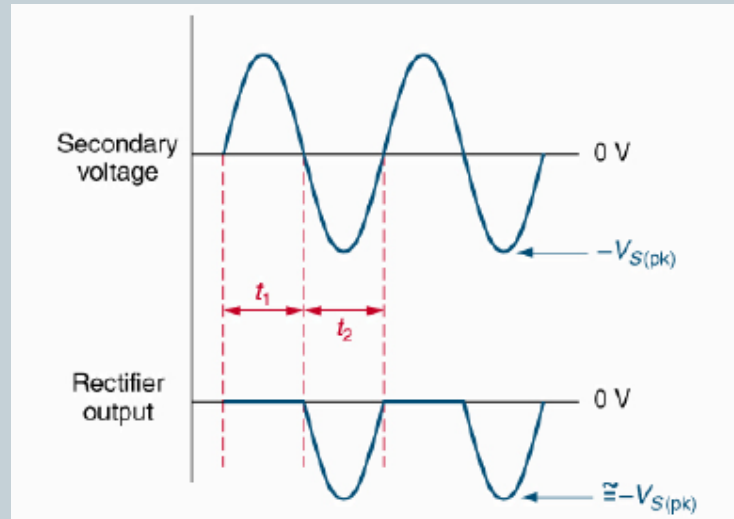This circuit converts an ac input to a series of negative pulses.



Positive half-cycle (D_1 is off)

(a)

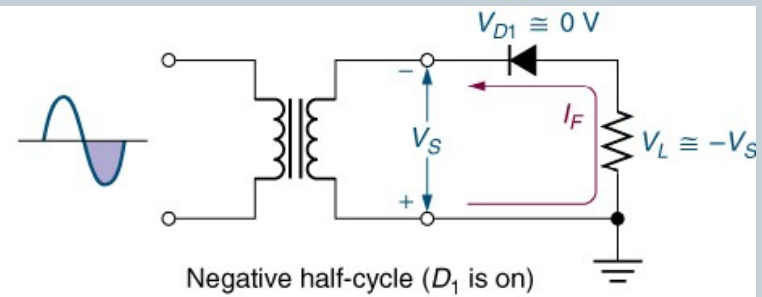

Negative half-cycle (D_1 is on)

(b)

Peak Inverse Voltage (PIV)



Peak inverse voltage (PIV) – The maximum diode reverse bias produced by a given circuit.

For the diode in a half-wave rectifier:

$$PIV = V_{S(pk)}$$

