
BJT transistors

FET (Field Effect Transistor)

Few important advantages of FET over conventional Transistors

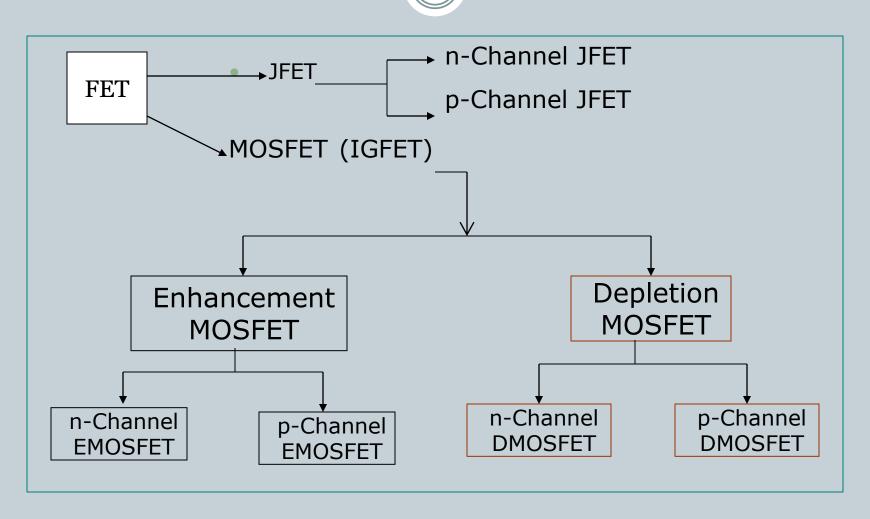- 1. Unipolar device i. e. operation depends on only one type of charge carriers (*h* or *e*)
- 2. Voltage controlled Device (gate voltage controls drain current)
- 3. Very high input impedance ($\approx 10^9 10^{12} \Omega$)
- 4. Source and drain are interchangeable in most Low-frequency applications
- 5. Low Voltage Low Current Operation is possible (Low-power consumption)
- 6. Less Noisy as Compared to BJT
- 7. No minority carrier storage (Turn off is faster)
- 8. Self limiting device
- 9. Very small in size, occupies very small space in ICs
- 10. Low voltage low current operation is possible in MOSFETS
- 11. Zero temperature drift of out put is possiblek

Types of Field Effect Transistors (The Classification)



The Junction Field Effect Transistor (JFET)


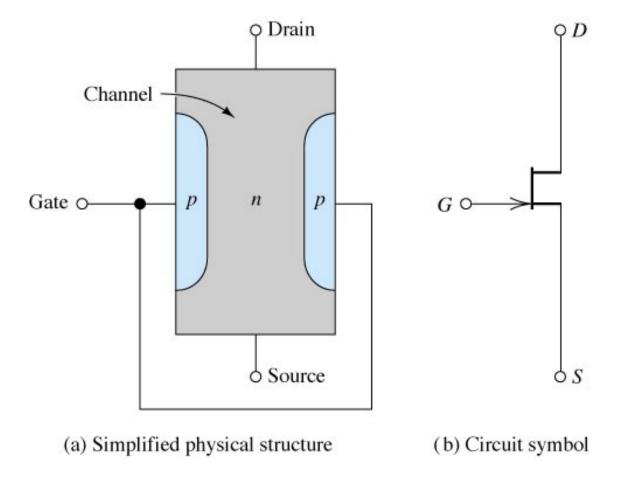


Figure: *n*-Channel JFET.

SYMBOLS

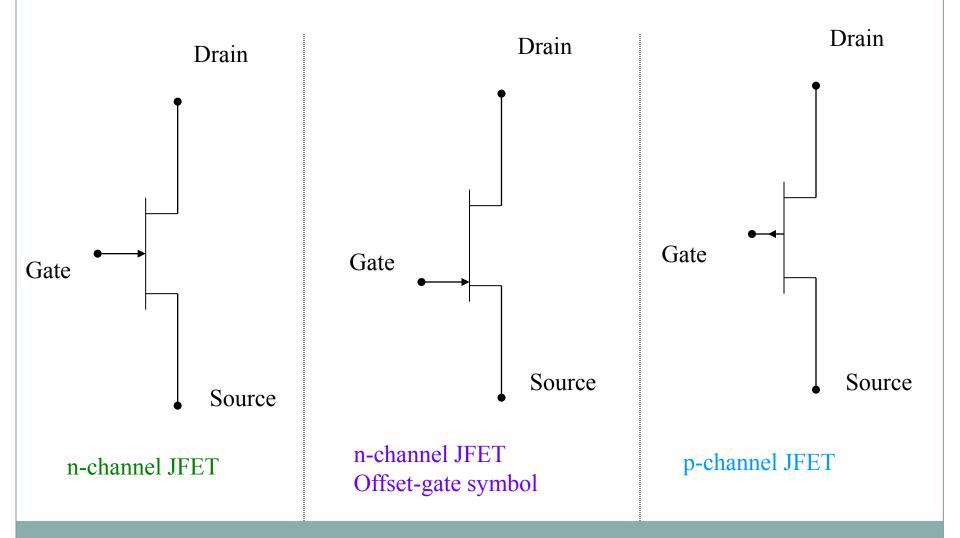

Biasing the JFET

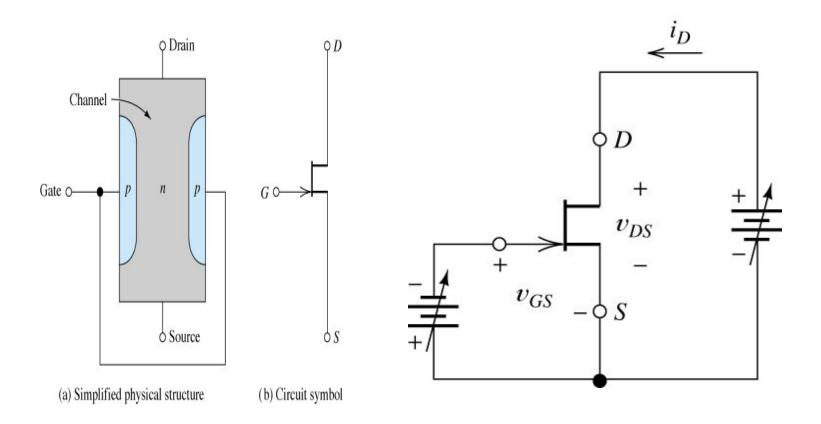


Figure: *n*-Channel JFET and Biasing Circuit.

Operation of JFET at Various Gate Bias Potentials


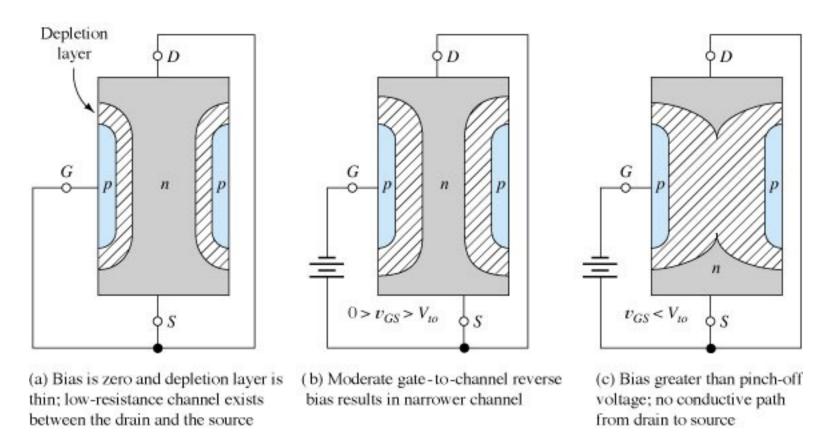


Figure: The nonconductive depletion region becomes broader with increased reverse bias. (*Note:* The two gate regions of each FET are connected to each other.)

Operation of a JFET

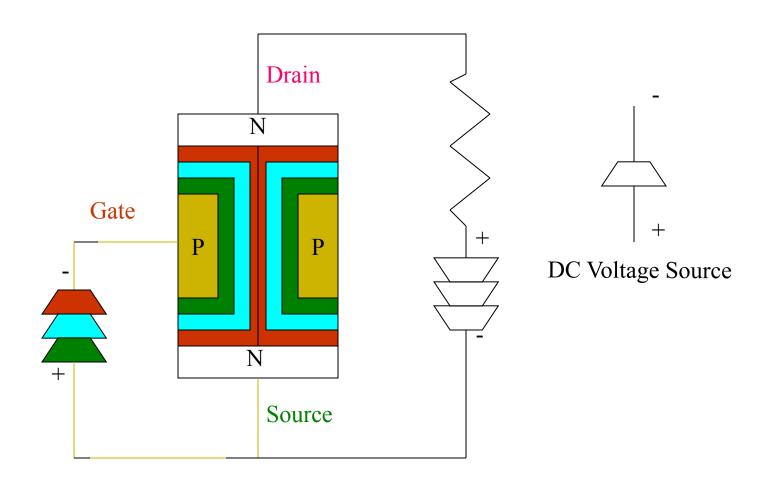

Output or Drain (V_D-I_D) Characteristics of n-JFET

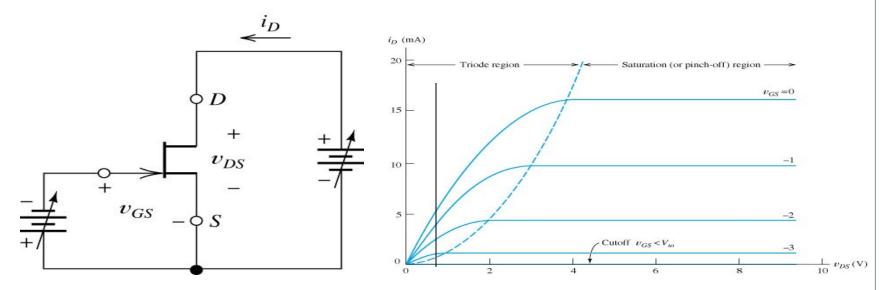


Figure: Circuit for drain characteristics of the *n*-channel JFET and its Drain characteristics.

Non-saturation (Ohmic) Region:

$$V_{DS} < \left(V_{GS} - V_{P}\right)$$

The drain current is given by
$$_{DS} = \frac{2I_{DSS}}{V_P^2} \left[\left(V_{GS} - V_P \right) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Saturation (or Pinchoff)

Region:

$$I_{DS} = \frac{I_{DSS}}{V_P^2} \left[\left(V_{GS} - V_P \right)^2 \right] \qquad \text{and } I_{DS} = I_{DSS} \left(\mathbf{1} - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{DS} \ge \left(V_{GS} - V_{P}\right)$$

and
$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_{P}} \right)^{2}$$

Where, I_{DSS} is the short circuit drain current, V_P is the pinch off voltage

Simple Operation and Break down of n-Channel JFET


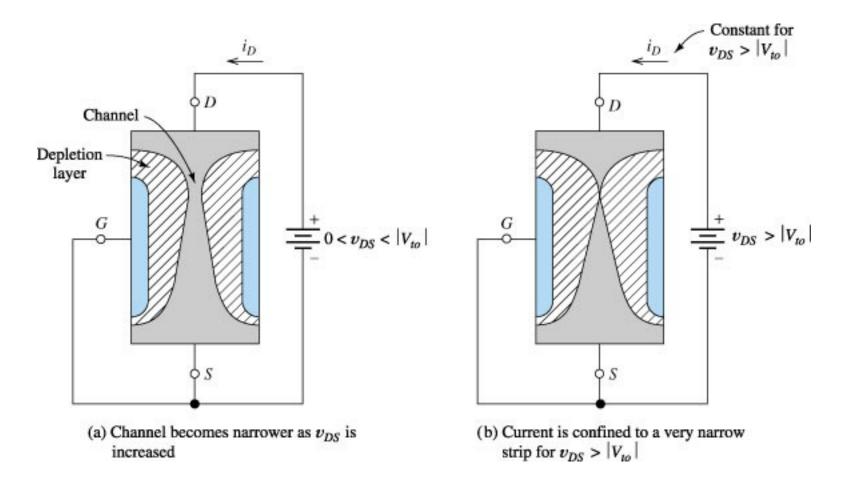


Figure: *n*-Channel FET for v_{GS} = 0.

JFET Transfer Curve

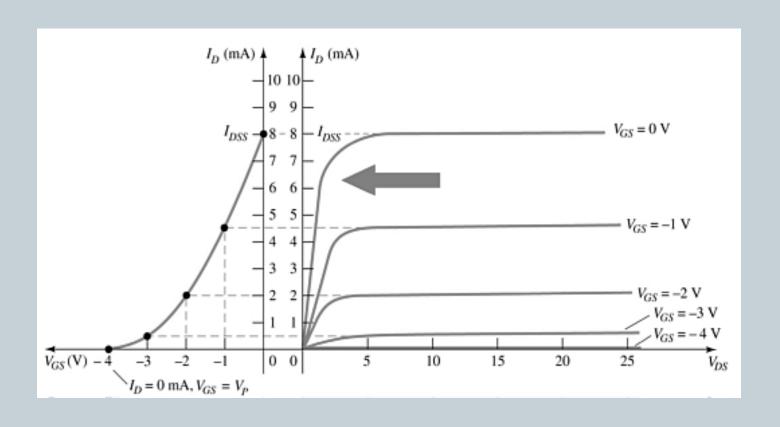This graph shows the value of $I_{\rm D}$ for a given value of $V_{\rm GS}$



Thank You