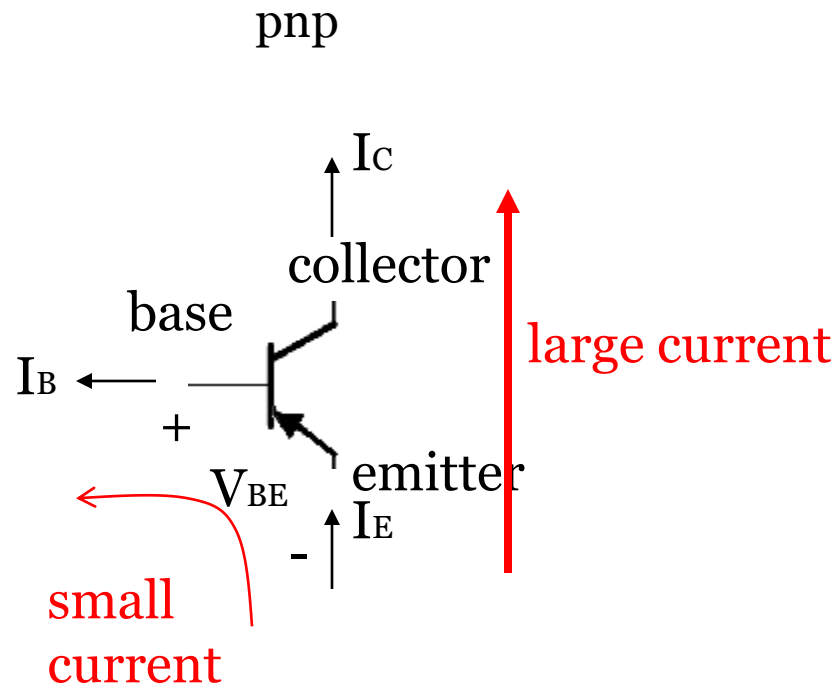


BJT transistors



Summary of pnp transistor behavior



Power Across BJT



- $P_{\text{BJT}} = V_{\text{CE}} * i_{\text{CE}}$
- Should be below the rated transistor power
- Should be kept in mind when considering heat dissipation
- Reducing power increases efficiency

Summary of equations for a BJT

4

$$I_E \approx I_C$$

$$I_C = \beta I_B$$

β is the current gain of the transistor ≈ 100

$$V_{BE} = 0.7V(\text{npn})$$

$$V_{BE} = -0.7V(\text{pnp})$$

Graphical representation of transistor characteristics

5

