


BJT transistors



FET Transistors – Regions




| Region | Criteria | Effect on Current |
|------------|--|--|
| Cut-off | $V_{GS} < V_{th}$ | $I_{DS} = 0$ |
| Linear | $V_{GS} > V_{th}$ And $V_{DS} < V_{GS} - V_{th}$ | Transistor acts like a variable resistor, controlled by V_{gs} |
| Saturation | $V_{GS} > V_{th}$ And $V_{DS} > V_{GS} - V_{th}$ | Essentially constant current |

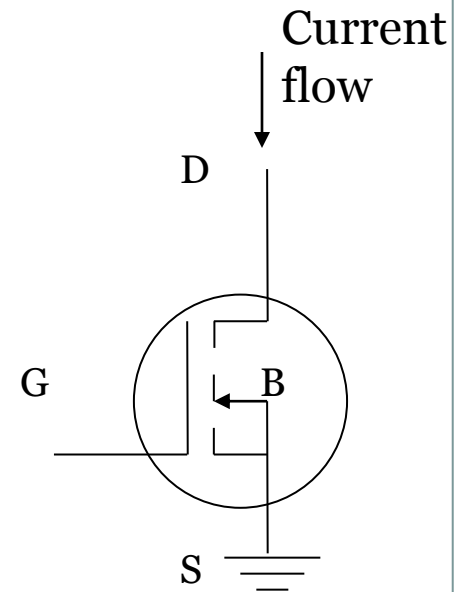


JFET vs MOSFET Transistors

| MOSFET | JFET |
|--|--|
| High switching speed | Will operate at $V_G < 0$ |
| Can have very low R_{DS} | Better suited for low signal amplification |
| Susceptible to ESD | |
| More commonly used as a power transistor | |

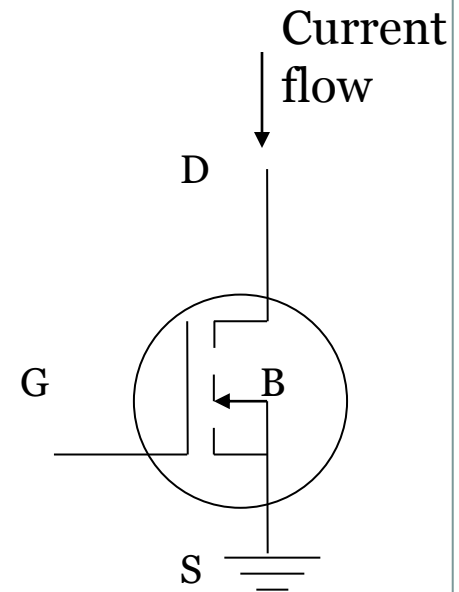

Power Transistors

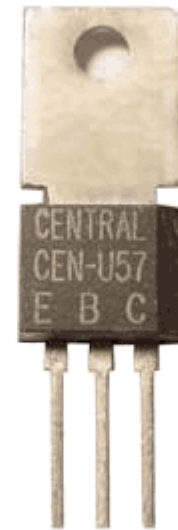- Additional material for current handling and heat dissipation
- Can handle high current and voltage
- Functionally the same as normal transistors



Transistor Uses




- Switching
- Amplification
- Variable Resistor

Analysis of transistor circuits at DC

6

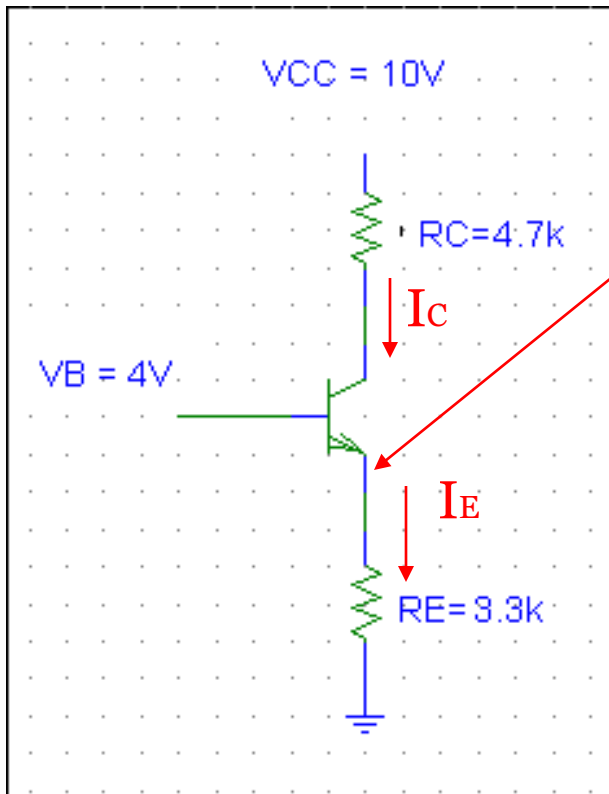For all circuits: assume transistor operates in linear region
write B-E voltage loop
write C-E voltage loop




B-E junction acts like a diode

$$V_E = V_B - V_{BE} = 4V - 0.7V = 3.3V$$

$$I_E = (V_E - 0)/R_E = 3.3/3.3K = 1mA$$

$$I_C \approx I_E = 1mA$$
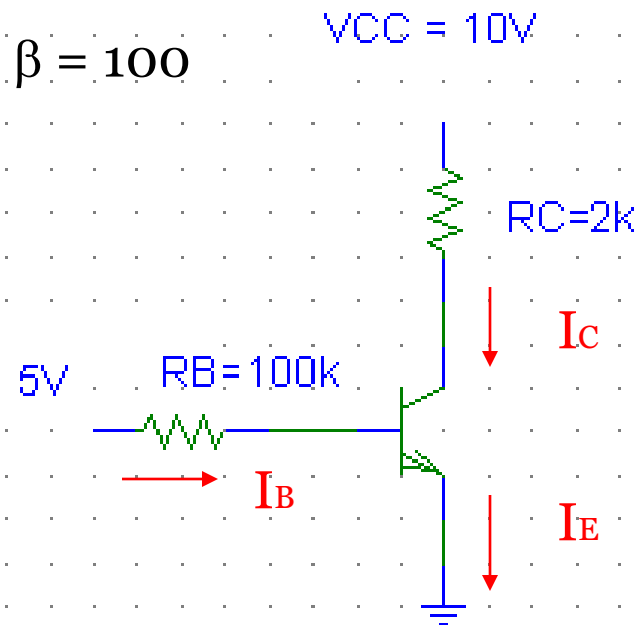
$$V_C = 10 - I_C R_C = 10 - 1(4.7) = 5.3V$$




B-E Voltage loop

$$5 = I_B R_B + V_{BE}, \text{ solve for } I_B$$

$$I_B = (5 - V_{BE}) / R_B = (5 - 0.7) / 100k = 0.043mA$$

$$I_C = \beta I_B = (100) 0.043mA = 4.3mA$$
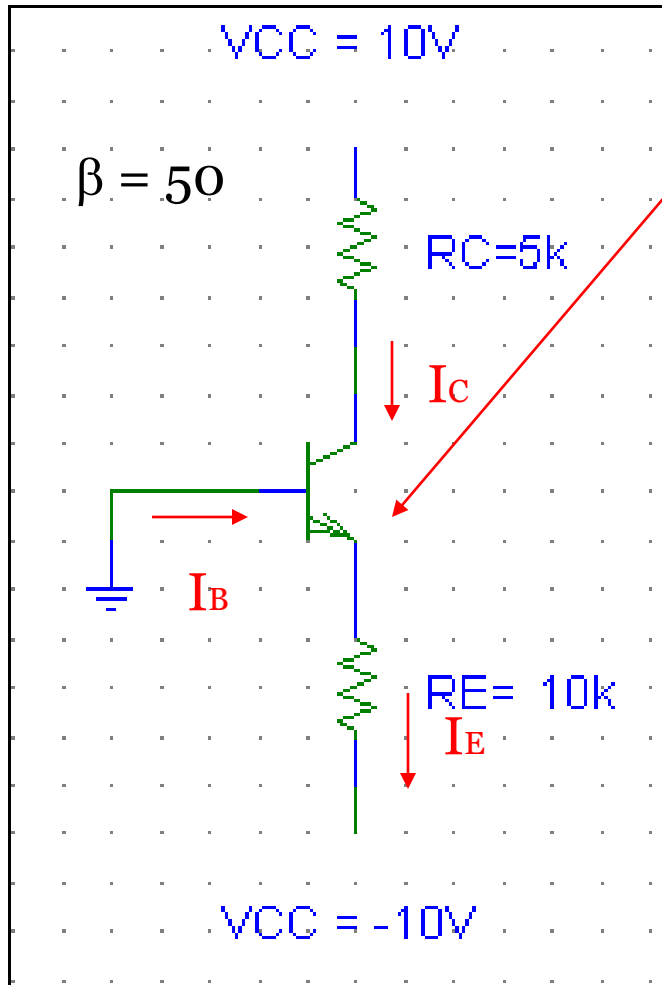
$$V_C = 10 - I_C R_C = 10 - 4.3(2) = 1.4V$$



$$V_E = 0 - .7 = -0.7V$$

$$I_E = (V_E - -10)/R_E = (-.7 + 10)/10K = 0.93mA$$

$$I_C \approx I_E = 0.93mA$$

$$I_B = I_C/\beta = .93mA/50 = 18.6\mu A$$

$$V_C = 10 - I_C R_C = 10 - .93(5) = 5.35V$$