


BJT transistors



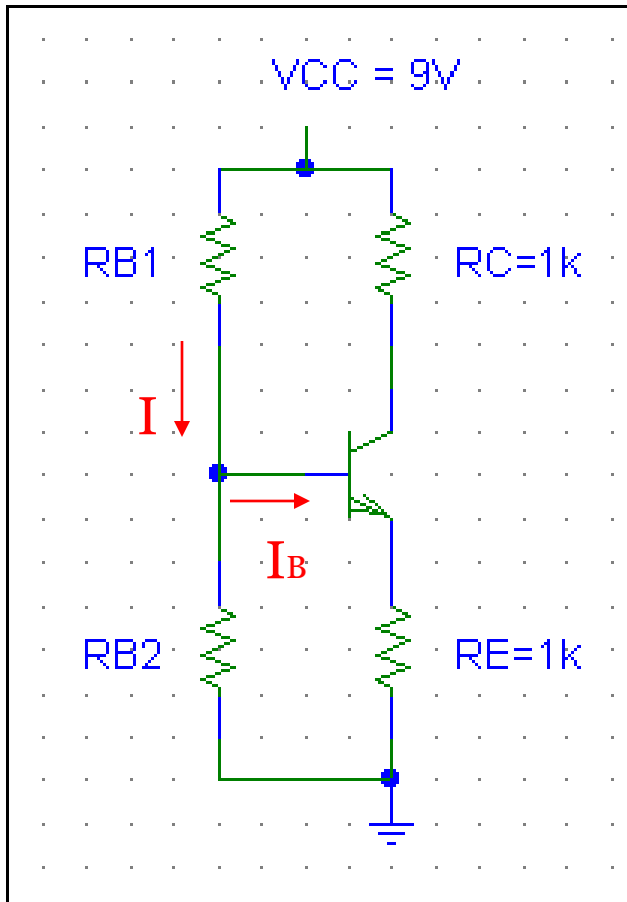Problem

2

- Use a voltage divider, R_{B1} and R_{B2} to bias V_B to avoid two power supplies.
- Make the current in the voltage divider about 10 times I_B to simplify the analysis. Use $V_B = 3V$ and $I = 0.2mA$.



(a) R_{B1} and R_{B2} form a voltage divider.

Assume $I \gg I_B$ $I = V_{CC}/(R_{B1} + R_{B2})$

$$.2mA = 9 / (R_{B1} + R_{B2})$$

AND

$$V_B = V_{CC}[R_{B2}/(R_{B1} + R_{B2})]$$


$3 = 9 [R_{B2}/(R_{B1} + R_{B2})]$, Solve for R_{B1} and R_{B2} .

$$R_{B1} = 30K\Omega, \text{ and } R_{B2} = 15K\Omega.$$

Problem

3

Find the operating point

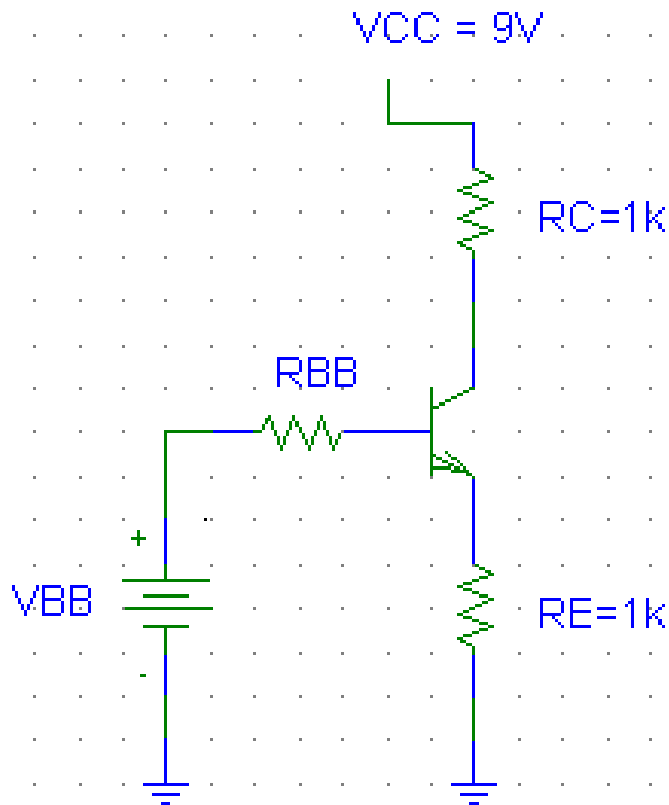

- Use the Thevenin equivalent circuit for the base

- Makes the circuit simpler

- $V_{BB} = V_B = 3V$


- R_{BB} is measured with voltage sources grounded

- $R_{BB} = R_{B1} || R_{B2} = 30K\Omega || 15K\Omega = .10K\Omega$

Problem

4

Write B-E loop and C-E loop

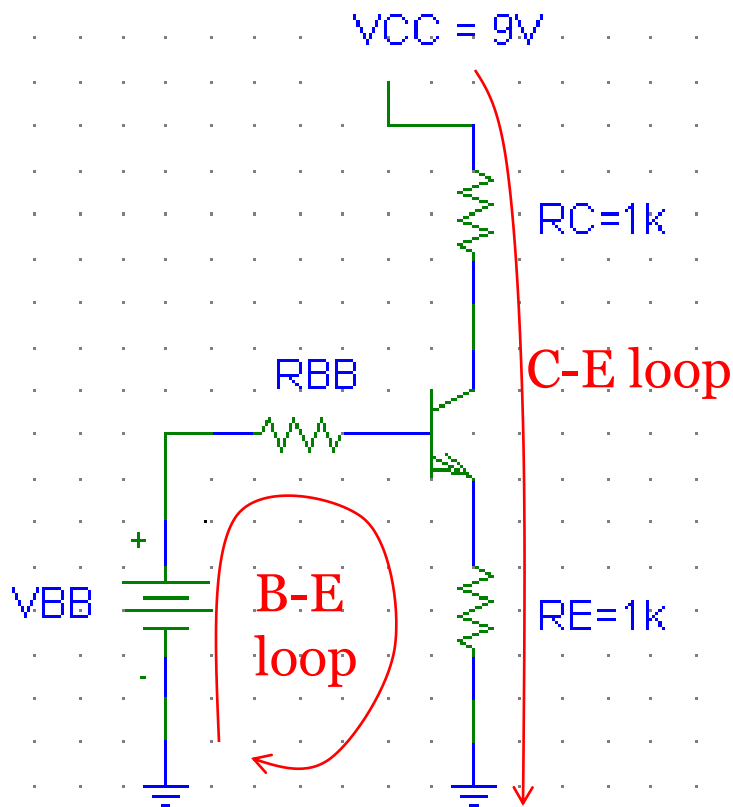

B-E loop

$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$

$$I_E = 2.09 \text{ mA}$$

C-E loop

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CE} = 4.8 \text{ V}$$

This is how all DC circuits are analyzed and designed!