


# BJT transistors



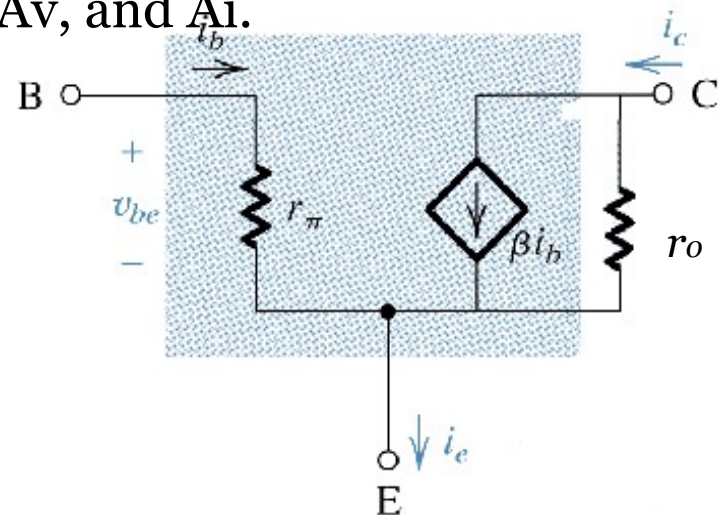
# Steps to analyze a transistor circuit

2

- 1 DC Analysis Set ac sources to zero, solve for DC quantities,  $I_C$  and  $V_{CE}$ .
- 2 Determine ac quantities from DC parameters  
Find  $g_m$ ,  $r_\pi$ , and  $r_o$ .
- 3 AC Analysis  
Set DC sources to zero, replace transistor by hybrid- $\pi$  model, find ac quantities,  $R_{in}$ ,  $R_{out}$ ,  $A_v$ , and  $A_i$ .



# Example

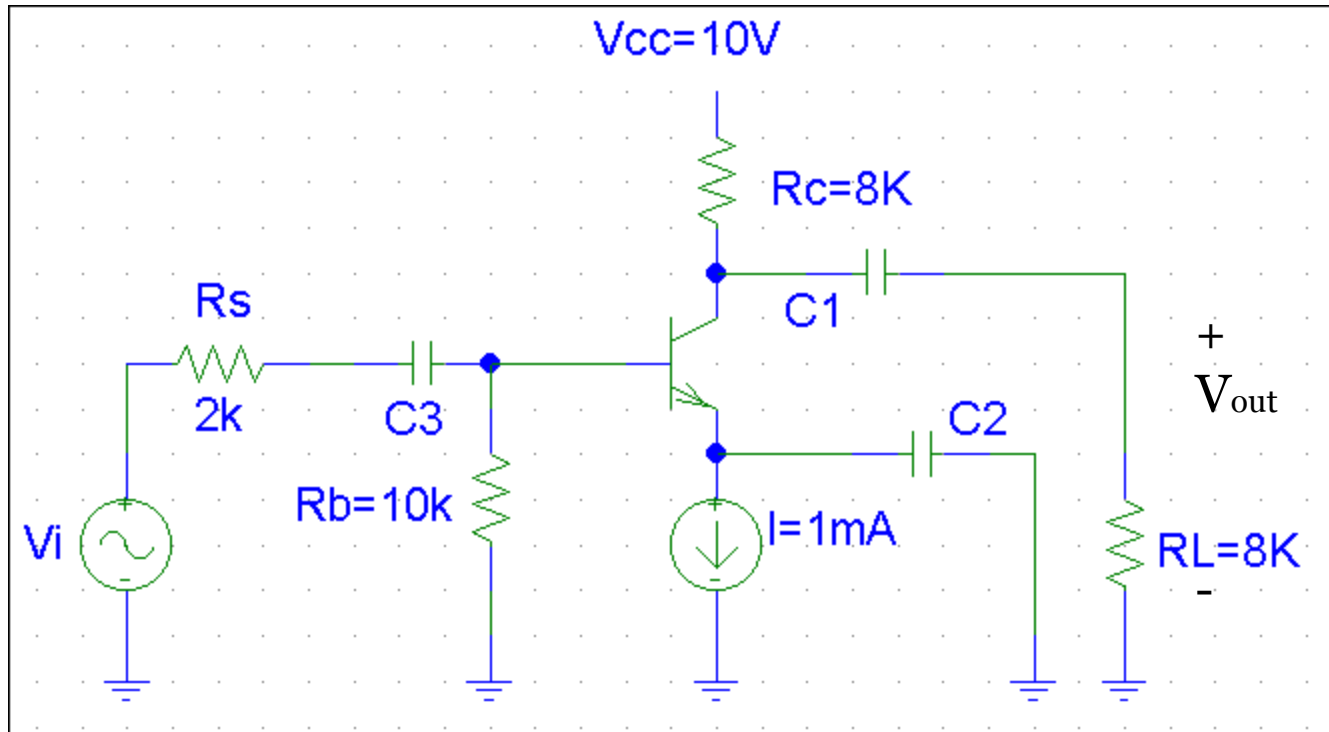

$$I_E = 1 \text{ mA}$$

$$I_B \approx I_E / \beta = 0.01 \text{ mA}$$

$$V_B = 0 - I_B R_B = -0.1 \text{ V}$$


$$V_E = V_B - V_{BE} = -0.1 - 0.7 = -0.8 \text{ V}$$

$$V_C = 10V - I_C R_C = 10 - 1(8) = 2V$$

$$g_m = I_C / V_T = 1 \text{ mA} / 25 \text{ mV} = 40 \text{ mA/V}$$

$$r_\pi = V_T / I_B = 25 \text{ mV} / 0.01 \text{ mA} = 2.5 \text{ K}$$

# ac equivalent circuit

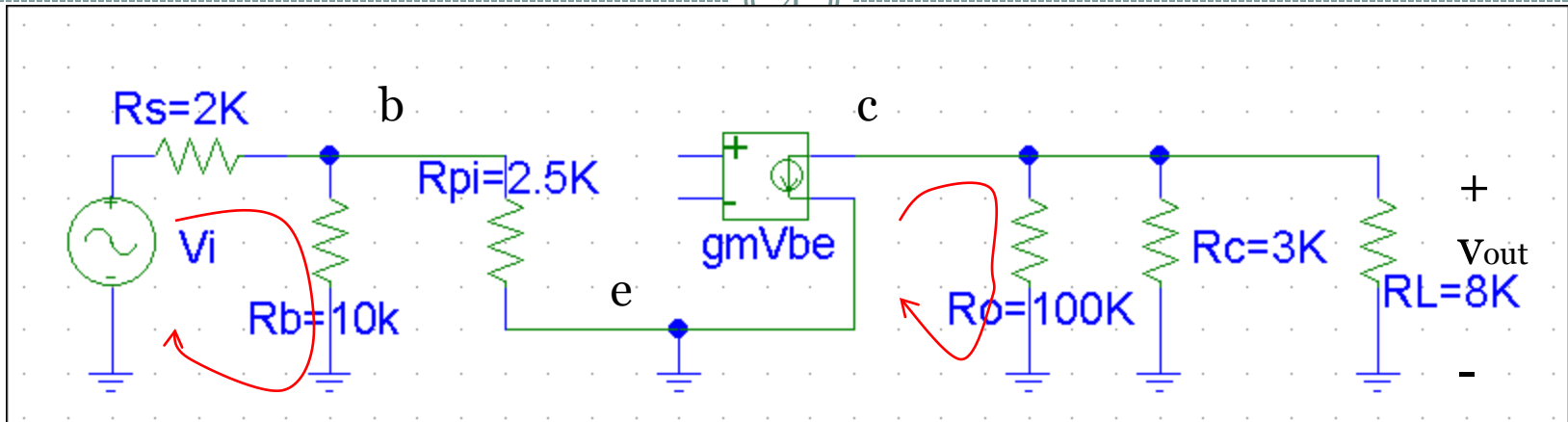

$$V_{be} = \frac{R_b || R_{pi}}{[(R_b || R_{pi}) + R_s]} V_i$$

$$V_{be} = 0.5 V_i$$

$$V_{out} = -(g_m V_{be}) || (R_o || R_c || R_L)$$

$$V_{out} = -154 V_{be}$$

$$A_v = V_{out} / V_i = -77$$


Neglecting  $R_o$

$$V_{out} = -(g_m V_{be}) || (R_c || R_L)$$

$$A_v = V_{out} / V_i = -80$$

# Graphical analysis

5

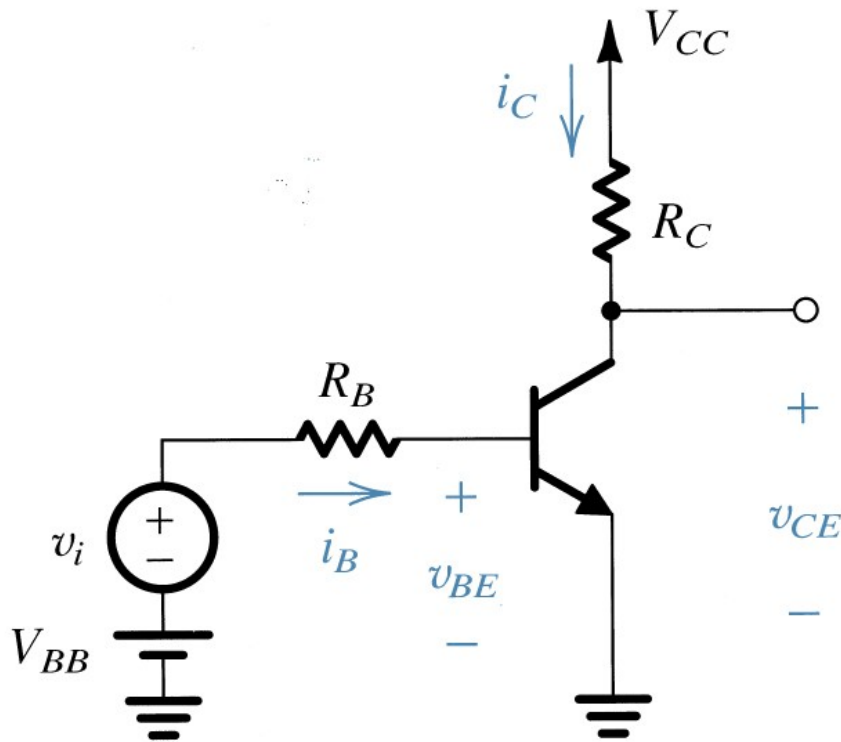


Input circuit  
B-E voltage loop

$$V_{BB} = I_B R_B + V_{BE}$$

$$I_B = (V_{BB} - V_{BE}) / R_B$$

# Graphical construction of $I_B$ and $V_{BE}$

6

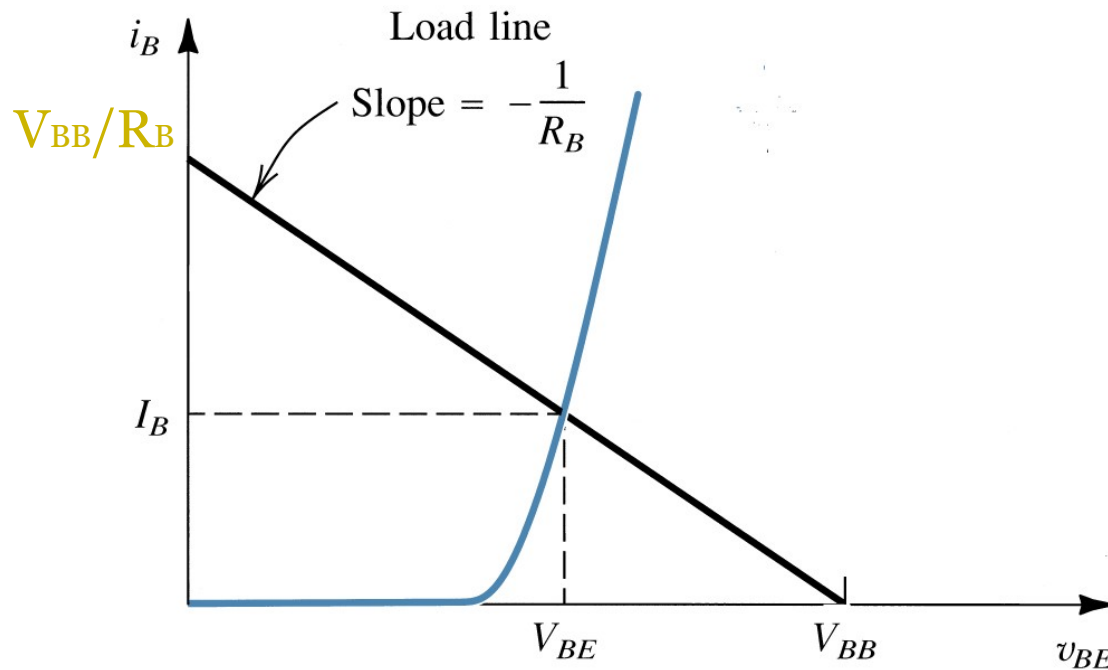


$$I_B = (V_{BB} - V_{BE})/R_B$$

$$\text{If } V_{BE} = 0, I_B = V_{BB}/R_B$$

$$\text{If } I_B = 0, V_{BE} = V_{BB}$$

# Load line

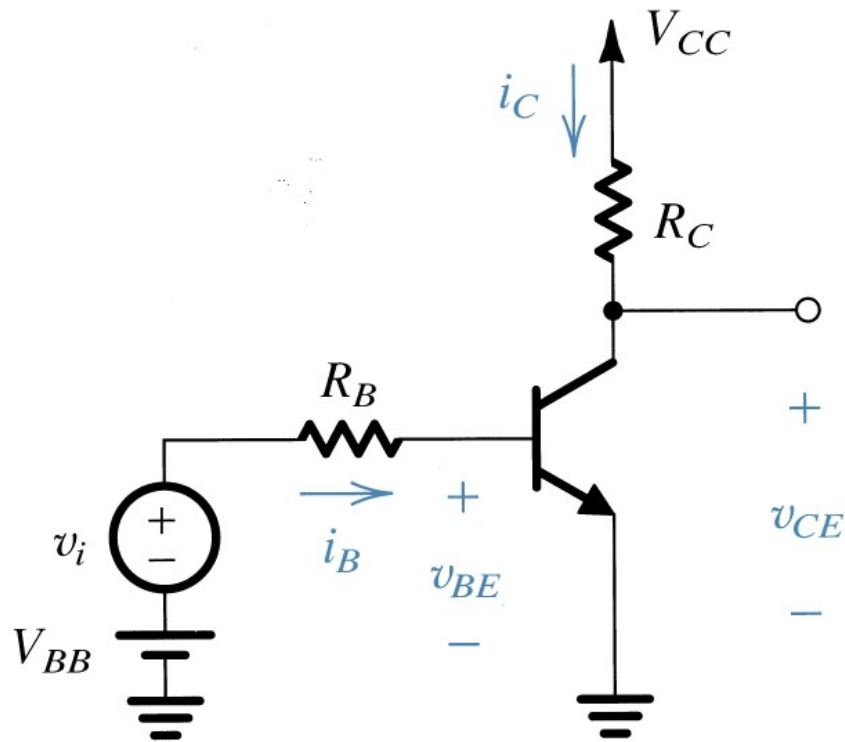


Output circuit  
C-E voltage loop

$$V_{CC} = I_C R_C + V_{CE}$$

$$I_C = (V_{CC} - V_{CE}) / R_C$$

# Graphical construction of $I_C$ and $V_{CE}$

8

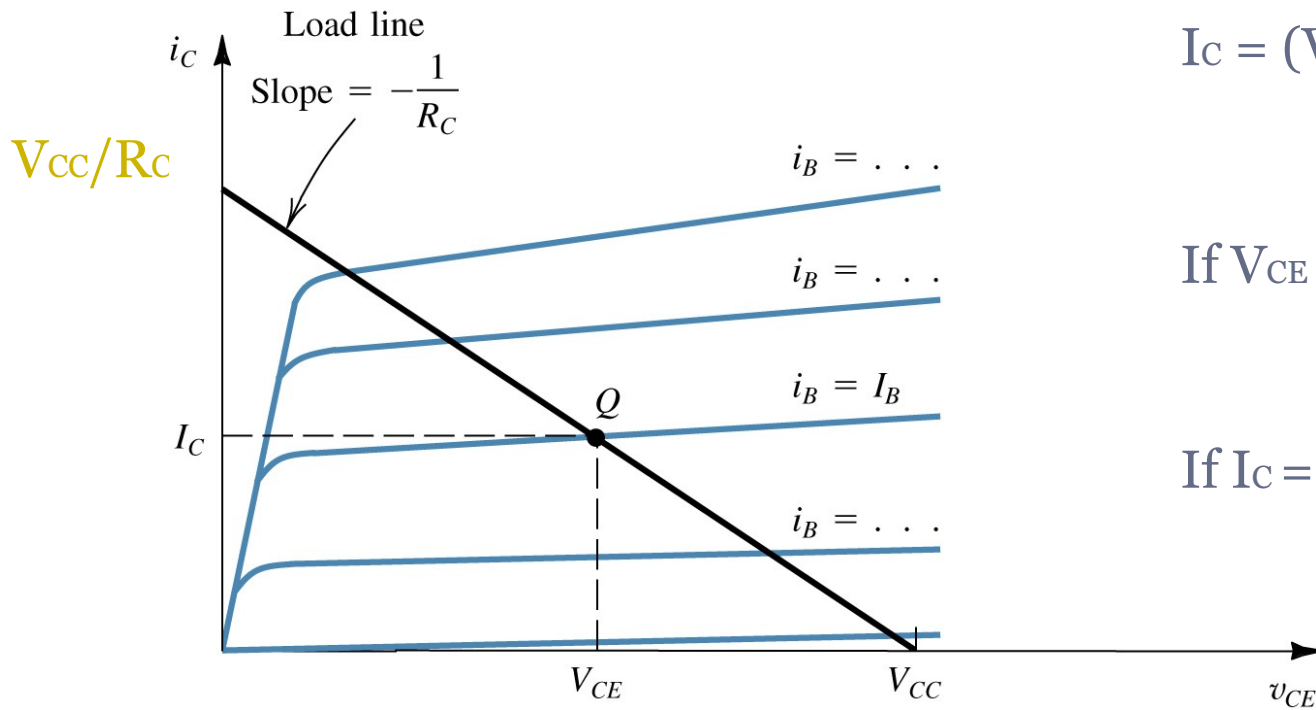

$$I_C = (V_{CC} - V_{CE})/R_C$$

If  $V_{CE} = 0$ ,  $I_C = V_{CC}/R_C$

If  $I_C = 0$ ,  $V_{CE} = V_{CC}$