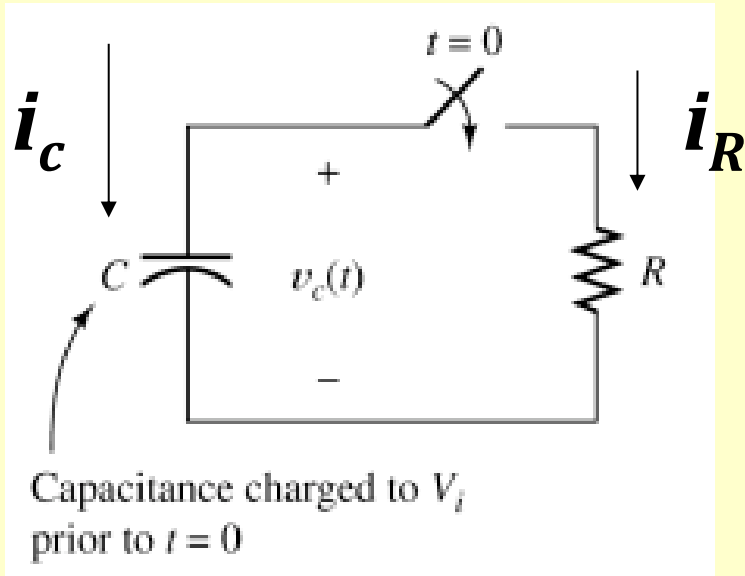


# **UNIT-1**

## **(Lecture-11)**

### **Solution of Network Equations**

## Discharge of a Capacitance through a Resistance



$$\sum i = 0, \quad i_C + i_R = 0$$

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0$$

**Solving the above equation with the initial condition**

$$V_c(0) = V_i$$

## Discharge of a Capacitance through a Resistance

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0$$

$$s = \frac{-1}{RC}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0$$


$$v_C(t) = Ke^{-t/RC}$$

$$\begin{aligned} v_C(0^+) &= V_i \\ &= Ke^{0/RC} \\ &= K \end{aligned}$$


$$v_C(t) = Ke^{st}$$

$$RCKse^{st} + Ke^{st} = 0$$

$$v_C(t) = V_i e^{-t/RC}$$

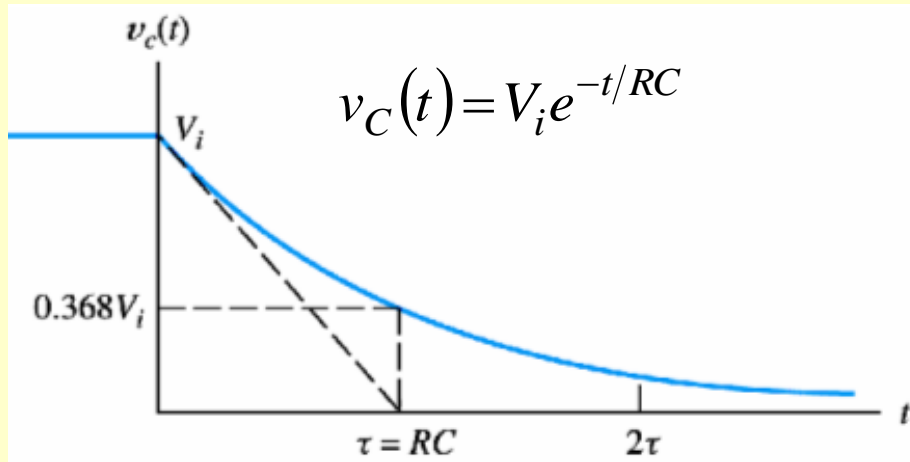

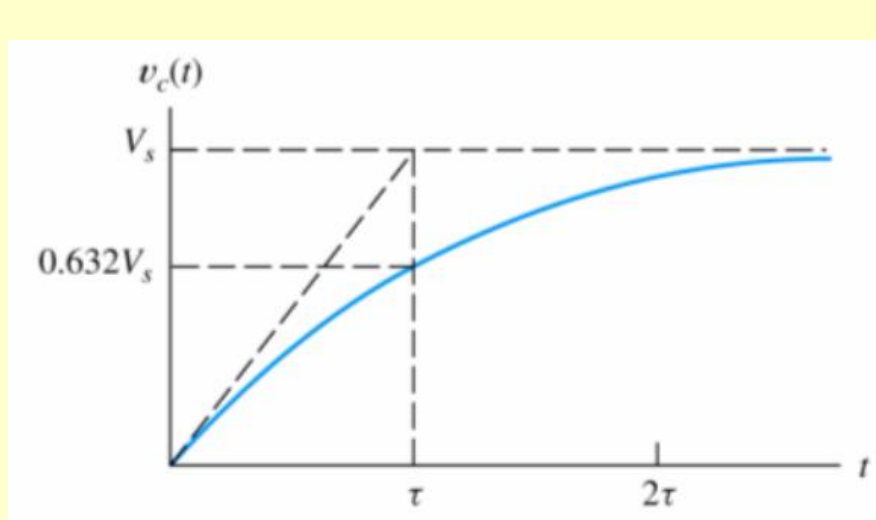
**Exponential decay waveform**  
**RC is called the time constant.**  
**At time constant, the voltage is 36.8% of the initial voltage.**




$$v_C(t) = V_i(1 - e^{-t/RC})$$

**Exponential rising waveform**  
**RC is called the time constant.**  
**At time constant, the voltage is 63.2% of the initial voltage.**


## RC CIRCUIT

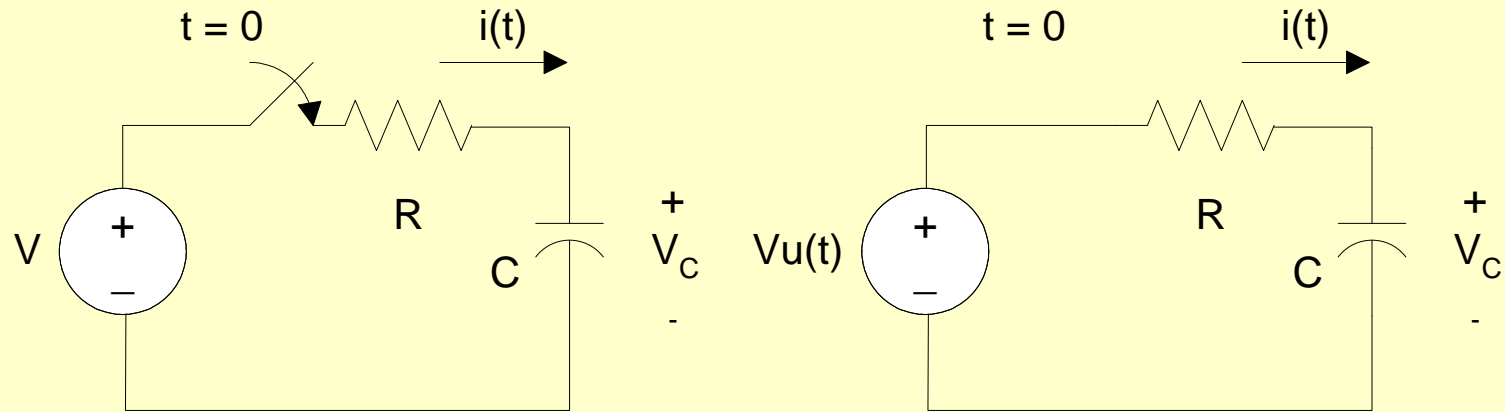

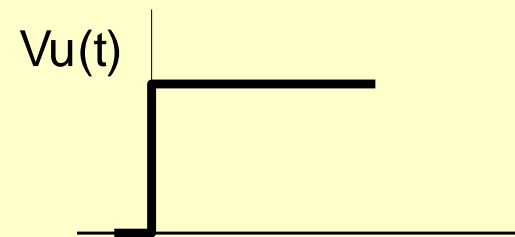for  $t = 0^-$ ,  $i(t) = 0$   
 $u(t)$  is voltage-step function




## RC CIRCUIT

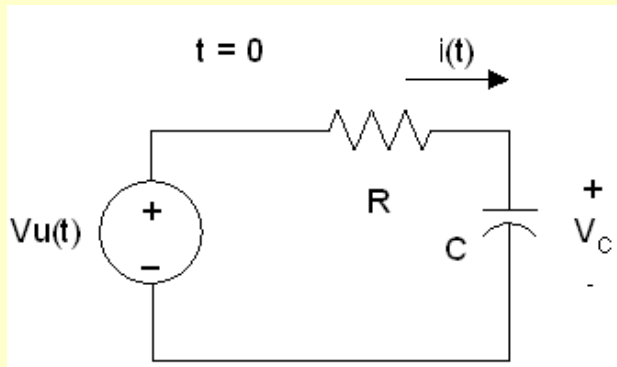

$$i_R = i_C$$

$$i_R = \frac{v_u(t) - v_C}{R}, \quad i_C = C \frac{dv_C}{dt}$$
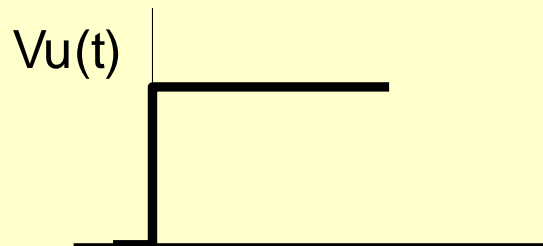
$$RC \frac{dv_C}{dt} + v_C = V, \quad v_u(t) = V \text{ for } t \geq 0$$




**Solving the differential equation**

## Complete Response

Complete response



= natural response + forced response

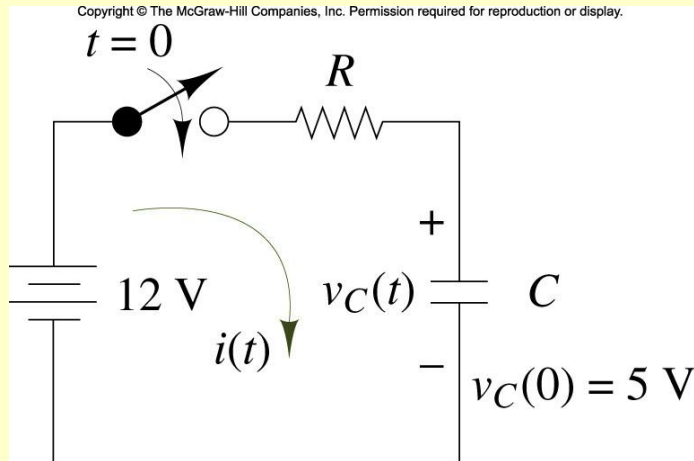- Natural response (source free response) is due to the initial condition
- Forced response is the due to the external excitation.



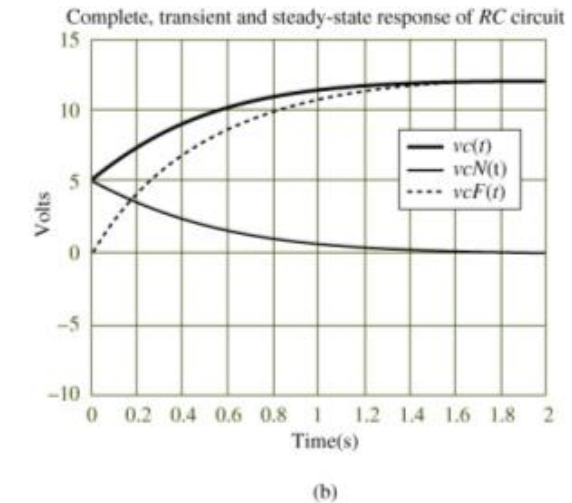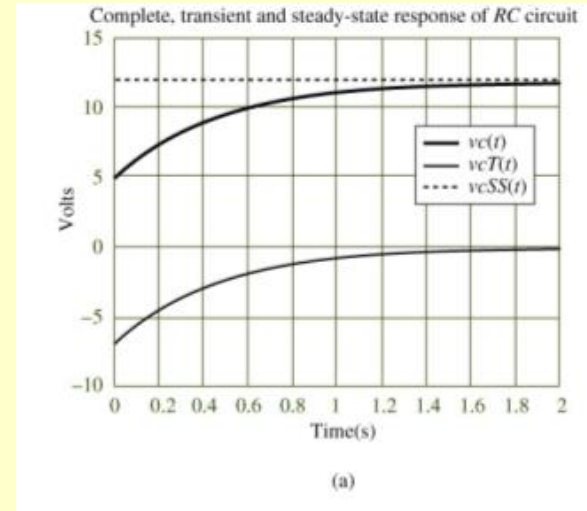
5.17, 5.18

- Complete, transient and steady state response
- Complete, natural, and forced responses of the circuit





# Circuit Analysis for RC Circuit

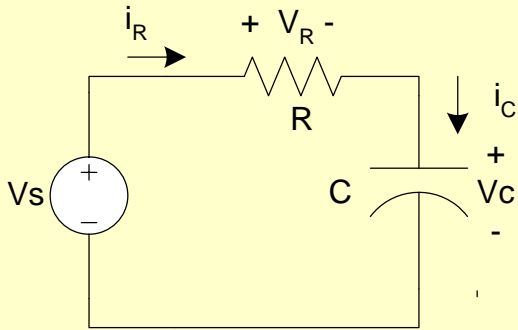

**Apply KCL**

$$i_R = i_C$$

$$i_R = \frac{v_s - v_R}{R}, i_C = C \frac{dv_C}{dt}$$

$$\frac{dv_C}{dt} + \frac{1}{RC} v_R = \frac{1}{RC} v_s$$

**$v_s$  is the source applied.**

## Solution to First Order Differential Equation

**Consider the general Equation**

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

**Let the initial condition be  $x(t = 0) = x(0)$ , then we solve the differential equation:**

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

**The complete solution consist of two parts:**

- **the homogeneous solution (natural solution)**
- **the particular solution (forced solution)**

## The Natural Response

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

Setting the excitation  $f(t)$  equal to zero,

$$\tau \frac{dx_N(t)}{dt} + x_N(t) = 0 \text{ or } \frac{dx_N(t)}{dt} = -\frac{x_N(t)}{\tau}$$

$$x_N(t) = \alpha e^{-t/\tau}$$

It is called the natural response.

## The Forced Response

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

Setting the excitation  $f(t)$  equal to  $F$ , a constant for  $t \geq 0$

$$\tau \frac{dx_F(t)}{dt} + x_F(t) = K_S F$$

$$x_F(t) = K_S F \text{ for } t \geq 0$$

It is called the forced response.

## The Complete Response

**Consider the general Equation      Solve for  $\alpha$ ,**

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

*for  $t = 0$*

$$x(t = 0) = x(0) = \alpha + x(\infty)$$

$$\alpha = x(0) - x(\infty)$$

**The complete response is:**

- the natural response +
- the forced response

$$\begin{aligned} x &= x_N(t) + x_F(t) \\ &= \alpha e^{-t/\tau} + K_S F \\ &= \alpha e^{-t/\tau} + x(\infty) \end{aligned}$$

**The Complete solution:**

$$x(t) = [x(0) - x(\infty)] e^{-t/\tau} + x(\infty)$$

$[x(0) - x(\infty)] e^{-t/\tau}$  called transient response

$x(\infty)$  called steady state response