


UNIT-1

(Lecture-12)

Examples

Example

Initial condition $V_C(0) = 0V$

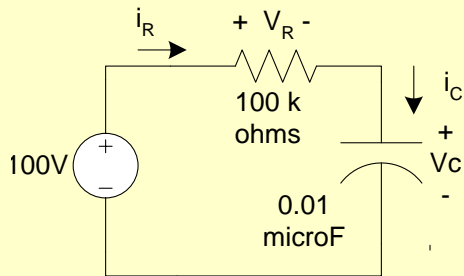


$$i_R = i_C$$

$$i_R = \frac{v_s - v_C}{R}, i_C = C \frac{dv_C}{dt}$$

$$RC \frac{dv_C}{dt} + v_C = v_s$$

$$10^5 \times 0.01 \times 10^{-6} \frac{dv_C}{dt} + v_C = 100$$

$$10^{-3} \frac{dv_C}{dt} + v_C = 100$$

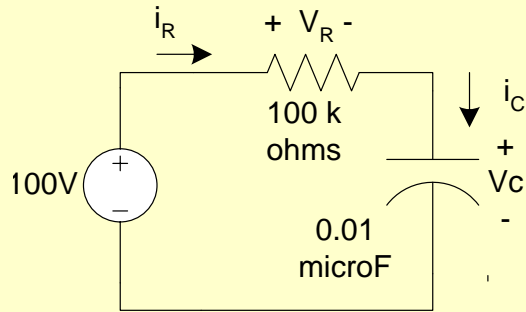

Initial condition $V_C(0) = 0V$

$$10^{-3} \frac{dv_C}{dt} + v_C = 100$$

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

and

$$\begin{aligned} x &= x_N(t) + x_F(t) \\ &= \alpha e^{-t/\tau} + K_S F \\ &= \alpha e^{-t/\tau} + x(\infty) \end{aligned}$$

$$v_C = 100 + A e^{-\frac{t}{10^{-3}}}$$

$$\text{As } v_C(0) = 0, 0 = 100 + A$$

$$A = -100$$

$$v_C = 100 - 100 e^{-\frac{t}{10^{-3}}}$$

Energy stored in capacitor

$$p = vi = Cv \frac{dv}{dt}$$


$$\int_{t_0}^t p dt = \int_{t_0}^t Cv \frac{dv}{dt} dt = C \int_{t_0}^t v dv$$

$$= \frac{1}{2} C \left\{ [v(t)]^2 - [v(t_0)]^2 \right\}$$

If the zero-energy reference is selected at t_0 , implying that the capacitor voltage is also zero at that instant, then

$$w_c(t) = \frac{1}{2} Cv^2$$

RC CIRCUIT

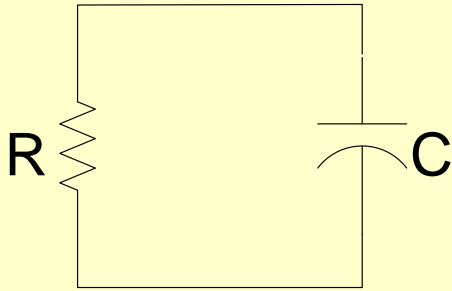

Power dissipation in the resistor is:

$$p_R = V^2/R = (V_o^2/R) e^{-2t/RC}$$

Total energy turned into heat in the resistor

$$W_R = \int_0^{\infty} p_R dt = \frac{V_o^2 \int_0^{\infty} e^{-2t/RC} dt}{R}$$


$$= V_o^2 R \left(-\frac{1}{2RC} \right) e^{-2t/RC} \Big|_0^{\infty}$$

$$= \frac{1}{2} C V_o^2$$

RL CIRCUITS

Initial condition


$$i(t = 0) = I_0$$

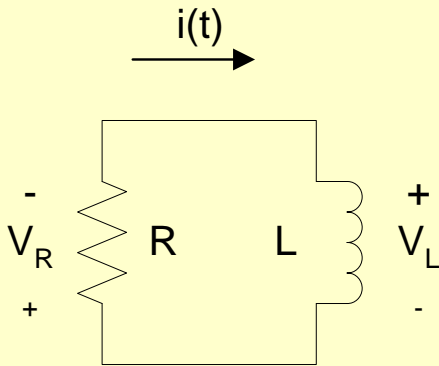

$$v_R + v_L = 0 = Ri + L \frac{di}{dt}$$

$$\frac{L}{R} \frac{di}{dt} + i = 0$$

Solving the differential equation

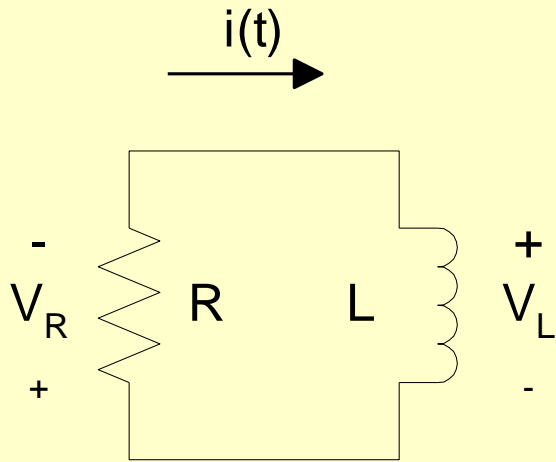RL CIRCUITS

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

$$\frac{di}{i} = -\frac{R}{L}dt, \quad \int_{I_o}^{i(t)} \frac{di}{i} = \int_0^t -\frac{R}{L}dt$$

$$\ln i \Big|_{I_o}^i = -\frac{R}{L}t \Big|_0^t$$

$$\ln i - \ln I_o = -\frac{R}{L}t$$

$$i(t) = I_o e^{-Rt/L}$$

Initial condition


$$i(t = 0) = I_o$$

RL CIRCUIT

Power dissipation in the resistor is:

$$p_R = i^2 R = I_o^2 e^{-2Rt/L} R$$


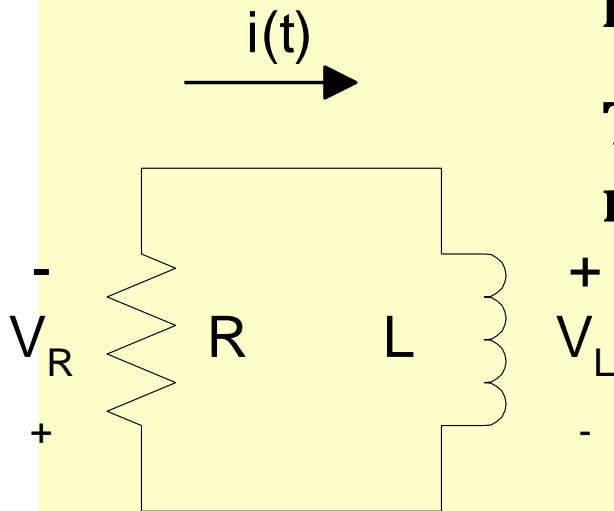
Total energy turned into heat in the resistor



$$\begin{aligned} W_R &= \int_0^{\infty} p_R dt = I_o^2 R \int_0^{\infty} e^{-2Rt/L} dt \\ &= I_o^2 R \left(-\frac{L}{2R} \right) e^{-2Rt/L} \Big|_0^{\infty} \\ &= \frac{1}{2} L I_o^2 \end{aligned}$$

It is expected as the energy stored in the inductor is $\frac{1}{2} L I_o^2$

RL CIRCUIT

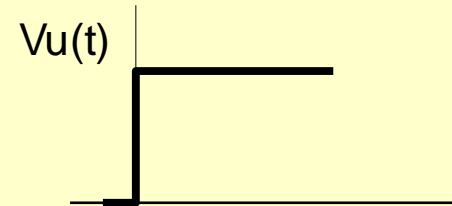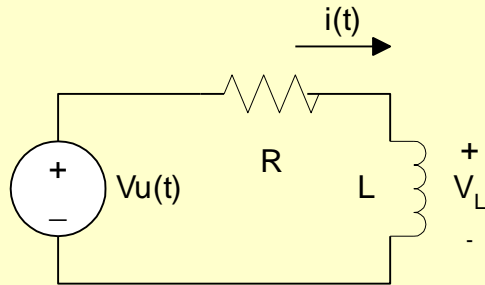

$$Ri + L \frac{di}{dt} = V$$

$$\frac{L di}{V - Ri} = dt$$

Integrating both sides,

$$-\frac{L}{R} \ln(V - Ri) = t + k$$

$$i(0^+) = 0, \text{ thus } k = -\frac{L}{R} \ln V$$

$$-\frac{L}{R} [\ln(V - Ri) - \ln V] = t$$

$$\frac{V - Ri}{V} = e^{-Rt/L} \quad \text{or}$$

$$i = \frac{V}{R} - \frac{V}{R} e^{-Rt/L}, \text{ for } t > 0$$

where L/R is the time constant

DC STEADY STATE

The steps in determining the forced response for *RL* or *RC* circuits with dc sources are:

- 1. Replace capacitances with open circuits.**
- 2. Replace inductances with short circuits.**
- 3. Solve the remaining circuit.**