

UNIT-1

(Lecture-9)

Introduction to Network Analysis

Transient Circuit Analysis

- Natural response and forced response,
- Transient response and steady state response for arbitrary inputs (DC and AC),
- Evaluation of time response both through classical and Laplace methods.

Solution to First Order Differential Equation

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

Let the initial condition be $x(t = 0) = x(0)$,
then we solve the differential equation:

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

The complete solution consists of two parts:

- the homogeneous solution (natural solution)
- the particular solution (forced solution)

The Natural Response

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

Setting the excitation $f(t)$ equal to zero,

$$\tau \frac{dx_N(t)}{dt} + x_N(t) = 0 \text{ or } \frac{dx_N(t)}{dt} = -\frac{x_N(t)}{\tau}, \frac{dx_N(t)}{x_N(t)} = -\frac{dt}{\tau}$$

$$\int \frac{dx_N(t)}{x_N(t)} = \int -\frac{dt}{\tau}, \quad x_N(t) = \alpha e^{-t/\tau}$$

It is called the natural response.

The Forced Response

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

Setting the excitation $f(t)$ equal to F , a constant for $t \geq 0$

$$\tau \frac{dx_F(t)}{dt} + x_F(t) = K_S F$$

$$x_F(t) = K_S F \text{ for } t \geq 0$$

It is called the forced response.

The Complete Response

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

for $t = 0$

Solve for α ,

$$x(t = 0) = x(0) = \alpha + x(\infty)$$

$$\alpha = x(0) - x(\infty)$$

The complete response is: the natural response + the forced response

The Complete solution: $x(t) = [x(0) - x(\infty)]e^{-t/\tau} + x(\infty)$


$[x(0) - x(\infty)]e^{-t/\tau}$ called transient response

$x = x_N(t) + x_F(t)$ $x(\infty)$ called steady state response


$$= \alpha e^{-t/\tau} + K_S F$$

$$= \alpha e^{-t/\tau} + x(\infty)$$

WHAT IS TRANSIENT RESPONSE

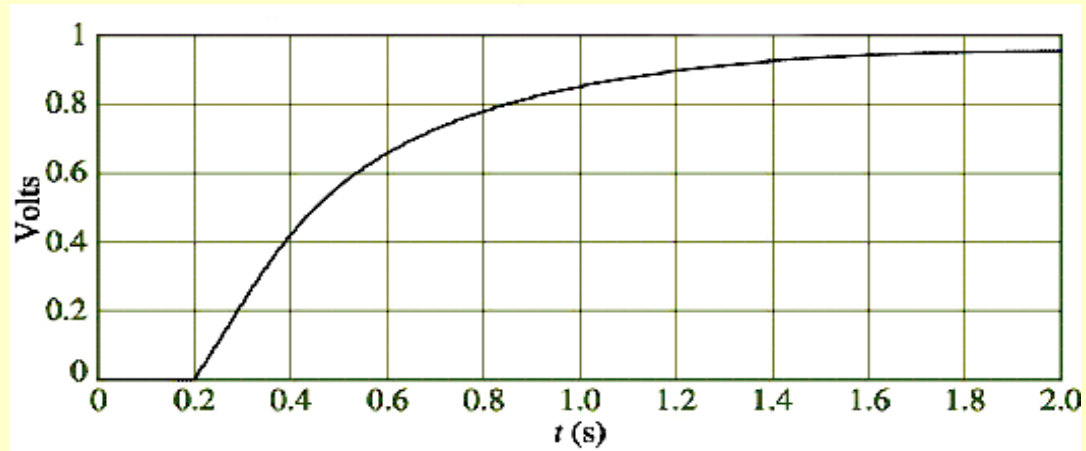

(a) Transient DC voltage

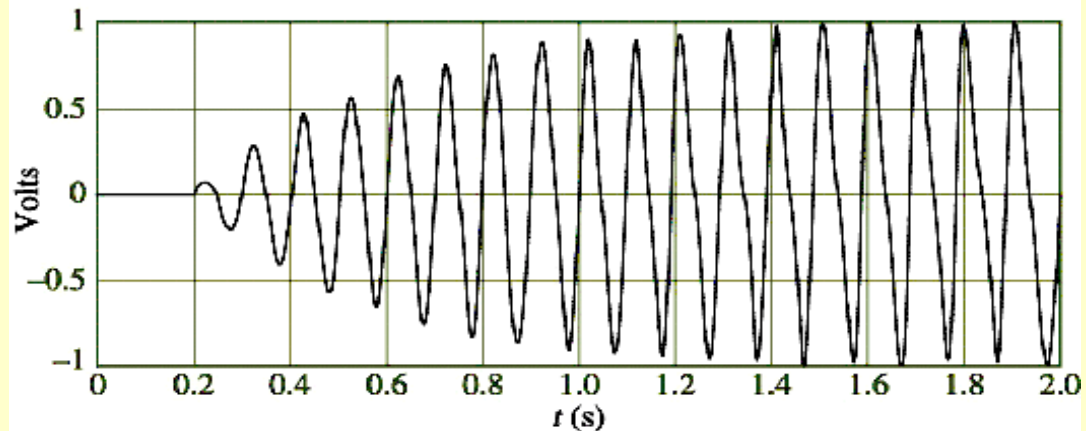

(b) Transient sinusoidal voltage

Why there is a transient response?



- The voltage across a capacitor cannot be changed instantaneously.

$$V_C(0^-) = V_C(0^+)$$

- The current across an inductor cannot be changed instantaneously.

$$I_L(0^-) = I_L(0^+)$$

Example

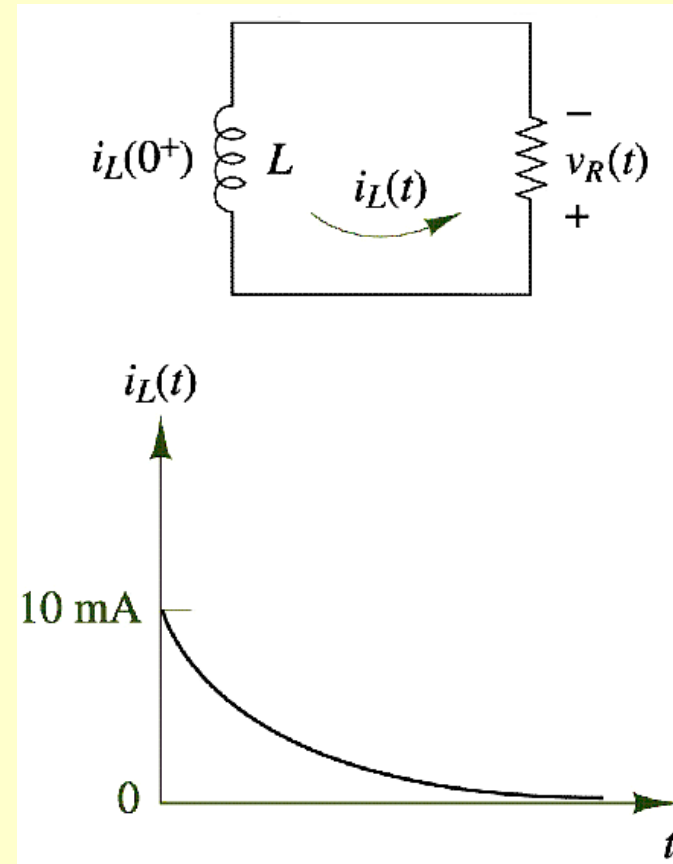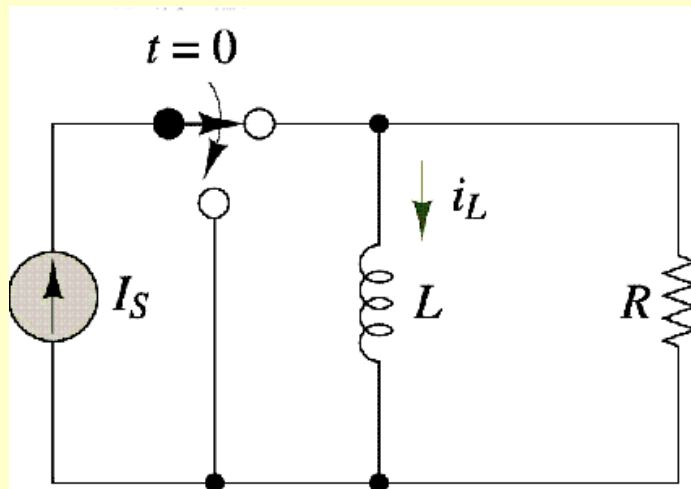

Transients Analysis

- 1. Solve first-order *RC* or *RL* circuits.**
- 2. Understand the concepts of transient response and steady-state response.**
- 3. Relate the transient response of first-order circuits to the time constant.**