

# UNIT-2


## (Lecture-9)

### Interconnection of Two Ports Parameter

# Interconnection Of Two Port Networks

Three ways that two ports are interconnected:


\* Parallel

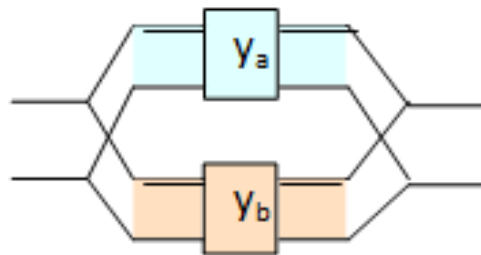

*Y parameters*

$$[y] = [y_a] + [y_b]$$


\* Series

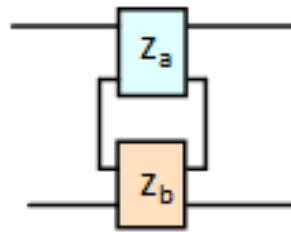

*Z parameters*

$$[z] = [z_a] + [z_b]$$

\* Cascade

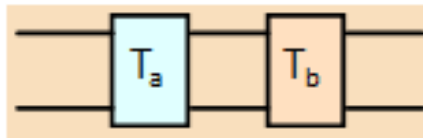


*ABCD parameters*

$$[T] = [T_a] [T_b]$$

**Interconnection Of Two Port Networks**

**Consider the following network:**

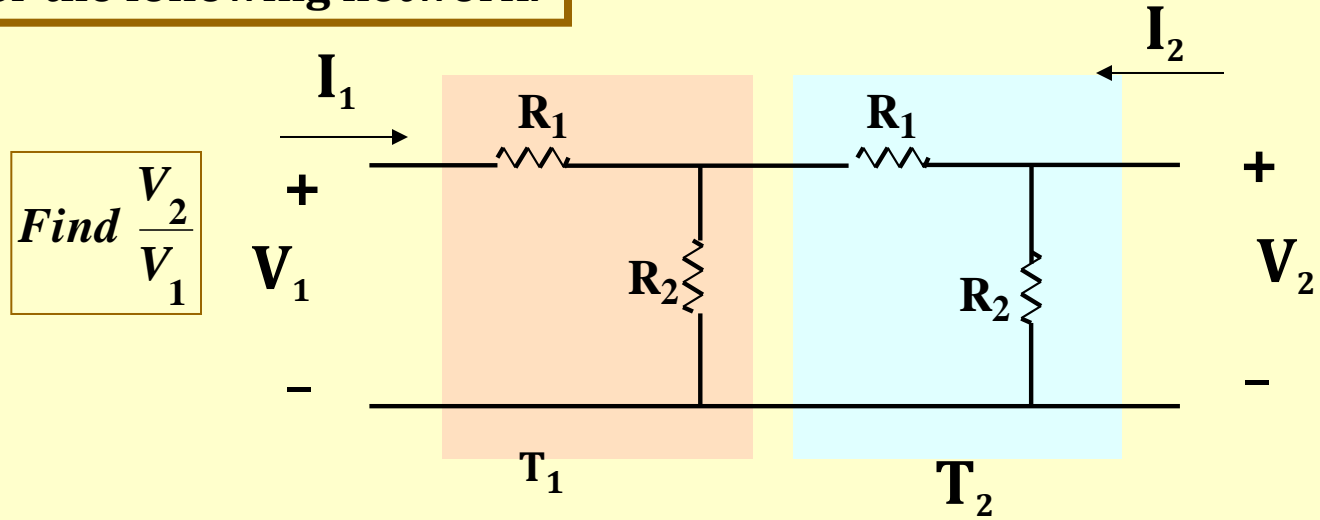

*Find*  $\frac{V_2}{V_1}$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ \frac{1}{R_2} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

## Interconnection Of Two Port Networks

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ 1 & R_2 \end{bmatrix} \begin{bmatrix} \frac{R_1 + R_2}{R_2} & R_1 \\ 1 & R_2 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Multiply out the first row:

$$V_1 = \left[ \left[ \left( \frac{R_1 + R_2}{R_2} \right)^2 + \frac{R_1}{R_2} \right] V_2 + \left[ \left( \frac{R_1 + R_2}{R_2} \right) R_1 + R_1 \right] (-I_2) \right]$$

Set  $I_2 = 0$  ( as in the diagram )

$$\frac{V_2}{V_1} = \frac{R_2^2}{R_1^2 + 3R_1R_2 + R_2^2}$$

Can be verified directly by solving the circuit