

UNIT-4

(Lecture-2)

Transfer Functions

Transfer Functions

The transfer formation is used to describe networks which have at least two ports. In general, the transfer function relates the transform of a quantity at one port to the transform of another quantity at another port. Thus transfer functions have the following possible forms

- I. The ratio of one voltage to another current or one current to another voltage; $Z(s)$ or $Y(s)$
- II. The ratio of one voltage to another voltage, or the voltage transfer function; $G(s)$
- III. The ratio of one current to another current or the current transfer function; $\alpha(s)$

Transfer Functions

In terms of the two port network , the output quantities are $V_2(s)$ and $I_2(s)$ and the input quantities are $V_1(s)$ and $I_1(s)$. Using these quantities there are only four basic transfer function for the two port networks and these are given as

1. Transfer impedance function; $Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$
2. Transfer admittance function; $Y_{21}(s) = \frac{I_2(s)}{V_1(s)}$
3. Voltage transfer function; $G_{21}(s) = \frac{V_2(s)}{V_1(s)}$
4. Current transfer function; $\alpha_{21}(s) = \frac{I_2(s)}{I_1(s)}$

Transfer Functions

The ratio of an input quantity to an output quantity is termed as the 'Inverse transfer function' i.e.,

1. The inverse transfer impedance function; $Z_{12}(s) = \frac{V_1(s)}{I_2(s)}$
2. The inverse transfer admittance function; $Y_{12}(s) = \frac{I_1(s)}{V_2(s)}$
3. The inverse voltage transfer function; $G_{12}(s) = \frac{V_1(s)}{V_2(s)}$
4. The inverse current transfer function; $\alpha_{12}(s) = \frac{I_1(s)}{I_2(s)}$