


UNIT-5

(Lecture-2)

High-Pass RC Network

A High-Pass RC Network

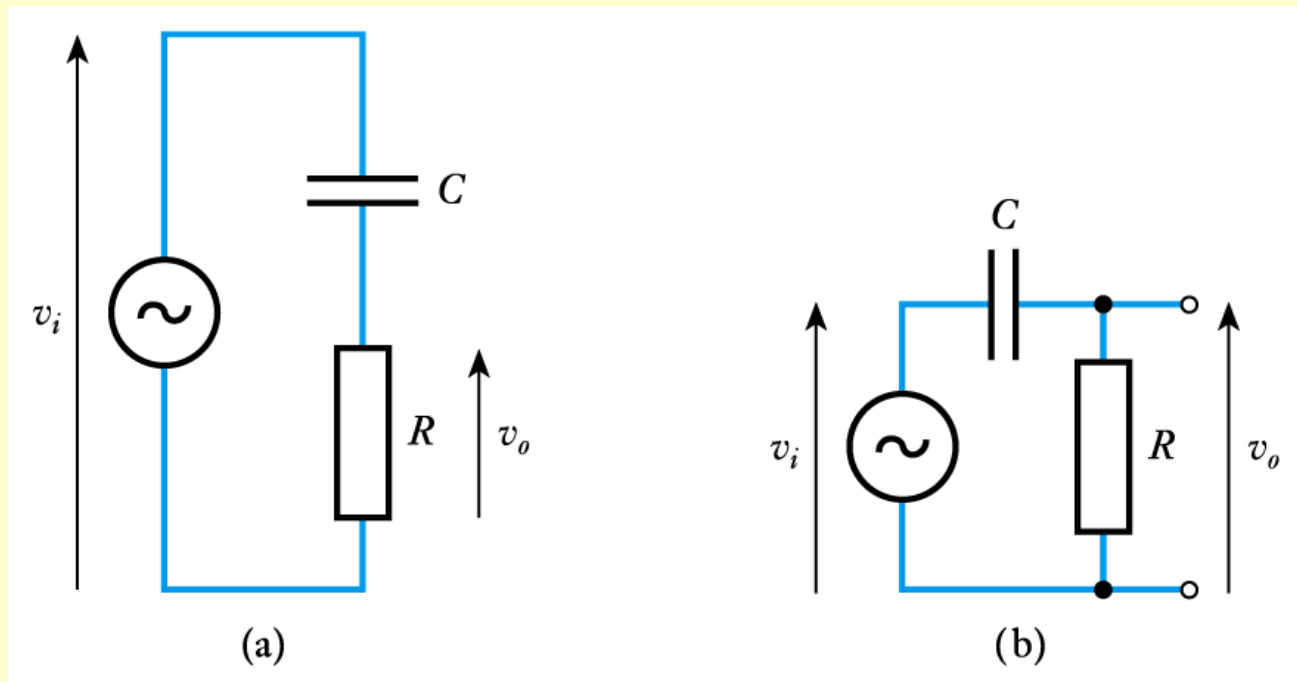
- Consider the following circuit
 - which is shown re-drawn in a more usual form



- Clearly the transfer function is

$$\frac{v_o}{v_i} = \frac{\mathbf{Z}_R}{\mathbf{Z}_R + \mathbf{Z}_C} = \frac{R}{R - j\frac{1}{\omega C}} = \frac{1}{1 - j\frac{1}{\omega CR}}$$

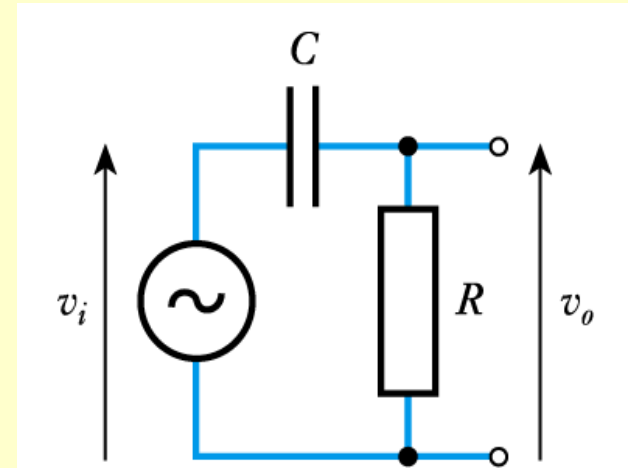- At high frequencies
 - ω is large, voltage gain ≈ 1
- At low frequencies
 - ω is small, voltage gain $\rightarrow 0$




- Since the denominator has real and imaginary parts, the *magnitude* of the voltage gain is

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1^2 + \left(\frac{1}{\omega CR}\right)^2}}$$

- When $1/\omega CR = 1$

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

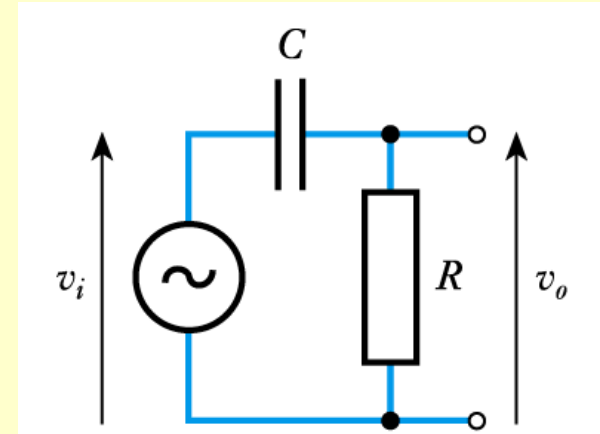- This is a halving of power, or a fall in gain of 3 dB



- The half power point is the **cut-off frequency** of the circuit

- the angular frequency ω_c at which this occurs is given by

$$\frac{1}{\omega_c CR} = 1$$

$$\omega_c = \frac{1}{CR} = \frac{1}{T} \text{ rad/s}$$

- where T is the time constant of the CR network. Also

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi CR} \text{ Hz}$$