

# **UNIT-5**

## **(Lecture-3)**

### **High-Pass RC Network (Phasor Diagram)**

- Substituting  $\omega = 2\pi f$  and  $CR = 1/2\pi f_c$  in the earlier equation gives

$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{1}{\omega CR}} = \frac{1}{1 - j\frac{1}{(2\pi f)\left(\frac{1}{2\pi f_c}\right)}} = \frac{1}{1 - j\frac{f_c}{f}}$$

- This is the general form of the gain of the circuit
- It is clear that both the *magnitude* of the gain and the *phase angle* vary with frequency

- Consider the behaviour of the circuit at different frequencies:
- **When  $f \gg f_c$** 
  - $f_c/f \ll 1$ , the voltage gain  $\approx 1$


- **When  $f = f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{f_c}{f}} = \frac{1}{1 - j} = \frac{1 \times (1 + j)}{(1 - j) \times (1 + j)} = \frac{(1 + j)}{2} = 0.5 + 0.5j$$

- **When  $f \ll f_c$**

$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{f_c}{f}} \approx \frac{1}{-j\frac{f_c}{f}} = j\frac{f}{f_c}$$

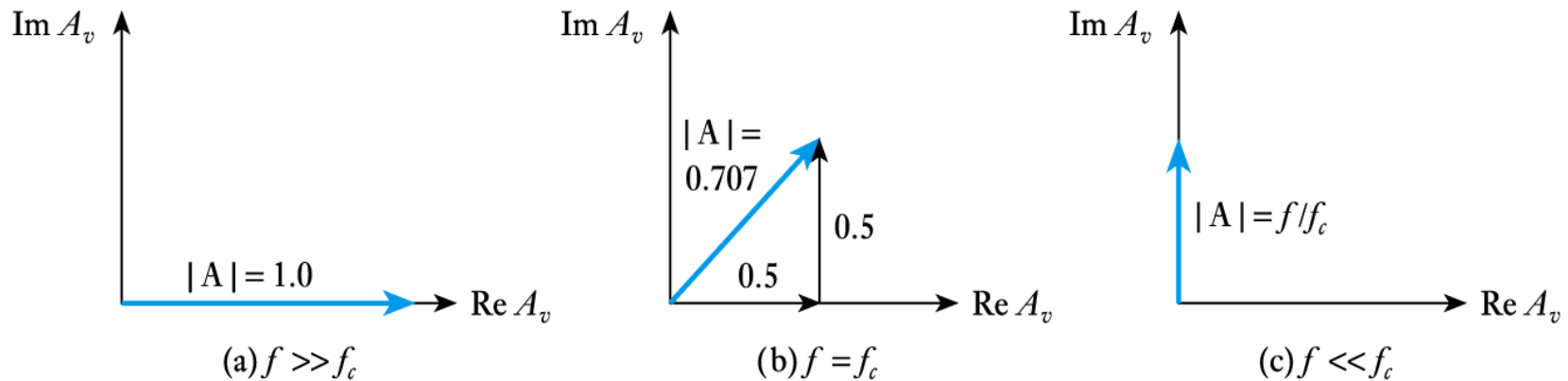- The behaviour in these three regions can be illustrated using phasor diagrams



- At *low* frequencies the gain is linearly related to frequency. It falls at -6dB/octave (-20dB/decade)