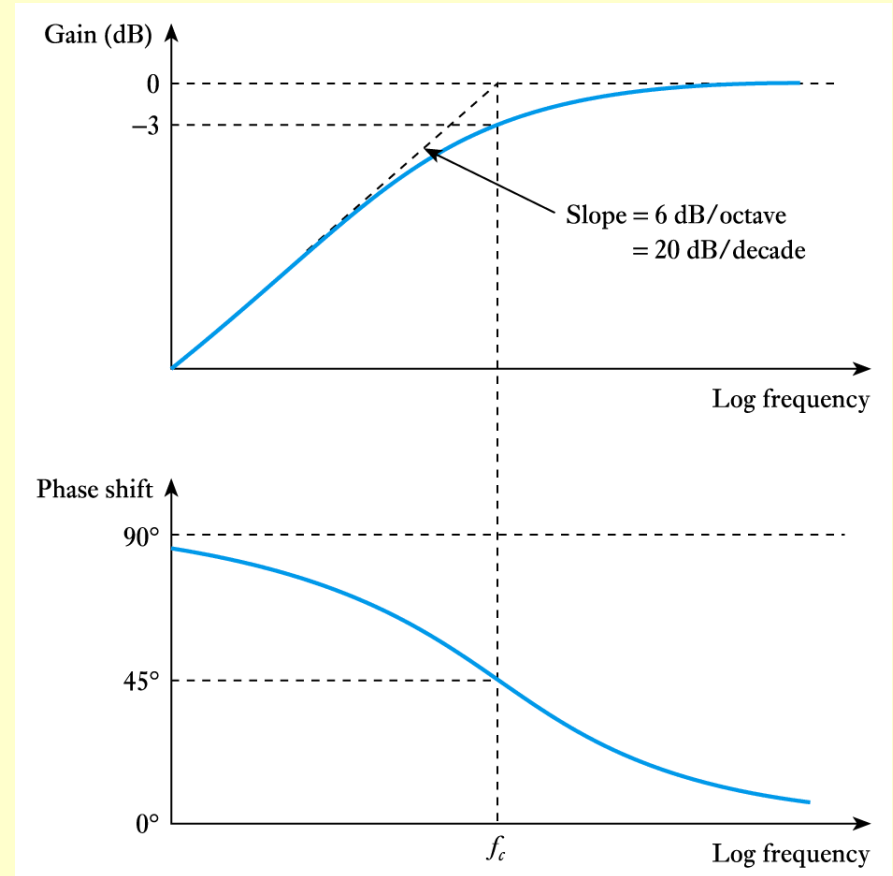


UNIT-5

(Lecture-4)

Frequency Response of High-Pass Network

- Frequency response of the high-pass network
 - the gain response has two *asymptotes* that meet at the cut-off frequency
 - figures of this form are called **Bode diagrams**




A Low-Pass RC Network

- Transposing the C and R gives

$$\frac{v_o}{v_i} = \frac{\mathbf{Z}_C}{\mathbf{Z}_R + \mathbf{Z}_C} = \frac{-j\frac{1}{\omega C}}{R - j\frac{1}{\omega C}} = \frac{1}{1 + j\omega CR}$$

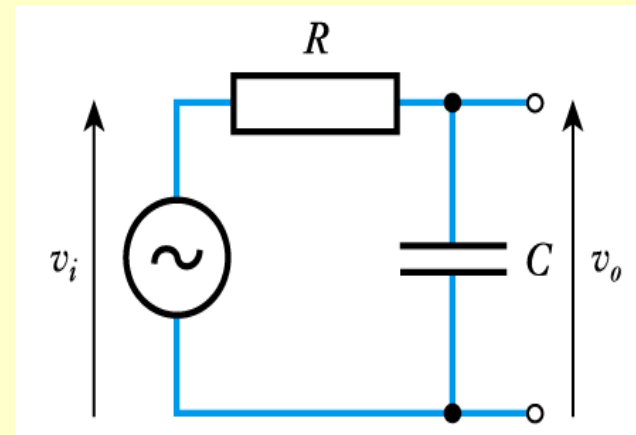
- At high frequencies
 - ω is large, voltage gain $\rightarrow 0$
- At low frequencies
 - ω is small, voltage gain ≈ 1



A Low-Pass RC Network

- A similar analysis to before gives

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$

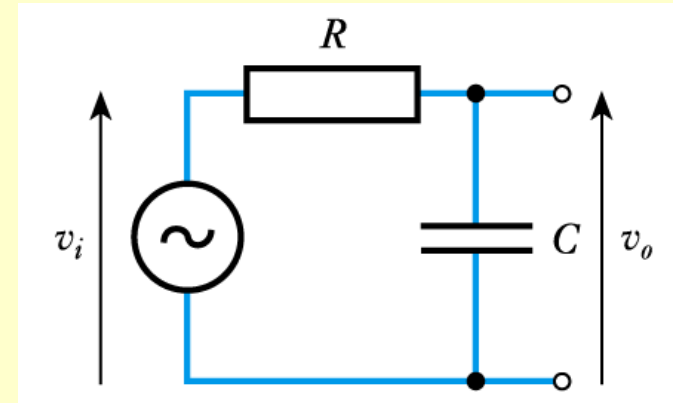

- Therefore when, when $\omega CR = 1$

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

- Which is the cut-off frequency