
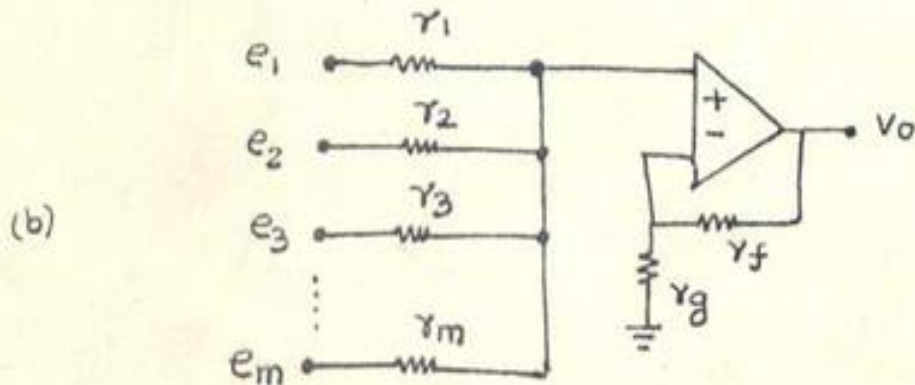


UNIT-5

(Lecture-8)

OP-AMP CIRCUITS

Weighted Summers : Active synthesis invariably requires circuits capable of performing summation of analog voltages . Realisations of inverting , noninverting and generalised summers are shown in Fig. 14 (a)-(c).

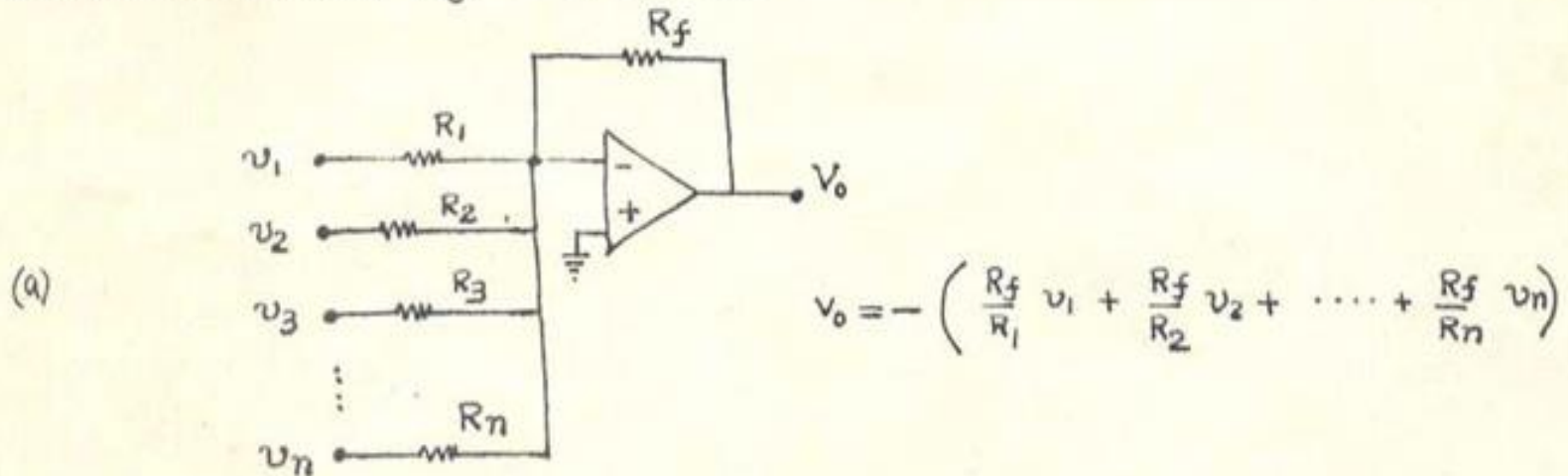

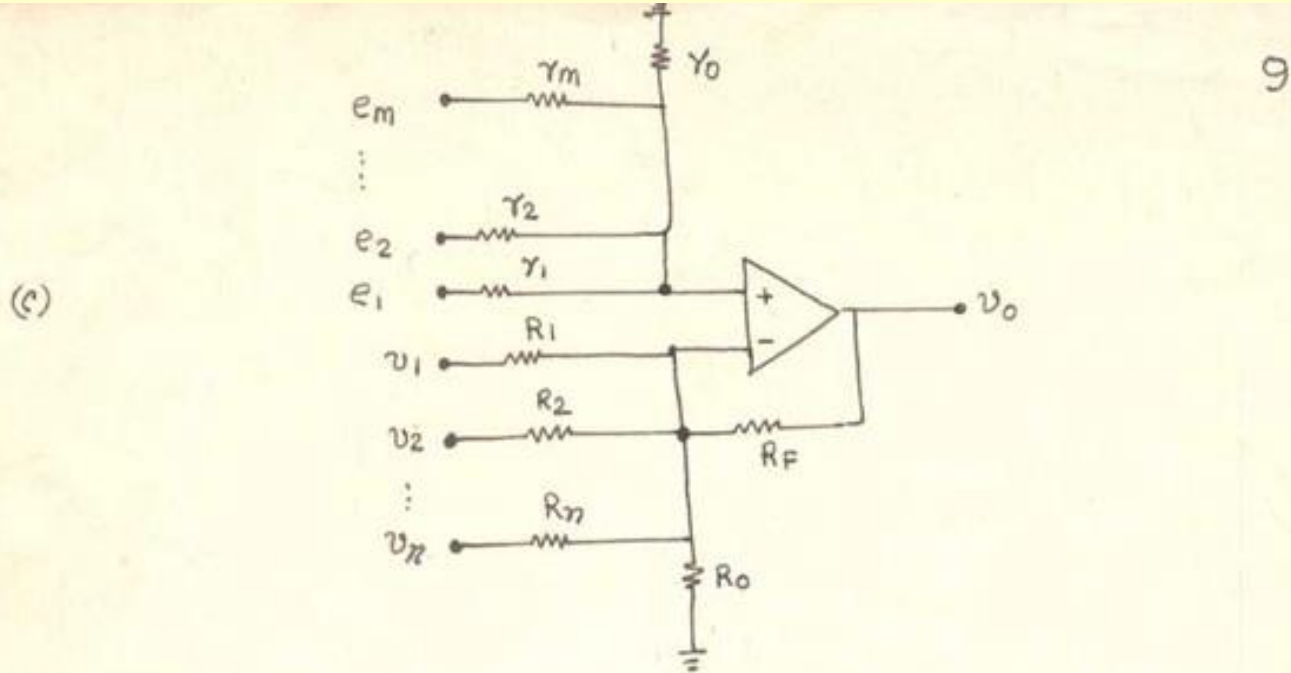


Fig. 14 Realisation of various summers (a) inverting summer (b) noninverting summer (c) generalised weighted summer.

3. Miscellaneous Circuits and Techniques :

In the following some interesting circuits and techniques are presented which can be understood and analysed on the basis of understanding of the building blocks discussed in the previous section.

discussed in the previous section.

3.1 capacitance multiplier :

The given circuit has

$$Z_{in} = \frac{v_1}{i_1} = \frac{1}{\beta C \left(1 + \frac{R_2}{R_1}\right)}$$

thus, behaving as an

equivalent capacitance $C_{eq} = C \left(1 + \frac{R_2}{R_1}\right)$

This circuit is useful in creating artificially large values of capacitances while using low-valued C which is normally available.

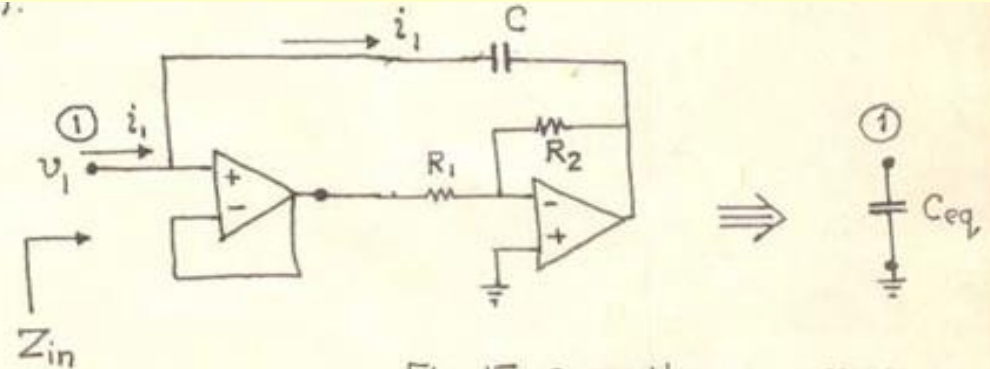


Fig.15 capacitance multiplier

3.2 Inductance Simulator :

The circuit has

$$Z_{in} = R_1 + \beta C R_1 R_2$$

thus, representing an inductance

$L_{eq} = C R_1 R_2$ Henries with quality factor equal to $Q_{eq} = \frac{\omega L_{eq}}{R_{eq}} = \omega C R_2$

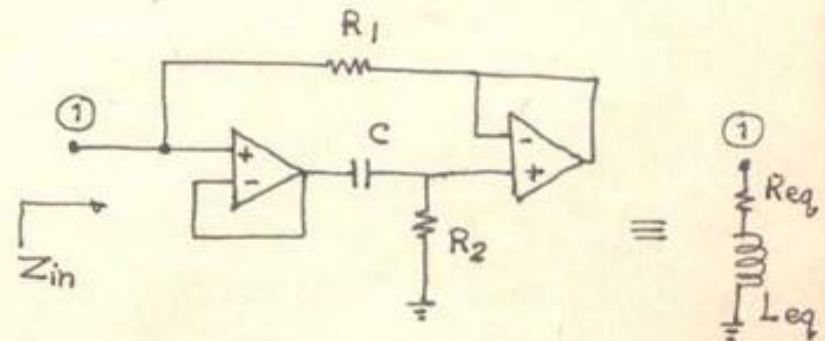


Fig. 16

3.3 Non inverting Integrator :

Although Inverting integrator followed by an inverting amplifier gives noninverting integrator, this approach needs two op-amps. A circuit which does this job with just one op-amp is Deboo's integrator shown here. Analysis gives

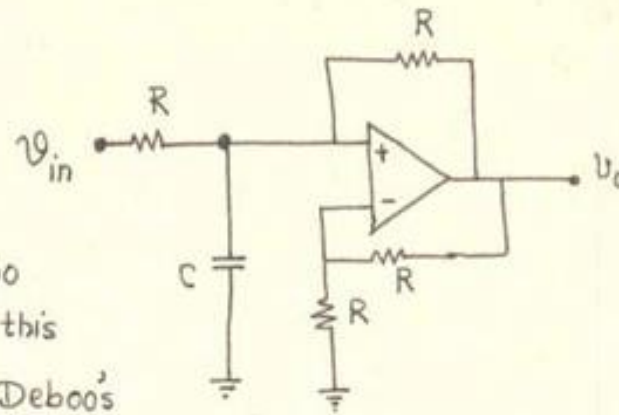


Fig. 17 Deboo's integrator

$$V_o(t) = +\frac{2}{CR} \int V_{in}(t) dt \quad \text{or} \quad \frac{V_o(s)}{V_i(s)} = +\frac{2}{sCR}$$

3.4 Noninverting Differentiator :

The accompanying circuit by proposed by Horrocks. Analysis shows

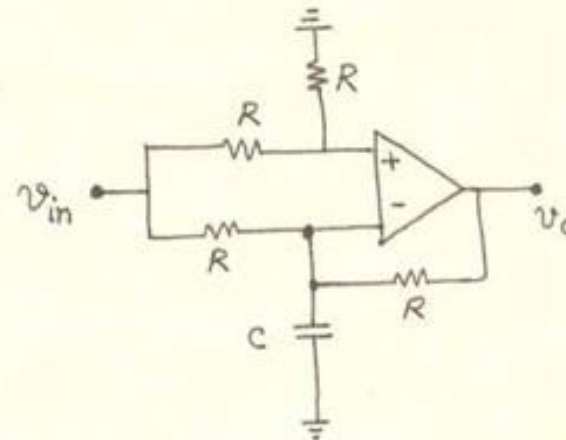


Fig. 18 Horrocks' differentiator

$$V_o(t) = \frac{CR}{2} \frac{dV_{in}(t)}{dt}$$

or equivalently

$$\frac{V_o(s)}{V_i(s)} = +\frac{sCR}{2}$$