

# **UNIT-5**


## **(Lecture-9)**

### **OP-AMP CIRCUITS**


3.5 Inverse function Generation :

Fig. 19 (a) and (b) show an interesting concept according to which if a network having  $e_o = T e_i$  is put in the feedback path of an op-amp the overall circuit generates  $v_o = T^{-1} v_{in}$

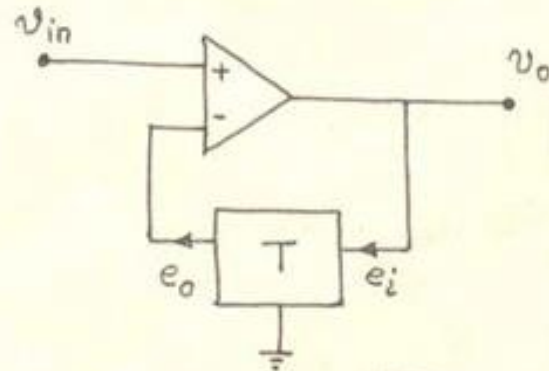
As an example in Fig 19 (c) we show by putting an integrator in the feedback path, one obtains a differentiator.



(a)

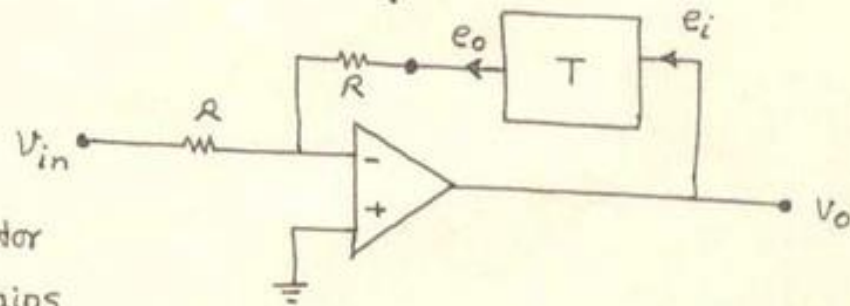

(b)

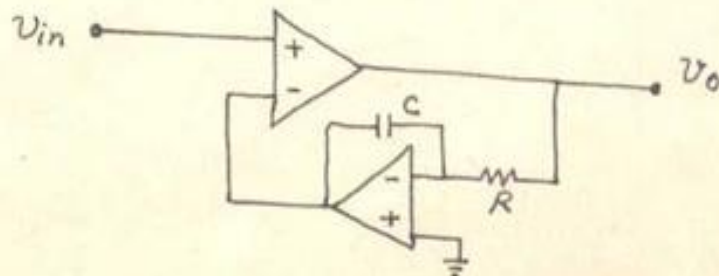

(c)

- Fig. 19 (a)  $v_o = T^{-1} v_{in}$   
 (b)  $v_o = -T^{-1} v_{in}$   
 (c)  $v_o = -sCR v_{in}$

The following fig. shows how this idea can be implemented on a given single


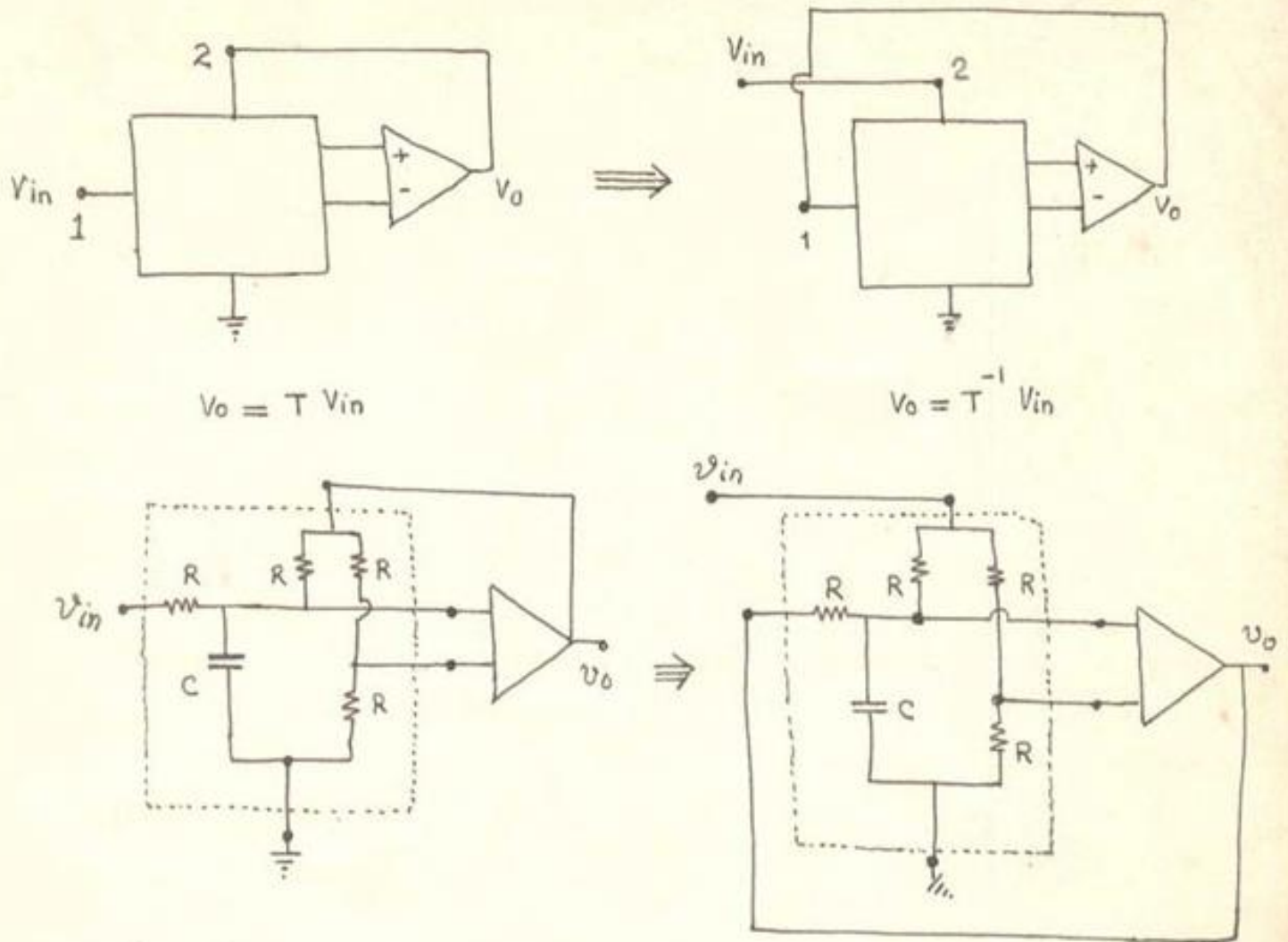


Fig. 20


op-amp circuit without requiring any additional op-amp. As an example, Deboo's integrator and Horrocks differentiator are shown to be derivable from each other.
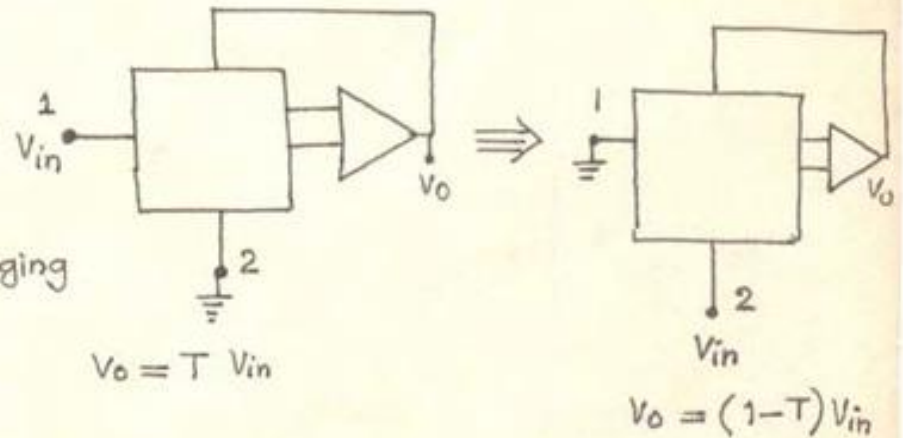
### 3.6 Complementary function generation:

In some cases one requires to generate a complementary function  $(1-T)$  starting from a given function  $T$  (relating  $V_o$  and  $V_{in}$ ). This can be accomplished by simply interchanging input and ground terminals as shown in Fig. 21



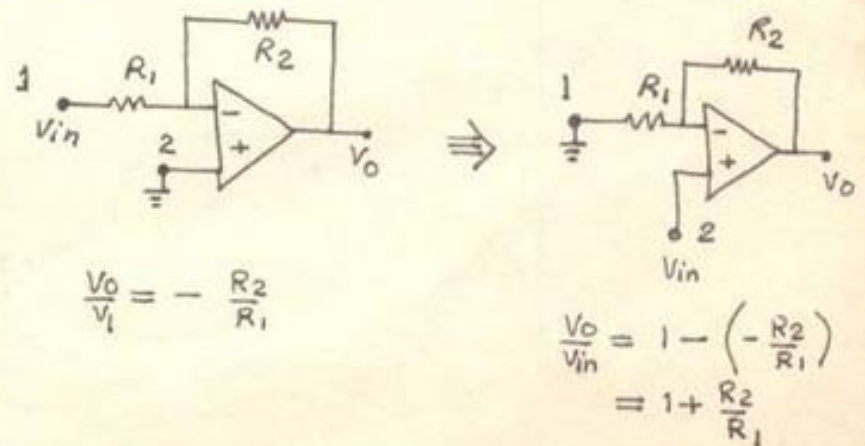Note that inverting amplifier and non-inverting amplifier can be seen to be related to each other by this transformation.



An important application of this transformation is in deriving a notch filter circuit starting from a bandpass circuit and vice versa.

Fig. 21 The complementary transformation (Hilberman's Theorem)