Combinational Logic: Combinational circuits, analysis procedure & design procedure Lecture 1

Dronacharya group of institutions

# **Combinational v.s Sequential**

### Circuits

- Logic circuits may be combinational or sequential Combinational circuits:
- Consist of logic gates only.
- Outputs are determined from the present values of inputs.
- Operations can be specified by a set of Boolean functions. **Sequential circuits:**
- Consist of logic gates and storage elements
- Outputs are a function of the inputs and the state of the storage elements.
- Depend not only on present inputs, but also on past values
- Circuit behavior must be specified by a time sequence of inputs and internal states.

# **Combinational Circuit**

A combinational circuit consists of

- Input variables
- Logic gates
- Output variables
- Block diagram of Combinational Circuit



# **Combinational Circuit**

- Each input and output variable is a binary signal Represent logic 1 and logic 0.
- There are 2 n possible binary input combinations for n input variable.
- Only one possible output value for each possible input combination.
- Can be specified with a truth table.
- Can also be described by m Boolean functions, one for each output variable.
- Each output function is expressed in terms of n input variables.

# **Analysis Procedure**

- Analysis: determine the function that the circuit implements
  - Often start with a given logic diagram
- The analysis can be performed by
  - Manually finding Boolean functions
  - Manually finding truth table
  - Using a computer simulation program
- First step: make sure that circuit is combinational
  - Without feedback paths or memory elements
- Second step: obtain the output Boolean functions or the truth table

### **Output Boolean Functions**

- Step 1:
- Label all gate outputs that are a function of input variables.
- Determine Boolean functions for each gate output.



 $F_2 = AB + AC + BC$  $T_1 = A + B + C$  $T_2 = ABC$ 

### **Output Boolean Functions**

- Step 2:
- Label the gates that are a function of input variables and previously labeled gates.
- Find the Boolean function for these gates





### **Output Boolean Functions**

- Step 3:
- Obtain the output Boolean function in term of input variables.
- By repeated substitution of previously defined functions.

 $F_{1} = T_{3} + T_{2} = F'_{2} T_{1} + ABC$ = (AB + AC + BC) ' (A + B + C) + ABC = (A' + B')(A' + C')(B' + C') (A + B + C) + ABC = (A' + B'C')(AB' + AC' + BC' + B'C) + ABC = A' BC' + A' B'C + AB'C' + ABC

# **Truth Table**

To obtain the truth table from the logic diagram:

1. Determine the number of input variables.

For n inputs:

- 2 n possible combinations
- List the binary numbers from 0 to 2 n-1 in a table
- 2. Label the outputs of selected gates.
- 3. Obtain the truth table for the outputs of those gates that are a function of the input variables only.
- 4. Obtain the truth table for those gates that are a function of previously defined variables at step 3.
  - Repeatedly until all outputs are determined

# **Design Procedure**

Design procedure:

- Input: the specification of the problem
- Output: the logic circuit diagram (or Boolean functions)
- Step 1: determine the required number of inputs and outputs from the specification.
- Step 2: derive the truth table that defines the required relationship between inputs and outputs.
- Step 3: obtain the simplified Boolean function for each output as a function of the input variables.
- Step 4: draw the logic diagram and verify the correctness of the design.

# **Code Conversion Example**

- Convert from BCD code to Excess-3 code.
- The 6 input combinations not listed are don't cares.
- These values have no meaning in BCD.
- We can arbitrary assign them to 1 or o.

| Input BCD |   |   |   | Output Excess-3 Code |   |   |   |
|-----------|---|---|---|----------------------|---|---|---|
| Α         | В | С | D | w                    | x | у | z |
| 0         | 0 | 0 | 0 | 0                    | 0 | 1 | 1 |
| 0         | 0 | 0 | 1 | 0                    | 1 | 0 | 0 |
| 0         | 0 | 1 | 0 | 0                    | 1 | 0 | 1 |
| 0         | 0 | 1 | 1 | 0                    | 1 | 1 | 0 |
| 0         | 1 | 0 | 0 | 0                    | 1 | 1 | 1 |
| 0         | 1 | 0 | 1 | 1                    | 0 | 0 | 0 |
| 0         | 1 | 1 | 0 | 1                    | 0 | 0 | 1 |
| 0         | 1 | 1 | 1 | 1                    | 0 | 1 | 0 |
| 1         | 0 | 0 | 0 | 1                    | 0 | 1 | 1 |
| 1         | 0 | 0 | 1 | 1                    | 1 | 0 | 0 |

### **Maps for Code Converter**

• The six don't care minterms (10~15) are marked with X.



### **Maps for Code Converter**



#### **Logic Diagram for the Converter**

- There are various possibilities for a logic diagram that implements a circuit.
- A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps.
- The expressions may be manipulated algebraically to use common gates for two or more outputs.

• Reduce tł

z = D'y = CD + C' D' = CD + (C + D) ' x = B'C + B'D + BC' D' = B' (C + D) + BC' D' = B' (C + D) + B(C + D)' W = A + BC + BD = A + B(C + D)

#### **Logic Diagram for the Converter**

