

Asynchronous Sequential Logic

LECTURE 4


- **Circuits With Latches**
- **Design Procedure**

Dronacharya Group of Institutions

Circuits with Latches

SR Latch

 The circuit diagram and truth table of the *SR* latch are shown as follows,



(a) Crossed-coupled circuit


S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(After $SR = 10$)
0	1	0	1	
0	0	0	1	(After $SR = 01$)
1	1	0	0	

(b) Truth table

Circuits with Latches

SR Latch

 The circuit diagram of the *SR* latch can be redrawn as follows,



(c) Circuit showing feedback

	00	01	11	10
0	0	0	0	1
1	1	0	0	1

$$Y = SR' + R'y$$

$$Y = S + R'y \text{ when } SR = 0$$

(d) Transition table


Circuits with Latches

SR Latch

$$Y = [(S + y)' + R]'$$
$$= (S + y)R' = SR' + R'y$$

$$\left. \begin{array}{l} SR' + SR = S(R' + R) = S \\ SR = 0 \end{array} \right\} SR' = S$$
 
$$\Rightarrow Y = SR' + R'y = S + R'y \quad \text{when } SR=0$$



Circuits with Latches

Analysis Example

$$S_1 = x_1 y_2$$


$$S_2 = x_1 x_2$$

$$R_1 = x'_1 x'_2$$

$$R_2 = x'_2 y_1$$

$$S_1 R_1 = x_1 y_2 x'_1 x'_2 = 0$$

$$S_2 R_2 = x_1 x_2 x'_2 y_1 = 0$$

 

Circuits with Latches

Analysis Example

$$Y_1 = S_1 + R'_1 y_1 = x_1 y_2 + (x_1 + x_2) y_1$$

$$Y_2 = S_2 + R'_2 y_2 = x_1 x_2 + (x_2 + y'_1) y_2$$

There is a critical race condition

	$x_1 x_2$			
	00	01	11	10
$y_1 y_2$ 00	00	00	01	00
01	01	01	11	11
11	00	11	11	10
10	00	10	11	10

Circuits with Latches

Latch Excitation Table

A table that lists the required inputs S and R for each of the possible transitions from y to Y

The first two columns list the four possible transitions from y to Y .

y	Y	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	1

(b) Latch excitation table

The next two columns specify the required input values that will result in the specified transition.

Circuits with Latches

Implementation Example

	x_1x_2			
	00	01	11	10
y				
0	0	0	0	1
1	0	0	1	1

(a) Transition table

$$Y = x_1x'_2 + x_1y$$

y	Y	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	1

(b) Latch excitation table

	x_1x_2			
	00	01	11	10
y				
0	0	0	0	1
1	0	0	X	X

(c) Map for $S = x_1x'_2$

	x_1x_2			
	00	01	11	10
y				
0	X	X	X	0
1	1	1	0	0

(d) Map for $R = x'_1$




Circuits with Latches


Implementation Example

$$S = x_1 x'_2 \quad R = x'_1$$

Circuit with
NOR latch

 

Circuit with
NAND latch

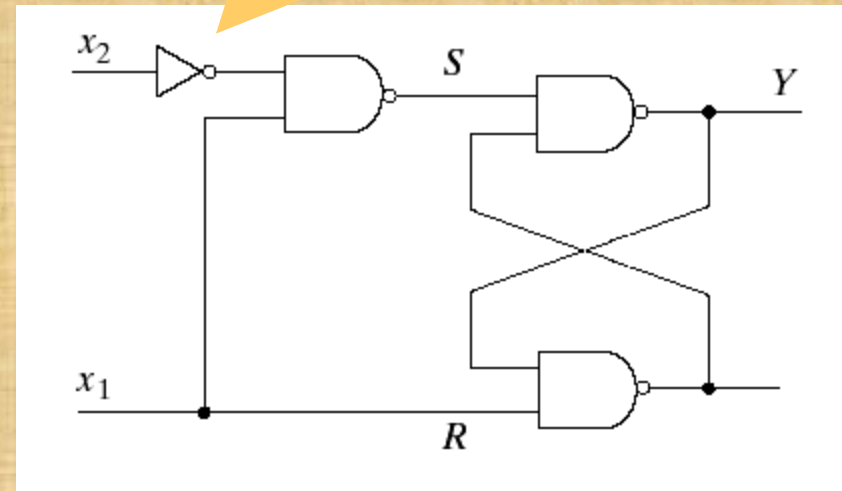

Design Procedure

Design Example

Design a gated latch circuit with two inputs G (gate) and D (data), and one output Q .

Gated-Latch
Total States

State	Inputs		Output	comments
	D	G	Q	
a	0	1	0	$D = Q$ because $G = 1$
b	1	1	1	$D = Q$ because $G = 1$
c	0	0	0	After state a or d
d	1	0	0	After state c
e	1	0	1	After state b or f
f	0	0	1	After state e

Design Procedure

Design Example

State	Inputs		Output
	D	G	Q
a	0	1	0
b	1	1	1
c	0	0	0
d	1	0	0
e	1	0	1
f	0	0	1



	DG			
	00	01	11	10
a	$c, -$	$a, 0$	$b, -$	$-, -$
b	$-, -$	$a, -$	$b, 1$	$e, -$
c	$c, 0$	$a, -$	$-, -$	$d, -$
d	$c, -$	$-, -$	$b, -$	$d, 0$
e	$f, -$	$-, -$	$b, -$	$e, 1$
f	$f, 1$	$a, -$	$-, -$	$e, -$

Two or more rows in the primitive flow table can be merged into one row if there are **non-conflicting** states and outputs in each of the columns.

	<i>DG</i>			
	00	01	11	10
<i>a</i>	<i>c</i> , -	<i>a</i> , 0	<i>b</i> , -	- , -
<i>b</i>	- , -	<i>a</i> , -	<i>b</i> , 1	<i>e</i> , -
<i>c</i>	<i>c</i> , 0	<i>a</i> , -	- , -	<i>d</i> , -
<i>d</i>	<i>c</i> , -	- , -	<i>b</i> , -	<i>d</i> , 0
<i>e</i>	<i>f</i> , -	- , -	<i>b</i> , -	<i>e</i> , 1
<i>f</i>	<i>f</i> , 1	<i>a</i> , -	- , -	<i>e</i> , -



	<i>DG</i>			
	00	01	11	10
<i>a</i>	<i>c</i> , -	<i>a</i> , 0	<i>b</i> , -	- , -
<i>c</i>	<i>c</i> , 0	<i>a</i> , -	- , -	<i>d</i> , -
<i>d</i>	<i>c</i> , -	- , -	<i>b</i> , -	<i>d</i> , 0

	<i>DG</i>			
	00	01	11	10
<i>b</i>	- , -	<i>a</i> , -	<i>b</i> , 1	<i>e</i> , -
<i>e</i>	<i>f</i> , -	- , -	<i>b</i> , -	<i>e</i> , 1
<i>f</i>	<i>f</i> , 1	<i>a</i> , -	- , -	<i>e</i> , -

Reduction of the Primitive Flow Table

Design Procedure

Reduction of the Primitive Flow Table

DG

	00	01	11	10
<i>a, c, d</i>	<i>c</i> , 0	<i>a</i> , 0	<i>b</i> , -	<i>d</i> , 0
<i>b, e, f</i>	<i>f</i> , 1	<i>a</i> , -	<i>b</i> , 1	<i>e</i> , 1



DG

	00	01	11	10
<i>a</i>	<i>c</i> , -	<i>a</i> , 0	<i>b</i> , -	- , -
<i>c</i>	<i>c</i> , 0	<i>a</i> , -	- , -	<i>d</i> , -
<i>d</i>	<i>c</i> , -	- , -	<i>b</i> , -	<i>d</i> , 0

DG

	00	01	11	10
<i>b</i>	- , -	<i>a</i> , -	<i>b</i> , 1	<i>e</i> , -
<i>e</i>	<i>f</i> , -	- , -	<i>b</i> , -	<i>e</i> , 1
<i>f</i>	<i>f</i> , 1	<i>a</i> , -	- , -	<i>e</i> , -

DG

	00	01	11	10
<i>a</i>	<i>a</i> , 0	<i>a</i> , 0	<i>b</i> , -	<i>a</i> , 0
<i>b</i>	<i>b</i> , 1	<i>a</i> , -	<i>b</i> , 1	<i>b</i> , 1

Design Procedure


Transition Table and Logic Diagram

		<i>DG</i>			
<i>y</i>		00	01	11	10
0		0	0	1	0
1		1	0	1	1

(a) $Y = DG + G'y$

		<i>DG</i>			
<i>y</i>		00	01	11	10
0		0	0	1	0
1		1	0	1	1

(b) $Q = Y$

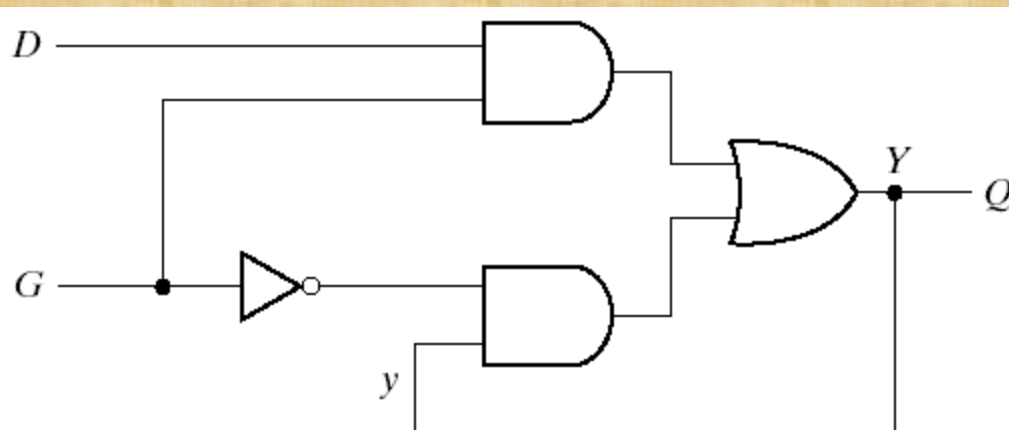

Design Procedure


Circuit With *SR* Latch

	<i>DG</i>			
<i>y</i>	00	01	11	10
0	0	0	1	0
1	X	0	X	X

(a) $S = DG$

	<i>DG</i>			
<i>y</i>	00	01	11	10
0	X	X	0	X
1	0	1	0	0

$R = D'G$

 

Design Procedure

Assigning Output to Unstable States

1. Assign a **0** to an output variable associated with an unstable state that is a transient state between two stable states that have a **0** in the corresponding output variable.
2. Assign a **1** to an output variable associated with an unstable state that is a transient state between two stable states that have a **1** in the corresponding output variable.
3. Assign a **don't-care** condition to an output variable associated with an unstable state that is a transient state between two stable states that have **different values** in the corresponding output variable.