

REGISTERS -

Introduction to Registers

Shift Registers

Lecture 1

Dronacharya Group of Institutions


Introduction: Registers

- An *n*-bit register has a group of *n* flip-flops and some logic gates and is capable of storing *n* bits of information.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
 - ❖ retrieve data from register
 - ❖ store/load new data into register (serial or parallel)
 - ❖ shift the data within register (left or right)



Simple Registers

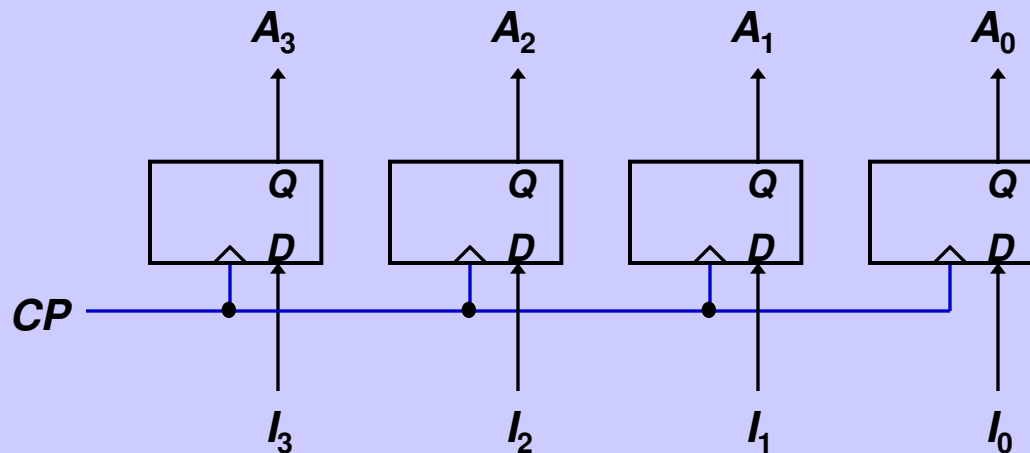- No external gates.
- Example: A 4-bit register. A new 4-bit data is loaded every clock cycle.




Registers With Parallel Load

- Instead of loading the register at every clock pulse, we may want to control when to load.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.




Registers With Parallel Load

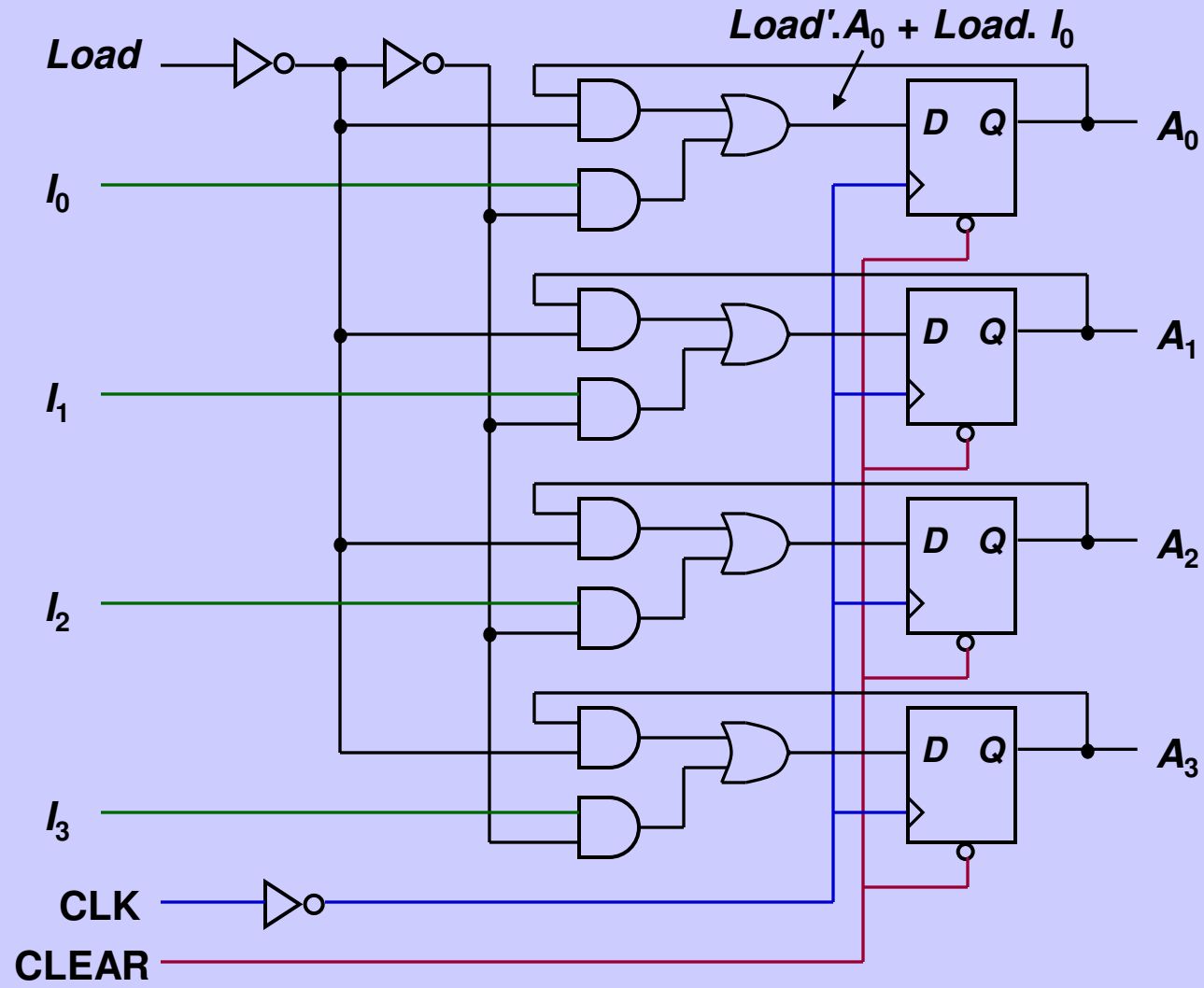

Using Registers to implement Sequential Circuits

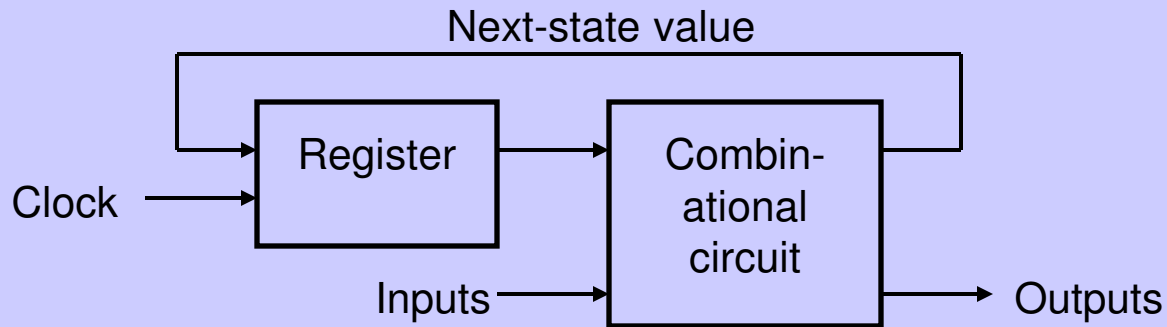- A sequential circuit may consist of a *register* (memory) and a *combinational circuit*.



- The external inputs and present states of the register determine the next states of the register and the external outputs, through the combinational circuit.
- The combinational circuit may be implemented by any of the methods covered in *MSI components* and *Programmable Logic Devices*.

Using Registers to implement Sequential Circuits


■ Example 1:

$$A_1^+ = \Sigma m(4,6) = A_1 \cdot x'$$

$$A_2^+ = \Sigma m(1,2,5,6) = A_2 \cdot x' + A_2' \cdot x = A_2 \oplus x$$

$$y = \Sigma m(3,7) = A_2 \cdot x$$

Present state		Input	Next State		Output
A_1	A_2		A_1^+	A_2^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

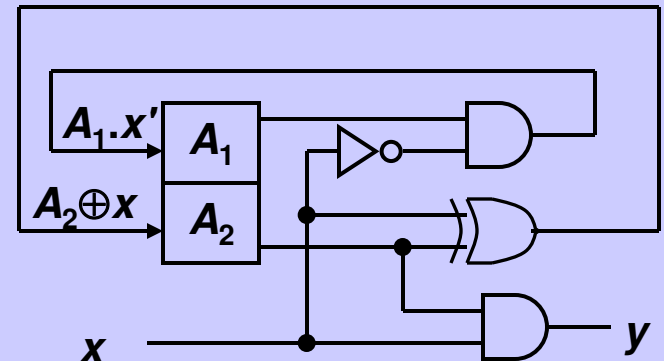


Using Registers to implement Sequential Circuits

- Example 2: Repeat example 1, but use a ROM.

Address			Outputs		
1	2	3	1	2	3
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

ROM truth table

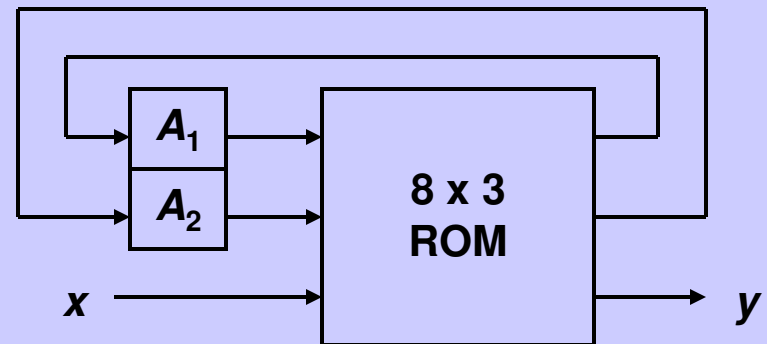


Shift Registers

- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.




Shift Registers

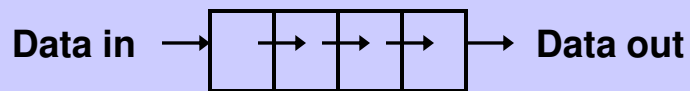
- Basic data movement in shift registers (four bits are used for illustration).




(a) Serial in/shift right/serial out

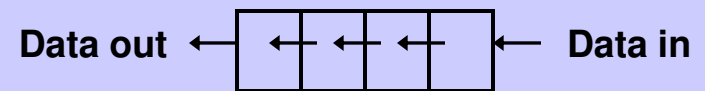


(b) Serial in/shift left/serial out

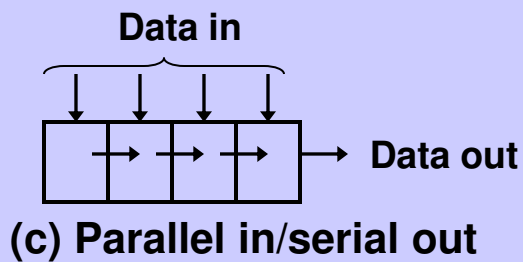


(c) Parallel in/serial out

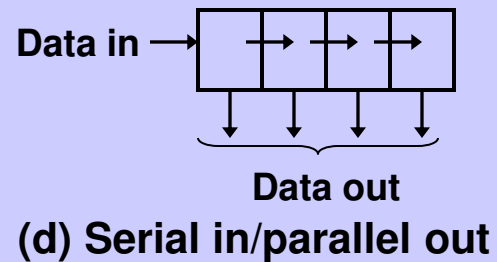


(d) Serial in/parallel out

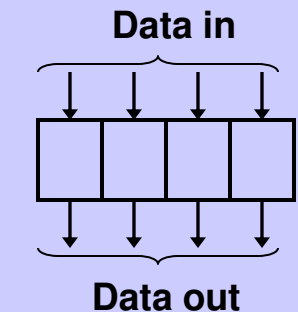

(e) Parallel in / parallel out

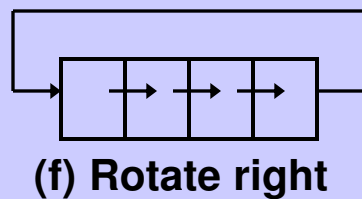


(f) Rotate right

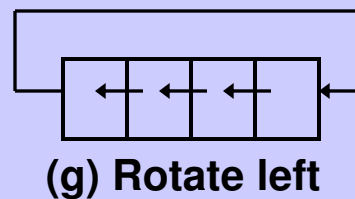

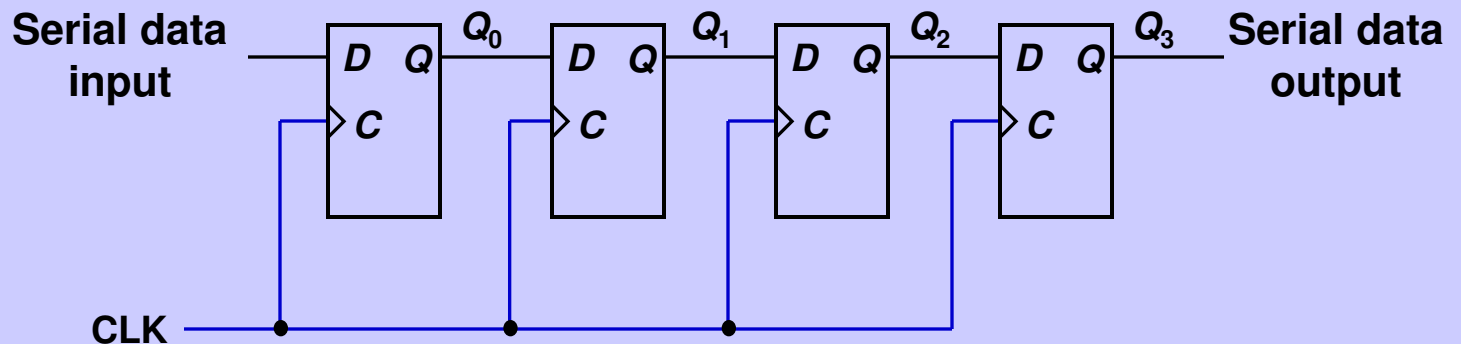(g) Rotate left


Serial In/Serial Out Shift Registers

- Accepts data serially – one bit at a time – and also produces output serially.



Serial In/Serial Out Shift Registers

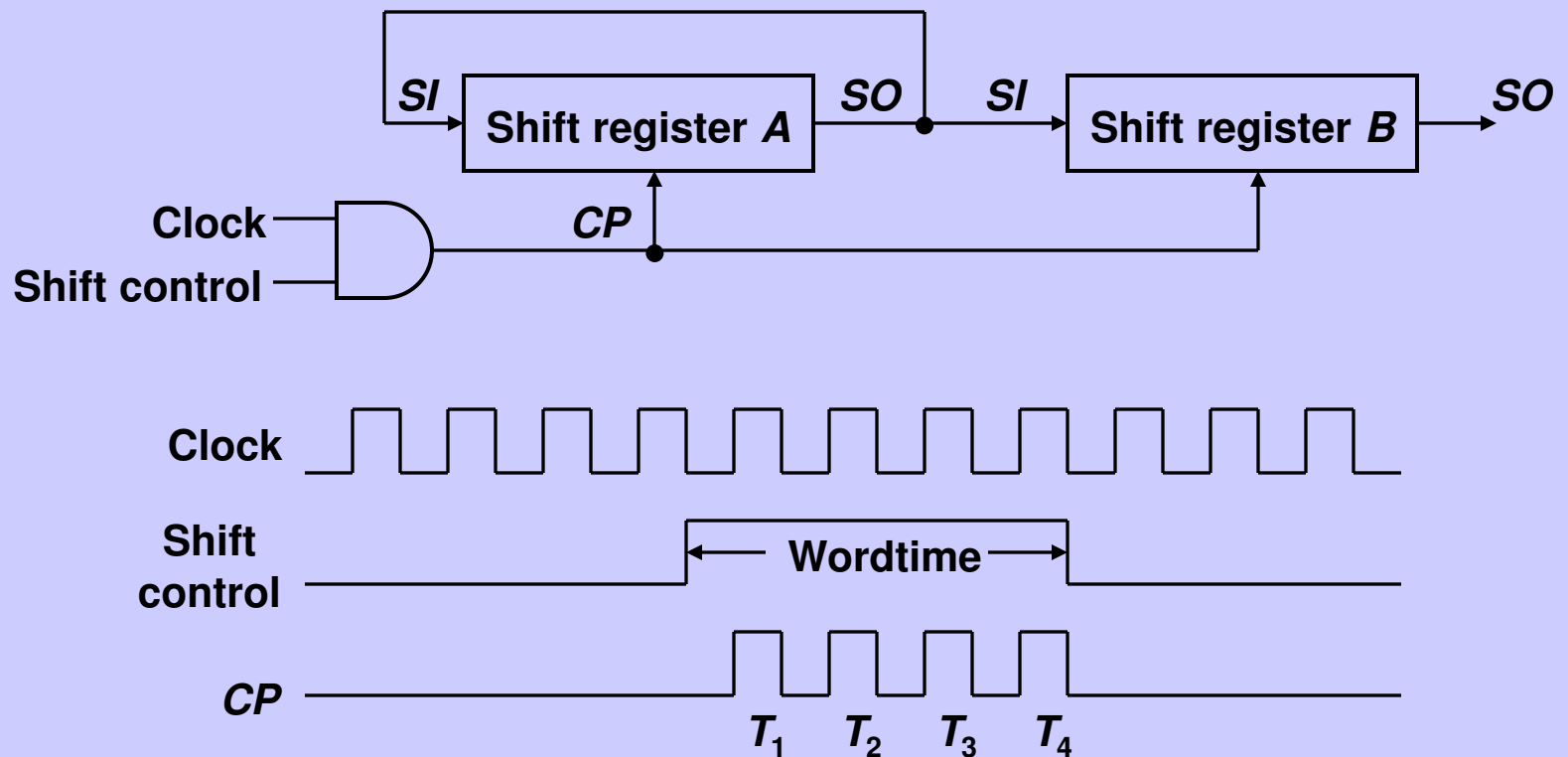- Application: Serial transfer of data from one register to another.





Serial In/Serial Out Shift Registers

- Serial-transfer example.

Timing Pulse	Shift register <i>A</i>	Shift register <i>B</i>	Serial output of <i>B</i>
Initial value	1 0 1 1	0 0 1 0	0
After T_1	1 1 0 1	1 0 0 1	1
After T_2	1 1 1 0	1 1 0 0	0
After T_3	0 1 1 1	0 1 1 0	0
After T_4	1 0 1 1	1 0 1 1	1

Serial In/Parallel Out Shift Registers

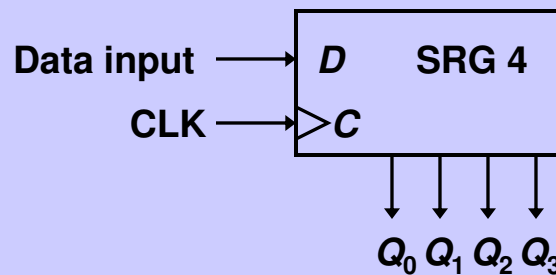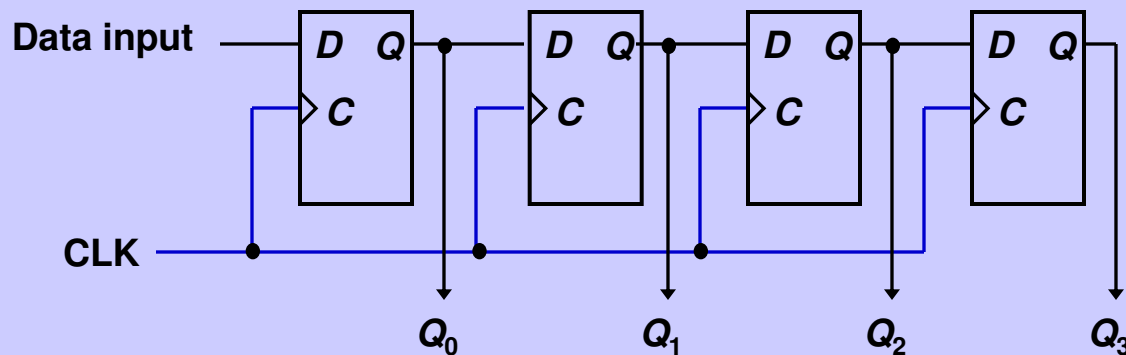
- Accepts data serially.
- Outputs of all stages are available simultaneously.



Logic symbol


Parallel In/Serial Out Shift Registers

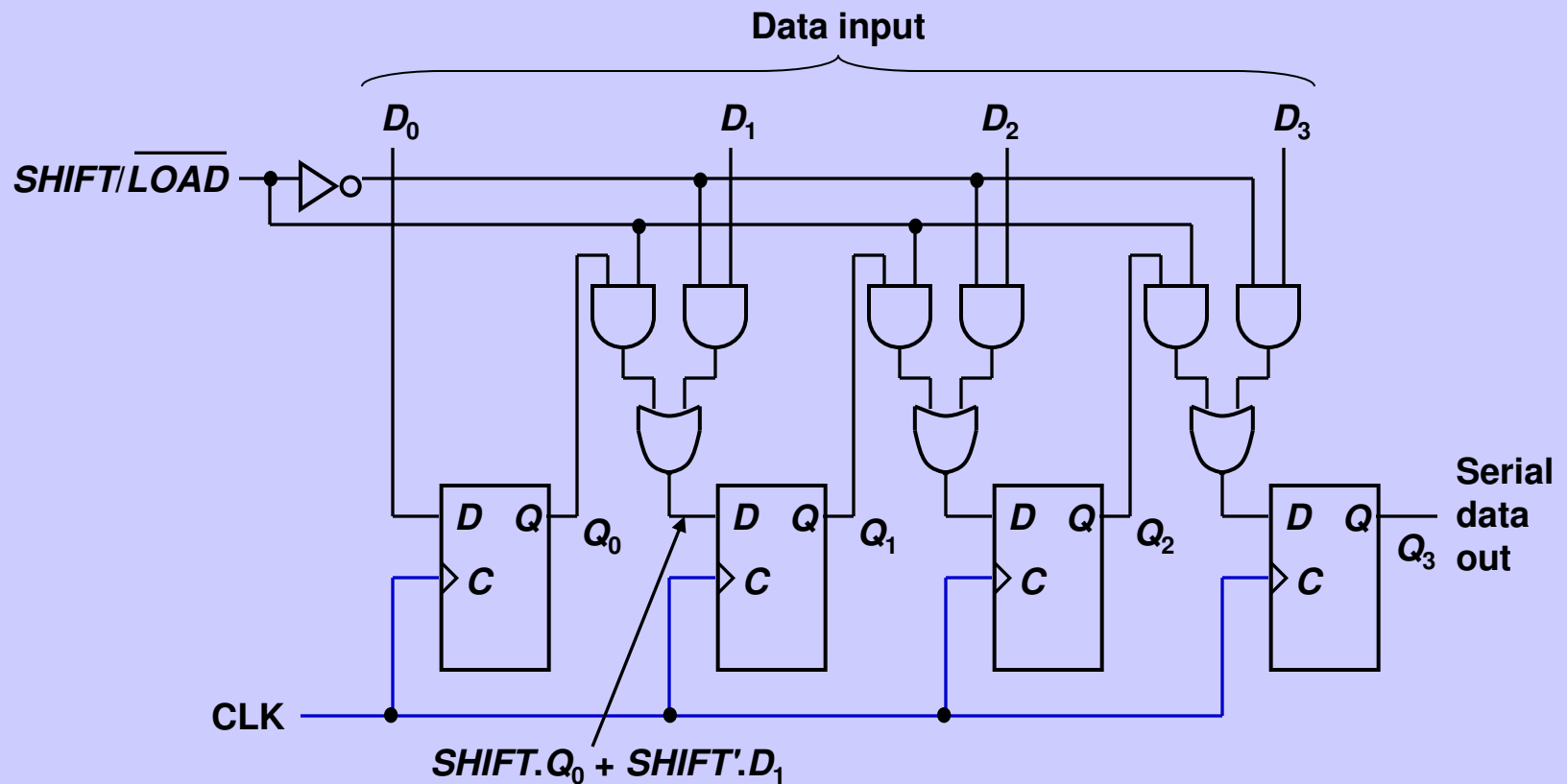- Bits are entered simultaneously, but output is serial.



Parallel In/Serial Out Shift Registers

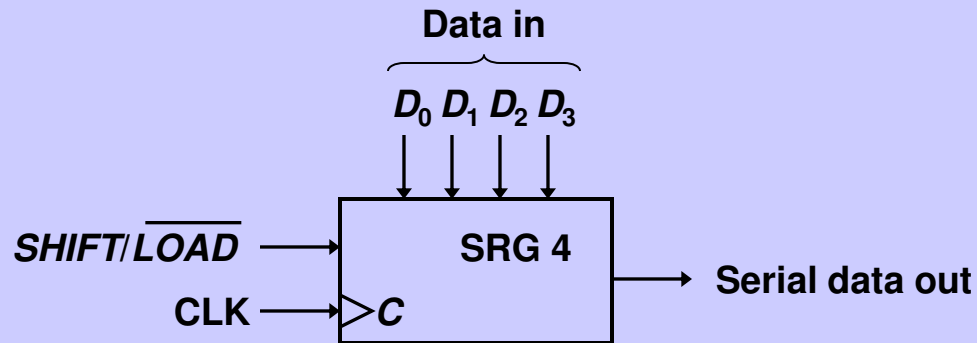
- Bits are entered simultaneously, but output is serial.



Logic symbol


Parallel In/Parallel Out Shift Registers

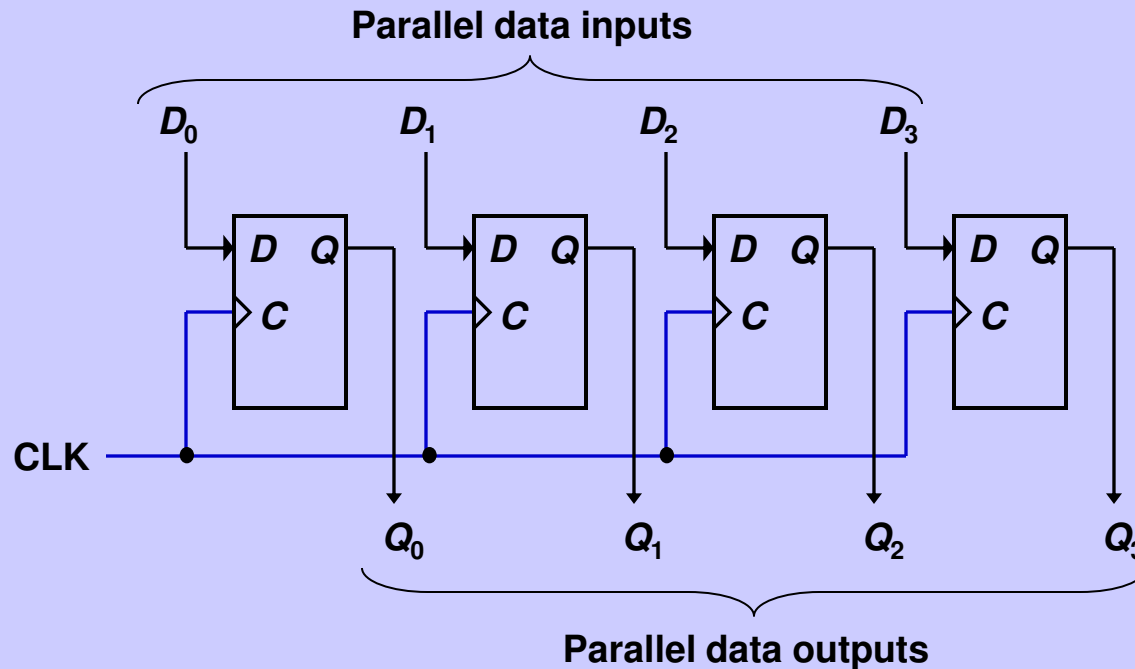- Simultaneous input and output of all data bits.




Bidirectional Shift Registers

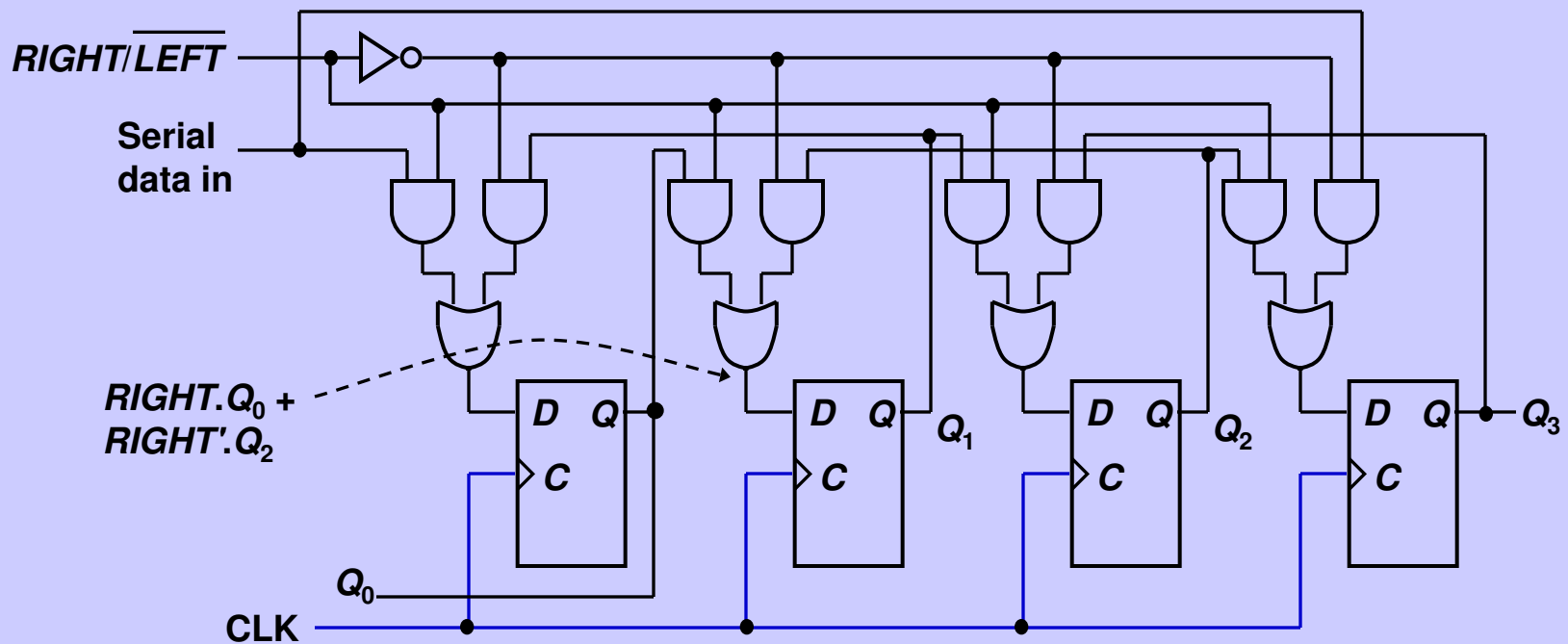- Data can be shifted either left or right, using a control line *RIGHT/LEFT* (or simply *RIGHT*) to indicate the direction.



Bidirectional Shift Registers

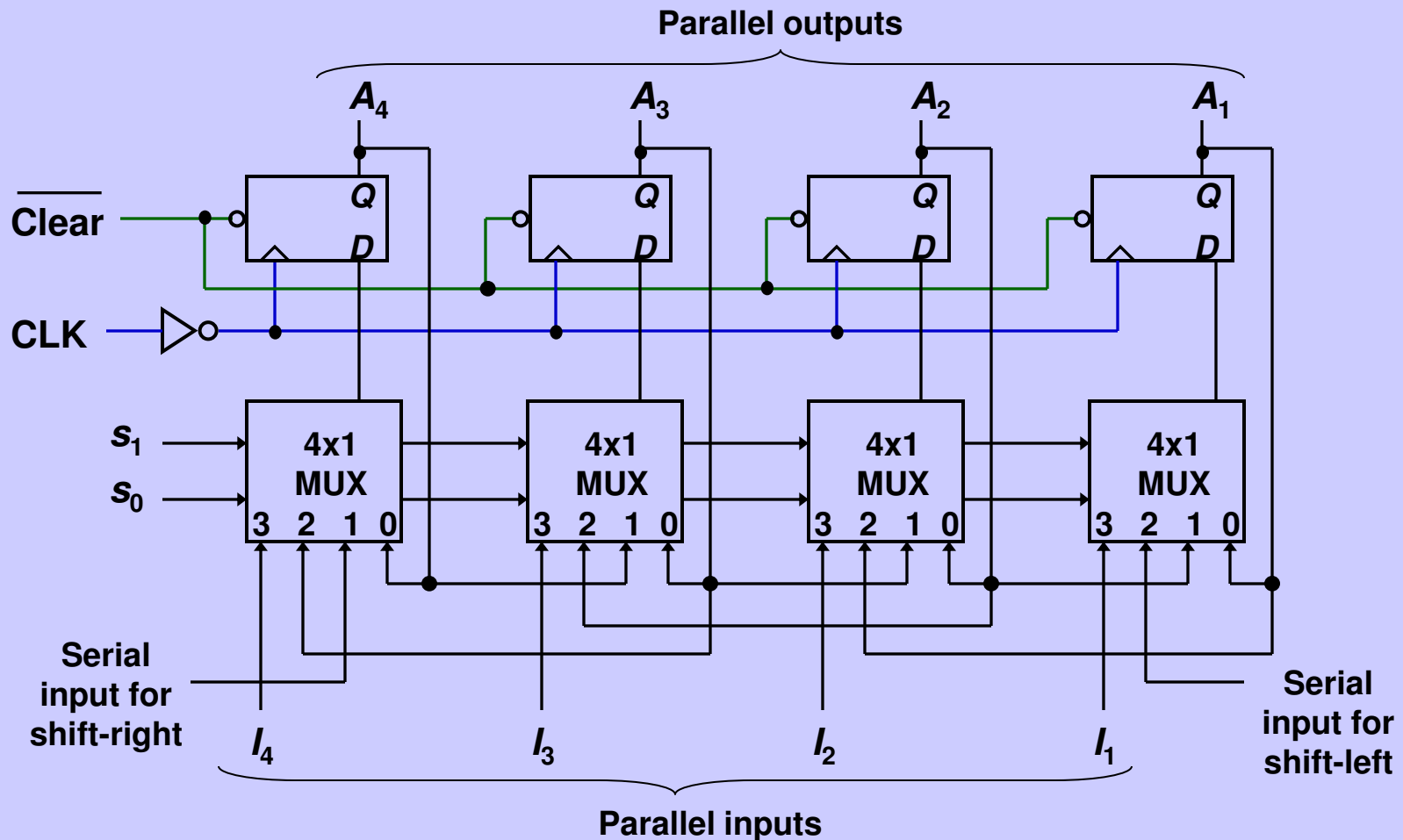- 4-bit bidirectional shift register with parallel load.




Bidirectional Shift Registers

- 4-bit bidirectional shift register with parallel load.

<i>Mode Control</i>		<i>Register Operation</i>
<i>s₁</i>	<i>s₀</i>	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

An Application – Serial Addition

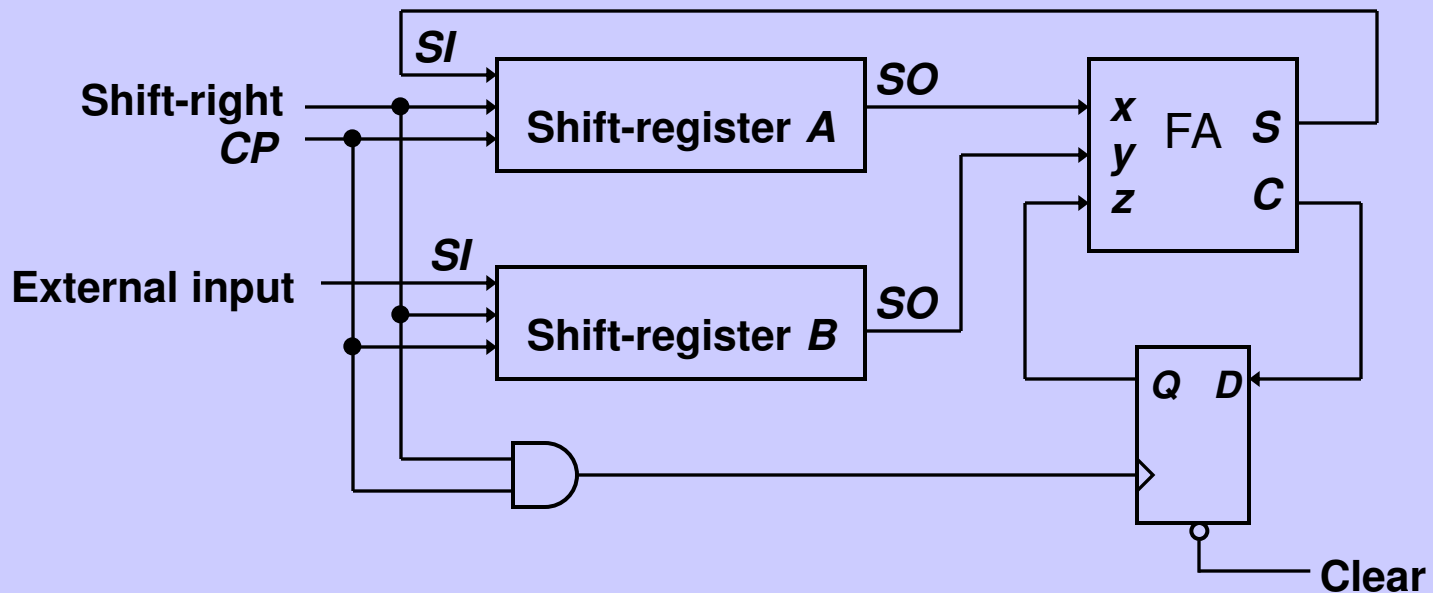- Most operations in digital computers are done in parallel. Serial operations are slower but require less equipment.
- A serial adder is shown below. $A \leftarrow A + B$.



An Application – Serial Addition

- $A = 0100$; $B = 0111$. $A + B = 1011$ is stored in A after 4 clock pulses.

Initial:	A: 0 1 0 <u>0</u> B: 0 1 1 <u>1</u>	Q: <u>0</u>
Step 1: $0 + 1 + 0$ S = 1, C = 0	A: 1 0 1 <u>0</u> B: x 0 1 <u>1</u>	Q: <u>0</u>
Step 2: $0 + 1 + 0$ S = 1, C = 0	A: 1 1 0 <u>1</u> B: x x 0 <u>1</u>	Q: <u>0</u>
Step 3: $1 + 1 + 0$ S = 0, C = 1	A: 0 1 1 <u>0</u> B: x x x <u>0</u>	Q: <u>1</u>
Step 4: $0 + 0 + 1$ S = 1, C = 0	A: 1 0 1 1 B: x x x x	Q: <u>0</u>