

Asynchronous Counters

Lecture 3

Dronacharya Group of Institutions



Asynchronous (Ripple) Counters

- **Asynchronous counters**: the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.
- n flip-flops \rightarrow a MOD (modulus) 2^n counter. (Note: A MOD- x counter cycles through x states.)
- Output of the last flip-flop (MSB) divides the input clock frequency by the MOD number of the counter, hence a counter is also a *frequency divider*.



Asynchronous (Ripple) Counters

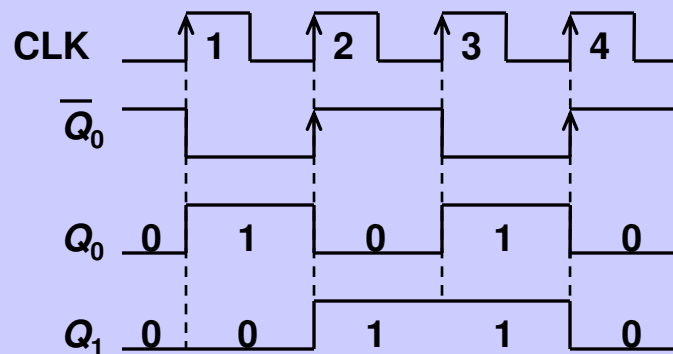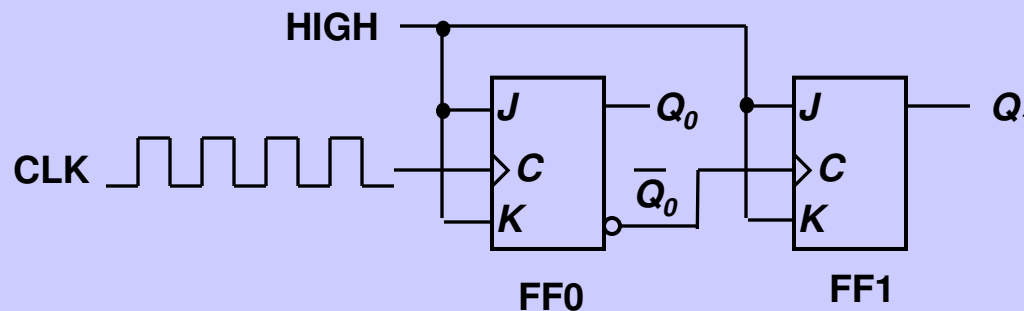- Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.




Timing diagram

00 → 01 → 10 → 11 → 00 ...


Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

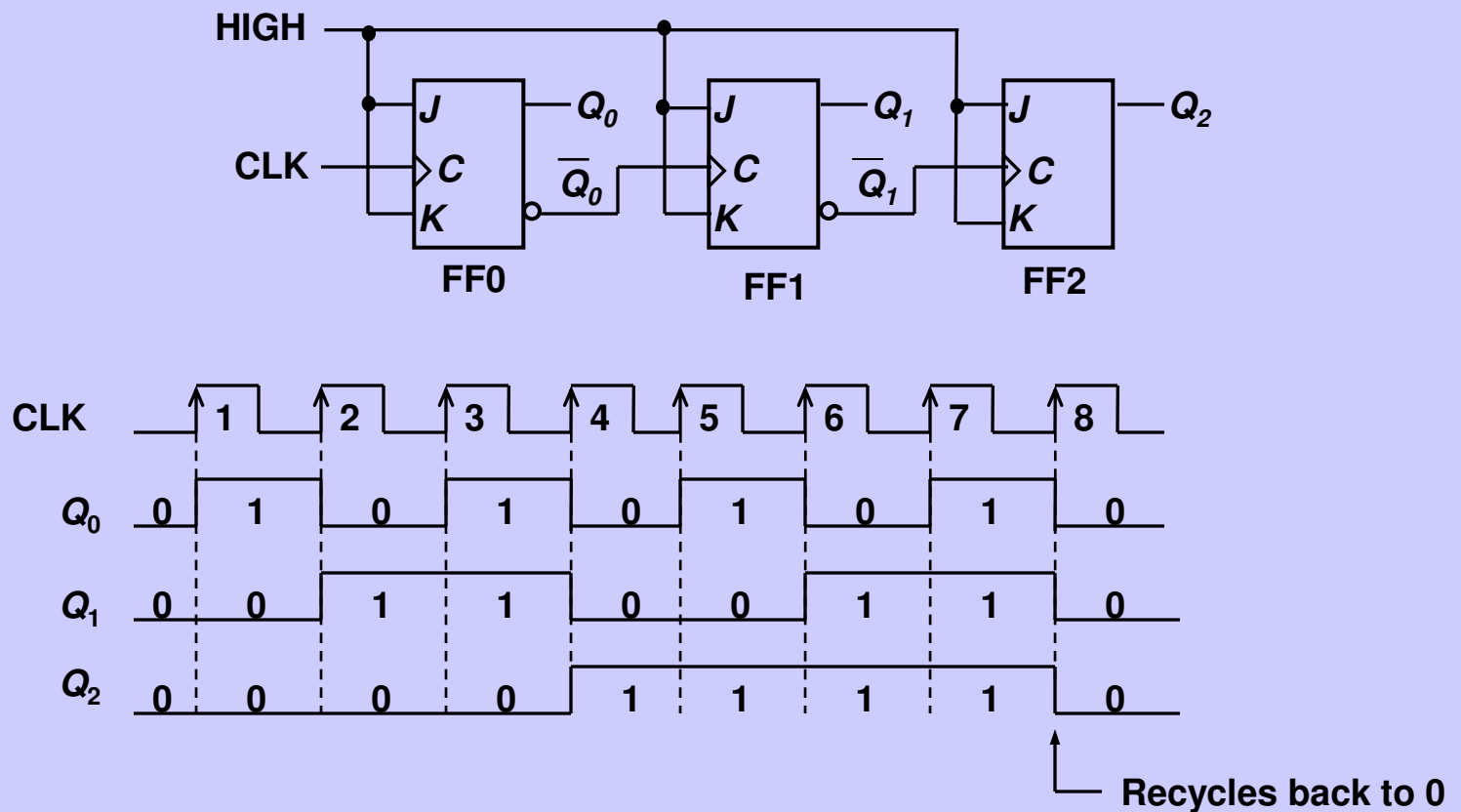


Asynchronous (Ripple) Counters

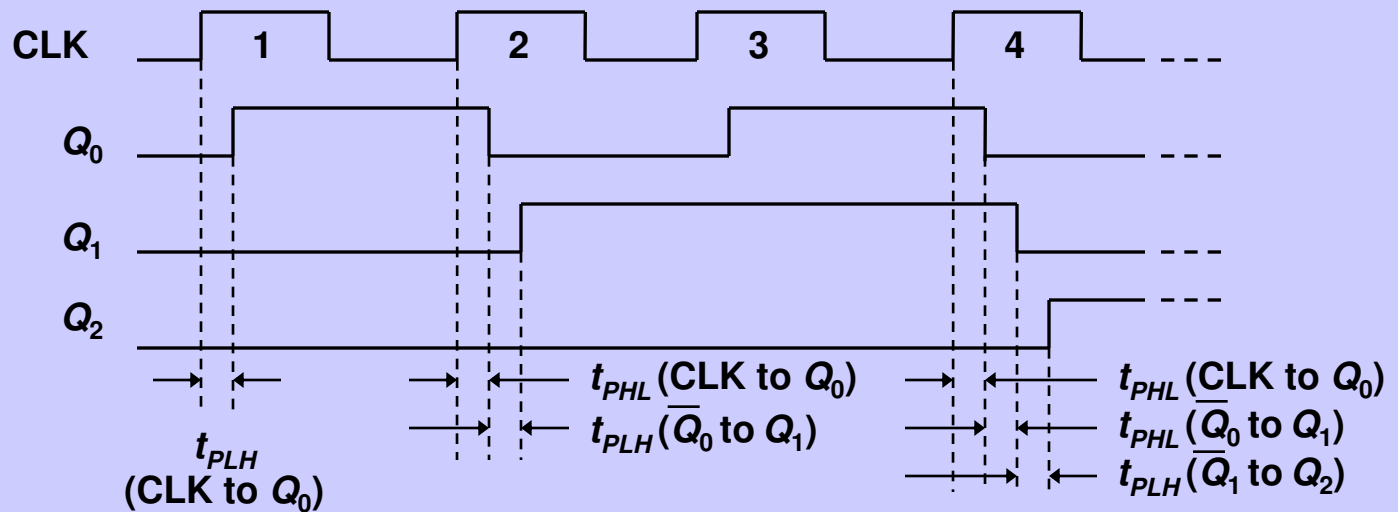- Propagation delays in an asynchronous (ripple-clocked) binary counter.
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!



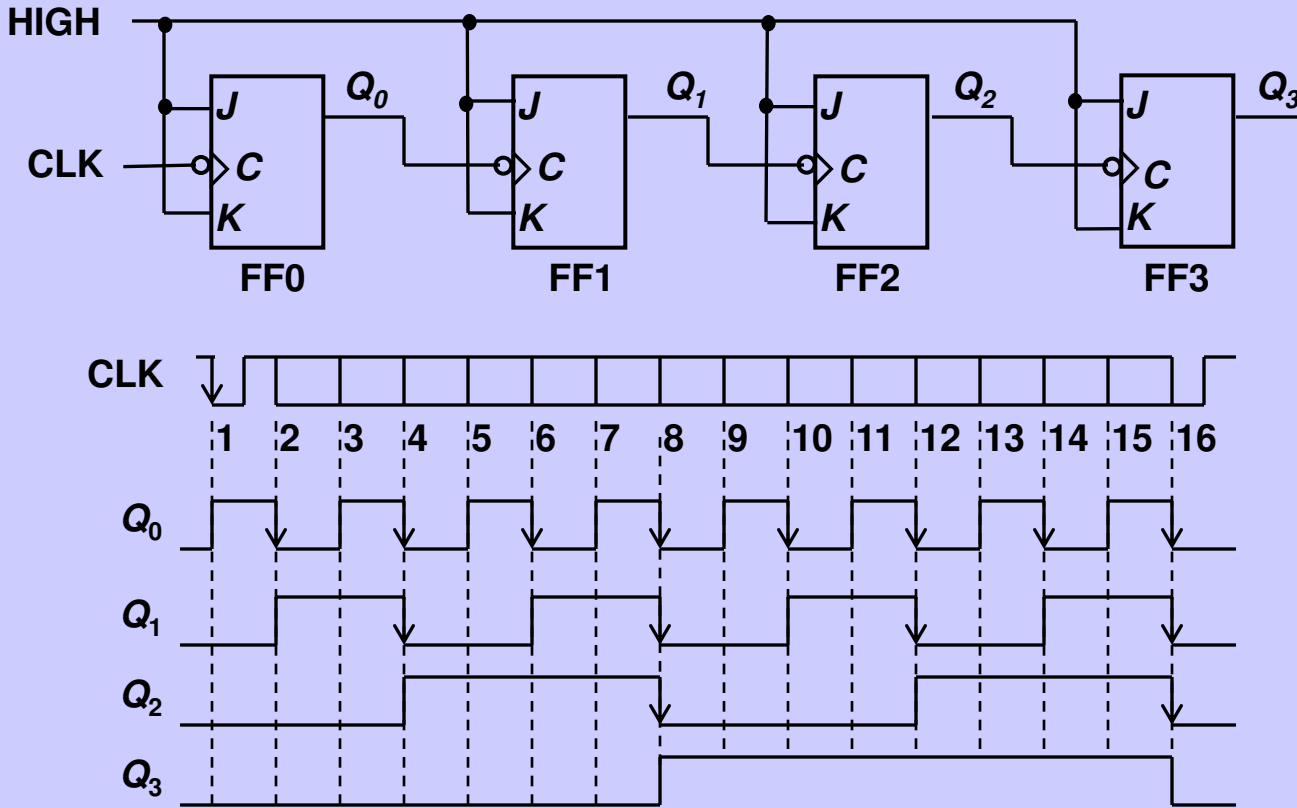
- Example: 4-bit ripple binary counter (negative-edge triggered).



Asyn. Counters with MOD no. $< 2^n$



- States may be skipped resulting in a **truncated sequence**.
- Technique: force counter to *recycle before going through all of the states* in the binary sequence.
- Example: Given the following circuit, determine the counting sequence (and hence the modulus no.)

All J, K inputs are 1 (HIGH).

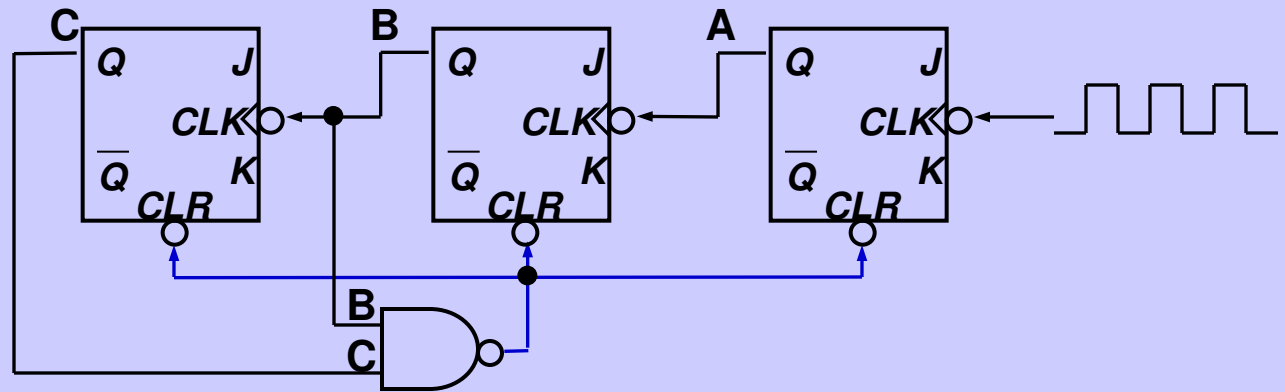

Asyn. Counters with MOD no. $< 2^n$



■ Example (cont'd):

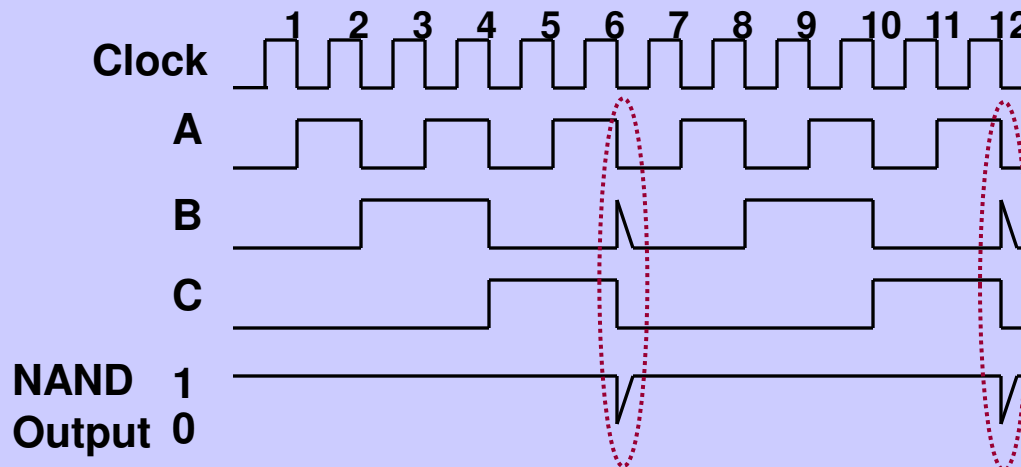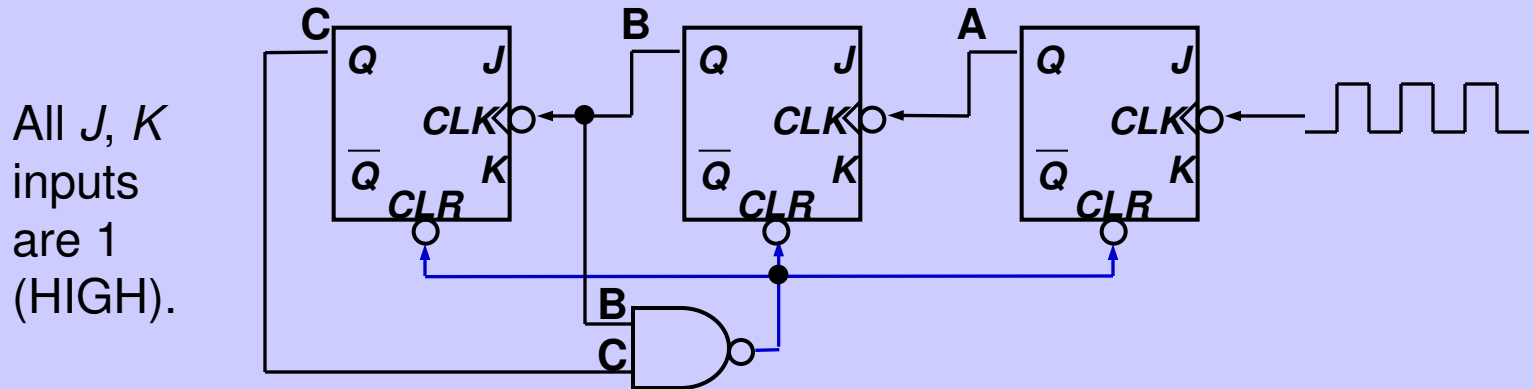

MOD-6 counter
produced by
clearing (a MOD-8
binary counter)
when count of six
(110) occurs.

Asyn. Counters with MOD no. $< 2^n$

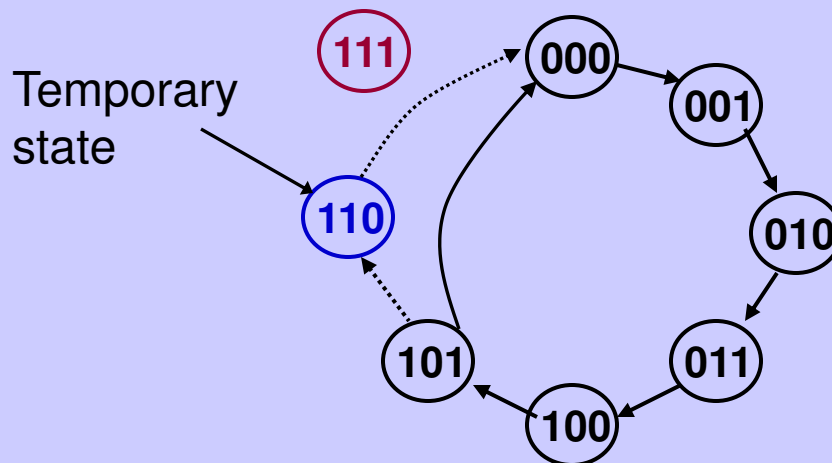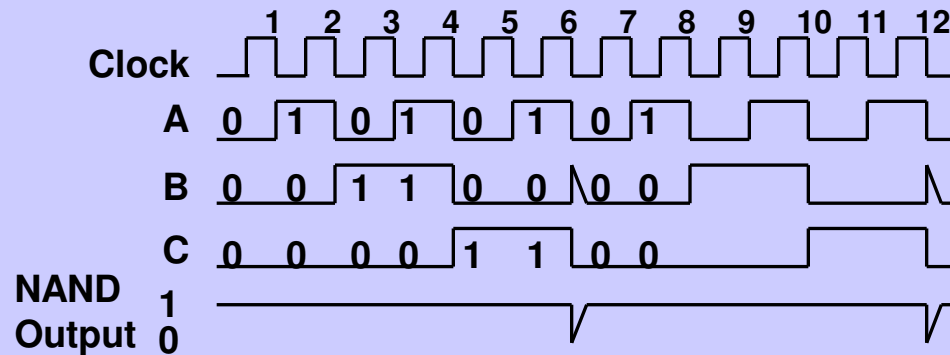
- Example (cont'd): Counting sequence of circuit (in CBA order).



Counter is a MOD-6 counter.


Asyn. Counters with MOD no. $< 2^n$

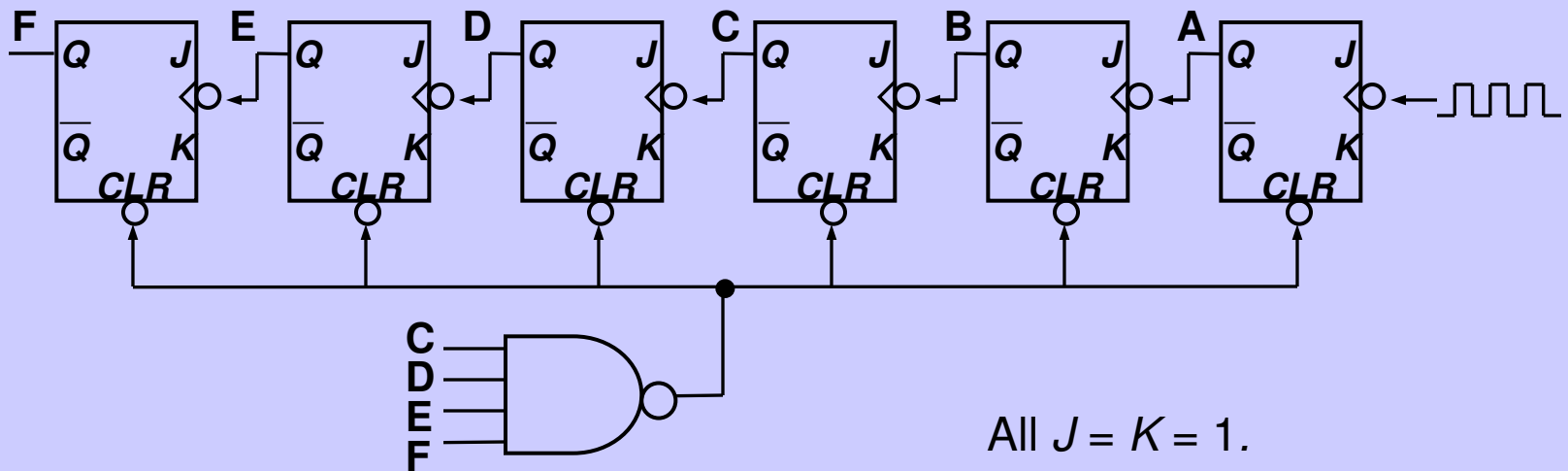- *Exercise:* How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
- *Question:* The following is a MOD-? counter?





Asyn. Counters with MOD no. $< 2^n$

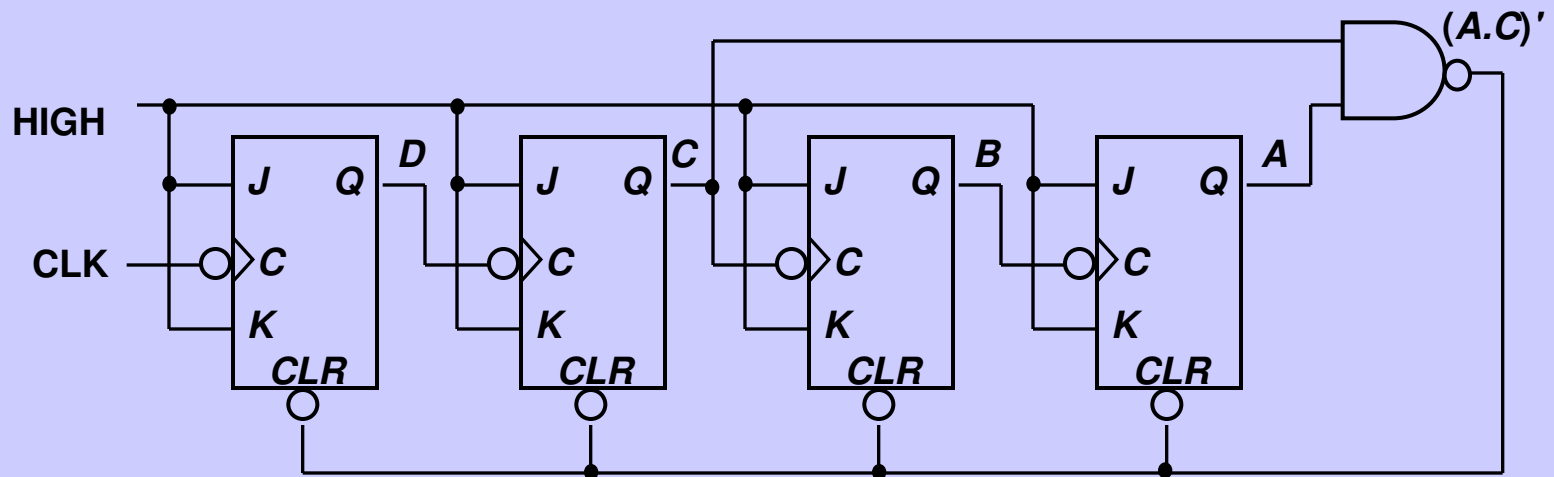- **Decade counters** (or **BCD counters**) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an asynchronous decade counter.




Asyn. Counters with MOD no. $< 2^n$

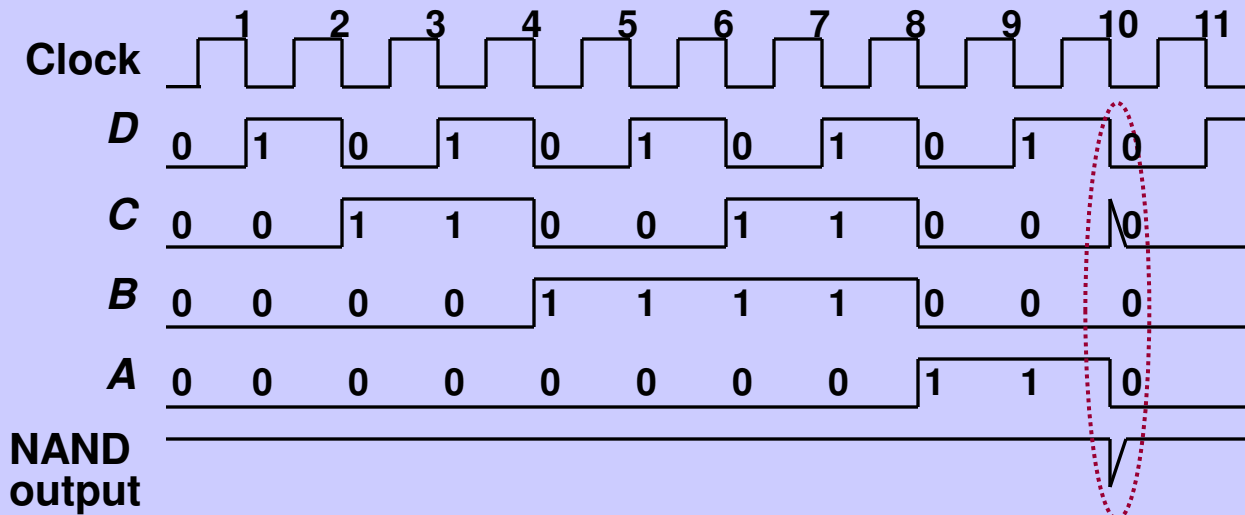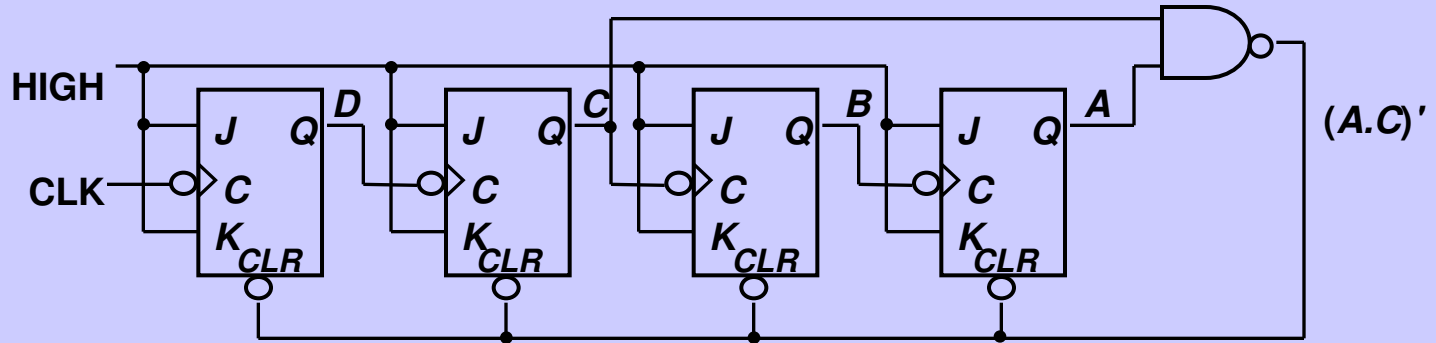- Asynchronous decade/BCD counter (cont'd).




Asynchronous Down Counters

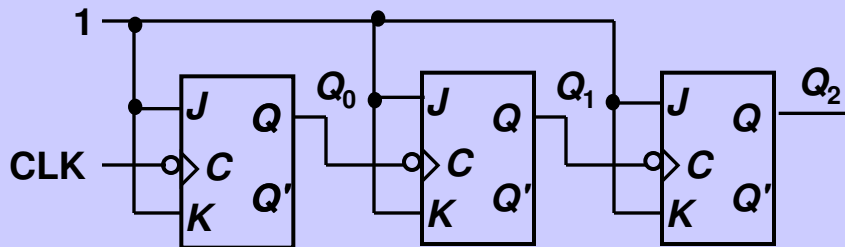- So far we are dealing with *up counters*. *Down counters*, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A 3-bit binary (MOD-2³) down counter.




3-bit binary
up counter

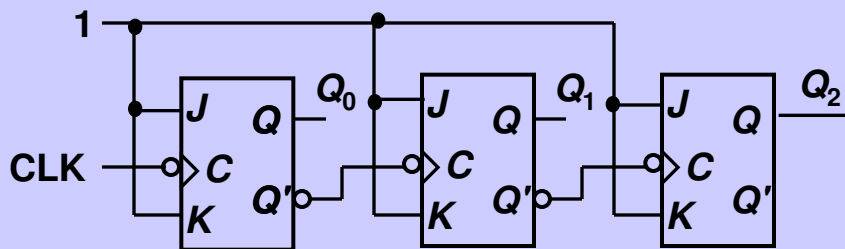

3-bit binary
down counter


Asynchronous Down Counters

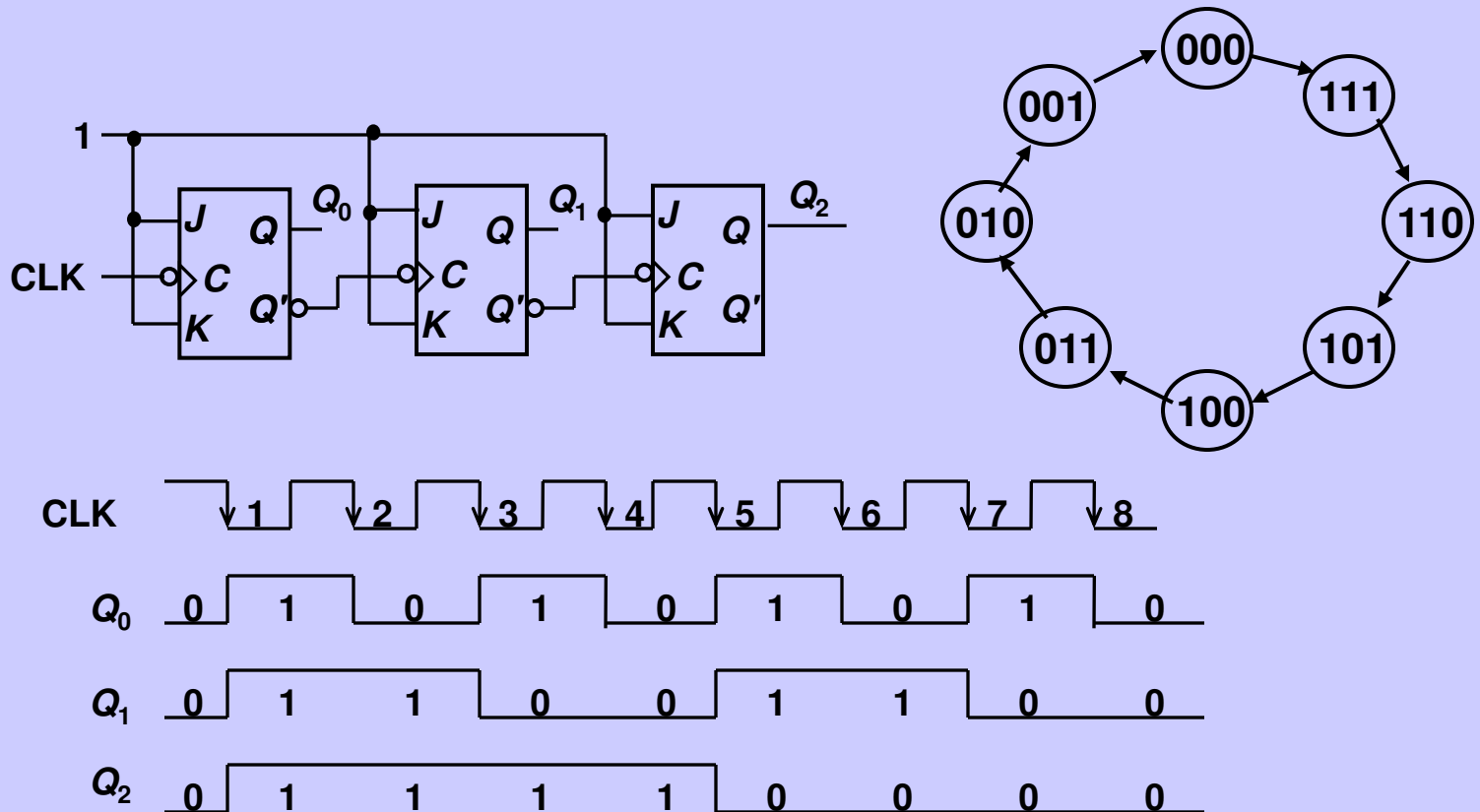- Example: A 3-bit binary (MOD-8) down counter.




Cascading Asynchronous Counters

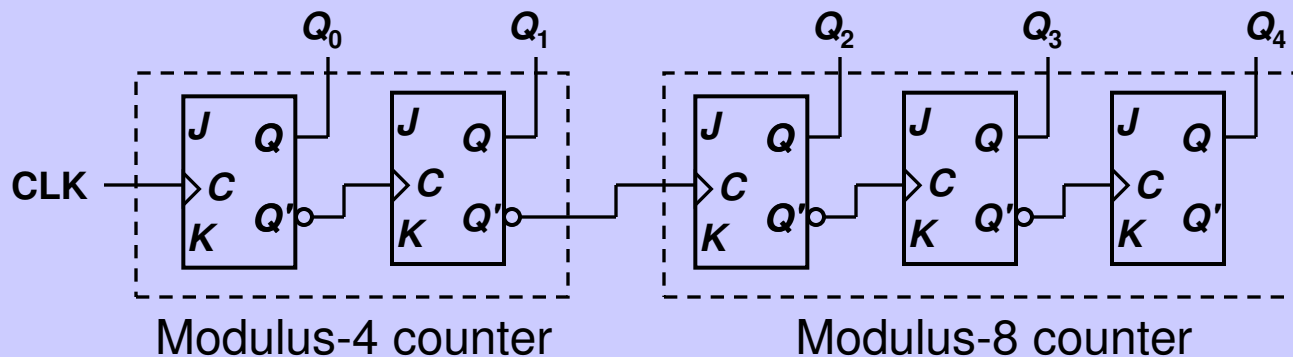- Larger asynchronous (ripple) counter can be constructed by cascading smaller ripple counters.
- Connect last-stage output of one counter to the clock input of next counter so as to achieve higher-modulus operation.
- Example: A modulus-32 ripple counter constructed from a modulus-4 counter and a modulus-8 counter.



Cascading Asynchronous Counters

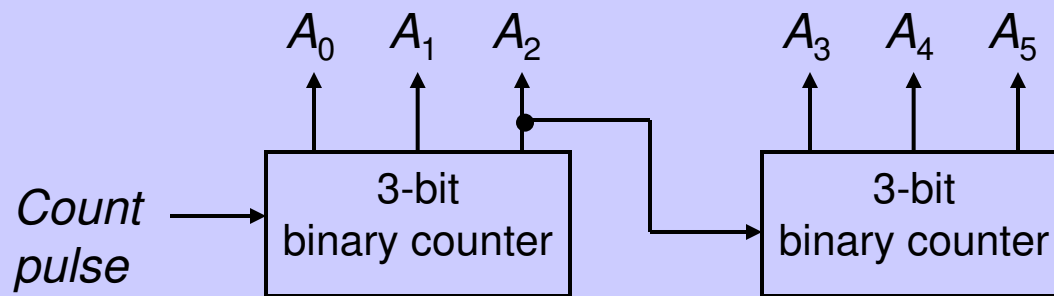
- Example: A 6-bit binary counter (counts from 0 to 63) constructed from two 3-bit counters.



A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	0
0	0	0	0	0	1
0	0	0	:	:	:
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	0	1
:	:	:	:	:	:

Cascading Asynchronous Counters

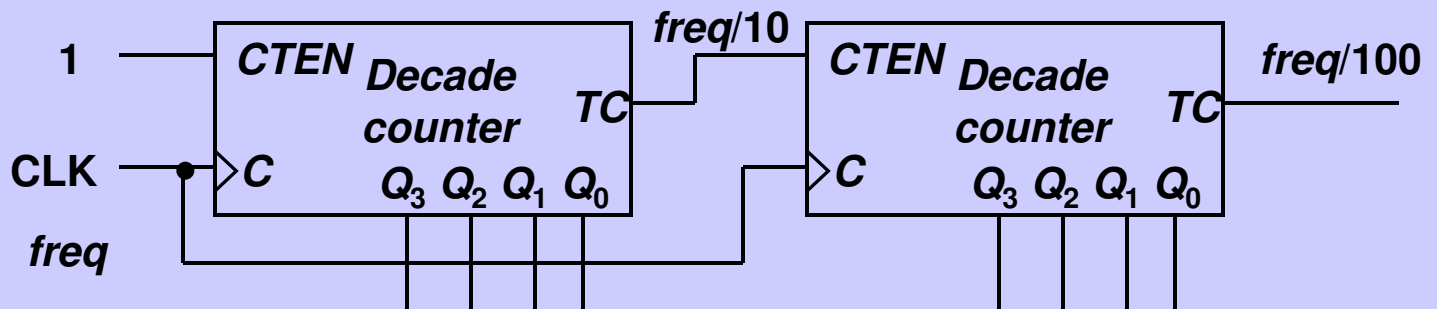- If counter is not a binary counter, requires additional output.
- Example: A modulus-100 counter using two decade counters.



$TC = 1$ when counter recycles to 0000