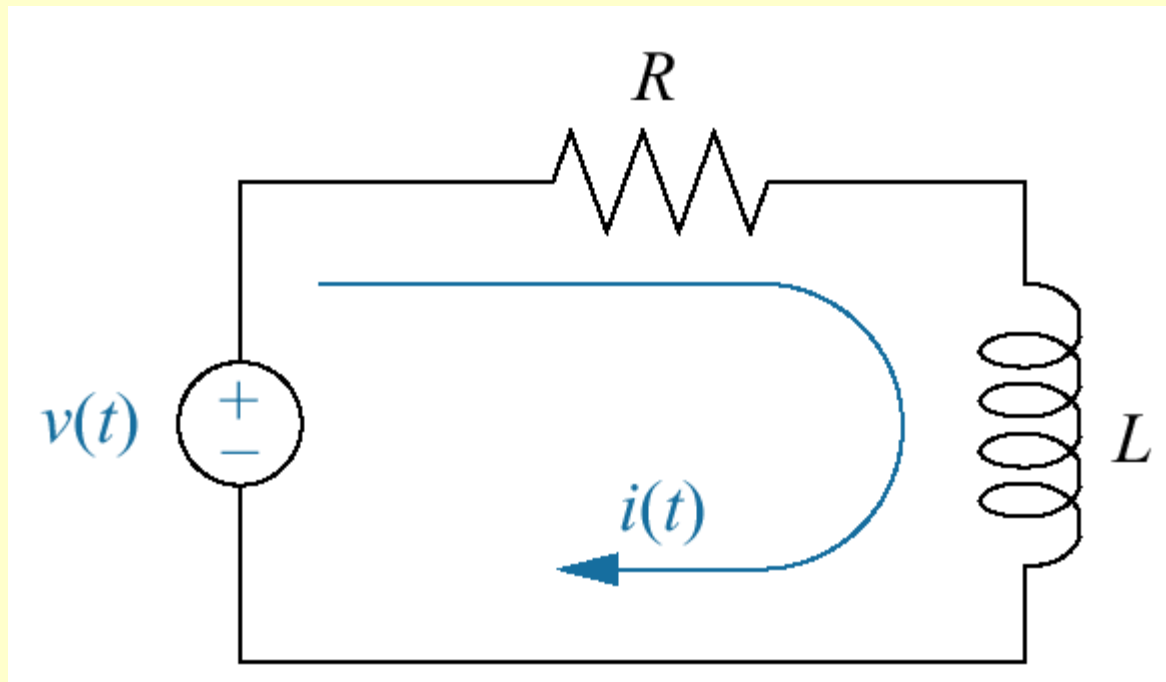


UNIT-2

(Lecture-7)

Application to Network Circuits

RL network



1. Select $i(t)$ As state variables

2. Write loop equation $L \frac{di}{dt} + Ri = v(t)$ (1)

3. Solve the equation using Laplace transform

$$L[sI(s) - i(0)] + RI(s) = V(s)$$

Assumption $v(t)$: Unit step

$$I(s) = \frac{1}{R} \left(\frac{1}{s} - \frac{1}{s + R/L} \right) + \frac{i(0)}{s + R/L}$$

$$\downarrow$$


$$i(t) = \frac{1}{R} (1 - e^{-(R/L)t}) + i(0)e^{-(R/L)t}$$


4. We can solve all other network variables

Output equations $\begin{cases} v_R(t) = Ri(t) \\ v_L(t) = v(t) - Ri(t) \end{cases}$ (2)

(3)

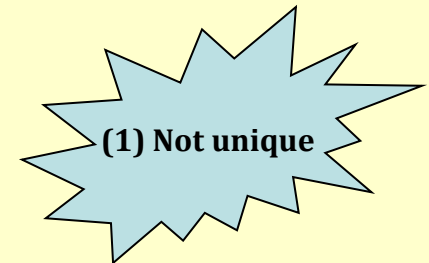(1), (2), (3) : state-space representation



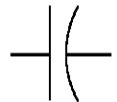

Capacitor

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} q(t)$$

$$\frac{1}{C_s}$$

$$C_s$$



Resistor


$$v(t) = Ri(t)$$

$$i(t) = \frac{1}{R} v(t)$$

$$v(t) = R \frac{dq(t)}{dt}$$

$$R$$

$$\frac{1}{R} = G$$

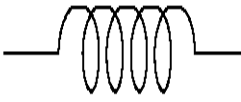

Inductor

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau$$


$$v(t) = L \frac{d^2 q(t)}{dt^2}$$

$$L_s$$

$$\frac{1}{L_s}$$

Note: The following set of symbols and units is used throughout this book: $v(t)$ = V (volts), $i(t)$ = A (amps), $q(t)$ = Q (coulombs), C = F (farads), R = Ω (ohms), G = $\mathfrak{U}$ (mhos), L = H (henries).

RLC network

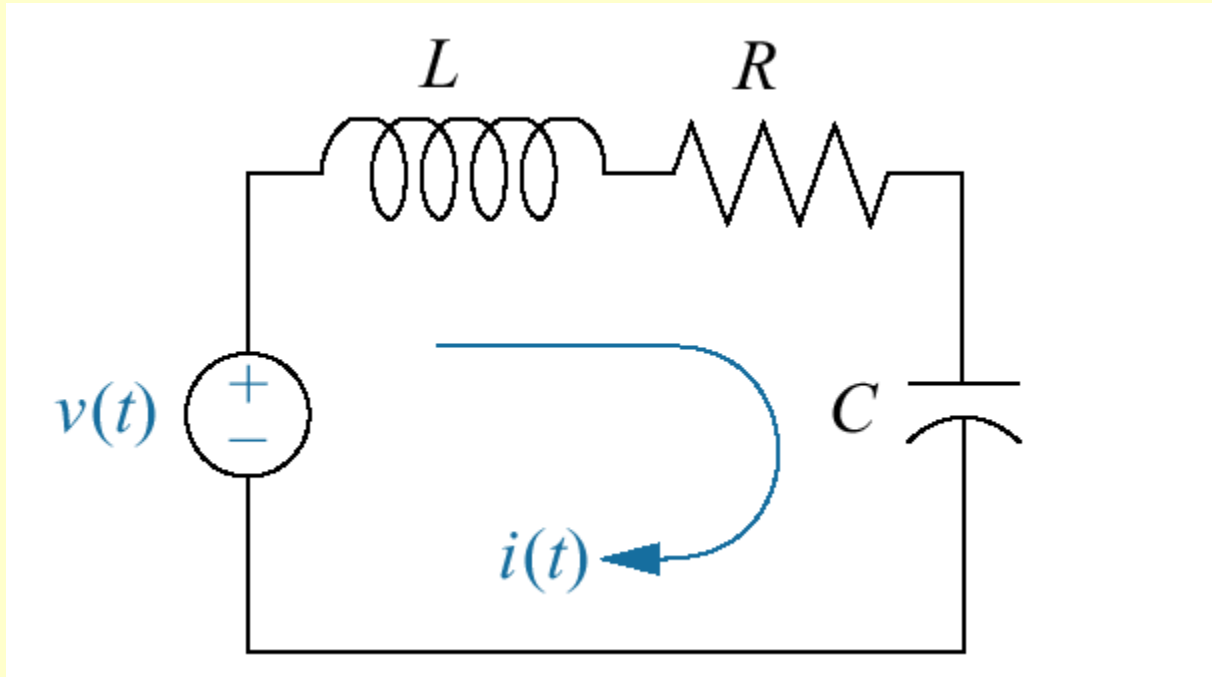

1. State variables $i(t)$ $q(t)$

2. $L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = v(t)$

Using $i(t) = dq/dt$



$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = v(t)$$

$$\frac{dq}{dt} = i$$

$$\frac{di}{dt} = -\frac{1}{LC} q - \frac{R}{L} i + \frac{1}{L} v(t) \quad (1)$$

3. $q(t) \ i(t)$ Can be solved using Laplace Transform

4. Other network variables can be obtained

$$v_L(t) = -\frac{1}{C} q(t) - Ri(t) + v(t) \quad (2)$$


5. (1),(2) : state-space representation

Other variables $v_R(t)$ $v_C(t)$

$$\frac{dv_R}{dt} = -\frac{R}{L}v_R - \frac{R}{L}v_C + \frac{R}{L}v(t)$$

$$\frac{dv_C}{dt} = \frac{1}{RC}v_R$$

Each variables : linearly independent

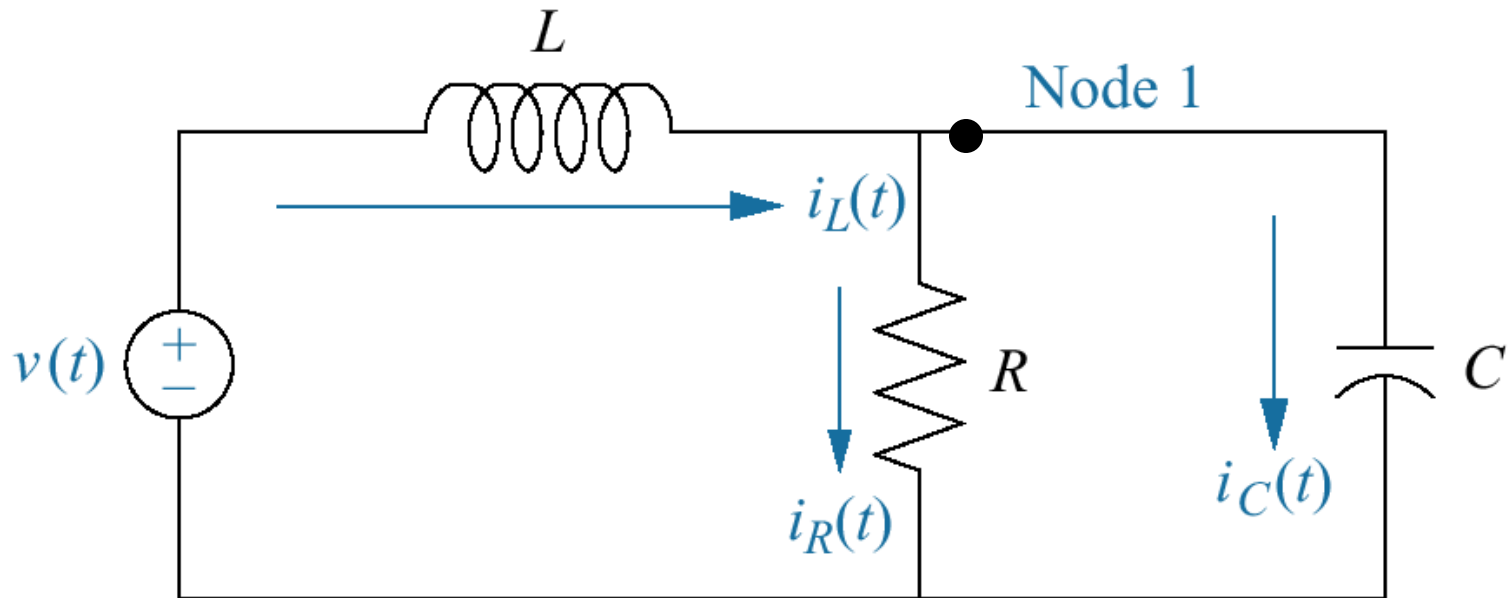Example 1**Electrical network**

1. Select state variables v_C i_L

$$C \frac{dv_C}{dt} = i_C \quad L \frac{di_L}{dt} = v_L \quad (1)$$


Express (1) using v_C i_L $v(t)$

$$\begin{aligned} 2. \quad i_C &= -i_R + i_L & v_L &= -v_C + v(t) \\ &= -\frac{1}{R}v_C + i_L \end{aligned} \quad (2)$$

$$\begin{aligned} 3. \quad \frac{dv_C}{dt} &= -\frac{1}{RC}v_C + \frac{1}{C}i_L \\ \frac{di_L}{dt} &= -\frac{1}{L}v_C + \frac{1}{L}v(t) \end{aligned} \quad (3)$$

4. Output equation $i_R = \frac{1}{R}v_C$

Example 2 & 3

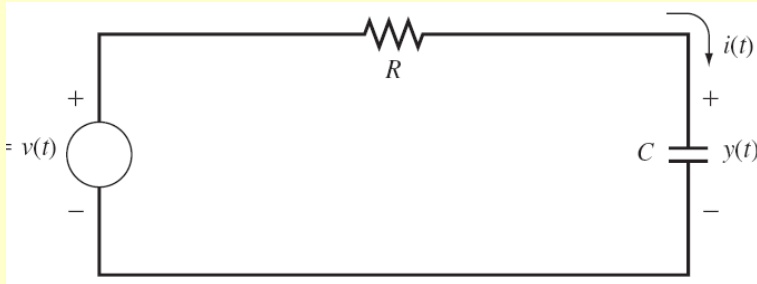


$$\frac{dy(t)}{dt} + \frac{1}{RC} y(t) = \frac{1}{RC} v(t)$$

$$\mathbf{A} = [-a_0] = \left[-\frac{1}{RC} \right]$$

$$\mathbf{B} = [b_0] = \left[\frac{1}{RC} \right] \quad \mathbf{C} = [1] \quad \mathbf{D} = 0$$

$$\begin{bmatrix} \dot{x}_1(t) \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} x_1(t) \end{bmatrix} + \begin{bmatrix} \frac{1}{RC} \end{bmatrix} v(t)$$
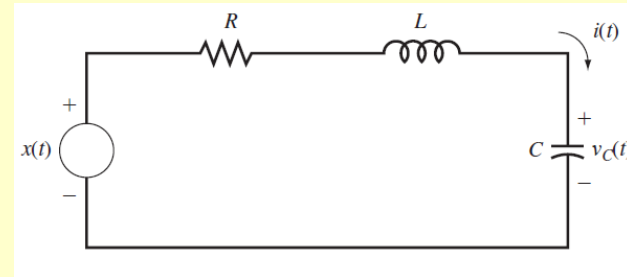
$$y(t) = \begin{bmatrix} 1 \end{bmatrix} \begin{bmatrix} x_1(t) \end{bmatrix}$$



$$\frac{d^2 y(t)}{dt^2} + \left(\frac{R}{L} \right) \frac{dy(t)}{dt} + \frac{1}{LC} y(t) = \frac{1}{LC} v(t)$$

$$\mathbf{A} = \begin{bmatrix} 0 & 1 \\ -a_0 & -a_1 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1/LC & -R/L \end{bmatrix}$$

$$\mathbf{B} = \begin{bmatrix} 0 \\ b_0 \end{bmatrix} = \begin{bmatrix} 0 \\ 1/LC \end{bmatrix}$$

$$\mathbf{C} = [1 \quad 0] \quad \mathbf{D} = 0$$

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1/LC & -R/L \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/LC \end{bmatrix} v(t)$$

$$y(t) = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$$