

Unit-1

Lecture -1

Current Mirrors using BJT
and MOSFETs, Simple current Mirror

Biasing Mechanism of IC's


- MOSFET Circuits
 - The basic MOSFET current source
 - MOS current-steering circuits
- BJT Circuits
 - The basic BJT current source
 - Current-steering

Biasing Mechanism of IC's

- Current-mirror circuits with improved performance
 - Cascode MOS mirrors
 - A bipolar mirror with base-current compensation
 - The wilson current mirror
 - The wilson MOS mirror
 - The widlar current source

Concept of a Current Mirror

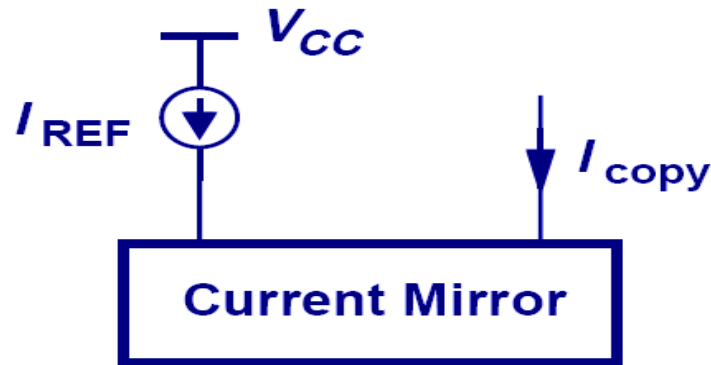- Circuit designs to provide a supply- and temperature-independent current exist, but require many transistors to implement.
 - “golden current source”
- A **current mirror** is used to replicate the current from a “golden current source” to other locations.




Features of Current Mirror

- A current mirror is a circuit block which functions to produce a copy of the current in one active device by replicating the current in second active device.
- An important feature of the current mirror is a relatively high output resistance which helps to keep the output current constant regardless of load conditions.
- Another feature of the current mirror is a relatively low input resistance which helps to keep the input current constant regardless of drive conditions.
- The current being 'copied' can be, and often is, a varying signal
- current.


Basic MOSFET Current Source

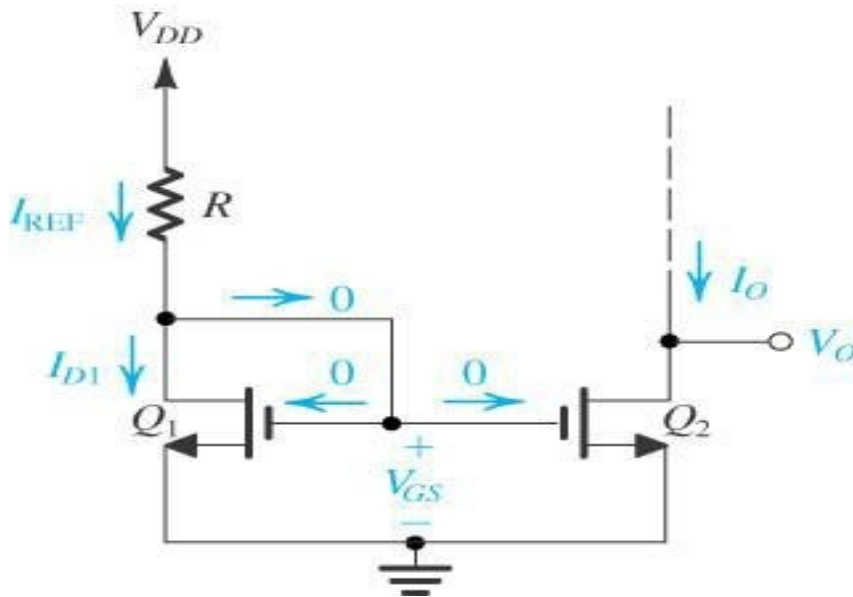A current mirror is a circuit block which functions to produce a copy of the current in one active device by replicating the current in second active device.




$$\frac{I_o}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

Basic MOSFET Current Mirror

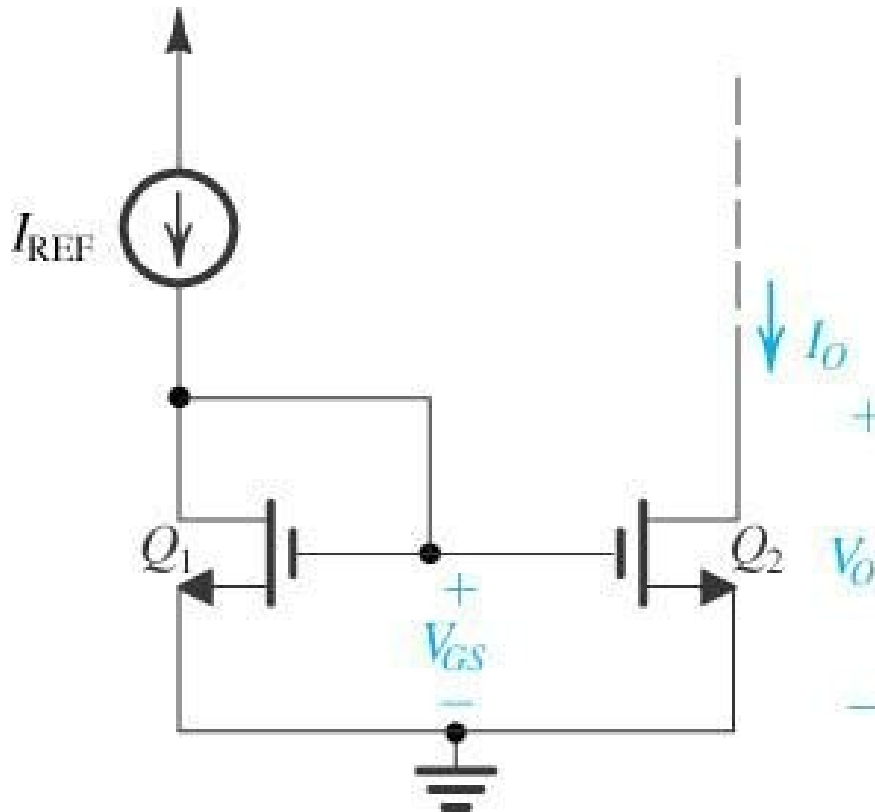

$$I_o = \frac{(W/L)_2}{(W/L)_1} I_{REF} \left(1 + \frac{V_o - V_{GS}}{V_{A2}} \right)$$

Output Characteristics

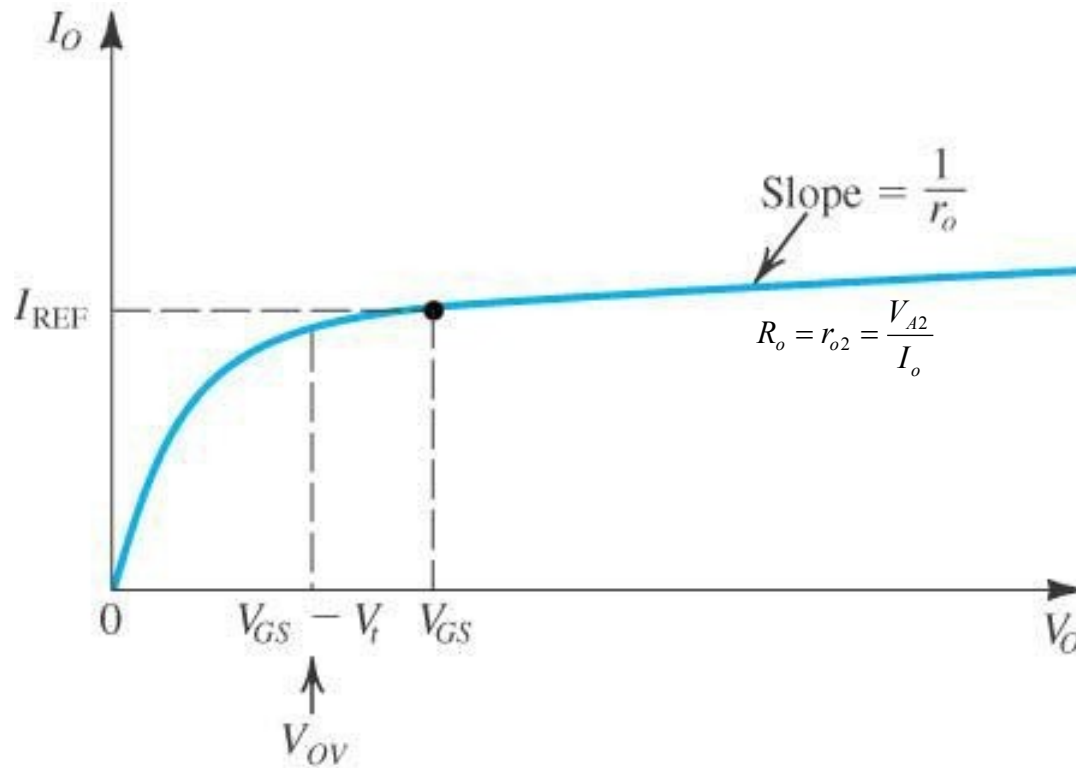

$$R_o = r_{o2} = \frac{V_{A2}}{I_o}$$