


# UNIT-2

## Lecture-3

V-I and I-V converters, generalized Impedance converter

# VCIS (Transconductance Amplifier) Summary

## Voltage to Current Converter

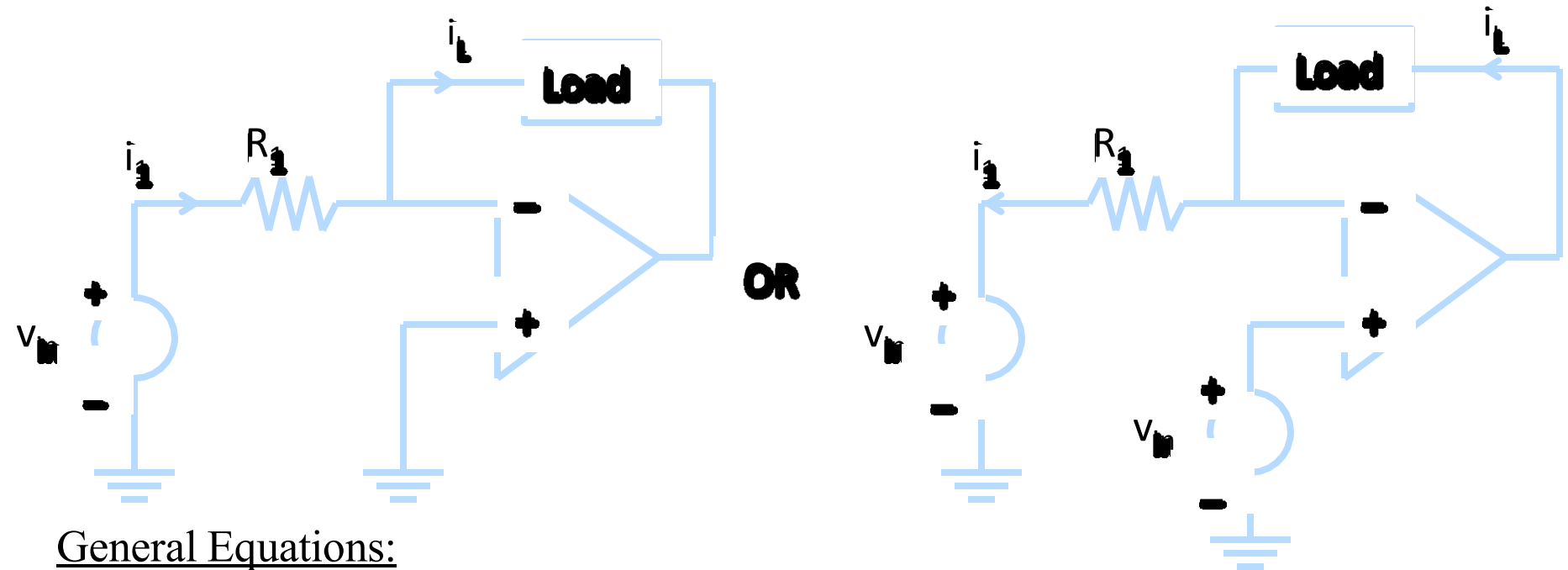

### General Equations:

$$i_L = i_1 = v_1/R_1$$

$$V_1 = V_{in}$$

$$\text{The transconductance, } g_m = i_o/V_{in} = 1/R_1$$


$$\text{Therefore, } i_L = i_1 = v_{in}/R_1 = g_m V_{in}$$

The maximum load resistance is determined by:

$$R_{L(max)} = v_{o(max)}/i_L$$

# VCIS (Transconductance Amplifier)

## Voltage to Current Converter Example

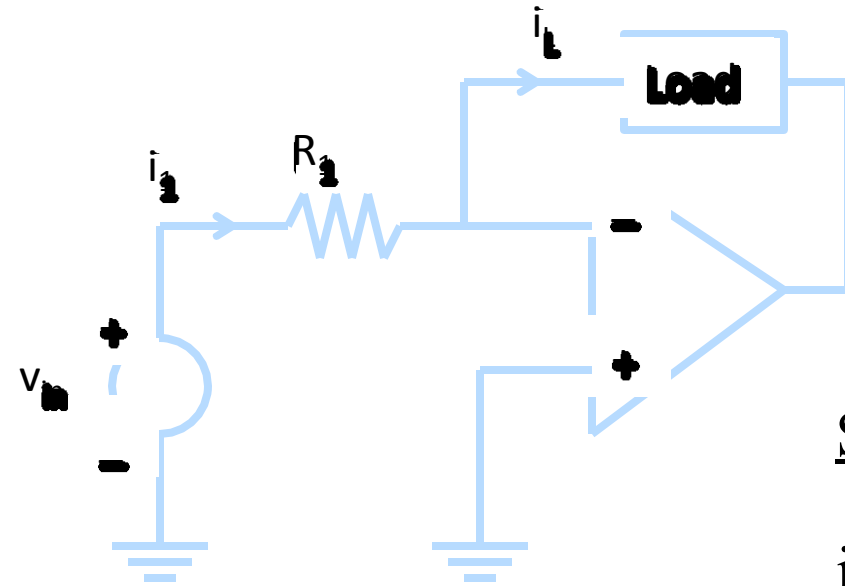

Given:  $v_{in} = 2 \text{ V}$ ,  $R_1 = 2 \text{ k}\Omega$

$V_{o(max)} = 10 \text{ V}$

Find:  $i_L$ ,  $g_m$  and  $R_{L(max)}$

Solution:

$$i_L = i_1 = v_{in}/R_1 = 2 / 2000 = 1 \text{ mA}$$

$$g_m = i_o/v_{in} = 1/R_1 = 1 / 2000 = 0.5 \text{ mS}$$


$$R_{L(max)} = v_{o(max)}/i_L = 10 \text{ V} / 1 \text{ mA} \\ = 10 \text{ k}\Omega$$

Note:

- If  $R_L > R_{L(max)}$  the op amp will saturate
- The output current,  $i_L$  is independent of the load resistance.

# VCIS (Transresistance Amplifier) Summary

## Current to Voltage Converter

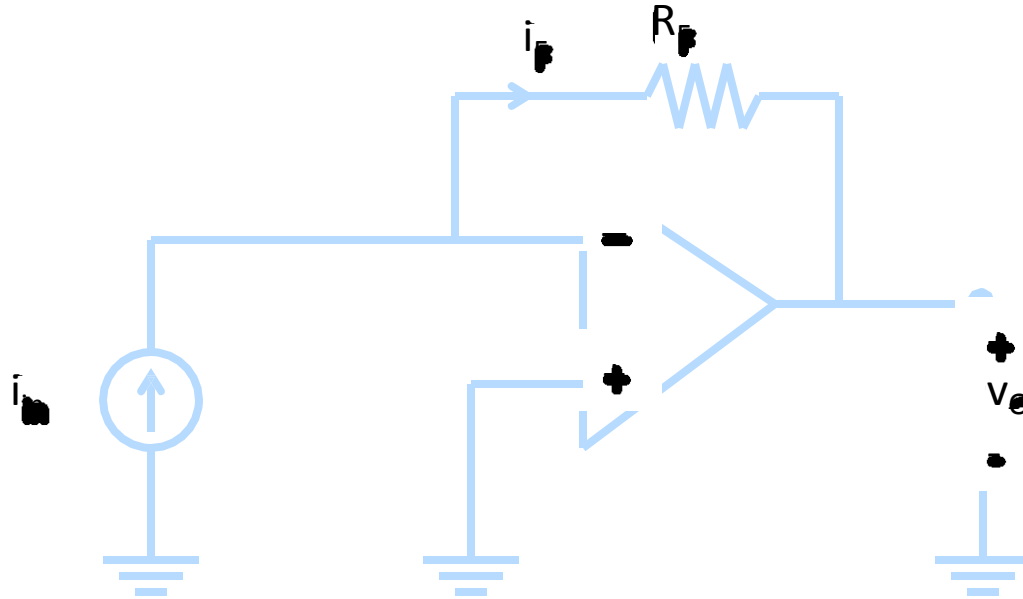

### General Equations:

$$i_F = i_{in}$$

$$V_o = -i_F R_F$$

$$r_m = V_o / i_{in} = R_F$$

# VCIS (Transresistance Amplifier) Summary

## Current to Voltage Converter

- Transresistance Amplifiers are used for low-power applications to produce an output voltage proportional to the input current.
- Photodiodes and Phototransistors, which are used in the production of solar power are commonly modeled as current sources.
- Current to Voltage Converters can be used to convert these current sources to more commonly used voltage sources.