

Unit-2

Lecture-6


**First and second order LP, HP, BP BS and All pass active filters, KHN,
Tow-Thomas and State Variable Biquad filters**

ACTIVE LOW-PASS FILTERS

Advantages of active filters over passive filters (R, L, and C elements only):

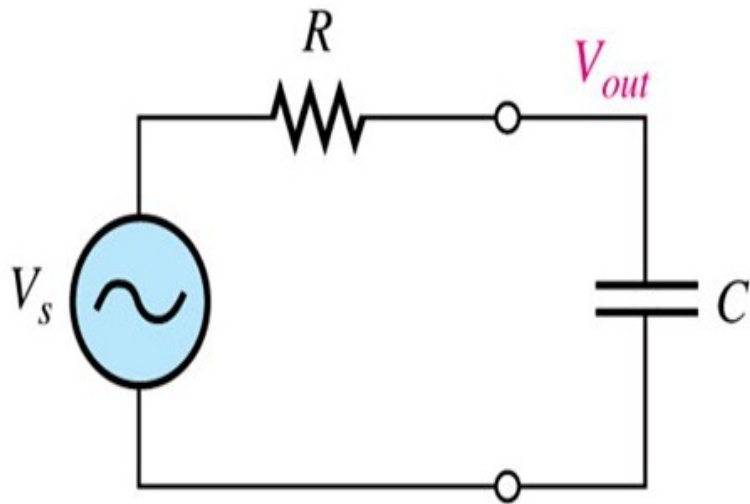1. By containing the op-amp, active filters can be designed to provide required gain, and hence **no signal attenuation** as the signal passes through the filter.
2. **No loading problem**, due to the high input impedance of the op-amp prevents excessive loading of the driving source, and the low output impedance of the op-amp prevents the filter from being affected by the load that it is driving.
3. **Easy to adjust over a wide frequency range** without altering the desired response.

➤ Figure below shows the basic Low-Pass filter circuit



(b) Basic low-pass circuit

At critical frequency,

Resistance = Capacitance

$$R = X_c$$


$$R = \frac{1}{\omega_c C}$$

$$R = \frac{1}{2\pi f_c C}$$


So, critical frequency ;

$$f_c = \frac{1}{2\pi RC}$$

Single-Pole Filter

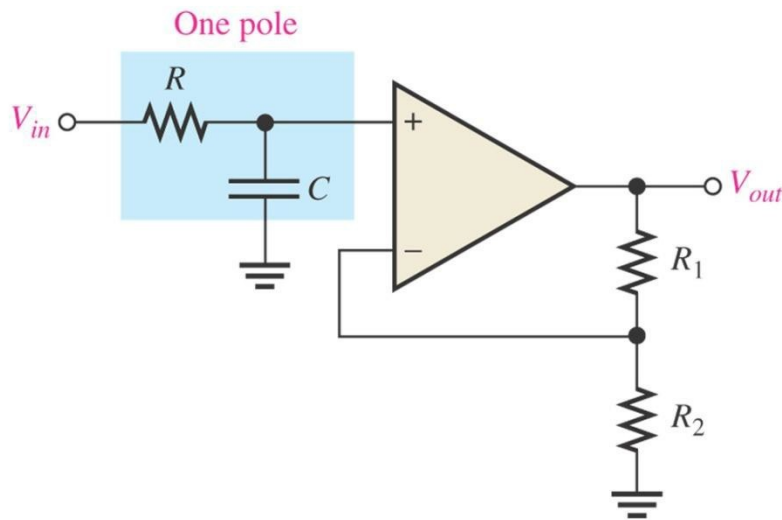

(a)

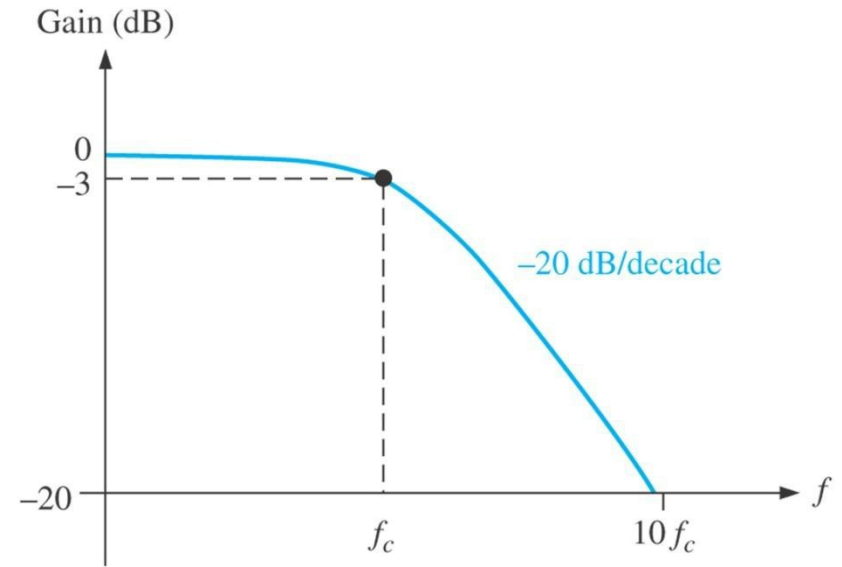

(b)

Single-pole active low-pass filter and response curve.

- This filter provides a roll-off rate of -20 dB/decade above the critical frequency.

➤ The op-amp in single-pole filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband is set by the values of R_1 and R_2 :


$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

➤ The critical frequency of the single-pole filter is :

$$f_c = \frac{1}{2\pi RC}$$

Sallen-Key Low-Pass Filter

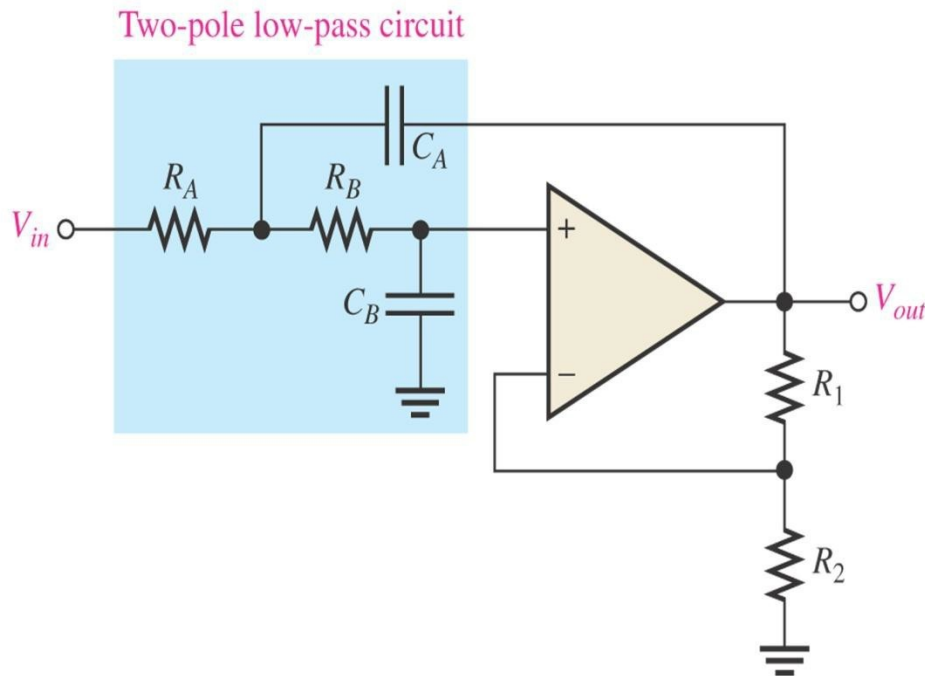➤ **Sallen-Key** is one of the most common configurations for a **second order** (two-pole) filter:



Basic Sallen-Key low-pass filter

➤ There are two low-pass RC circuits that provide a **roll-off of -40 dB/decade above f_c** (assuming a Butterworth characteristics).

➤ One RC circuit consists of **R_A and C_A** and the second circuit consists of **R_B and C_B**

- The critical frequency for the Sallen-Key filter is :


$$f_c = \frac{1}{2\pi \sqrt{R_A R_B C_A C_B}}$$

- For $R_A = R_B = R$ and $C_A = C_B = C$, thus the critical frequency :

$$f_c = \frac{1}{2\pi RC}$$


Cascading Low-Pass Filter

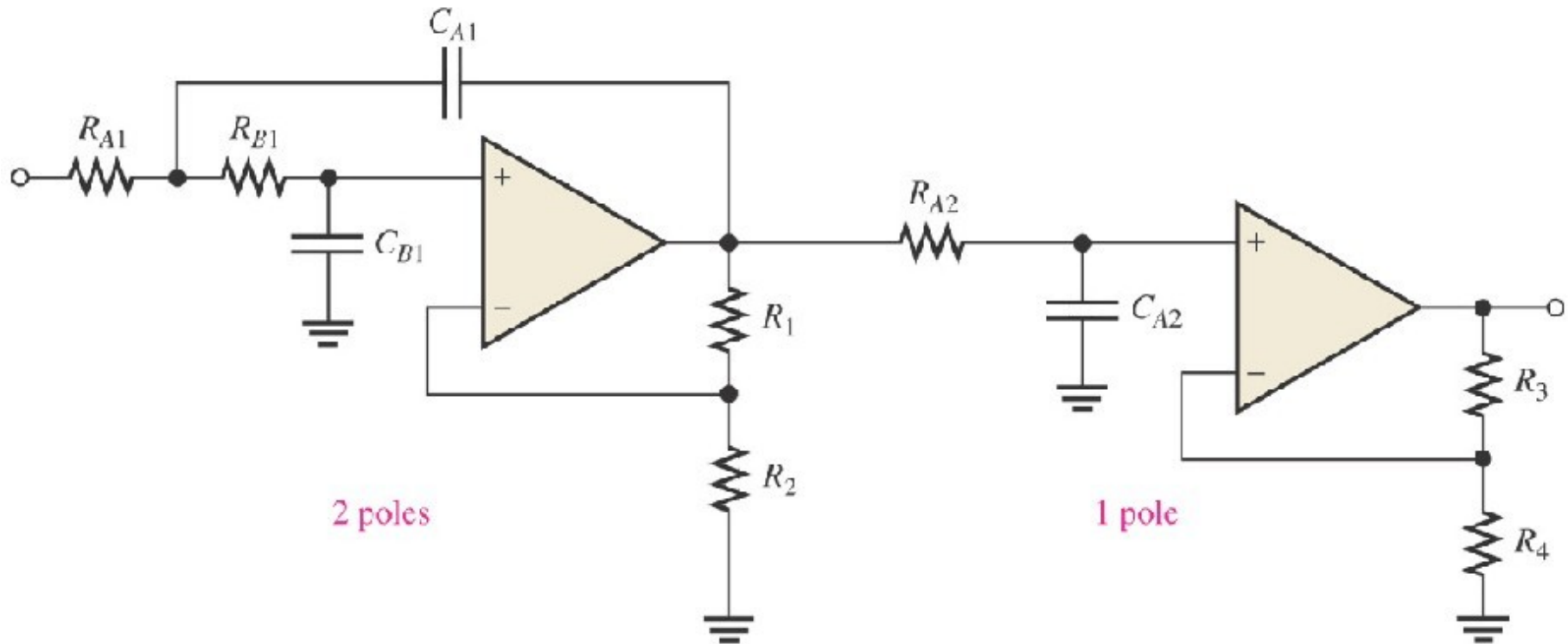➤ A **three-pole filter** is required to provide a roll-off rate of **-60 dB/decade**. This is done by cascading a **two-pole Sallen-Key low-pass filter** and a **single-pole low-pass filter**



Cascaded low-pass filter: third-order configuration.

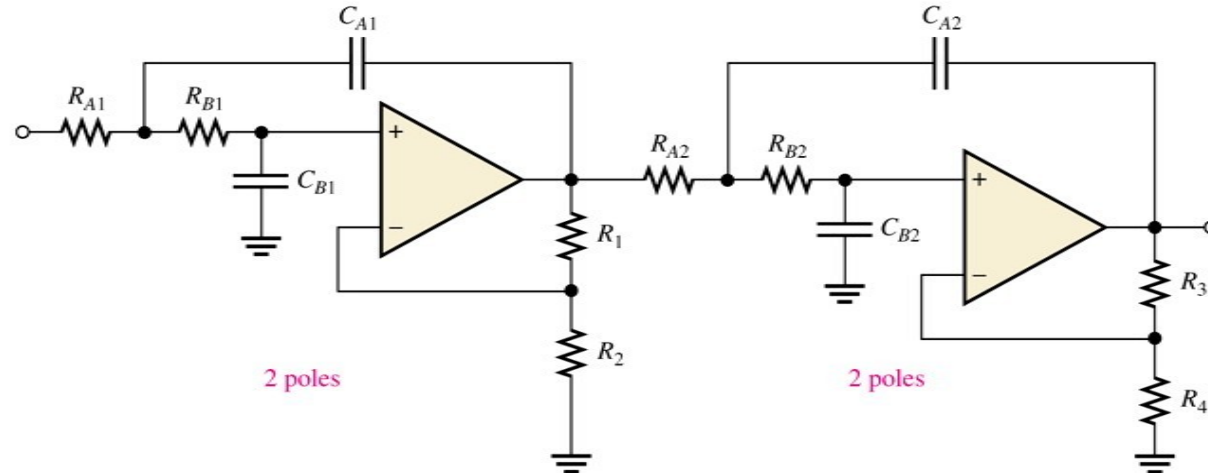➤ A four-pole filter is required to provide a roll-off rate of -80 dB/decade. This is done by cascading a two-pole Sallen-Key low-pass filter and a two-pole Sallen-Key low-pass filter.




(b) Fourth-order configuration

Cascaded low-pass filter: fourth-order configuration.

ACTIVE HIGH-PASS FILTERS

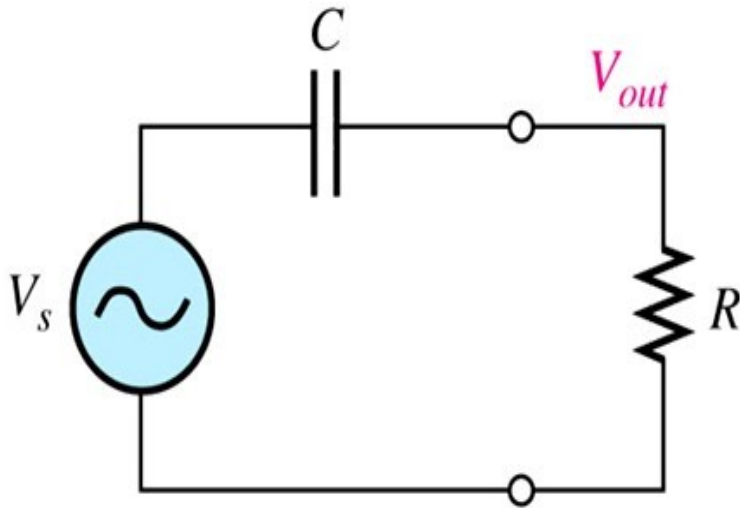➤ Figure below shows the basic High-Pass filter circuit :



(b) Basic high-pass circuit

At critical frequency,

Resistance = Capacitance

$$R = X_c$$

$$R = \frac{1}{\omega_c C}$$


$$R = \frac{1}{2\pi f_c C}$$

So, critical frequency ;


$$f_c = \frac{1}{2\pi RC}$$

Single-Pole Filter

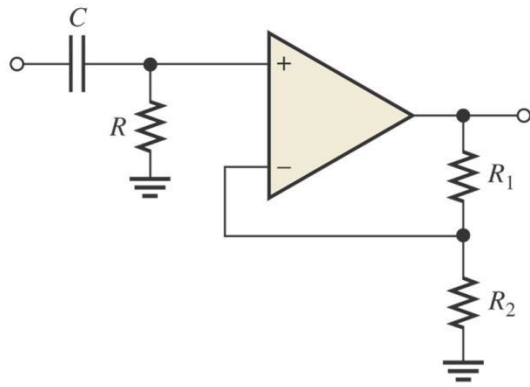- In high-pass filters, the roles of the capacitor and resistor are reversed in the RC circuits as shown from Figure (a). The negative feedback circuit is the same as for the low-pass filters.
- Figure (b) shows a high-pass active filter with a -20dB/decade roll-off



(a)

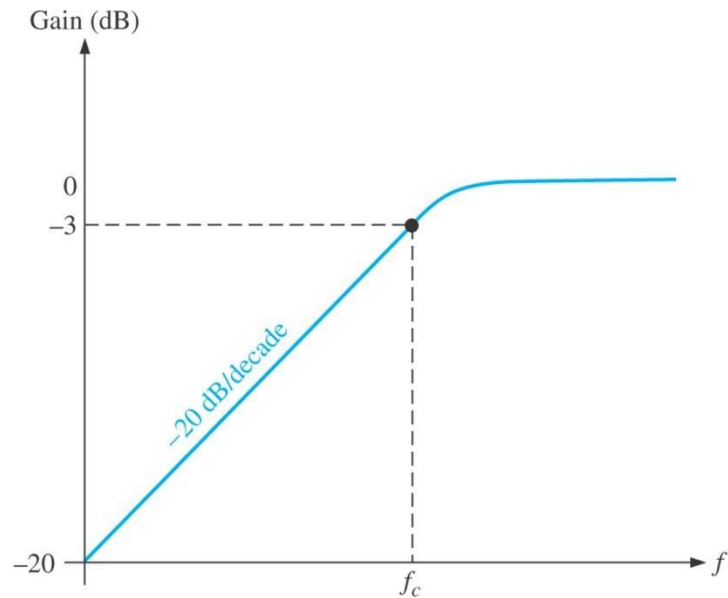

(b)

Single-pole active high-pass filter and response curve.

➤ The op-amp in single-pole filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband is set by the values of R_1 and R_2 :


$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

➤ The critical frequency of the single-pole filter is :

$$f_c = \frac{1}{2\pi RC}$$

Sallen-Key High-Pass Filter

- Components R_A , C_A , R_B and C_B form the **second order** (two-pole) frequency-selective circuit.
- The position of the resistors and capacitors in the frequency-selective circuit are **opposite** in low pass configuration.
- There are two high-pass RC circuits that provide a **roll-off of -40 dB/decade above f_c**
- The **response characteristics** can be optimized by proper selection of the **feedback resistors**, R_1 and R_2 .

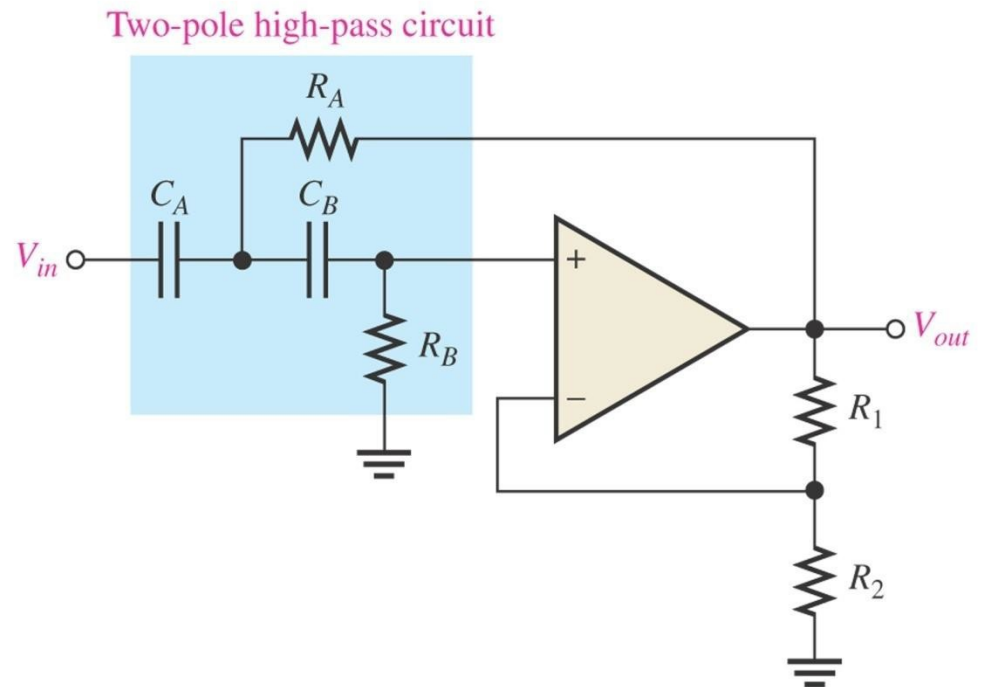

Basic Sallen-Key high-pass filter

➤ The critical frequency for the Sallen-Key filter is :


$$f_c = \frac{1}{2\pi \sqrt{R_A R_B C_A C_B}}$$

➤ For $R_A = R_B = R$ and $C_A = C_B = C$, thus the critical frequency :

$$f_c = \frac{1}{2\pi RC}$$

Cascading High-Pass Filter

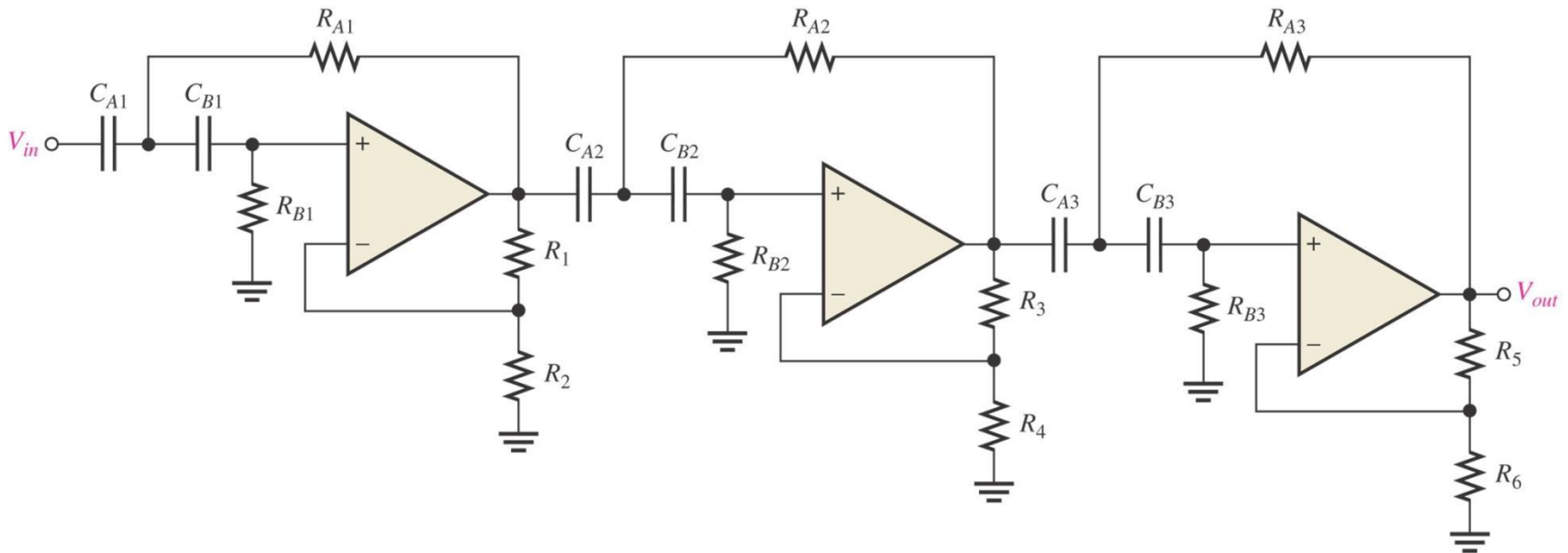- As with the low-pass filter, first- and second-order high-pass filters can be cascaded to provide three or more poles and thereby create faster roll-off rates.
- A **six-pole high-pass filter** consisting of **three Sallen-Key two-pole** stages with the roll-off rate of **-120 dB/decade**



Sixth-order high-pass filter