

# Unit-2


## Lecture-8

**Sinusoidal oscillators**

# Oscillators

- With the addition of a capacitor and resistor, the Schmitt trigger can be turned into a simple oscillator.
- Technically, it's known as an *astable multivibrator*.
- Before looking at the circuit, it is worth reviewing the transient response of a first order RC network.

# Transient Response

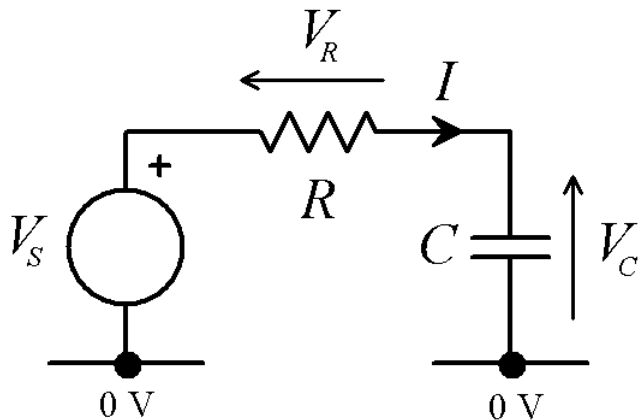

$$\begin{aligned} I &= C \frac{dV_C}{dt} = C \frac{d(V_S - V_R)}{dt} \\ &= C \frac{dV_S}{dt} - C \frac{dV_R}{dt} = -C \frac{dV_R}{dt} \end{aligned}$$

and

$$I = \frac{V_R}{R}$$

$$\therefore \frac{dV_R}{dt} = -\frac{V_R}{CR}$$

$\frac{dV_R}{dt} = -\frac{V_R}{CR}$  is a separable first order differential equation.


These are the easiest kind to solve!

First, rearrange:  $\frac{1}{V_R} dV_R = -\frac{1}{CR} dt$

and integrate each side:  $\ln(V_R) = -\frac{t}{CR} + k \Rightarrow V_R = \tilde{k} \exp\left[-\frac{t}{CR}\right]$

The constant,  $\tilde{k}$ , is the value of  $V_R$  when time=0, so:
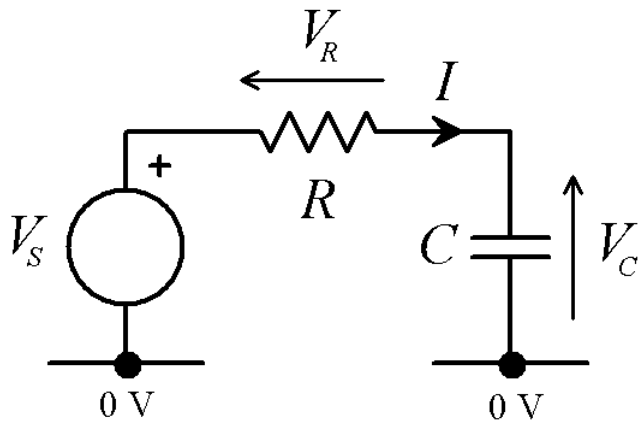
$$V_R(t) = V_R(0) \exp\left[-\frac{t}{CR}\right]$$




$$V_R(t) = V_R(0) \exp\left[-\frac{t}{CR}\right]$$

$$V_C = V_S - V_R$$


$$V_C(t) = V_S - V_R(0) \exp\left[-\frac{t}{CR}\right]$$
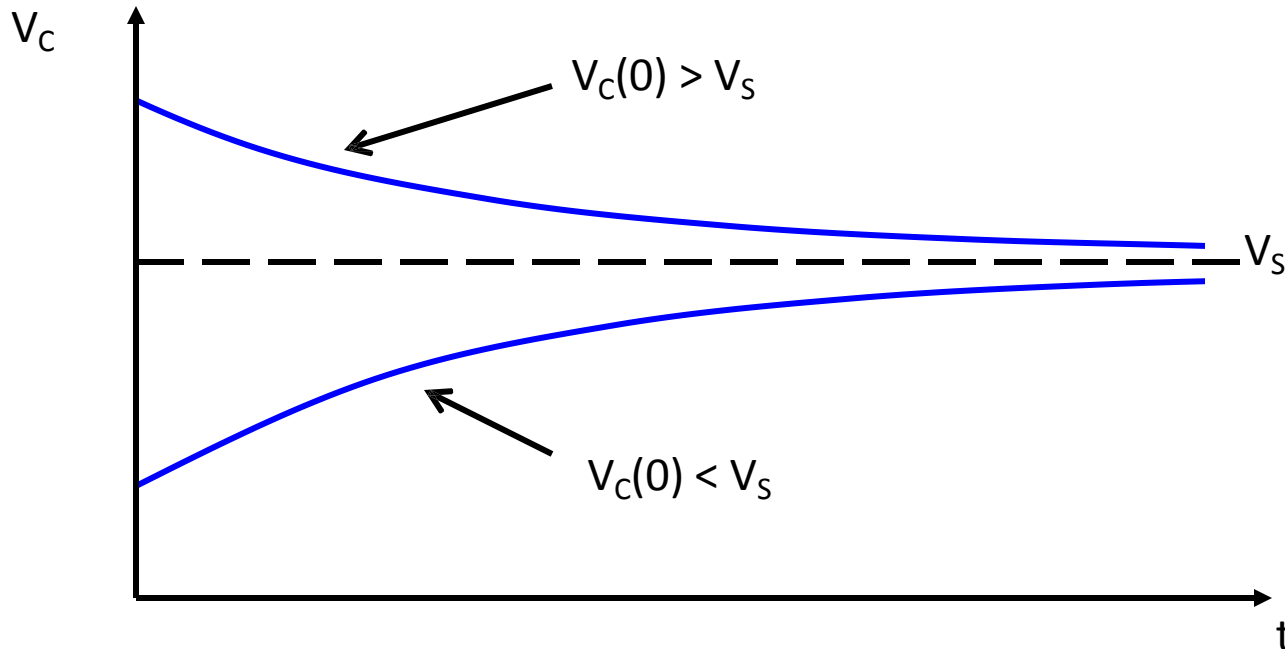
$$= V_S - [V_S - V_C(0)] \exp\left[-\frac{t}{CR}\right]$$




NB. In either case,  
 $V_C \rightarrow V_S$  as  $t \rightarrow \infty$ .  
 $V_C(\infty)$  is known as  
the *aiming*  
*potential*.

# Oscillator Circuit

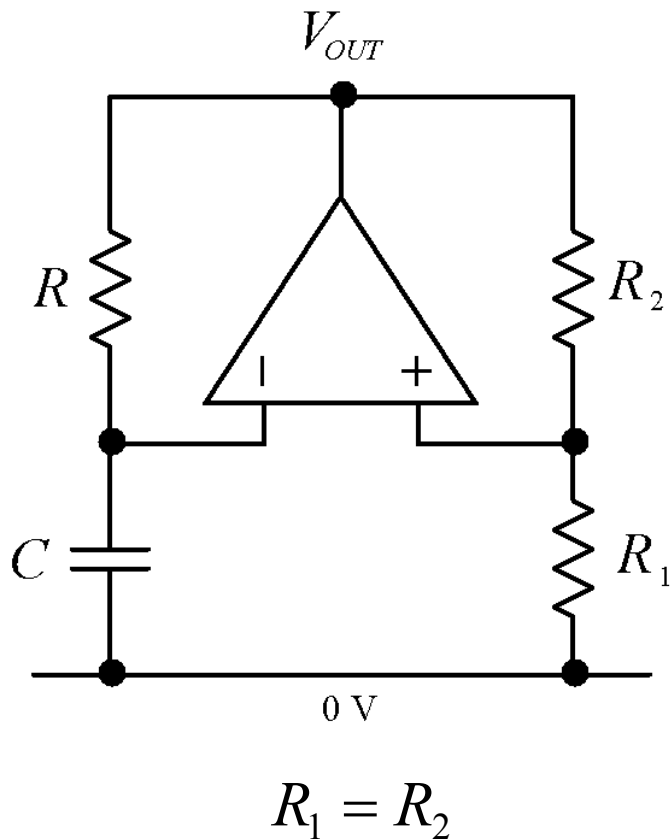


- The op-amp,  $R_1$  and  $R_2$  form an inverting Schmitt trigger
- As  $R_1 = R_2$ , threshold levels are  $\pm V_{SAT}/2$
- The output is fed-back to the inverting input via an RC network
- The aiming potential of the capacitor voltage will be either  $+V_{SAT}$  or  $-V_{SAT}$

# Waveforms

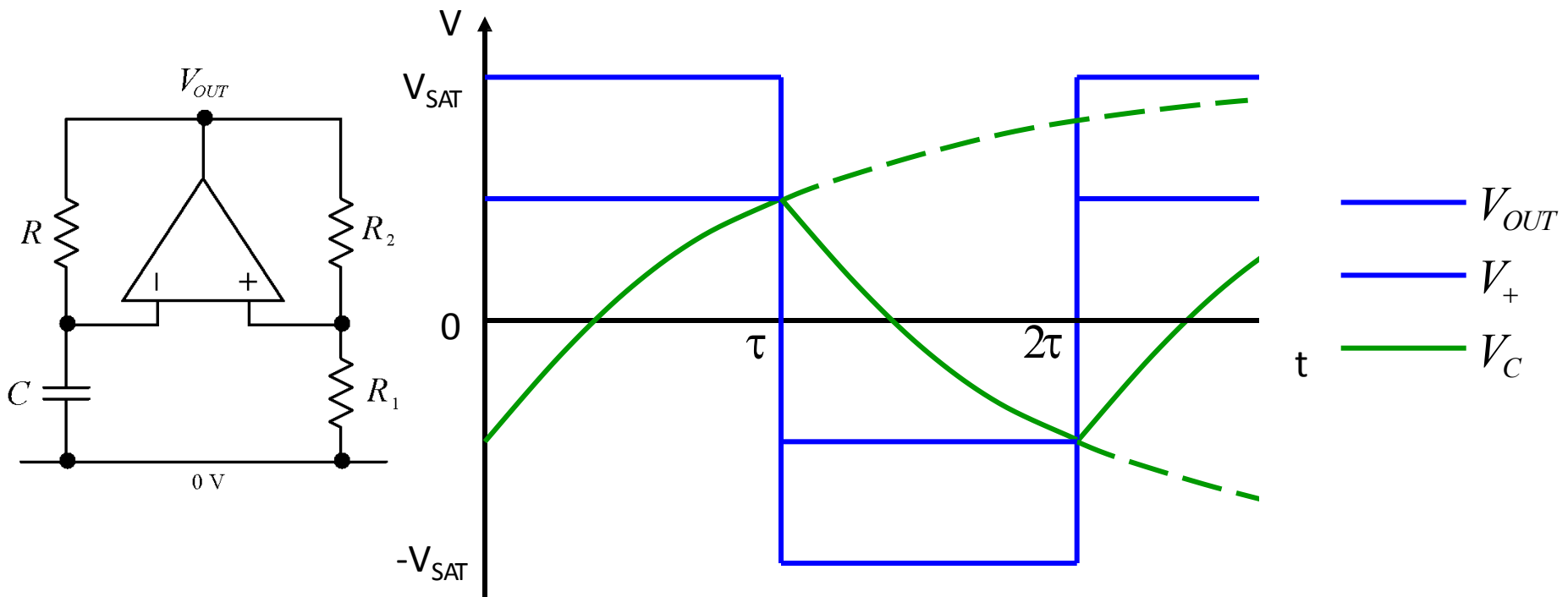
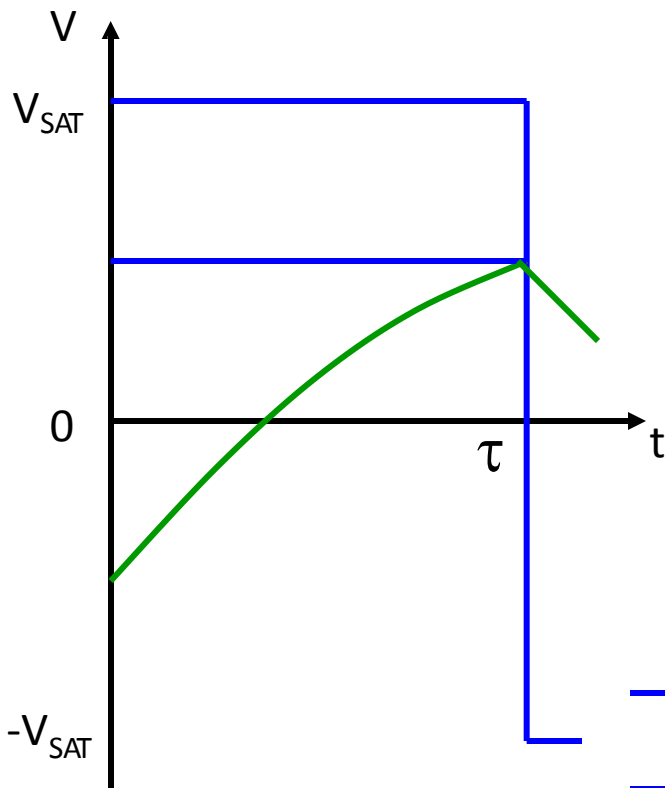
# Analysis

To calculate the time-period, consider just one half-cycle of the oscillation.



—  $V_{OUT}$


—  $V_+$

—  $V_C$

$$\begin{aligned}
 V_C(t) &= V_{SAT} - [V_{SAT} - V_C(0)] \exp\left[-\frac{t}{CR}\right] \\
 &= V_{SAT} - [V_{SAT} - (-V_{SAT}/2)] \exp\left[-\frac{t}{CR}\right] \\
 &= V_{SAT} \left(1 - \frac{3}{2} \exp\left[-\frac{t}{CR}\right]\right)
 \end{aligned}$$



# Analysis (cont)

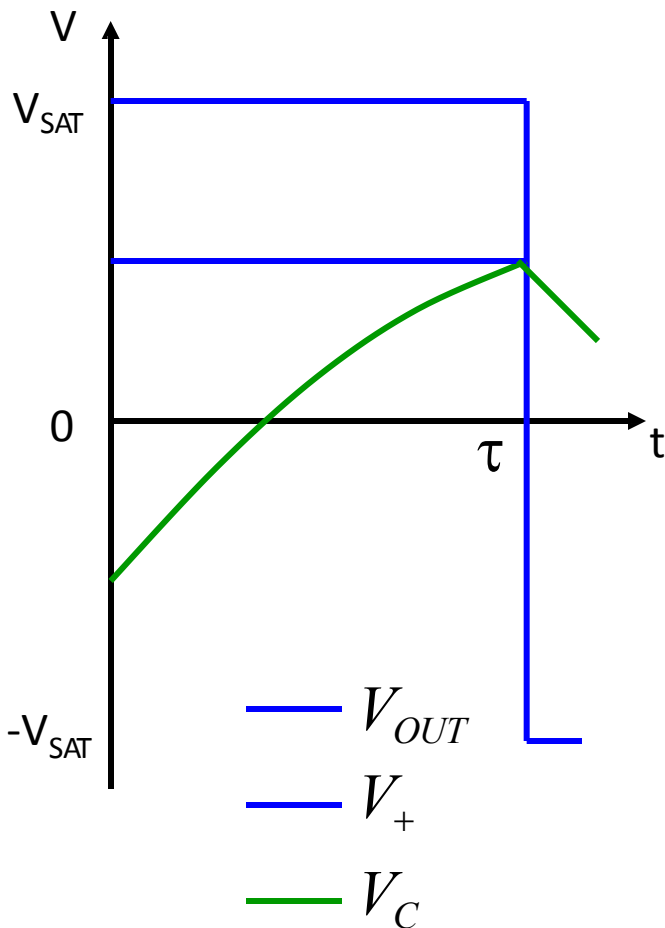

Half-cycle ends when  $V_C$  reaches  $V_{SAT}/2$

$$V_C(\tau) = \frac{V_{SAT}}{2} = V_{SAT} \left( 1 - \frac{3}{2} \exp \left[ -\frac{\tau}{CR} \right] \right)$$

$$\therefore \frac{1}{2} = 1 - \frac{3}{2} \exp \left[ -\frac{\tau}{CR} \right]$$

$$\Rightarrow \exp \left[ -\frac{\tau}{CR} \right] = \frac{1}{3}$$

$$\Rightarrow \tau = -CR \ln(1/3) = CR \ln(3)$$

Full period of oscillation is 2 half cycles,

$$T = 2\tau = 2CR \ln(3) \approx 2.2CR$$

# Oscillator Summary

- Using only a couple of extra components, the Schmitt trigger can be converted into a simple oscillator
- R & C set the period of oscillation independently of  $V_{SAT}$
- Many square wave oscillators work using the same basic principles