

UNIT-4

Lecture-1

**Log, Anti Log Amplifiers, Analog Multipliers
and their applications**


Nonlinear Op-Amp Circuits

- Most typical applications require op amp and its components to act linearly
 - I-V characteristics of passive devices such as resistors, capacitors should be described by linear equation (Ohm's Law)
 - For op amp, linear operation means input and output voltages are related by a constant proportionality (A_v should be constant)
- Some application require op amps to behave in nonlinear manner (logarithmic and antilogarithmic amplifiers)

Logarithmic Amplifier

- Output voltage is proportional to the logarithm of input voltage
- A device that behaves nonlinearly (logarithmically) should be used to control gain of op amp
 - Semiconductor diode
- Forward transfer characteristics of silicon diodes are closely described by Shockley's equation
$$I_F = I_s e^{(V_F/\eta V_T)}$$
 - I_s is diode saturation (leakage) current
 - e is base of natural logarithms ($e = 2.71828$)
 - V_F is forward voltage drop across diode
 - V_T is thermal equivalent voltage for diode (26 mV at 20°C)
 - η is emission coefficient or ideality factor (2 for currents of same magnitude as I_s to 1 for higher values of I_F)

Basic Log Amp operation


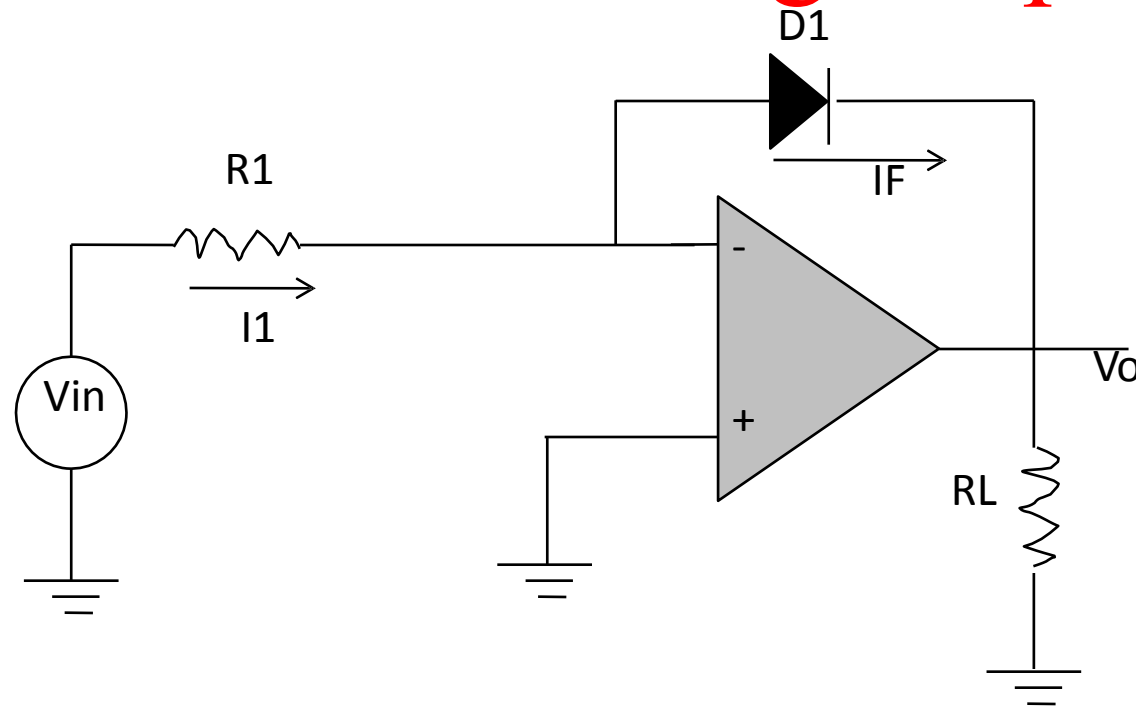


- $I1 = V_{in}/R1$
- $I_F = - I1$
- $I_F = - V_{in}/R1$
- $V_o = -V_F = -\eta V_T \ln(I_F/I_S)$
- $V_o = -\eta V_T \ln[V_{in}/(R1 I_S)]$
- $r_D = 26 \text{ mV} / I_F$
- $I_F < 1 \text{ mA (log amps)}$


• At higher current levels ($I_F > 1 \text{ mA}$) diodes begin to behave somewhat linearly

Logarithmic Amplifier

- Linear graph: voltage gain is very high for low input voltages and very low for high input voltages
- Semilogarithmic graph: straight line proves logarithmic nature of amplifier's transfer characteristic
- Transfer characteristics of log amps are usually expressed in terms of slope of V_o versus V_{in} plot in millivolts per decade
- η affects slope of transfer curve; I_S determines the y intercept

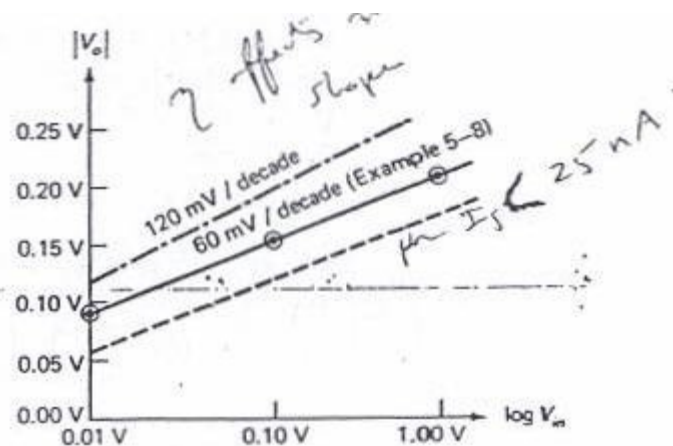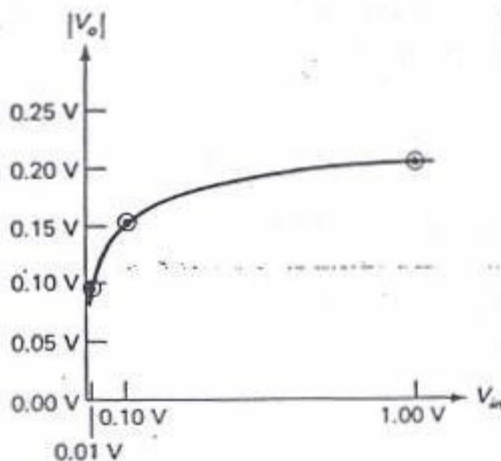

Additional Log Amp Variations


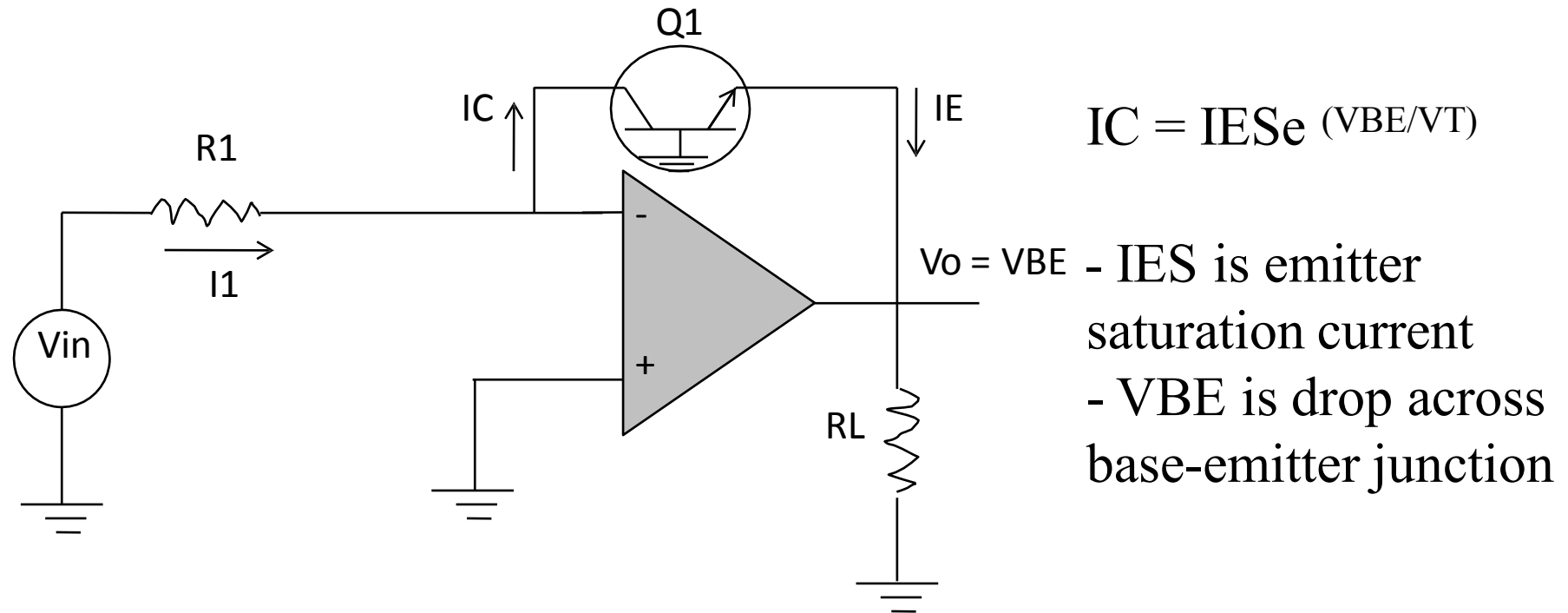


- Often a transistor is used as logging element in log amp (transdiode configuration)
- Transistor logging elements allow operation of log amp over wider current ranges (greater dynamic range)

Antilogarithmic Amplifier

- Output of an antilog amp is proportional to the antilog of the input voltage
- with diode logging element
 - $V_0 = -R_F I_S e^{(V_{in}/V_T)}$
- With transdiode logging element
 - $V_0 = -R_F I_{ES} e^{(V_{in}/V_T)}$
- As with log amp, it is necessary to know saturation currents and to tightly control junction temperature

Antilogarithmic Amplifier

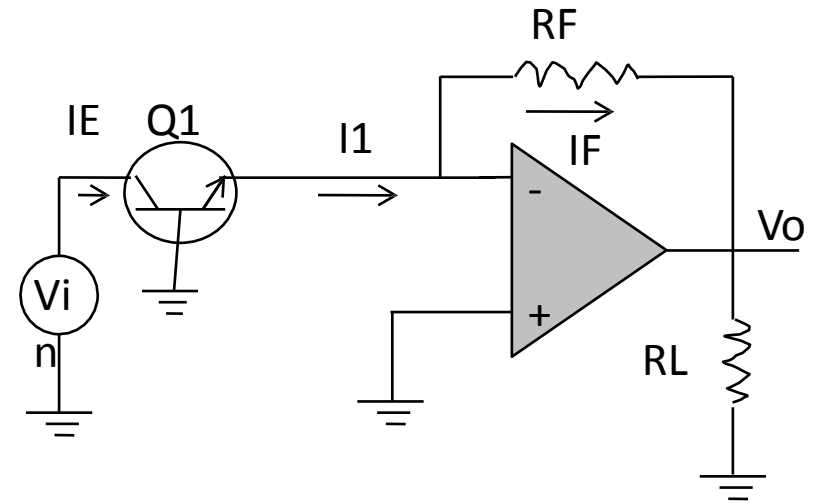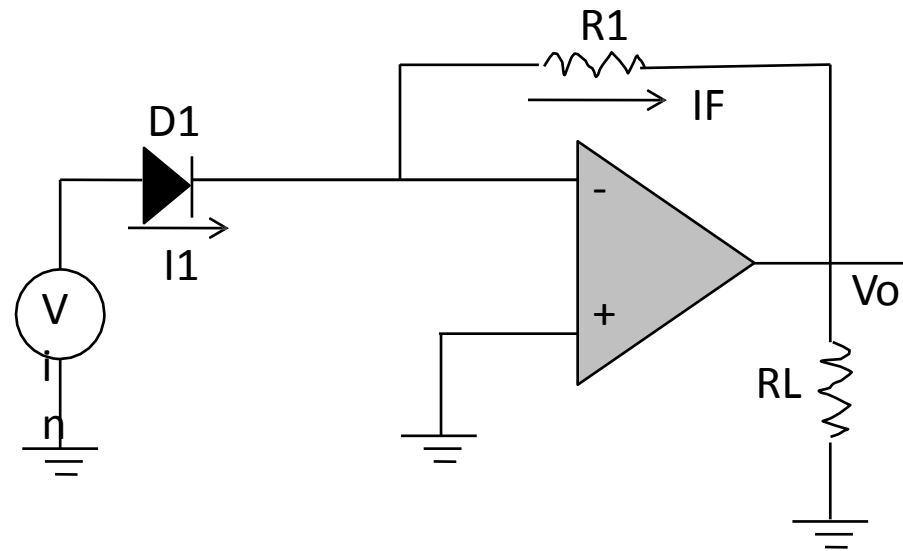


$$(\alpha = 1) I_1 = I_C = I_E$$


Logarithmic Amplifier Applications

- Logarithmic amplifiers are used in several areas
 - Log and antilog amps to form analog multipliers
 - Analog signal processing
- Analog Multipliers
 - $\ln xy = \ln x + \ln y$
 - $\ln (x/y) = \ln x - \ln y$


Analog Multipliers

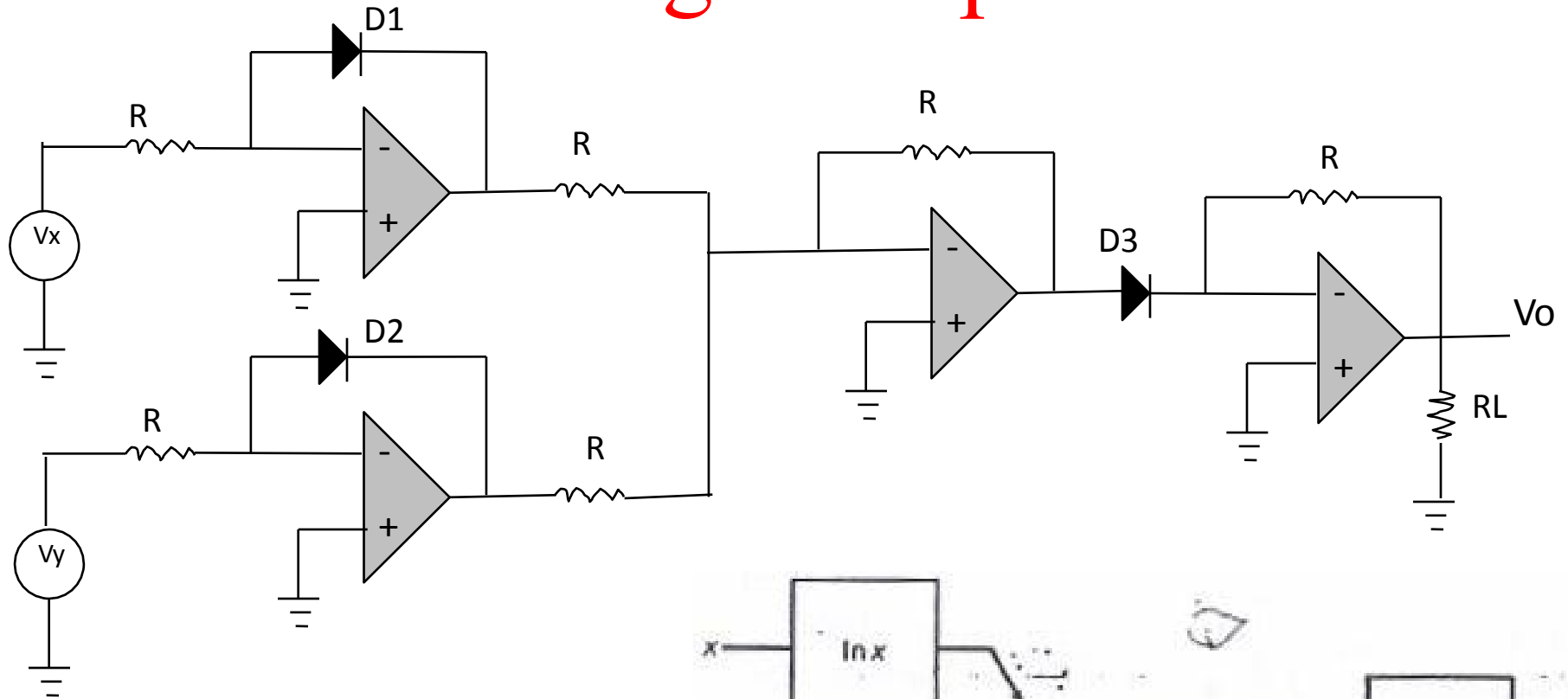

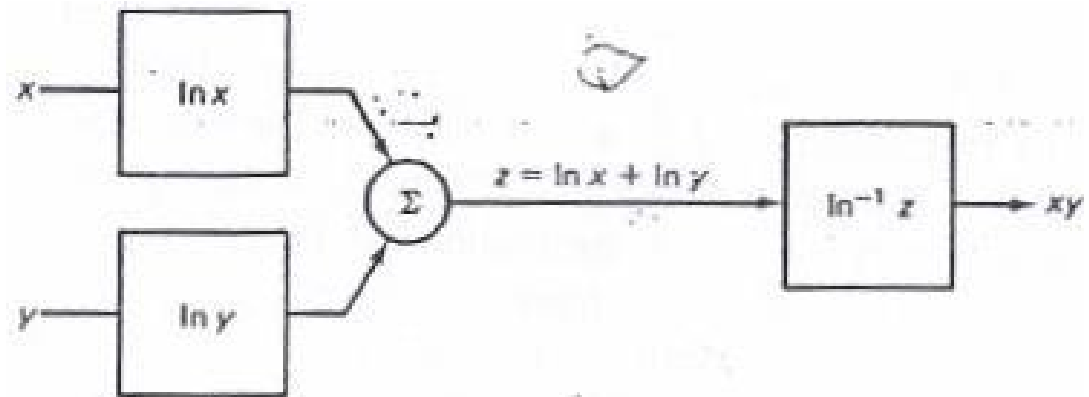One-quadrant multiplier: inputs must both be of same polarity




Analog Multipliers

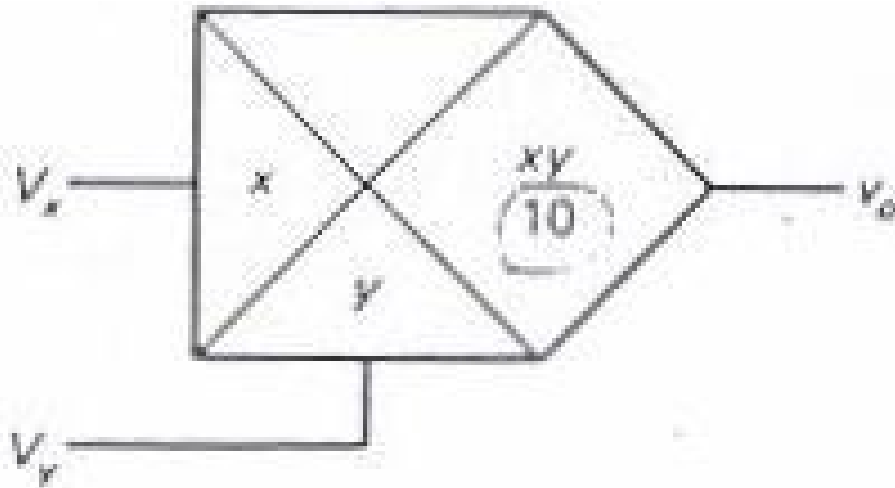

General symbol

Four quadrants
of operation

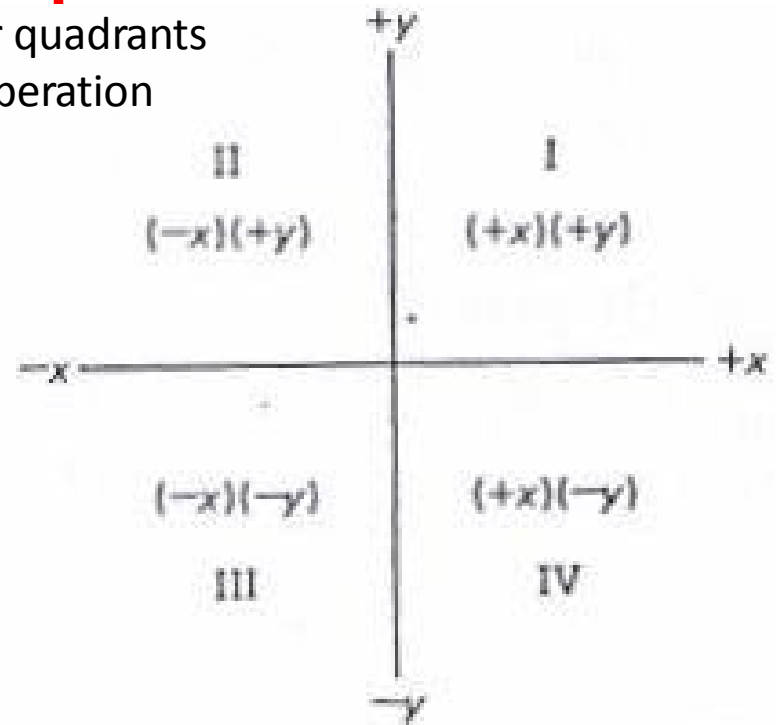


Two-quadrant multiplier: one input should have positive voltages, other input could have positive or negative voltages

Four-quadrant multiplier: any combinations of polarities on their inputs

Analog Multipliers

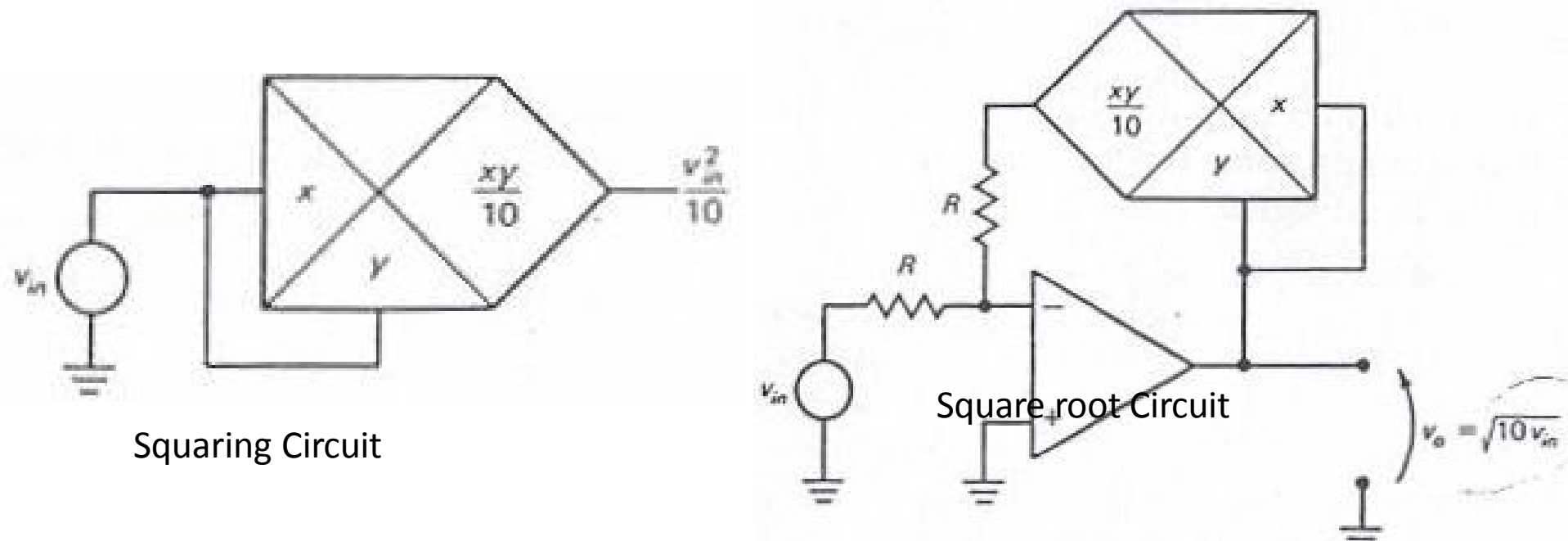Implementation of mathematical operations



Signal Processing

- Many transducers produce output voltages that vary nonlinearly with physical quantity being measured (thermistor)
- Often It is desirable to linearize outputs of such devices; logarithmic amps and analog multipliers can be used for such purposes
- Linearization of a signal using circuit with complementary transfer characteristics

