


# UNIT-4

## Lecture-2


**Precision Rectifiers, Op-amp as a comparator**
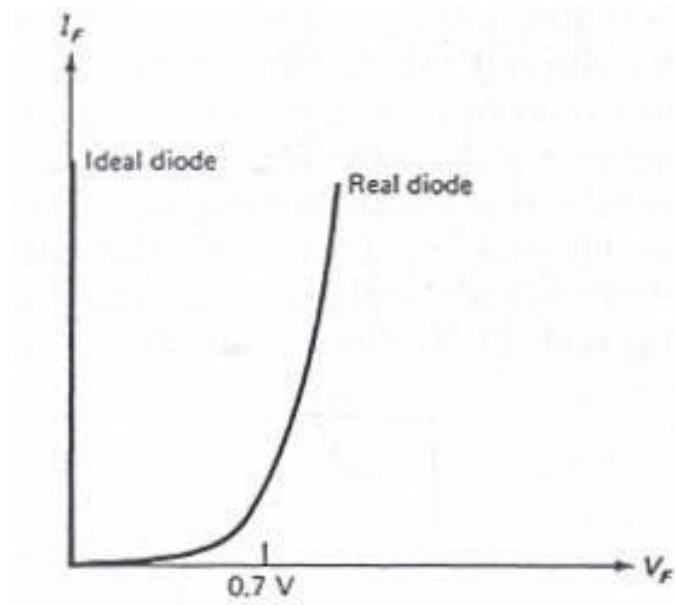
# Precision Rectifiers

- Op amps can be used to form nearly ideal rectifiers (convert ac to dc)
- Idea is to use negative feedback to make op amp behave like a rectifier with near-zero barrier potential and with linear I/O characteristic
- Transconductance curves for typical silicon diode and an ideal diode




# Precision Half-Wave Rectifier

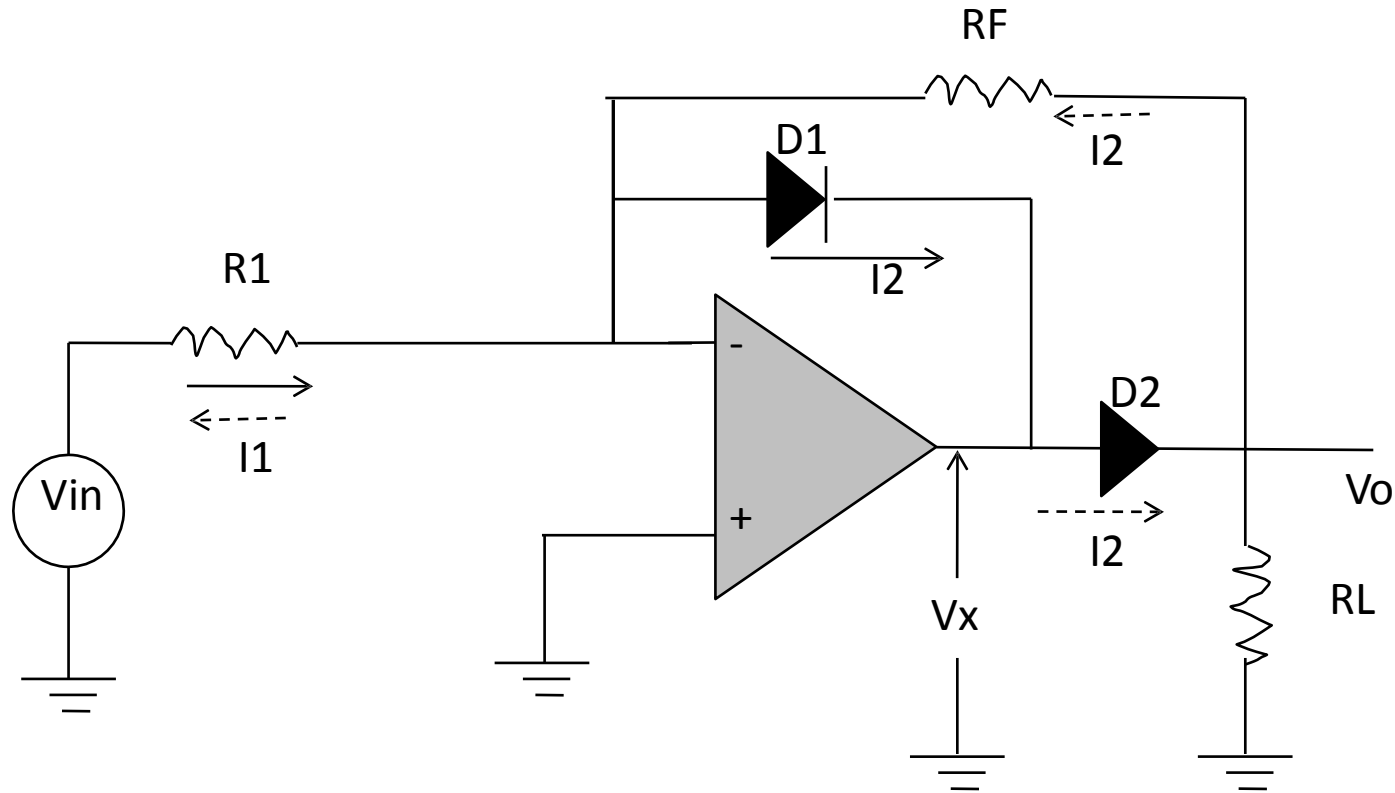


- Solid arrows represent current flow for positive half-cycles of  $V_{in}$  and dashed arrows represent current flow for negative half-cycles

# Precision Half-Wave Rectifier

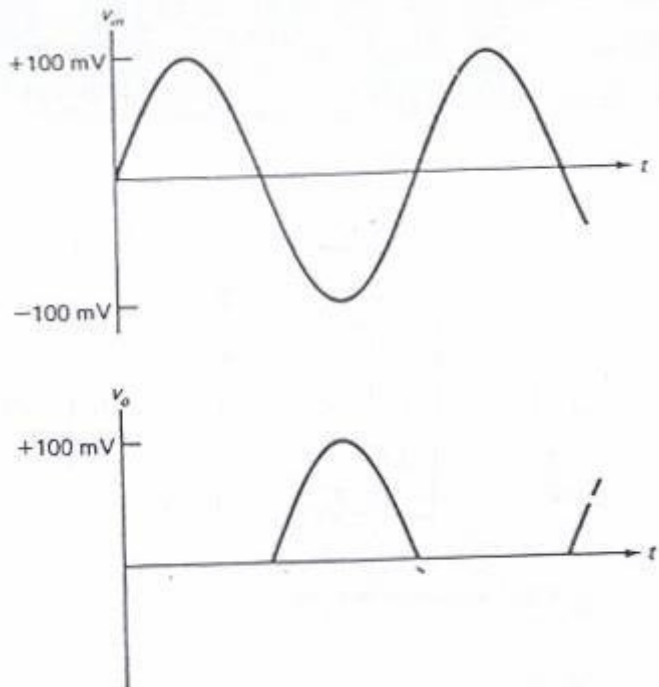

- If signal source is going positive, output of op amp begins to go negative, forward biasing  $D_1$ 
  - Since  $D_1$  is forward biased, output of op amp  $V_x$  will reach a maximum level of  $\sim -0.7V$  regardless of how far positive  $V_{in}$  goes
  - This is insufficient to appreciably forward bias  $D_2$ , and  $V_o$  remains at  $0V$
- On negative-going half-cycles,  $D_1$  is reverse-biased and  $D_2$  is forward biased
  - Negative feedback reduces barrier potential of  $D_2$  to  $0.7V/A_{OL}$  ( $\sim = 0$ )
  - Gain of circuit to negative-going portions of  $V_{in}$  is given by  $A_V = -R_F/R_1$

# Precision Full-Wave Rectifier

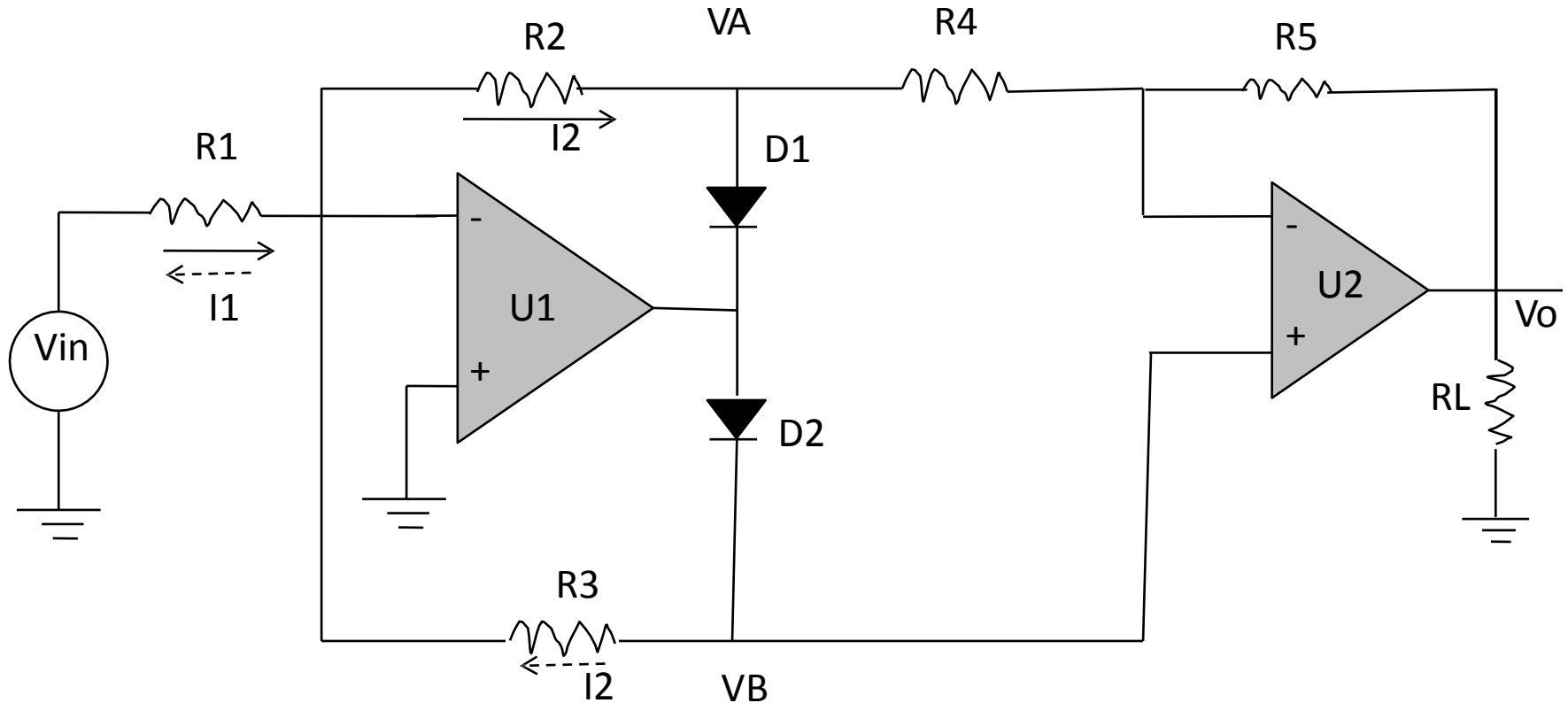


- Solid arrows represent current flow for positive half-cycles of  $V_{in}$  and dashed arrows represent current flow for negative half-cycles

# Precision Full-Wave Rectifier

- Positive half-cycle causes  $D_1$  to become forward-biased, while reverse-biasing  $D_2$ 
  - $V_B = 0 \text{ V}$
  - $V_A = -V_{in} R_2/R_1$
  - Output of  $U_2$  is  $V_0 = -V_A R_5/R_4 = V_{in} (R_2 R_5/R_1 R_4)$
- Negative half-cycle causes  $U_1$  output positive, forward-biasing  $D_2$  and reverse-biasing  $D_1$ 
  - $V_A = 0 \text{ V}$
  - $V_B = -V_{in} R_3/R_1$
  - Output of  $U_2$  (noninverting configuration) is
$$V_0 = V_B [1 + (R_5/R_4)] = -V_{in} [(R_3/R_1) + (R_3 R_5/R_1 R_4)]$$
  - if  $R_3 = R_1/2$ , both half-cycles will receive equal gain

# Comparators

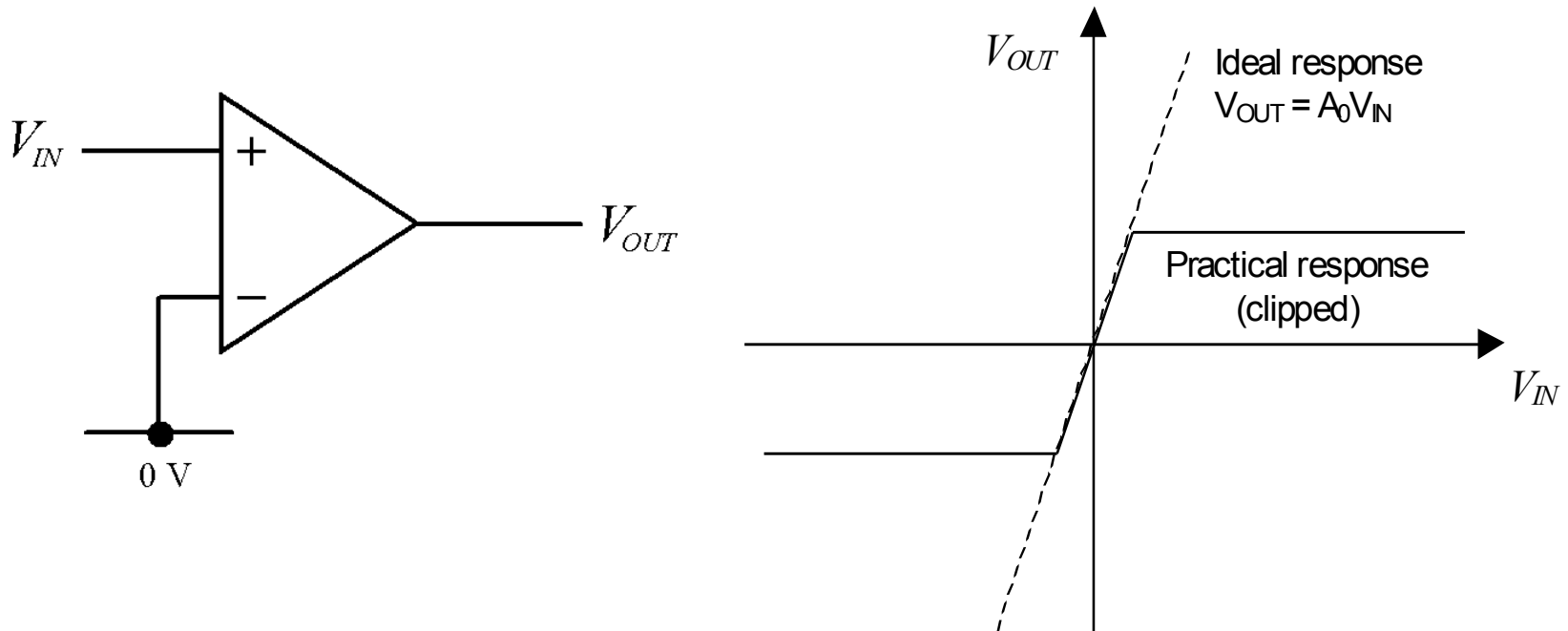

If  $A_0$  is large, practical response can be approximated as :

$$V_{IN} > 0 \Rightarrow V_+ > V_- \Rightarrow V_{OUT} = +V_{SAT}$$

$$V_{IN} < 0 \Rightarrow V_+ < V_- \Rightarrow V_{OUT} = -V_{SAT}$$

# Hysteresis

- A comparator with hysteresis has a ‘safety margin’.
- One of two thresholds is used depending on the current output state.

