
UNIT-5

Lecture-3

PLL Basics and Design

What is it?

- PLL = Phase Lock Loop
 - 1. A circuit which synchronizes an adjustable oscillator with another oscillator by the comparison of phase between the two signals.
 - 2. An electronic circuit that synchronizes itself to an external reference signal.
-

What is it for?


- To generate High Frequency Clock in Microprocessor.
 - In Mobile Communication to generate Carrier Frequency.
 - Can you think of any other Application?
Actually there are many.
-

What does Industry say?

- ST Microelectronics has vacancies for “PLL Designers”.
 - Texas Instruments (TI) want to recruit “PLL designers”.
 - A lot more Opportunities.....
 - Why it is so challenging?
-

Basic Block Diagram

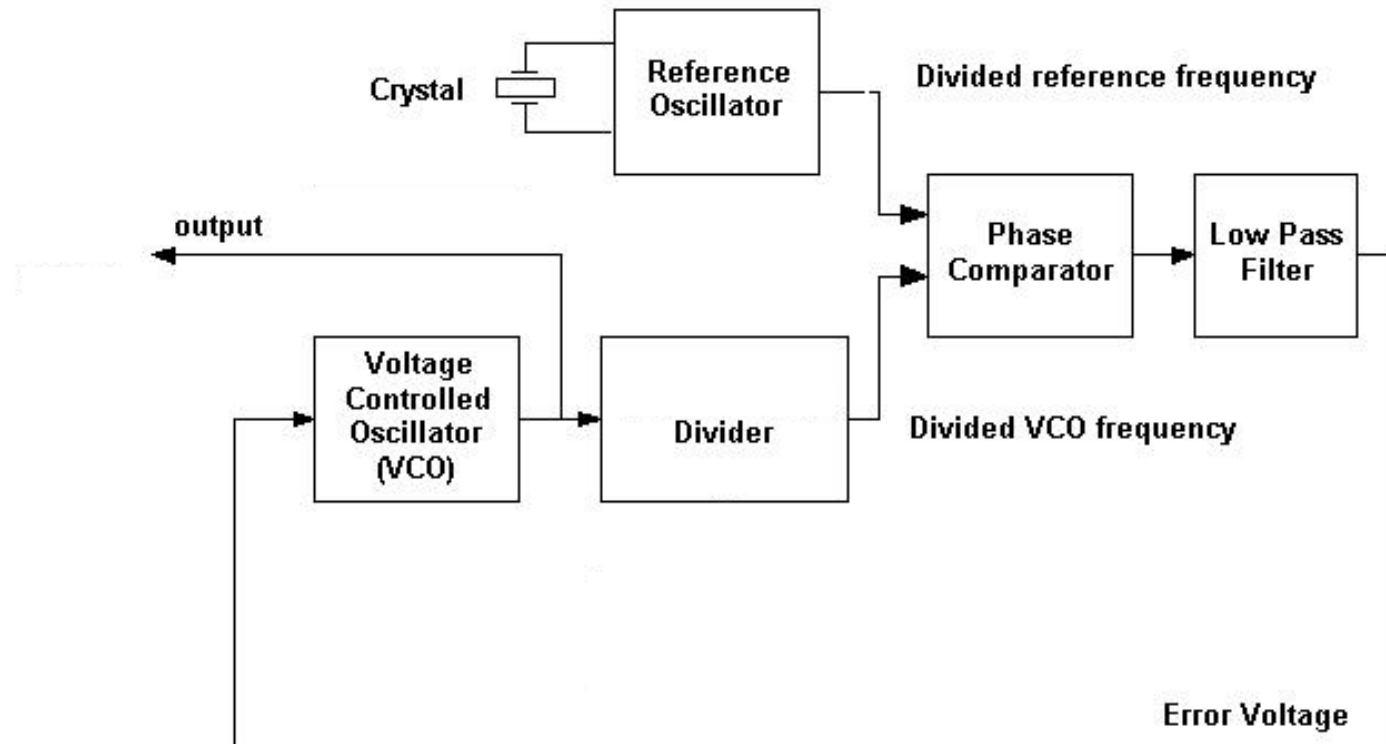Block Diagram of Phase Locked Loop Controlled Oscillator



1. Voltage Controlled Oscillator (VCO)



- What it does?
 - Requirements:
 - High Frequency Operation
 - Good Programmability Range
 - Less sensitive to environment
 - Basic Model: $F_{out} = K * V_{in}$
 - Different Oscillators in literature. How to Select?
 - A simple Example: Ring Oscillator
 - Common Challenges:
 - Programmability Range (Giga-Hertz Order)
 - Maximum Noise limit
-

2. Divider

- What it Does?
- Requirements:
 - Should work on High Frequency(Giga Hertz Order)
 - Should be less power Consuming
- Challenges:
 - Power Consumption (Power is proportional to frequency)
 - Switching Speed.

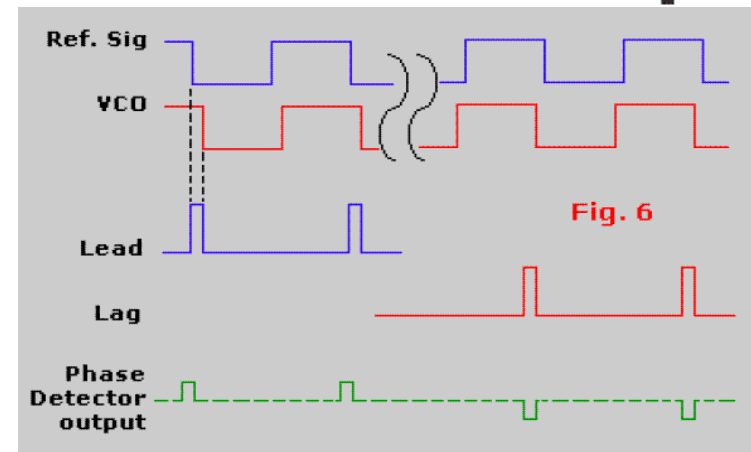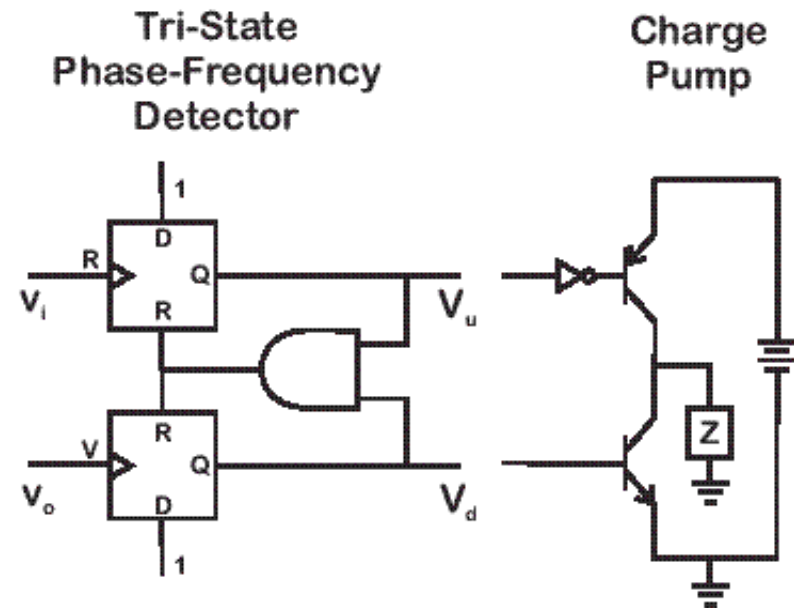
3. Phase-Frequency Detector (PFD)

- What it does?
- Requirement:
 - High Sensitivity
 - Moderate Frequency Operation
- Challenges:
 - Linearity of PFD
 - Gain of PFD




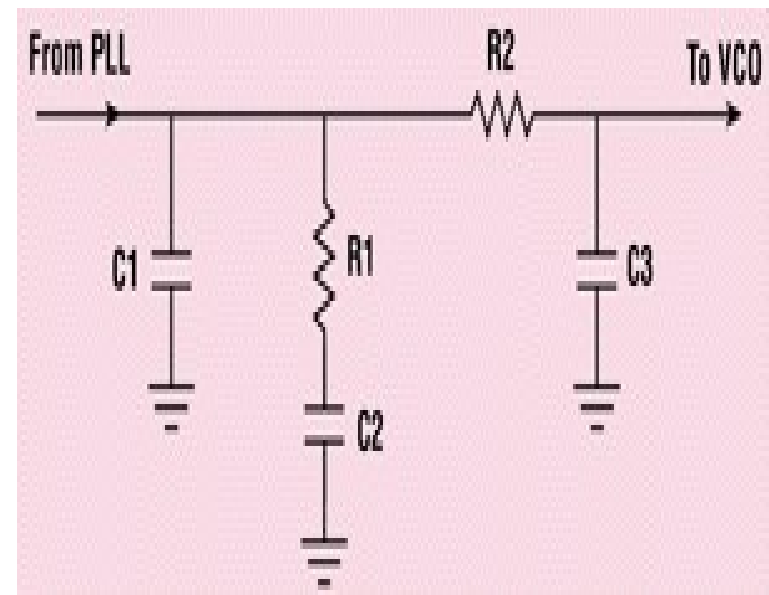4. Loop Filter

- Functionality
- Low pass filter
- Filters out noise of PLL loop



Control Model of PLL

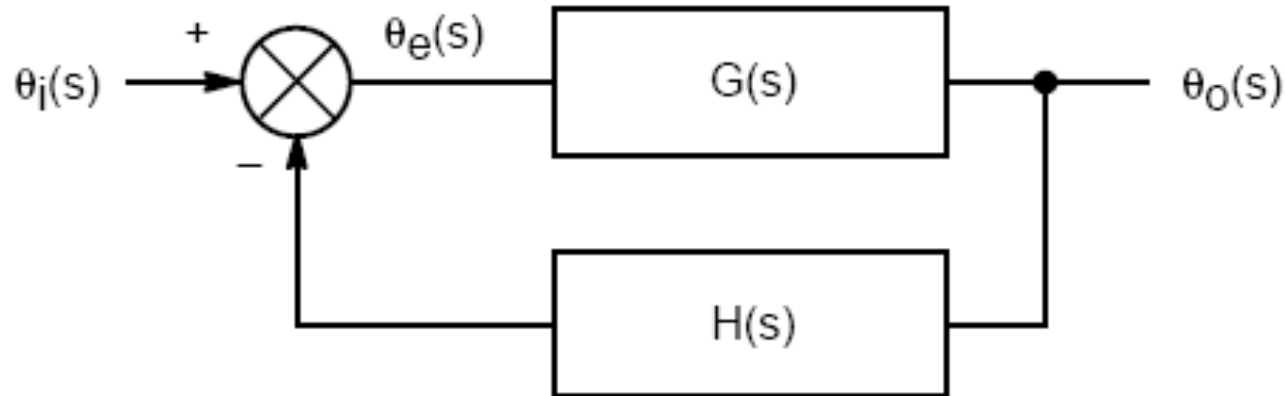

$\theta_i(s)$ Phase Input

$\theta_e(s)$ Phase Error

$\theta_o(s)$ Output Phase

$G(s)$ Product of the Individual Feed
Forward Transfer Functions

$H(s)$ Product of the Individual Feedback
Transfer Functions

Some definitions:

- Order of PLL – Highest degree of polynomial of characteristics equation ($1 + G(s)H(s)$)
- Type of PLL – No of poles of loop Transfer function ($G(s)H(s)$) locate at origin

Food for Thought

- What will be the resolution in terms of frequency of PLL? How will you increase it?
 - What changes you need to do to achieve above goal?
 - What will be specifications of PLL?
 - What is the performance metric of VCO?
 - For Microprocessor?
 - For Transmitter/Receiver IC?
-