

Unit 2

MOS Inverters

DC Response

- DC Response: V_{out} vs. V_{in} for a gate

- Ex: Inverter

- When $V_{in} = 0$ $\rightarrow V_{out} = V_{DD}$

- When $V_{in} = V_{DD}$ $\rightarrow V_{out} = 0$


- In between, V_{out} depends on transistor size and current

- By KCL, must settle such that

$$I_{dsn} = |I_{dsp}|$$

- We could solve equations

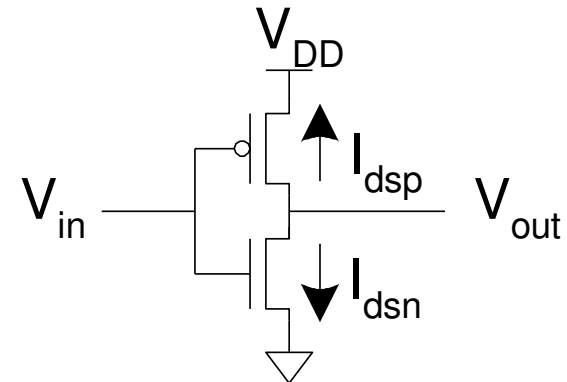- But graphical solution gives more insight




Transistor Operation


- Current depends on region of transistor behavior
- For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?

I-V Characteristics

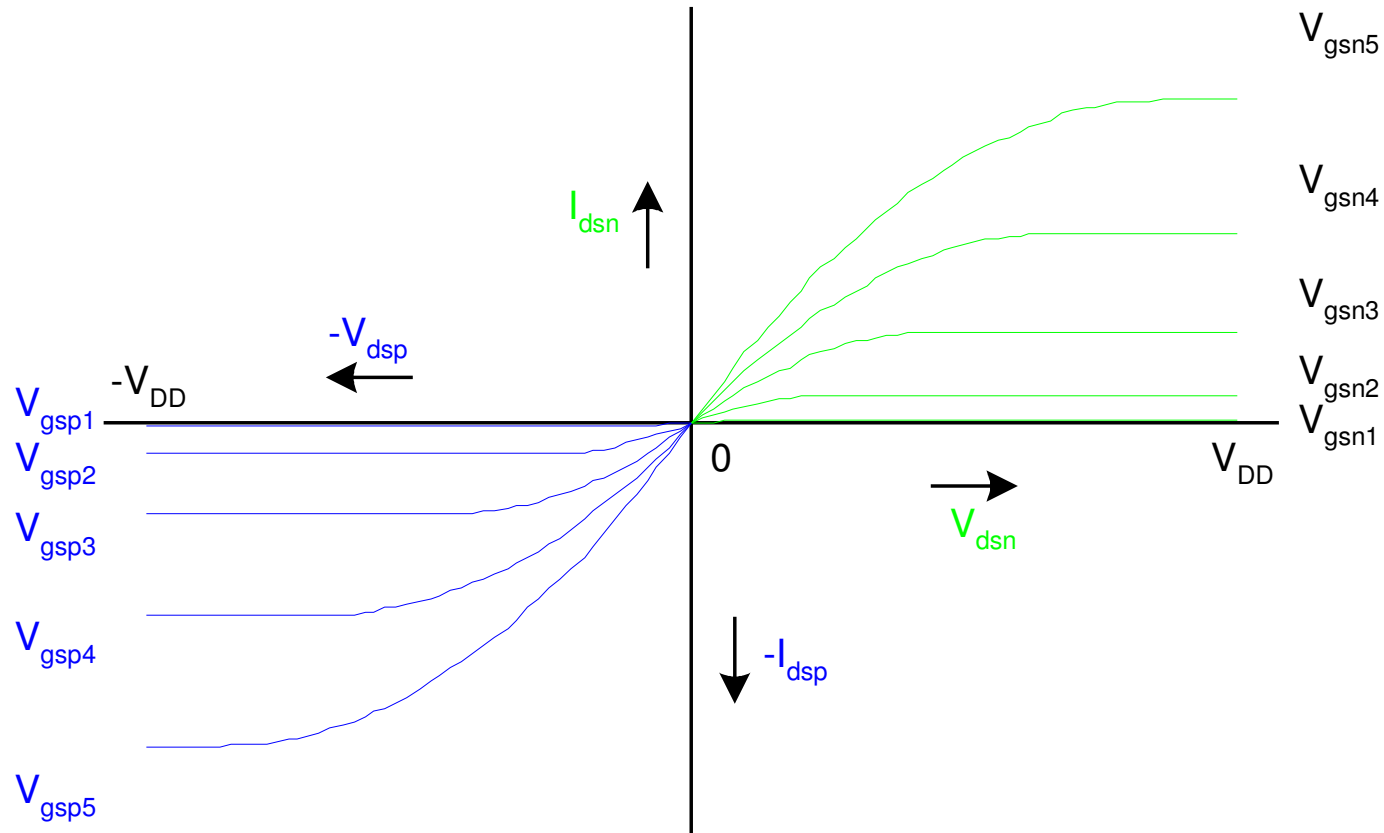- Make pMOS is wider than nMOS such that $\beta_n = \beta_p$




Current vs. V_{out} , V_{in}

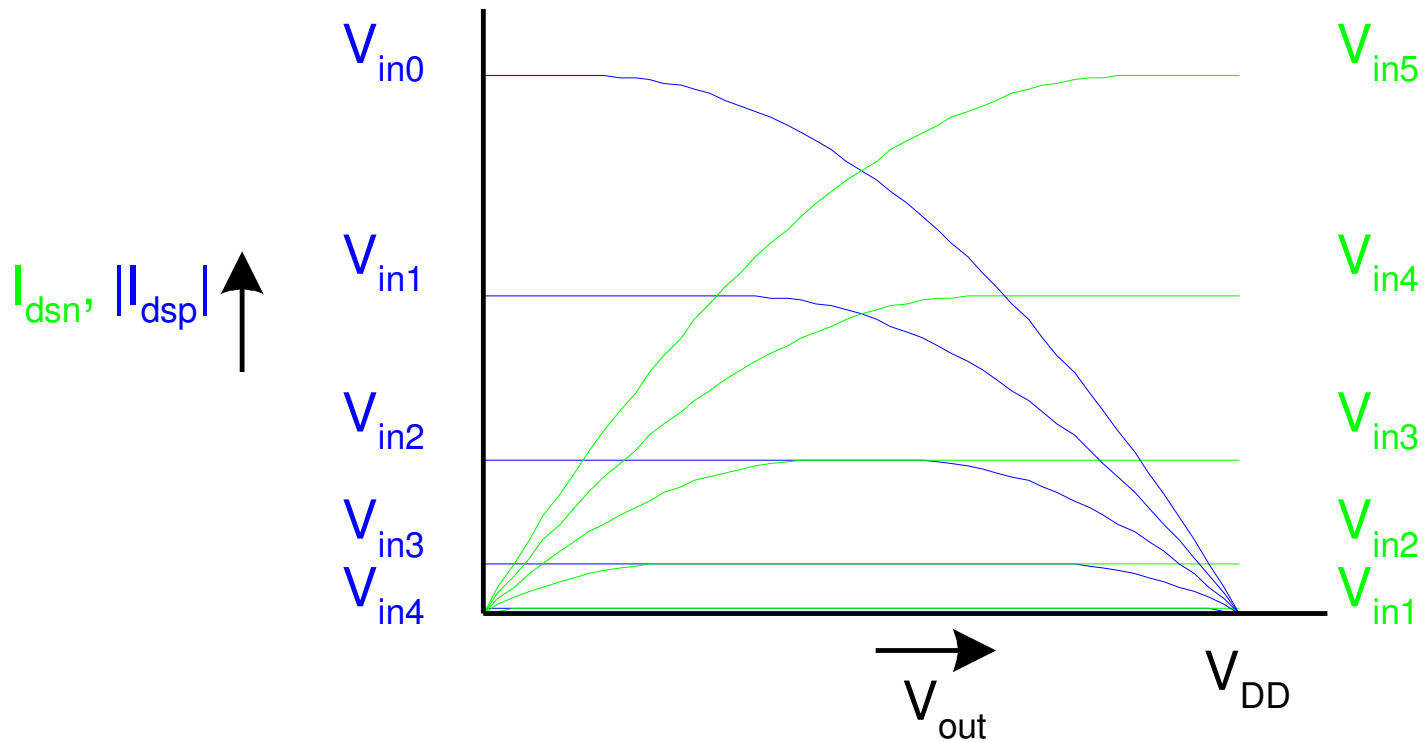


Load Line Analysis

- For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal in

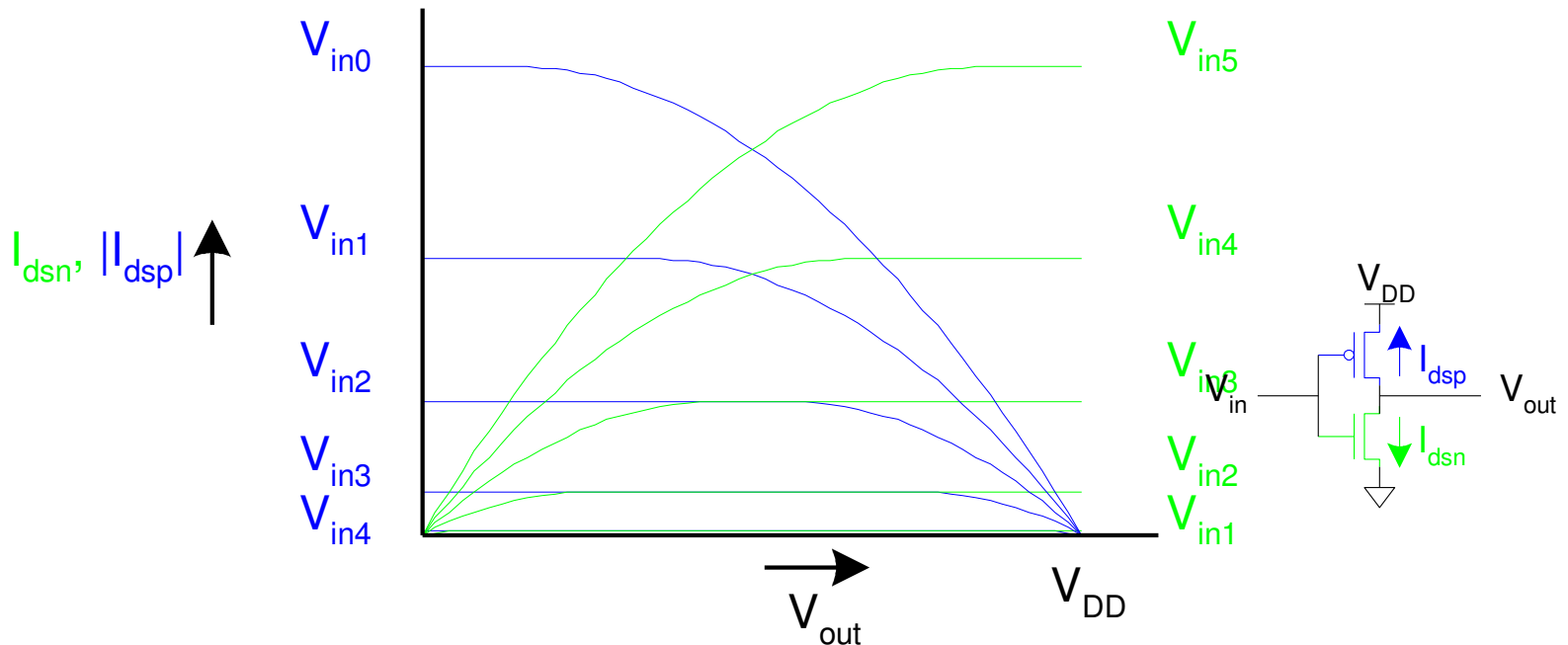


Load Line Analysis

- $V_{in} = 0$

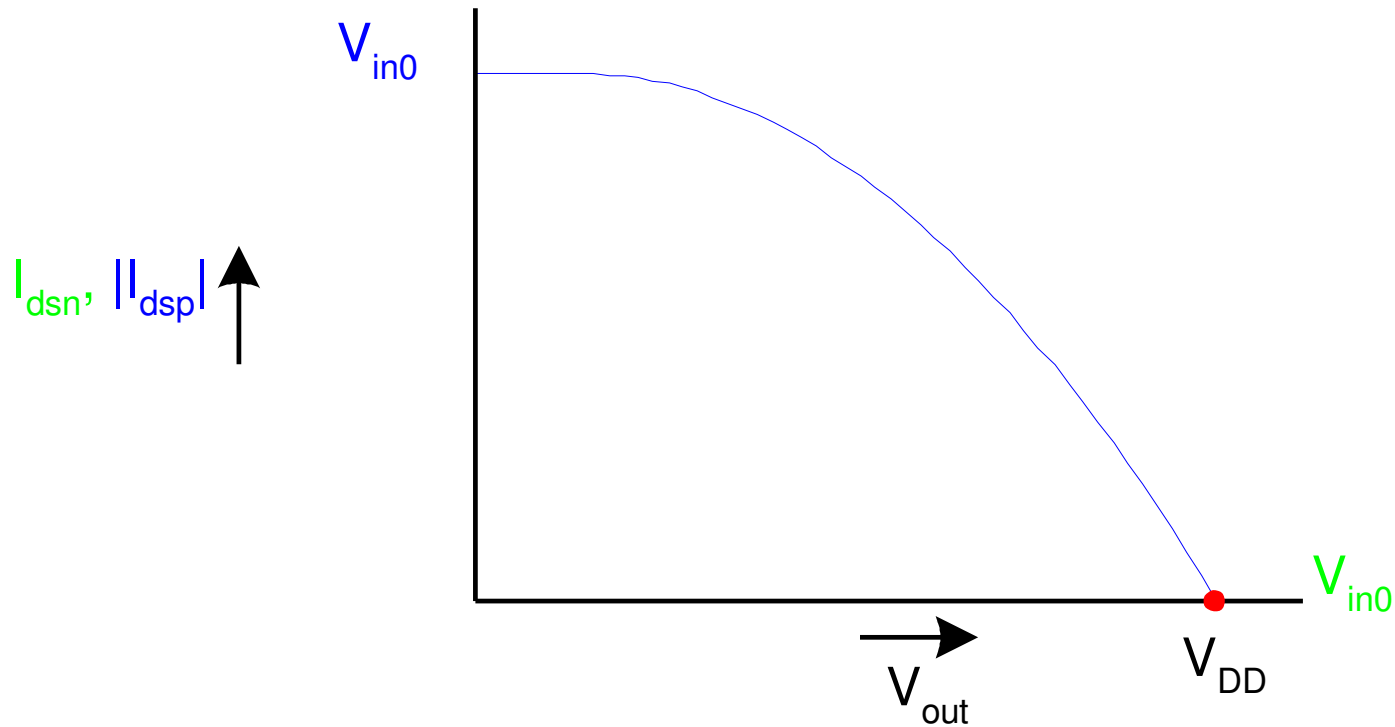


Load Line Analysis

- $V_{in} = 0.2V_{DD}$

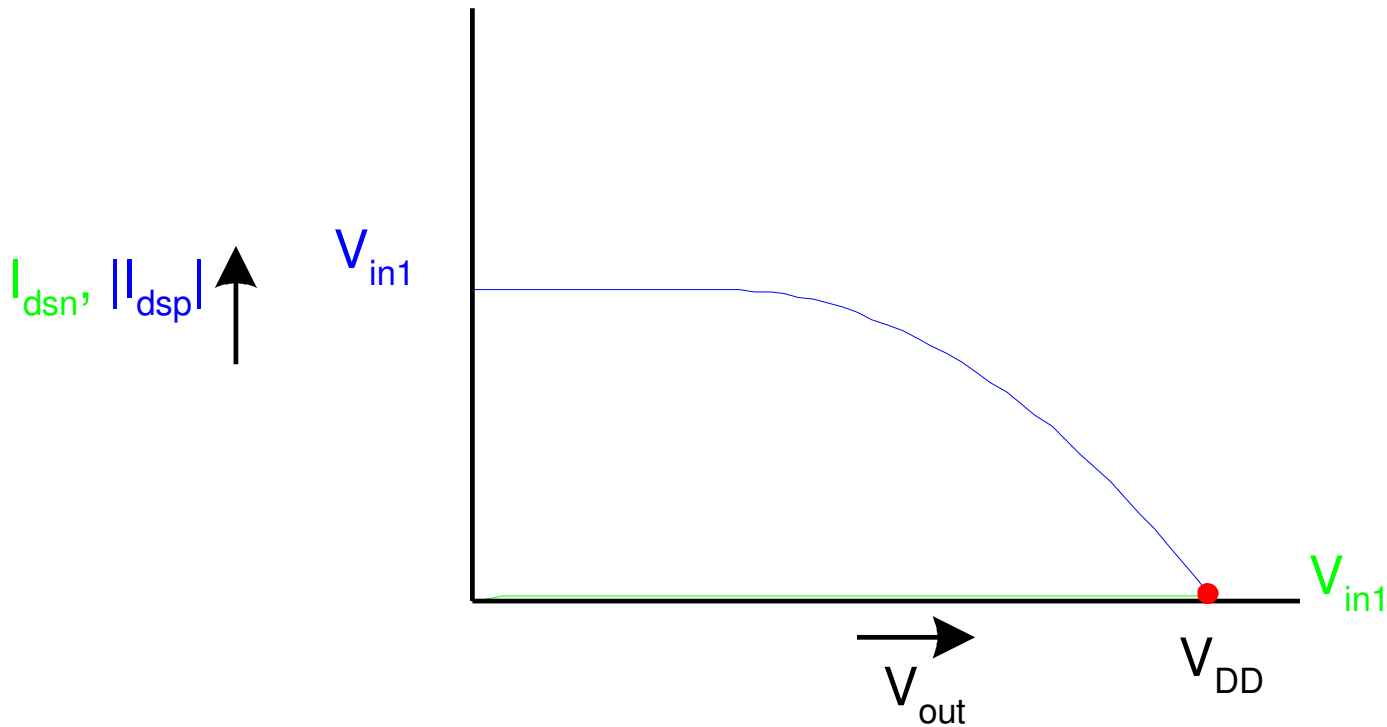


Load Line Analysis

- $V_{in} = 0.4V_{DD}$

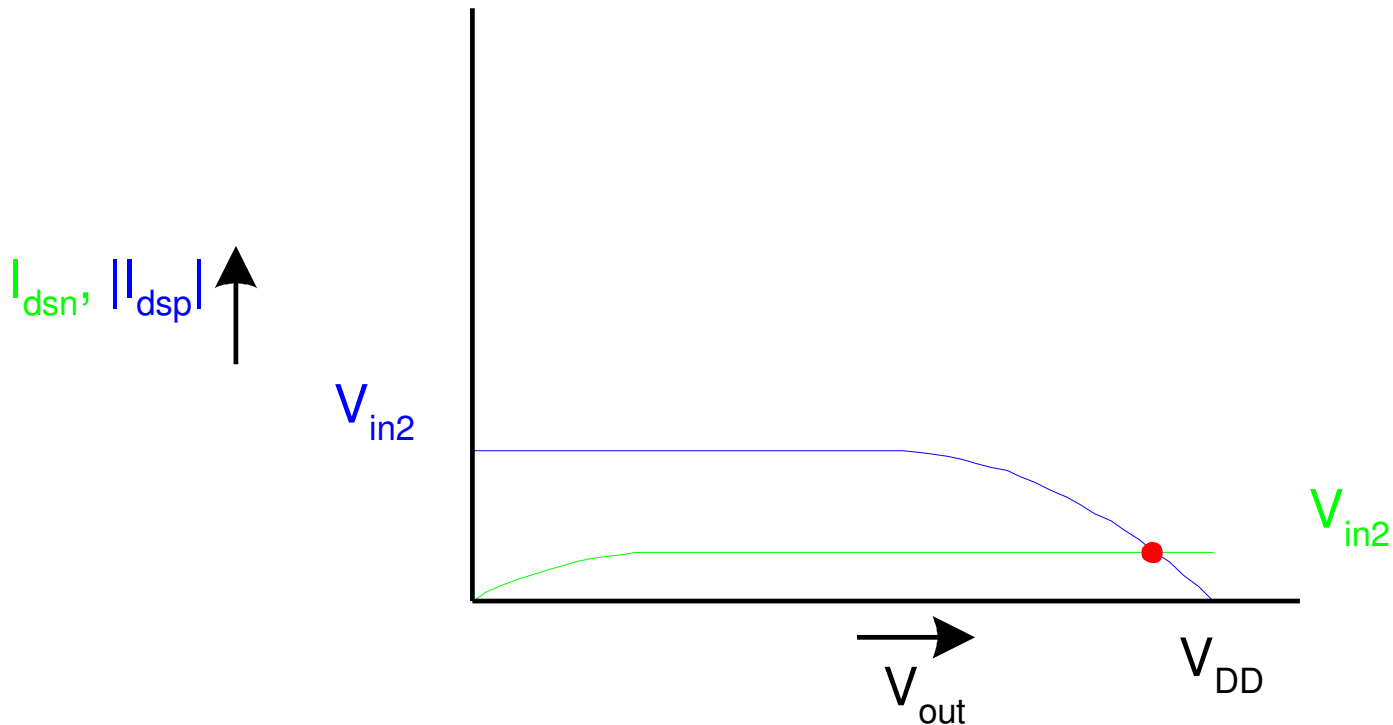


Load Line Analysis

- $V_{in} = 0.6V_{DD}$

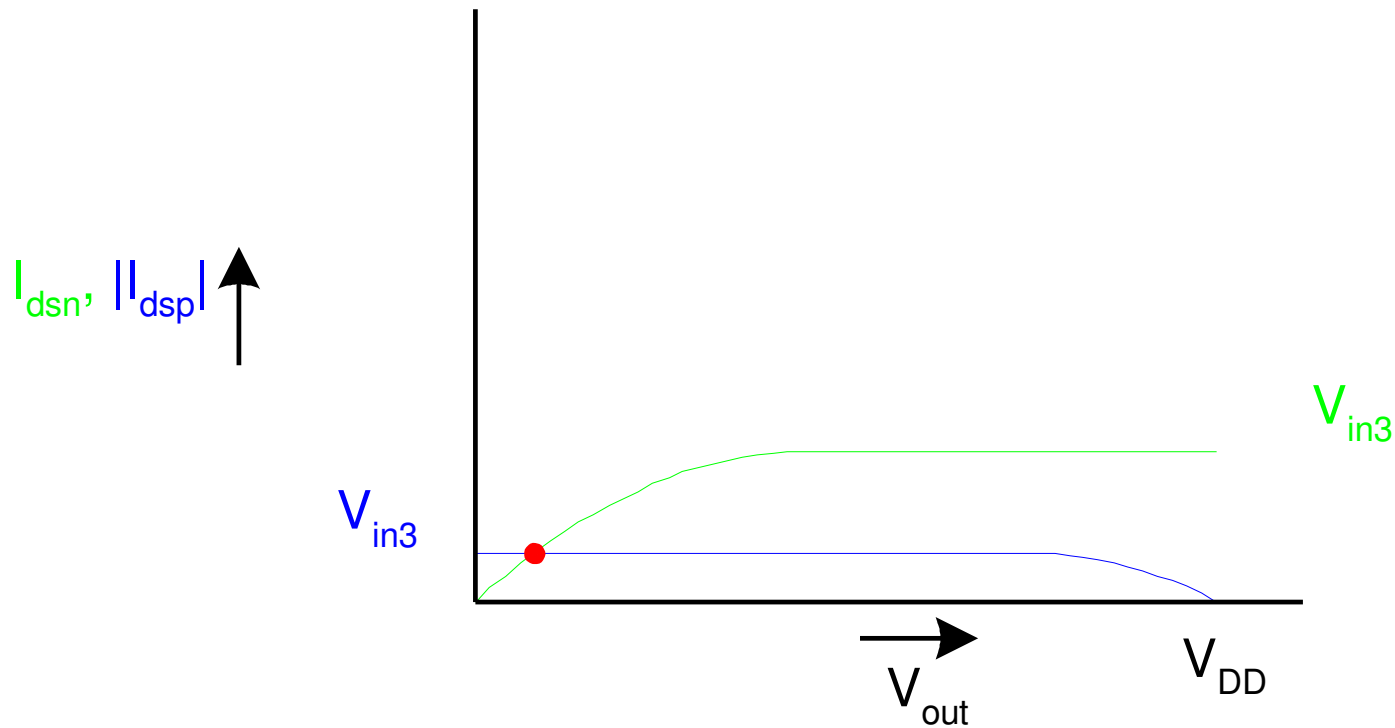


Load Line Analysis

- $V_{in} = 0.8V_{DD}$

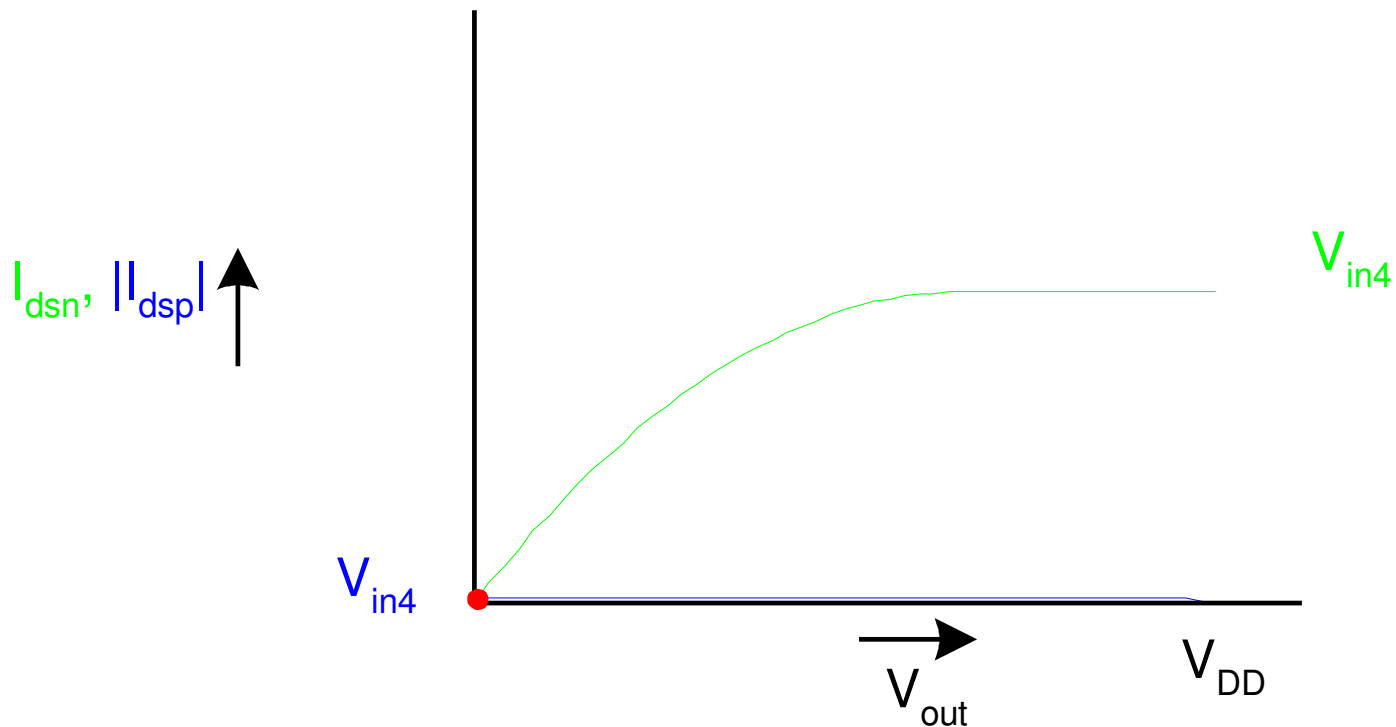


Load Line Analysis

- $V_{in} = V_{DD}$


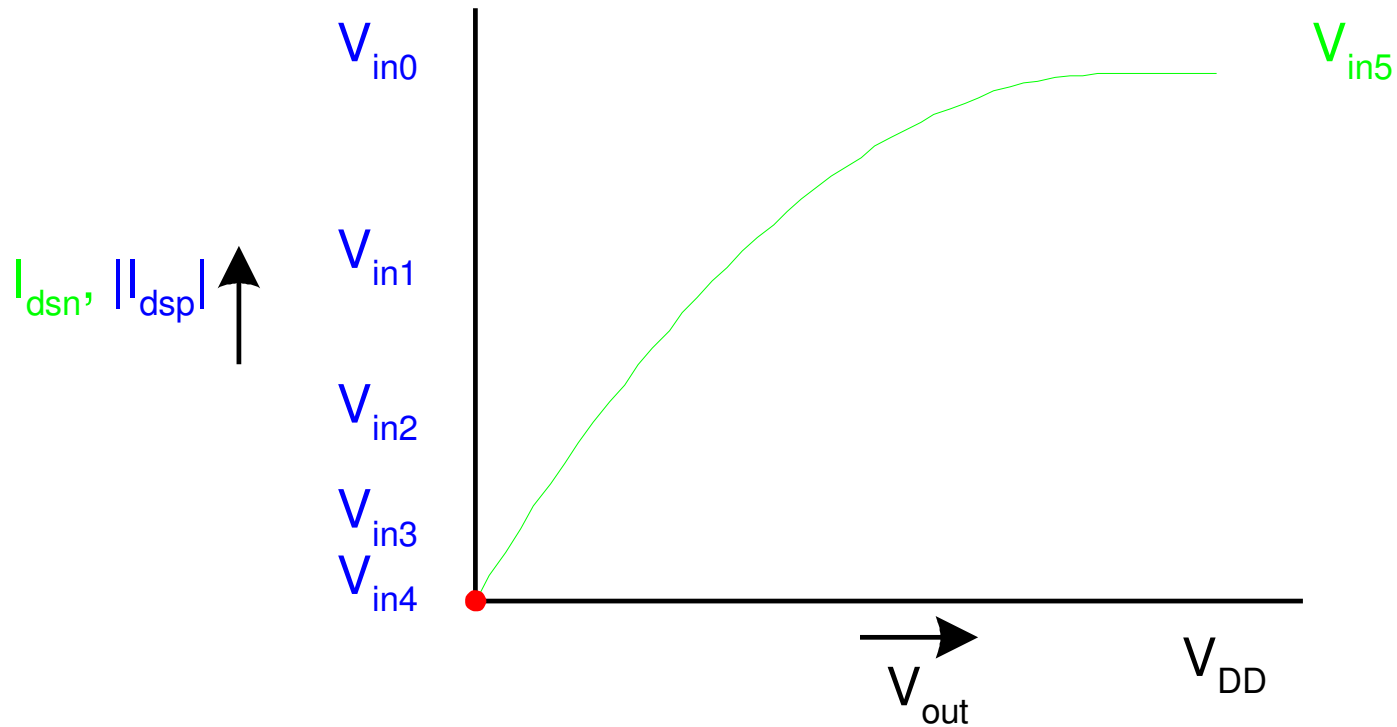


Load Line Summary

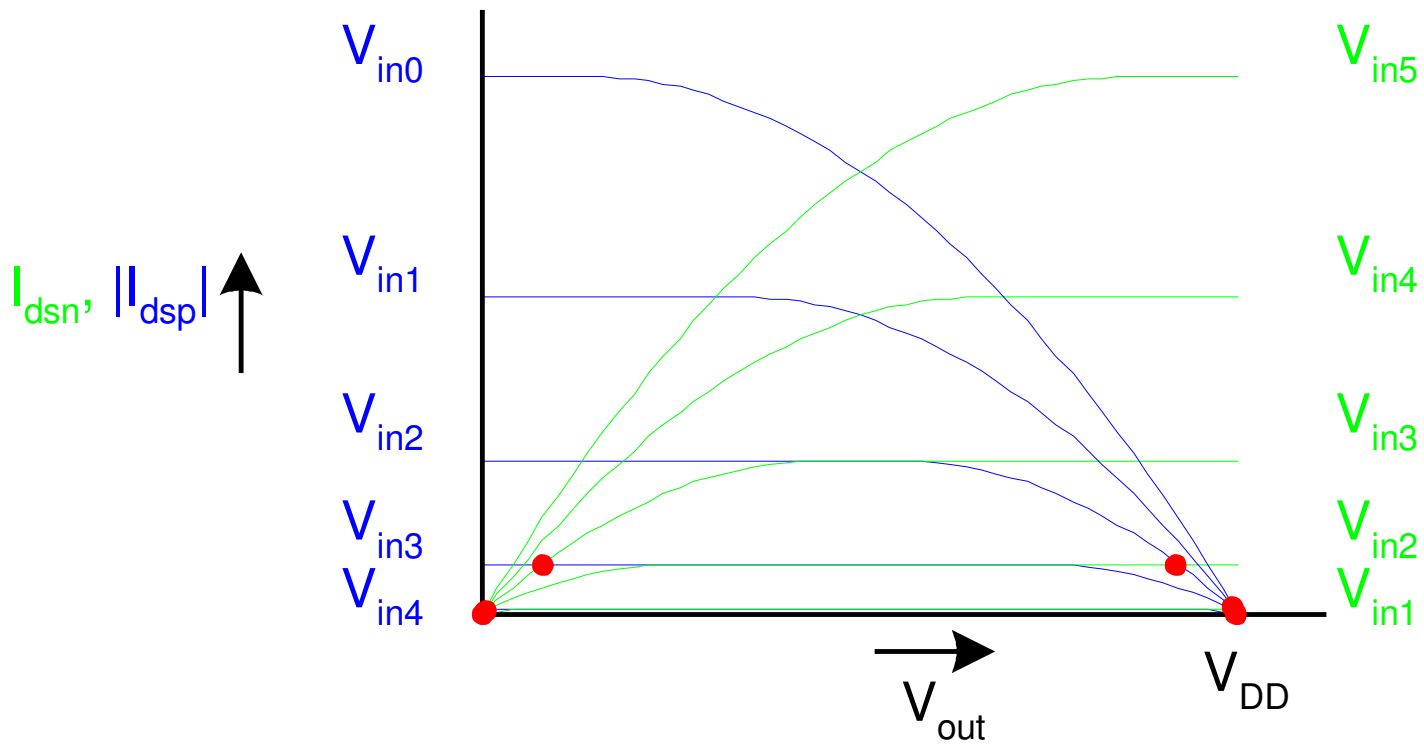

DC Transfer Curve

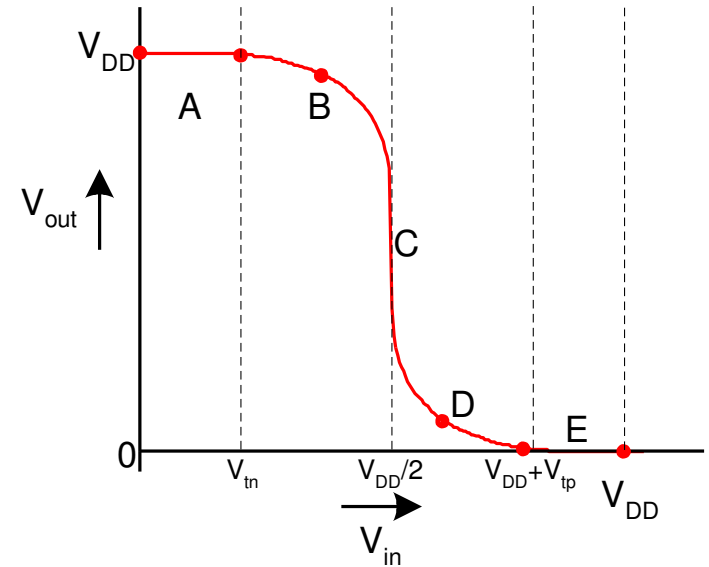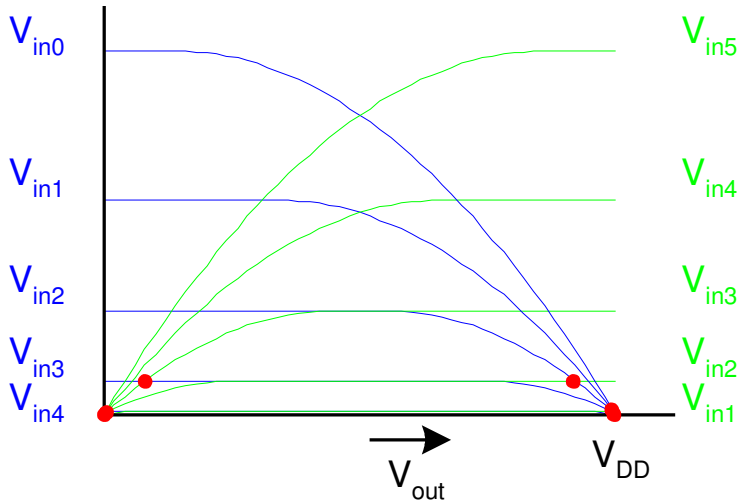
- Transcribe points onto V_{in} vs. V_{out} plot



Operating Regions


- Revisit transistor operating regions

Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

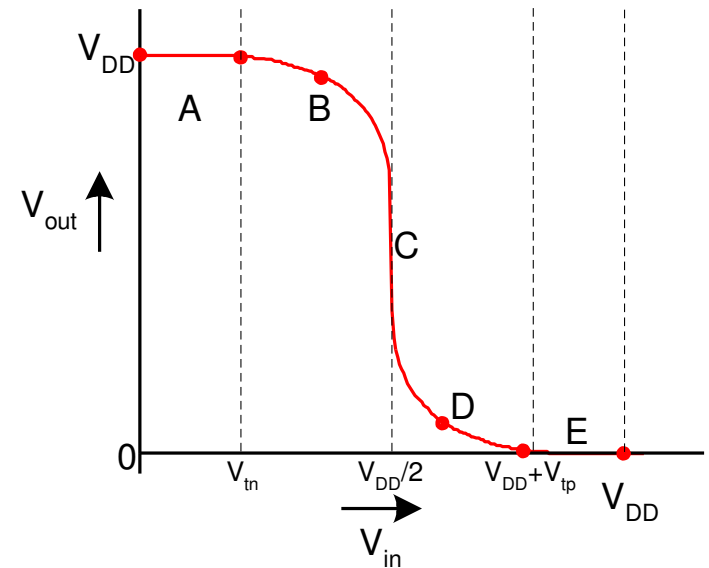


Beta Ratio

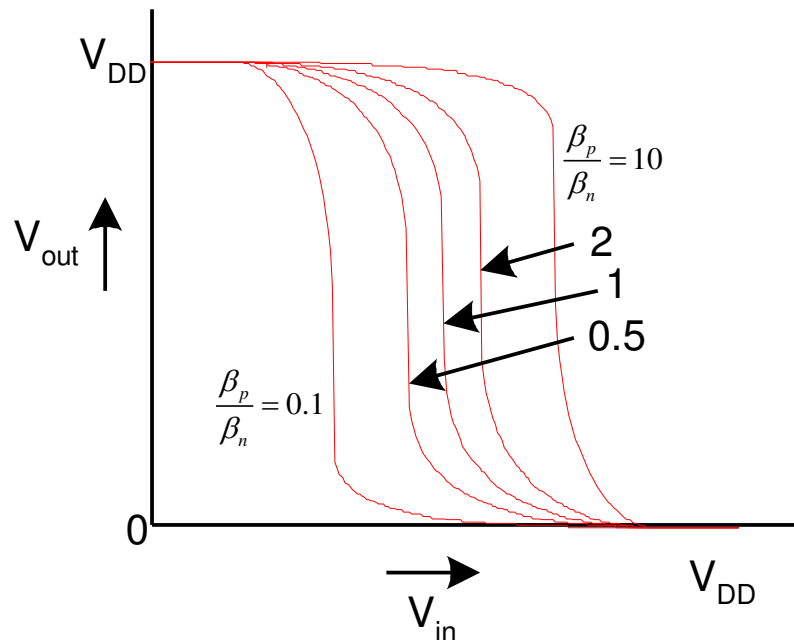- If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- Called *skewed* gate
- Other gates: collapse into equivalent inverter




Noise Margins

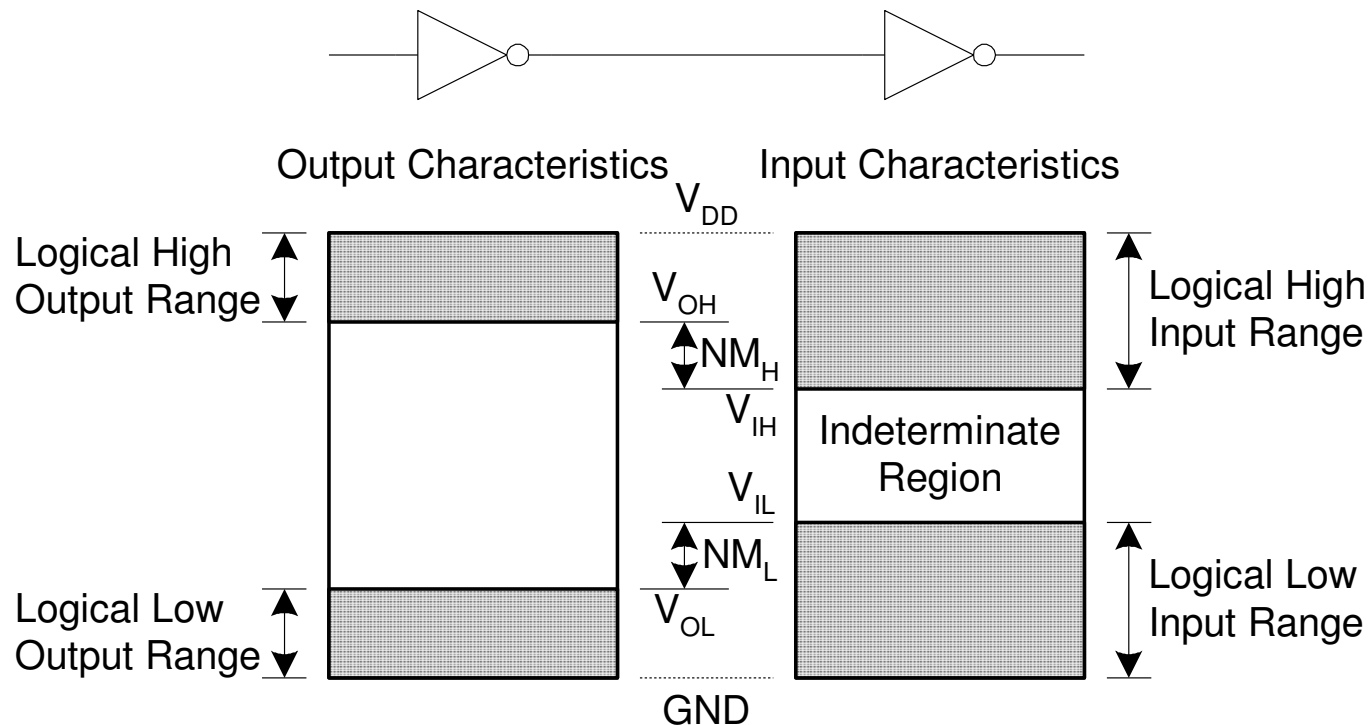- How much noise can a gate input see before it does not recognize the input?



Logic Levels

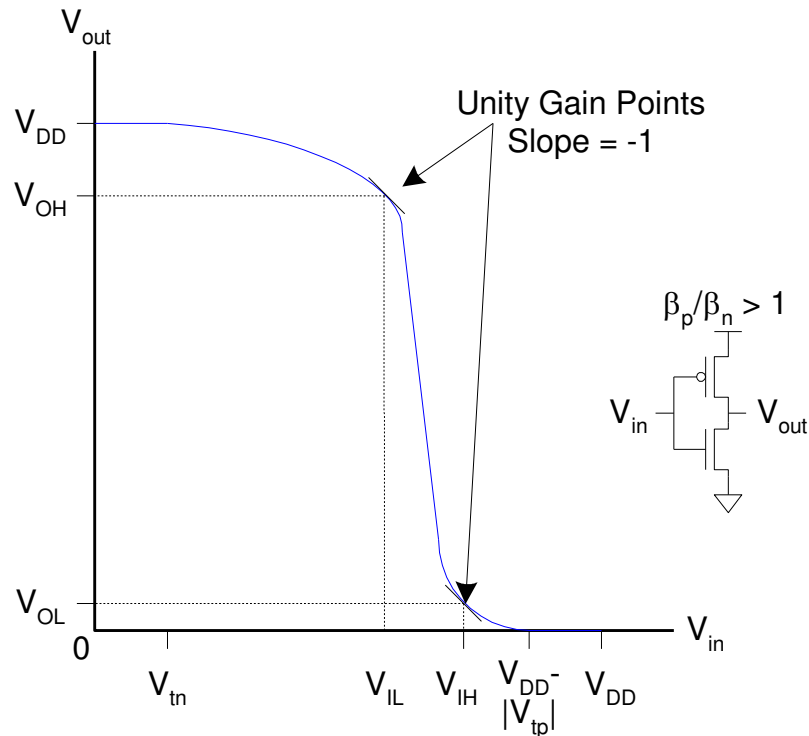- To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristic



Transient Response

- DC analysis tells us V_{out} if V_{in} is constant
- Transient analysis tells us $V_{\text{out}}(t)$ if $V_{\text{in}}(t)$ changes
 - Requires solving differential equations
- Input is usually considered to be a step or ramp
 - From 0 to V_{DD} or vice versa


Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) =$$

$$V_{out}(t < t_0) =$$

$$\frac{dV_{out}(t)}{dt} =$$

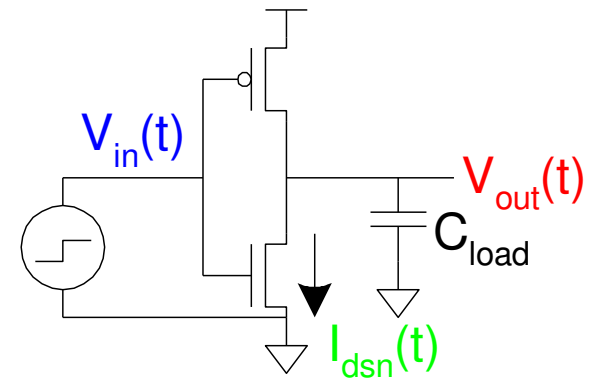


Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) =$$

$$\frac{dV_{out}(t)}{dt} =$$

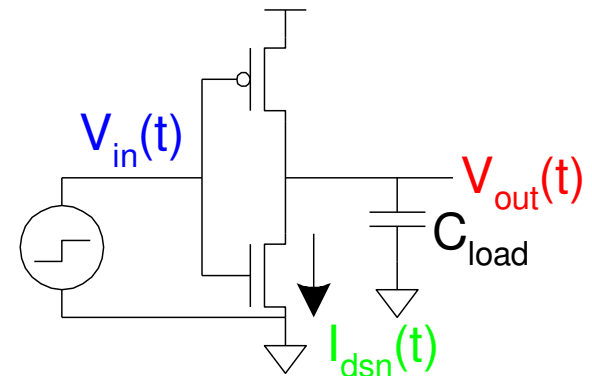


Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} =$$

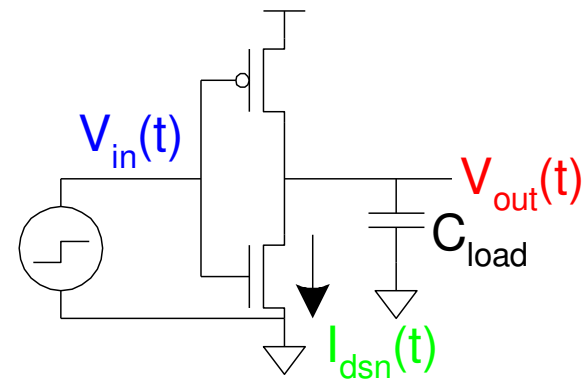

Inverter Step Response


- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
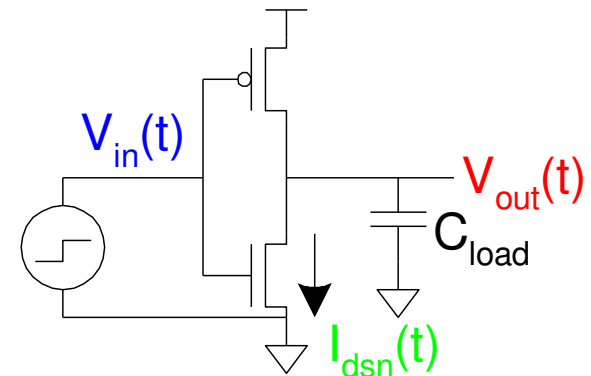
$$I_{dsn}(t) = \begin{cases} & t \leq t_0 \\ V_{out} > V_{DD} - V_t \\ V_{out} < V_{DD} - V_t \end{cases}$$



Inverter Step Response


- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
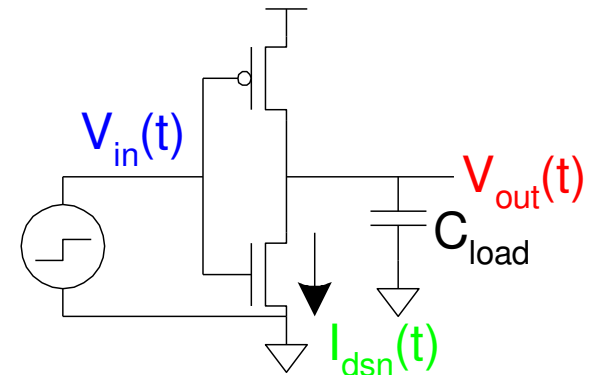
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Inverter Step Response



- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
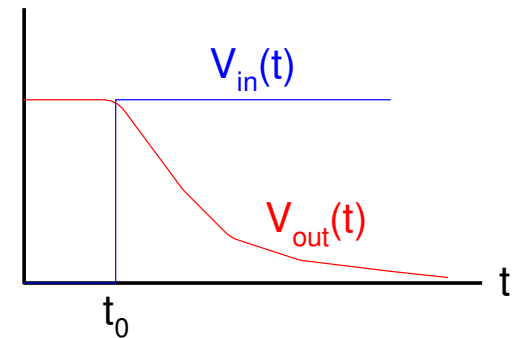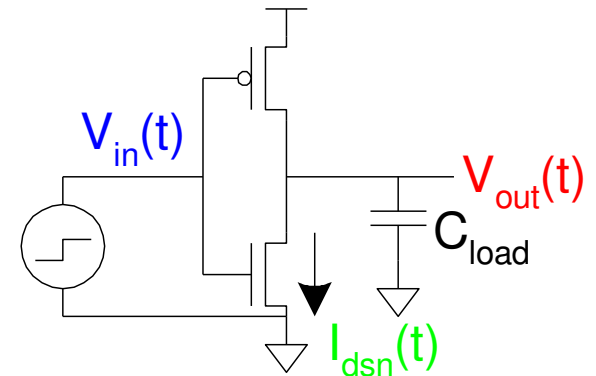
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Delay Definitions


- t_{pdr} : *rising propagation delay*
 - From input to rising output crossing $V_{\text{DD}}/2$
- t_{pdf} : *falling propagation delay*
 - From input to falling output crossing $V_{\text{DD}}/2$
- t_{pd} : *average propagation delay*
 - $t_{\text{pd}} = (t_{\text{pdr}} + t_{\text{pdf}})/2$
- t_{r} : *rise time*
 - From output crossing $0.2 V_{\text{DD}}$ to $0.8 V_{\text{DD}}$
- t_{f} : *fall time*
 - From output crossing $0.8 V_{\text{DD}}$ to $0.2 V_{\text{DD}}$

Delay Definitions

- t_{cdr} : *rising contamination delay*
 - From input to rising output crossing $V_{DD}/2$
- t_{cdf} : *falling contamination delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{cd} : *average contamination delay*
 - $t_{pd} = (t_{cdr} + t_{cdf})/2$

Simulated Inverter Delay

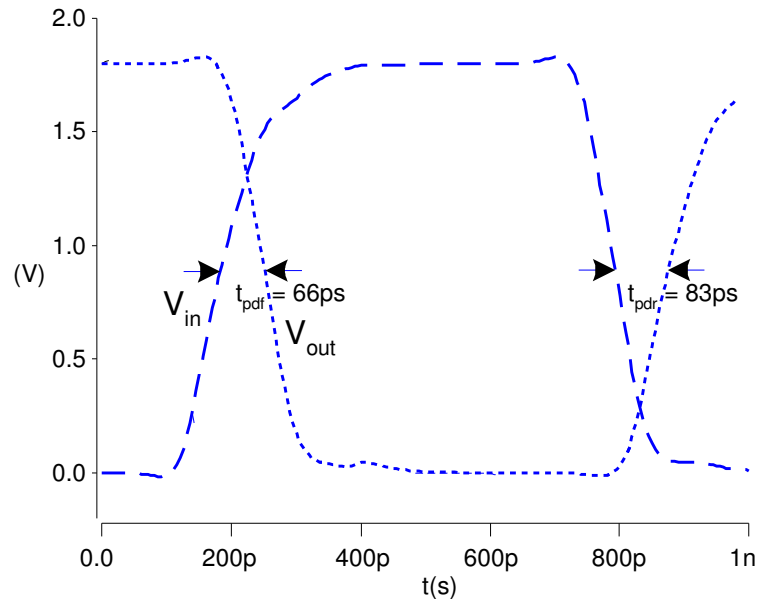- Solving differential equations by hand is too hard
- SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- But simulations take time to write





Delay Estimation

- We would like to be able to easily estimate delay
 - Not as accurate as simulation
- The step response usually looks like a 1st order RC response with a decaying exponential.
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches


RC Delay Models

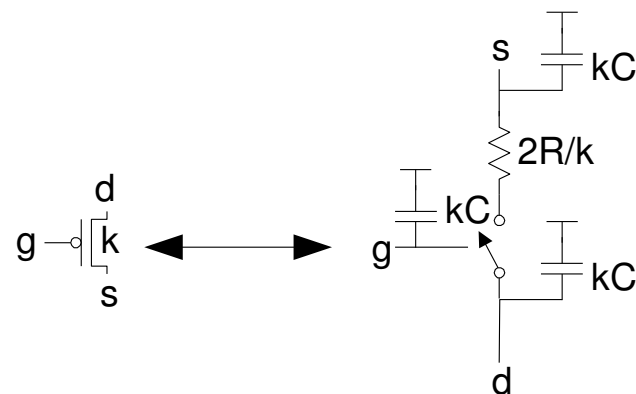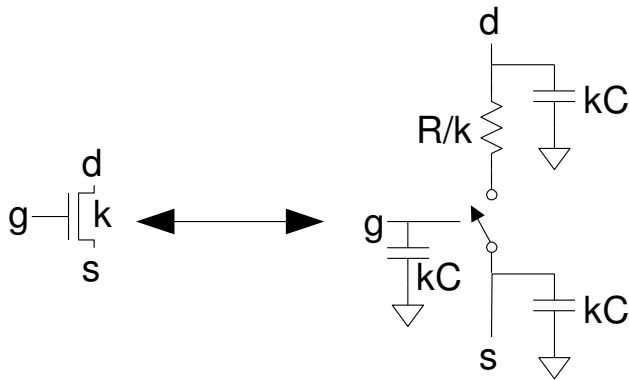- Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width



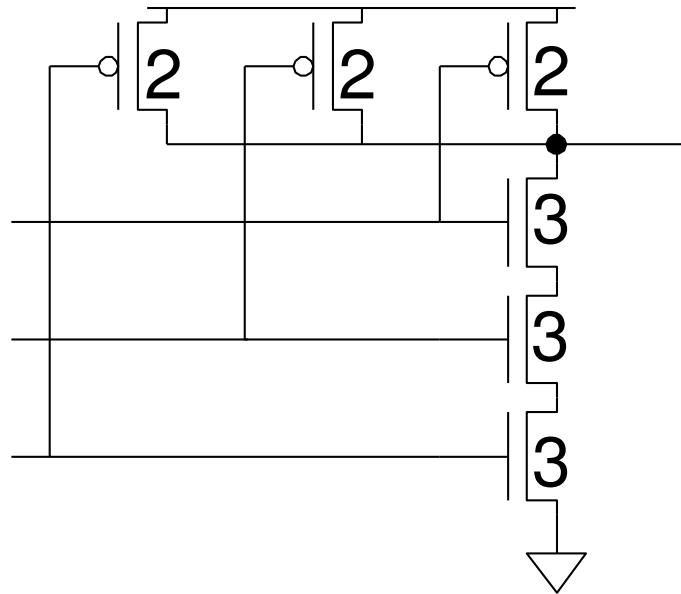Example: 3-input NAND

- A 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).




Elmore Delay

- ON transistors look like resistors
- Pullup or pulldown network modeled as *RC ladder*
- Elmore delay of RC ladder



$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
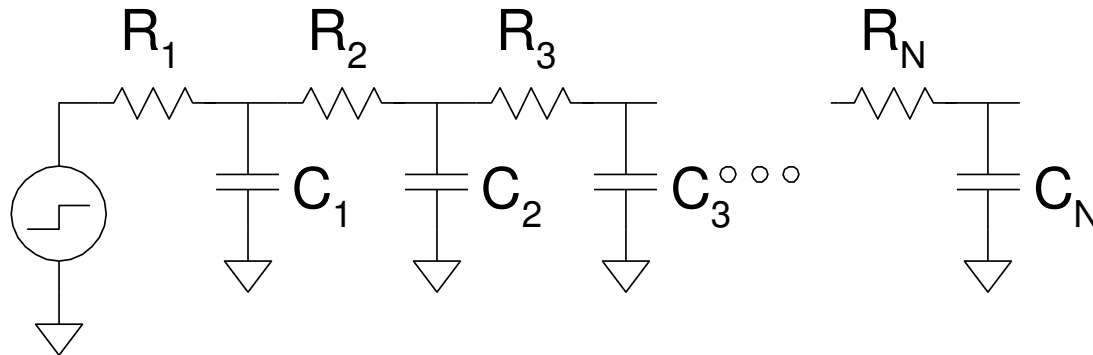
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



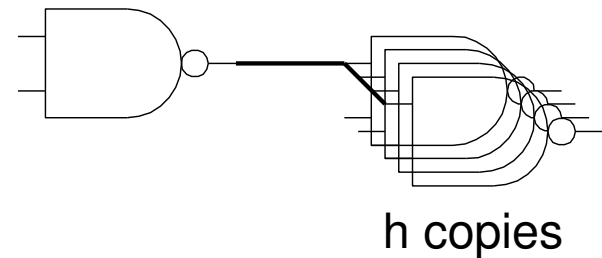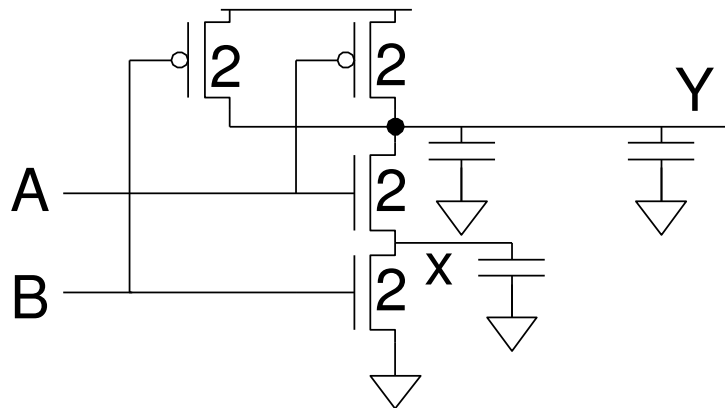
Example: 2-input NAND

- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates.




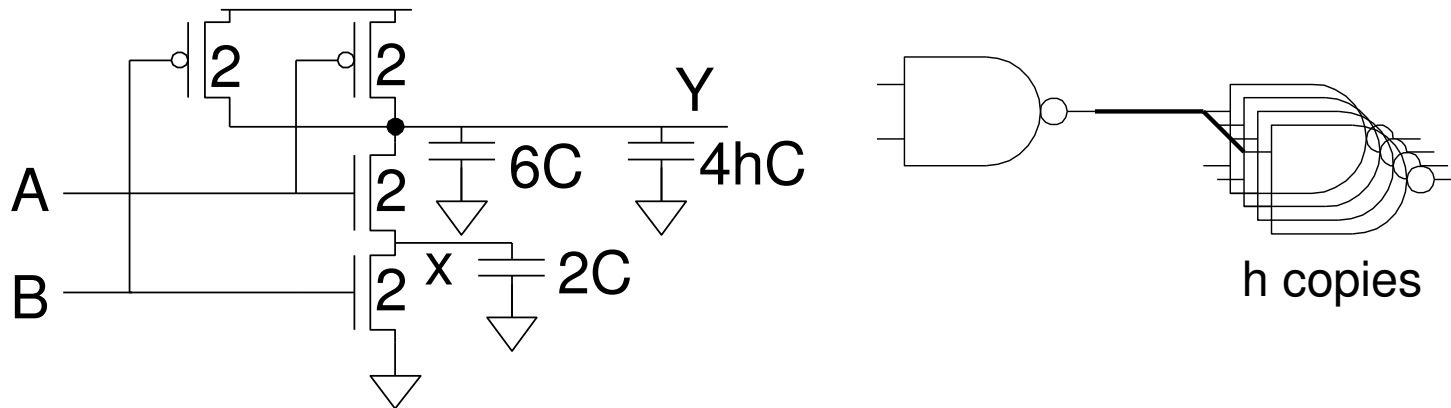
Example: 2-input NAND

- Estimate rising and falling propagation delays of a 2-input NAND driving h identical gates.



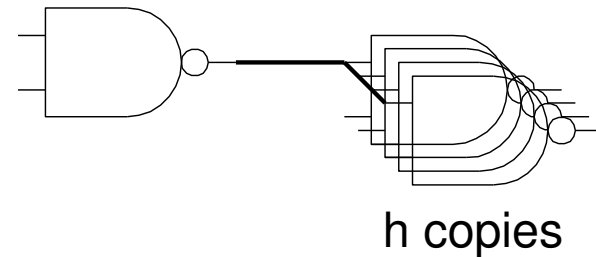
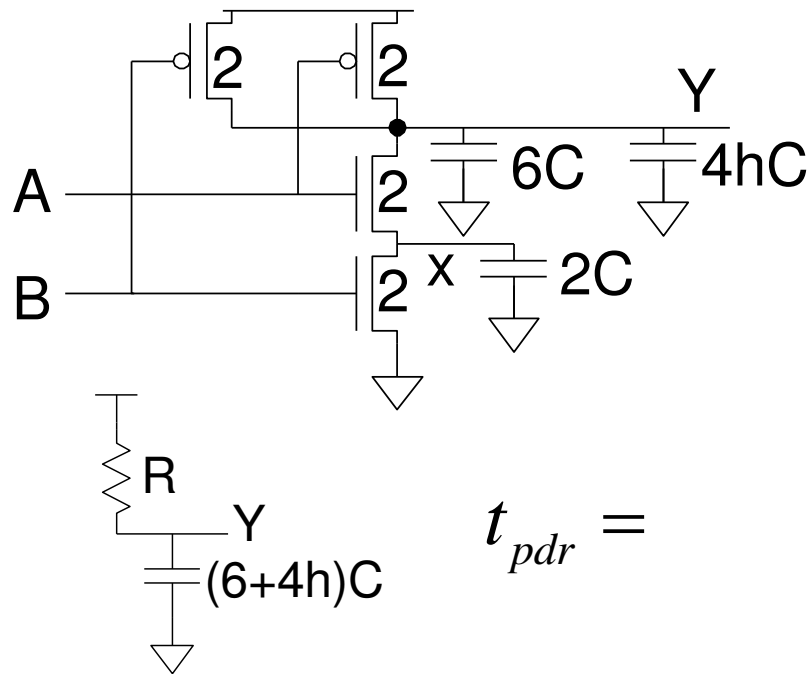
Example: 2-input NAND

- Estimate **rising** and falling propagation delays of a 2-input NAND driving h identical gates.



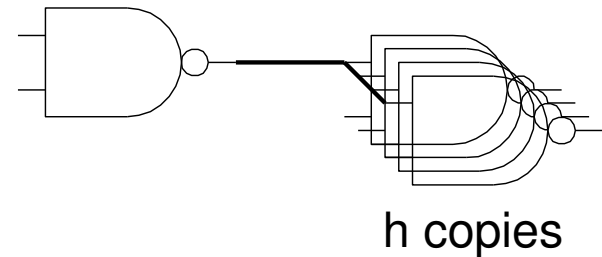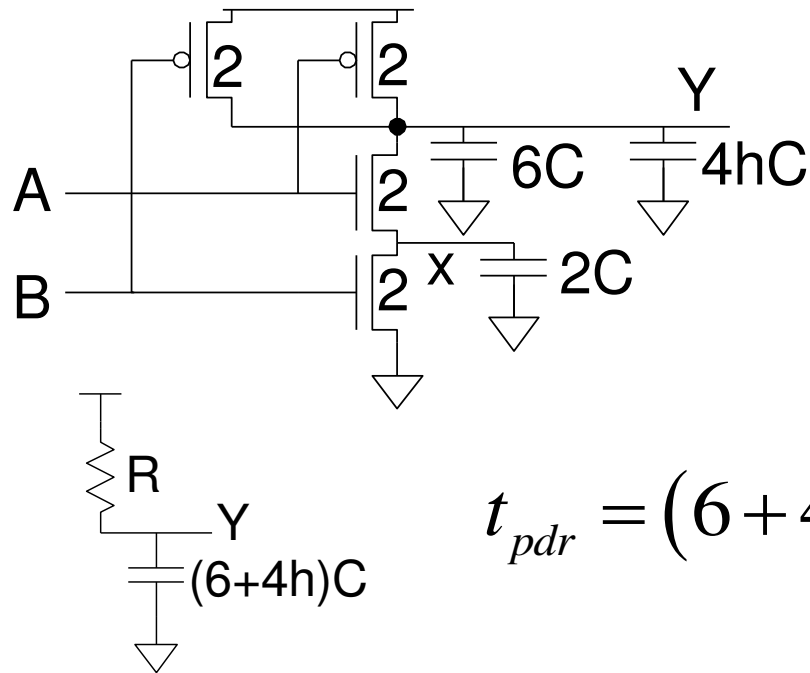Example: 2-input NAND



- Estimate **rising** and falling propagation delays of a 2-input NAND driving h identical gates.



$$t_{pdr} = (6 + 4h)RC$$

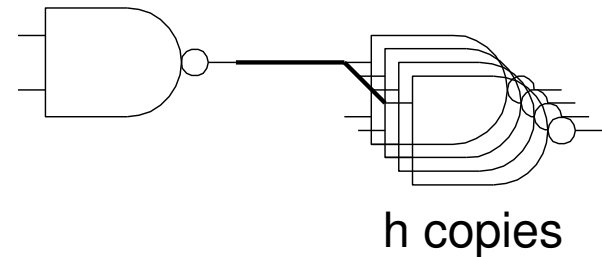
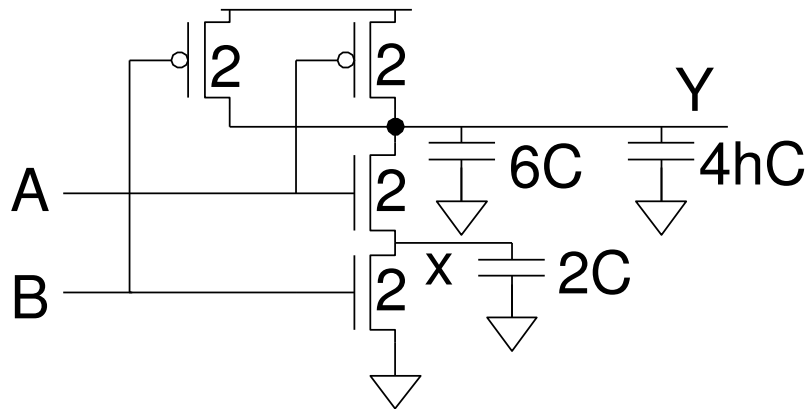
Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



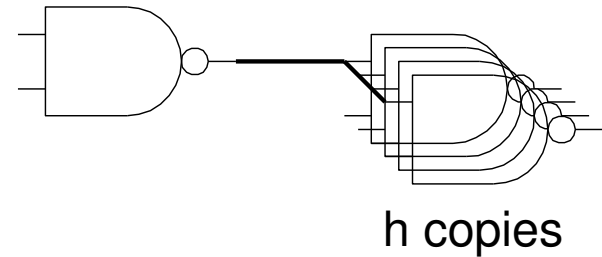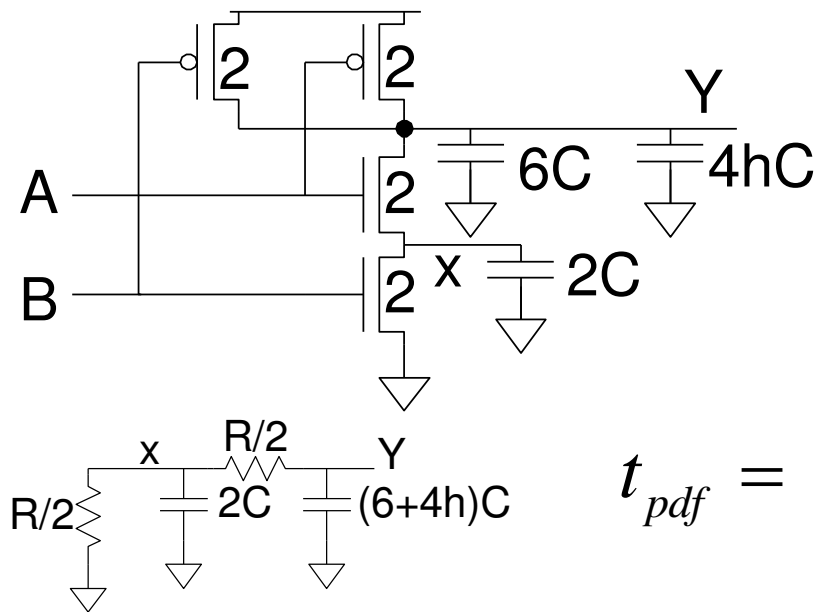Example: 2-input NAND




- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



$$t_{pdf} =$$

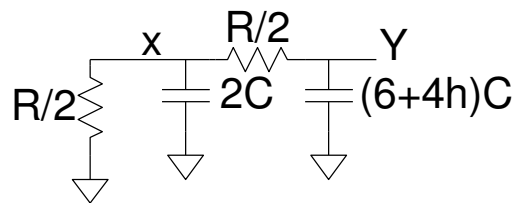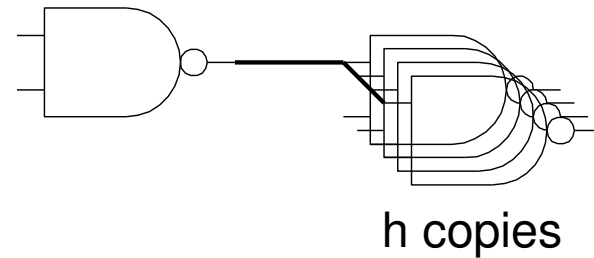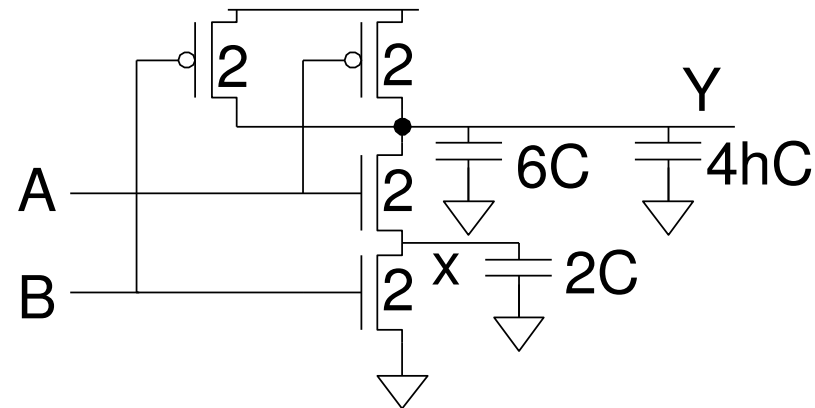Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.




$$\begin{aligned}
 t_{pdf} &= (2C)\left(\frac{R}{2}\right) + \left[(6+4h)C\right]\left(\frac{R}{2} + \frac{R}{2}\right) \\
 &= (7+4h)RC
 \end{aligned}$$

Delay Components

- Delay has two parts
 - *Parasitic delay*
 - 6 or 7 RC
 - Independent of load
 - *Effort delay*
 - 4h RC
 - Proportional to load capacitance

Contamination Delay

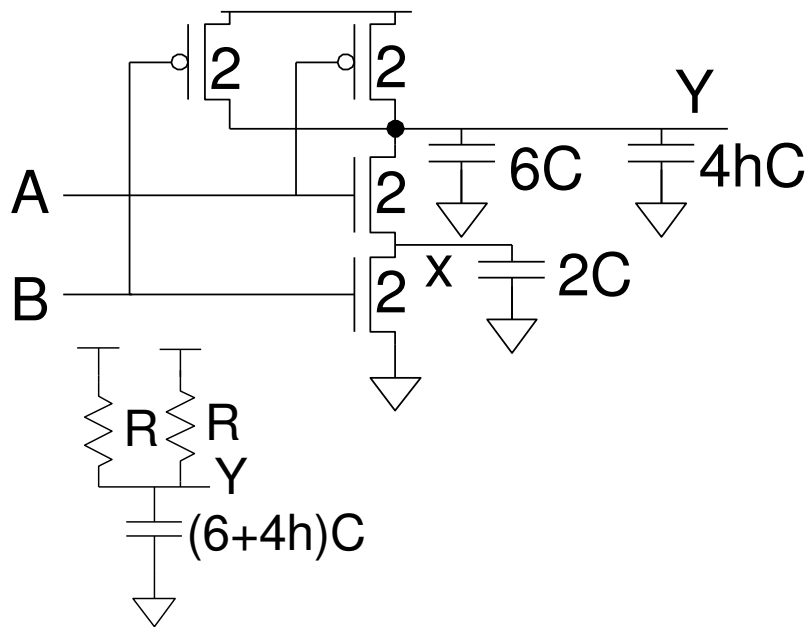- Best-case (contamination) delay can be substantially less than propagation delay.
- Ex: If both inputs fall simultaneously



$$t_{cdr} = (3 + 2h)RC$$