

# **Unit 3**

## **Combinational MOS Logic Circuits**

# Overview

## **Static CMOS**

**Conventional Static CMOS Logic**

**Ratioed Logic**


**Pass Transistor/Transmission Gate Logic**

## **Dynamic CMOS Logic**

**Domino**


**np-CMOS**

# Combinational vs. Sequential Logic

 

(a) Combinational

$$\text{Output} = f(\text{In})$$

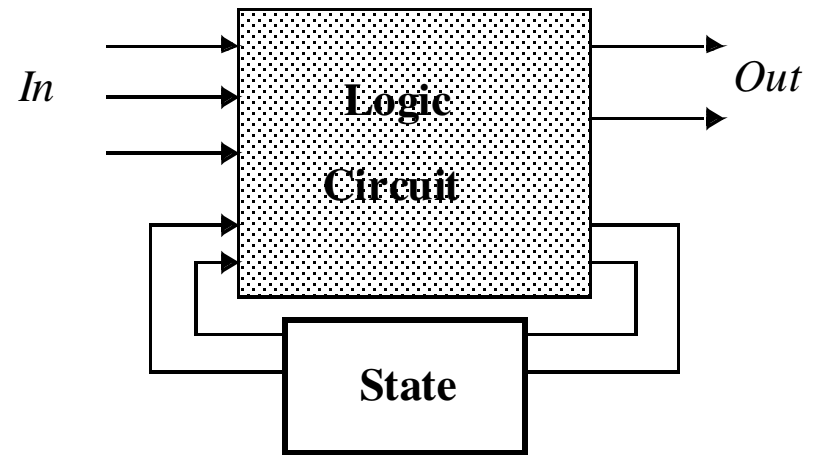

(b) Sequential

$$\text{Output} = f(\text{In}, \text{Previous In})$$


# Static CMOS Circuit

At every point in time (except during the switching transients) each *gate output is connected to either  $V_{DD}$  or  $V_{ss}$*  via a low-resistive path.

The outputs of the gates *assume at all times the value of the Boolean function*, implemented by the circuit (ignoring, once again, the transient effects during switching periods).

This is in contrast to the *dynamic* circuit class, which relies on temporary storage of signal values on the capacitance of high impedance circuit nodes.

# Static CMOS


 


**PUN and PDN are Dual Networks**
  
# NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal



NMOS switch closes when switch control input is high



**NMOS Transistors pass a “strong” 0 but a “weak” 1**

# PMOS Transistors in Series/Parallel Connection

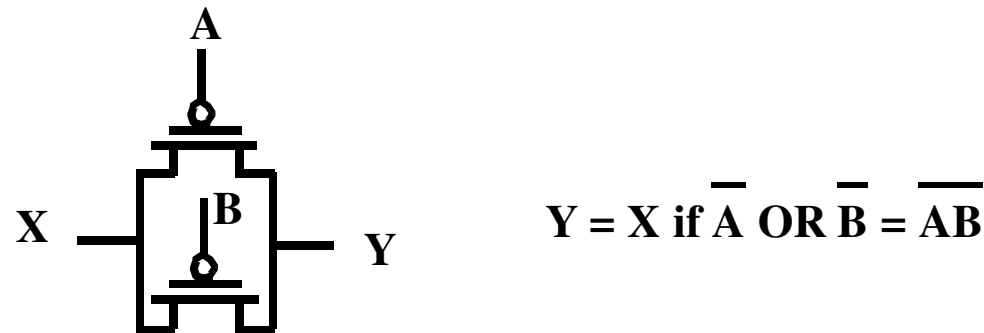 **PMOS switch closes when switch control input is low**



**PMOS Transistors pass a “strong” 1 but a “weak” 0**

# Complementary CMOS Logic Style Construction (cont.)

- PUP is the DUAL of PDN  
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{\bar{A}\bar{B}} = A + B$$

- The complementary gate is inverting




$$\text{AND} = \text{NAND} + \text{INV}$$



# Example Gate: NAND

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 0   |

Truth Table of a 2 input NAND gate

 

PDN:  $G = A B \Rightarrow$  Conduction to GND


PUN:  $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


# Example Gate: NOR

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 0   |


Truth Table of a 2 input NOR gate

 

# Example Gate: COMPLEX CMOS GATE

 

# Analysis of Propagation Delay

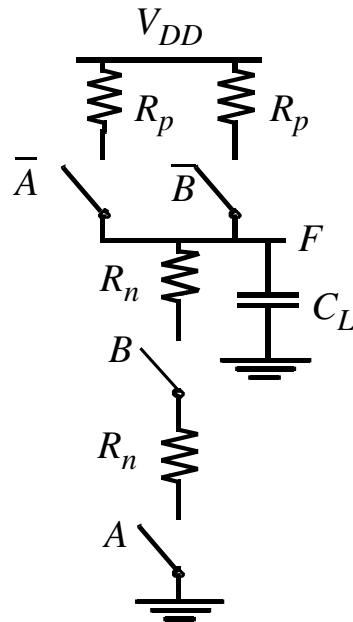

2-input NAND


1. Assume  $R_n = R_p$  = resistance of minimum sized NMOS inverter
2. Determine “Worst Case Input” transition (Delay depends on input values)
3. Example:  $t_{pLH}$  for 2input NAND
  - Worst case when only ONE PMOS Pulls up the output node
  - For 2 PMOS devices in parallel, the resistance is lower

$$t_{pLH} = 0.69 R_p C_L$$

4. Example:  $t_{pHL}$  for 2input NAND
  - Worst case : TWO NMOS in series


$$t_{pHL} = 0.69(2R_n)C_L$$

# Design for Worst Case

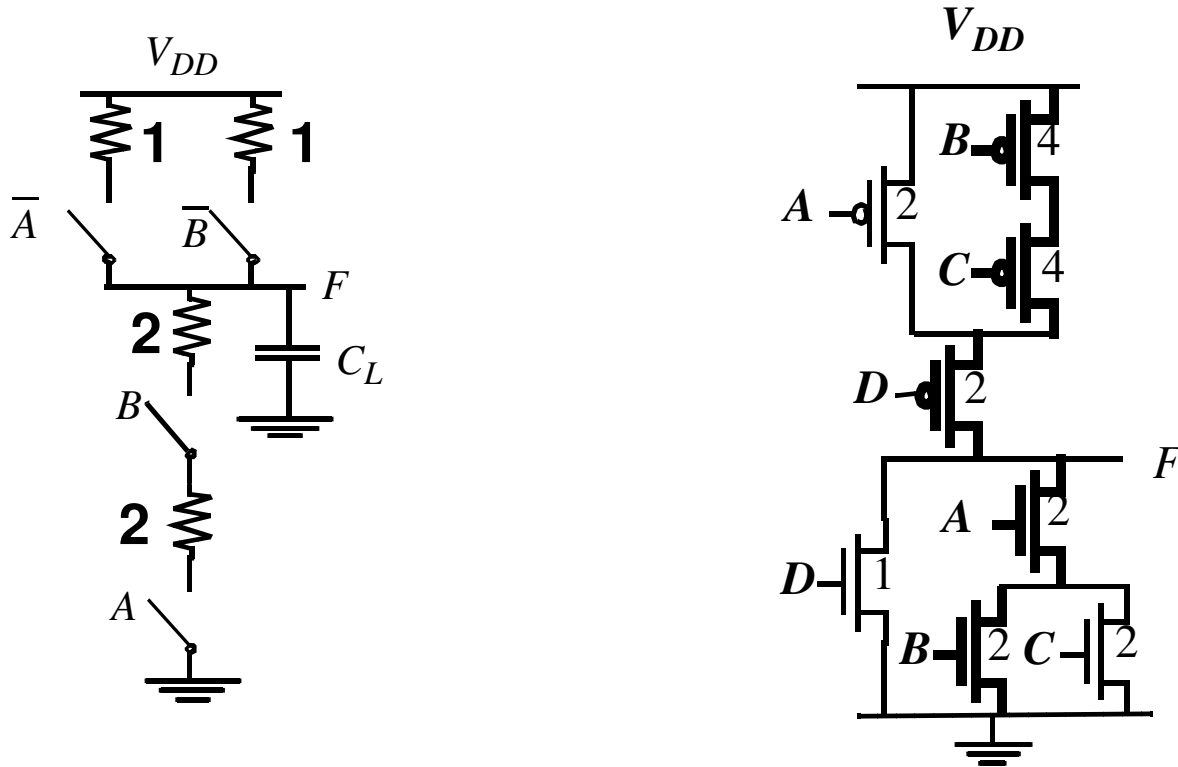

Here it is assumed that  $R_p = R_n$
 
# Influence of Fan-In and Fan-Out on Delay




*Fan-Out: Number of Gates Connected*  
*2 Gate Capacitances per Fan-Out*

*FanIn: Quadratic Term due to:*

- 1. Resistance Increasing*
  - 2. Capacitance Increasing*
- $(t_{pHL})$

$$t_p = a_1 FI + a_2 FI^2 + a_3 FO$$

# $t_p$ as a function of Fan-In

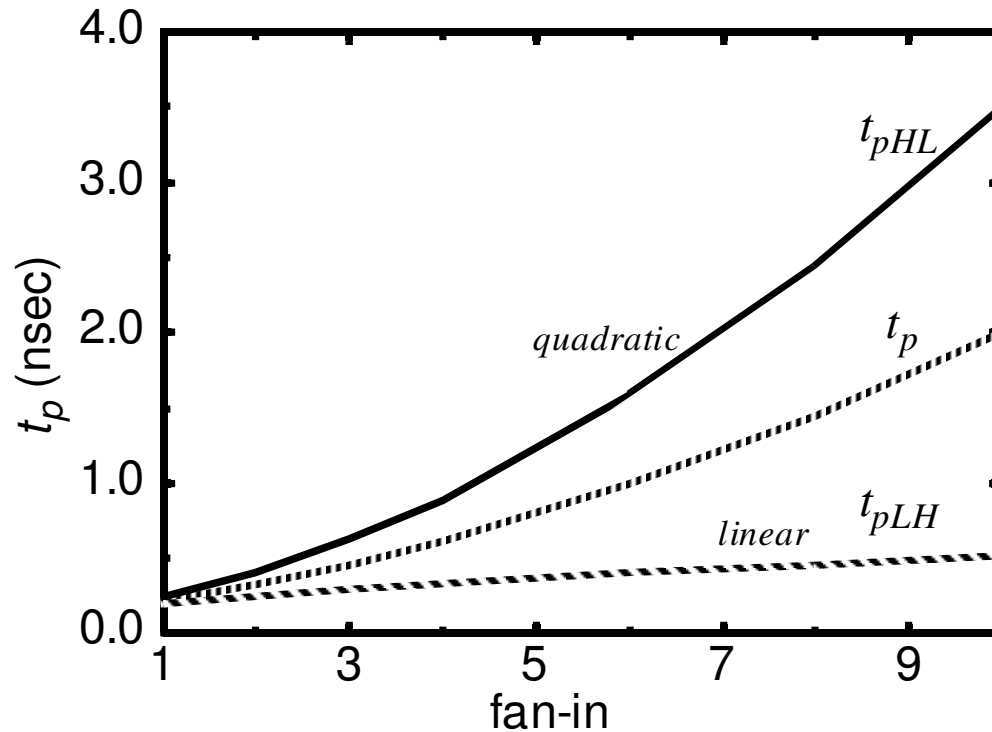


***AVOID LARGE FAN-IN GATES! (Typically not more than  $FI < 4$ )***

# Fast Complex Gate - Design Techniques

- **Transistor Sizing:**

As long as Fan-out Capacitance dominates

- **Progressive Sizing:**

 

$$M1 > M2 > M3 > MN$$



**Distributed RC-line**

**Can Reduce Delay with more than 30%!**




# Fast Complex Gate - Design Techniques (2)

- **Transistor Ordering**

  


# Fast Complex Gate - Design Techniques (3)

- **Improved Logic Design**

 

 
# Fast Complex Gate - Design Techniques (4)

- **Buffering: Isolate Fan-in from Fan-out**


 
# NMOS Inverter w/ Saturated Enhancement Load




- *A MOSFET replaces the resistive load, greatly improving the packing density.*
- *The two MOSFET's are fabricated with identical thresholds and process transconductance parameters, for simplicity and high circuit yield.*
- *The load has a positive threshold and has  $V_{GS} = V_{DS}$ ; therefore it is always saturated.*
- $V_{OH} = V_{DD} - V_T.$

# NMOS Inverter w/ Depletion Type Load

- *For the depletion type device,*

$$V_{GSL} = 0$$

 *This necessitates  $V_{TL} \leq 0$  for conduction in the load. Also, linear or saturated operation of the load is possible:*



$$V_{DD} - V_{OUT} > -V_{TL} \Rightarrow \text{saturation}$$

$$V_{DD} - V_{OUT} < -V_{TL} \Rightarrow \text{linear operation}$$

- *This circuit achieves  $V_{OH} = V_{DD}$  without the need for two supply voltages.*
- *The disadvantage is fabrication complexity, because transistors with two different threshold voltages are required.*

# n-Channel MOSFET connected as saturated load device

- An n-channel enhancement-mode MOSFET with the gate connected to the drain can be used as load device in an NMOS inverter.
- Since the gate and drain of the transistor are connected, we have

$$V_{GS} = V_{DS}$$

When  $V_{GS} = V_{DS} > V_{TN}$ , a non zero drain current is induced in the transistor and thus the transistor operates in **saturation only**. And following condition is satisfied.

$$V_{DS} > (V_{GS} - V_{TN})$$

$$V_{DS}(\text{sat}) = (V_{GS} - V_{TN}) \text{ because}$$

$$V_{GS} = V_{DS} \text{ or } V_{DS}(\text{sat}) = (V_{GS} - V_{TN})$$

In the saturation region the drain current is

$$i_D = K_n (V_{GS} - V_{TN})^2 = K_n (V_{DS} - V_{TN})^2$$


 


Figure 16.7 (a) n-channel MOSFET connected as saturated load device and (b) current-voltage characteristics of saturated load device

The  $i_D$  versus  $V_{DS}$  characteristics are shown in Figure 16.7(b), which indicates that this device acts as a nonlinear resistor.

 
## NMOS Inverter with Enhancement Load

- This basic inverter consist of two enhancement-only NMOS transistors
- Much more practical than the resister loaded inverter, because the resistors are thousand of times larger size than a MOSFET.


 
# NMOS Inverter with Enhancement Load

- An n-channel **enhancement-mode MOSFET** with gate connected to the drain can be used as a **load device**.



For  $v_{GS} = v_{DS} \leq V_{TN}$ , the drain current is zero.

$v_{GS} = v_{DS} > V_{TN}$ , a nonzero drain current is induced in the device.

$$v_{DS} > (v_{GS} - V_{TN}) = (v_{DS} - V_{TN}) = v_{DS}(\text{sat})$$

$$\underline{i_D} = K_n(v_{GS} - V_{TN})^2 = K_n(\underline{v_{DS}} - V_{TN})^2 \quad \text{Nonlinear resistor !!!}$$

A transistor with this connection always operates in the saturation region when not in cutoff.



# NMOS Inverter with Enhancement Load

When  $v_I < V_{TND}$  driver is cut off and the drain currents are zero.

$$i_{DL} = 0 = K_L(v_{DSL} - V_{TNL})^2$$



$$v_{DSL} = V_{DD} - v_O$$

$$v_{DSL} - V_{TNL} = V_{DD} - v_O - V_{TNL} = 0$$


maximum output voltage

$$v_{O,max} \equiv V_{OH} = V_{DD} - V_{TNL}$$

  For the enhancement-load NMOS inverter, the maximum output voltage, which is the logic 1 level, does not reach the full  $V_{DD}$  value.



# NMOS Inverter with Enhancement Load

 

As the input voltage increases, the driver Q-point moves up the load curve and the output voltage decreases linearly with  $v_I$ .


## NMOS Inverter with Enhancement Load

At the driver transition point,

$$v_{DSD}(\text{sat}) = v_{GSD} - V_{TND} \quad \text{or} \quad V_{OI} = V_H - V_{TND}$$

$$V_H = \frac{V_{DD} - V_{TNL} + V_{TND} \left( 1 + \sqrt{\frac{K_D}{K_L}} \right)}{1 + \sqrt{\frac{K_D}{K_L}}}$$
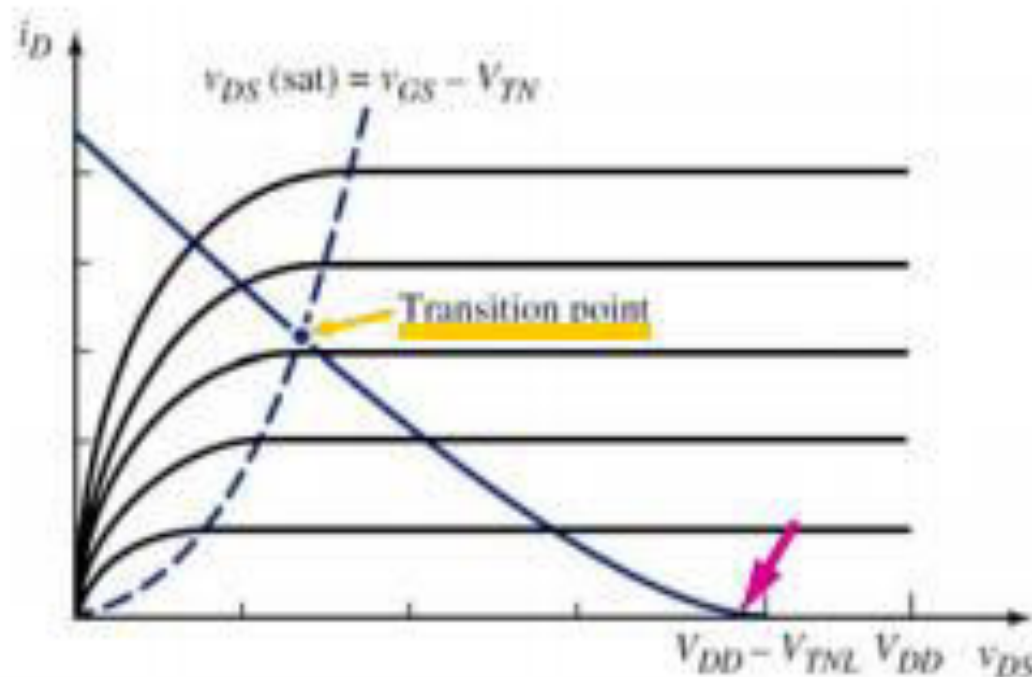
$$v_O = V_{DD} - V_{TNL} - \sqrt{\frac{K_D}{K_L}} (v_I - V_{TND})$$



# NMOS Inverter with Enhancement Load


When  $v_I > V_{th}$  the driver transistor  $Q$ -point continues to move up the load curve and the driver becomes biased in the nonsaturation region.

Since  $i_{DD} = i_{DL}$ ,

$$K_D[2(v_{GSD} - V_{TND})v_{DSD} - v_{DSD}^2] = K_L(v_{DSL} - V_{TNL})^2$$

$$K_D[2(v_I - V_{TND})v_O - v_O^2] = K_L(V_{DD} - v_O - V_{TNL})^2$$

 the relationship between  $v_I$  and  $v_O$  in this region is not linear.




Load:  
 $V_{TNL}, K_L$


Driver:  
 $V_{TND}, K_D$

$$K_D/K_L$$

 aspect ratio  
width-to-length parameters  
of the driver and load transistors.



## NMOS Inverter with Enhancement Load

 

Voltage transfer characteristics,  
 NMOS inverter with saturated load,  
 for three aspect ratios

# N-Channel Depletion-Mode MOSFET

- In n-channel depletion mode MOSFET, an n-channel region or inversion layer exists under the gate oxide layer even at zero gate voltage and hence term **depletion mode**.

 


Figure 5.12 Cross section of an n-channel depletion-mode MOSFET for (a)  $V_{gs} = 0$ ,  $V_{ds} = 0$ , (b)  $V_{gs} = 0$ ,  $V_{ds} = V_{ds}$ , (c)  $V_{gs} = -V_{gs}$ ,  $V_{ds} = 0$

- A negative voltage must be applied to the gate to turn the **device off**.
- The **threshold voltage** is always **negative** for this kind of device.



 


Figure 5.13 Family of  $I_d$  versus  $V_{ds}$  curves for an n-channel depletion-mode MOSFET

 using a different symbol for the depletion-mode device compared to the enhancement mode device is simply for clarity in a circuit diagram.



# NMOS Inverter with Depletion Load

 


Gate and source are connected,  $v_{GSL} = 0$

Since the threshold voltage of load transistor is negative.


$$v_{DSL}(\text{sat}) = v_{GSL} - V_{TNL} = -V_{TNL}$$

$v_{GSL} = 0$

 
 
## NMOS Inverter with Depletion Load

driver transistor characteristics and load curve





# NMOS Inverter with Depletion Load (cont.)

**Case I:** when  $V_i < V_{TND}$  (drive is cutoff): No drain current conduct in either transistor. That means the load transistor must be in the linear region of the operation and the output current can be expressed as follows

$$i_{DL}(\text{linear}) = K_L [2(V_{GSL} - V_{TNL})V_{DSL} - V_{DSL}^2]$$



Since  $V_{GSL} = 0$ , and  $i_{DL} = 0$

$$0 = -K_L [2V_{TNL}V_{DSL} + V_{DSL}^2]$$

Which gives  $V_{DSL} = 0$  thus

$$V_O = V_{DD}$$

  
*This is the advantage of the depletion load inverter over the enhancement load inverter.*


 
# NMOS Inverter with Depletion Load

When  $v_I > V_{TND}$

driver turns on and in the saturation region; however, load is in the nonsaturation region. Q-point lies between points A and B



two drain currents equal,  $i_{DD} = i_{DL}$

Load:  
 $V_{TNL} < K_L$


$$K_D[v_{GSD} - V_{TND}]^2 = K_L[2(v_{GSL} - V_{TNL})v_{DSL} - v_{DSL}^2]$$

$v_{GSL} = 0$

$$K_D[v_I - V_{TND}]^2 = K_L[2(-V_{TNL})(V_{DD} - v_O) - (V_{DD} - v_O)^2]$$

Driver:  
 $V_{TND} < K_D$

 There are two transition points  
one for the load and one for the driver.




transition point for the load

$$v_{DSL} = V_{DD} - V_{O1} = v_{GSL} - V_{TNL} = -V_{TNL}$$

$$V_{O1} = V_{DD} + V_{TNL} \text{ Since } V_{TNL} \text{ is negative, the output voltage at the transition point is less than } V_{DD}$$

# NMOS Inverter with Depletion Load

 

transition point for the driver

$$v_{DSD} = v_{GSD} - V_{TND}$$

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$V_{OI} = V_{II} - V_{TND}$$

Load:  
 $V_{TNL}, K_L$


Driver:  
 $V_{TND}, K_D$

When the  $Q$ -point lies between points  $B$  and  $C$  both devices are in the saturation region,


$$K_D(v_{GSD} - V_{TND})^2 = K_L(v_{GSL} - V_{TNL})^2$$

$$\sqrt{\frac{K_D}{K_L}}(v_I - V_{TND}) = -V_{TNL}$$

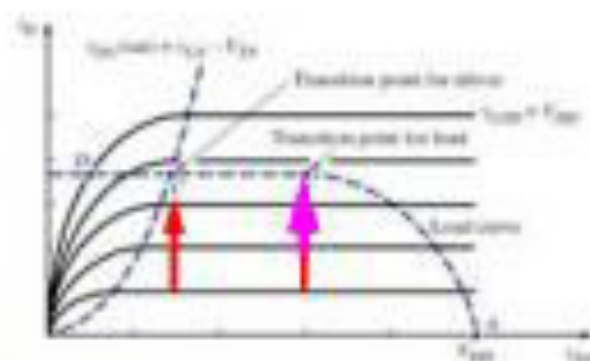This implies that input voltage is constant as the  $Q$ -point passes this region.



# NMOS Inverter with Depletion Load

 


driver is biased in the nonsaturation region while the load is in the saturation region. Q-point is between points C and D

$$K_D [2(v_{GSD} - V_{TNL})v_{DSD} - v_{DSD}^2] = K_L (v_{GSL} - V_{TNL})^2$$

$$\frac{K_D}{K_L} [2(v_I - V_{TNL})v_O - v_O^2] = (-V_{TNL})^2$$

 This implies that input and output voltages are not linear in this region.



# NMOS Inverter with Depletion Load

Voltage transfer characteristics,  
NMOS inverter with depletion load,

