



# **Unit 3**

## **Combinational MOS Logic Circuits**

# Introduction to CMOS Logic Circuits



- CMOS stands for ***Complementary Metal Oxide Semiconductor***
  - **Complementary:** there are N-type and P-type transistors. N-type transistors use electrons as the current carriers. P-type transistors use holes as the current carriers.
    - Electrons are free carriers in the conduction band with energy of  $E_c$  or just above the conduction band edge. Free electrons are generated by doping the silicon with an N-type impurity such as phosphorous or arsenic.
    - A hole is a current carrier due to the absence of an electron in a covalent bond state, i.e. a missing electron which would otherwise be part of a silicon-to-silicon bond. Holes are free carriers in the valence band with energy of  $E_v$  or just below the valence band edge. Holes are generated by doping the silicon with a P-type impurity such as boron.
  - **Metal:** the gate of the transistor was made of aluminum metal in the early days, but is made of polysilicon today (for the past 25 years or more).
  - **Oxide:** silicon dioxide is the material between the gate and the channel
  - **Semiconductor:** the semiconductor material is silicon, a type IV element in the periodic chart. Each silicon atom bonds to four other silicon atoms in a tetrahedral crystal structure.

# CMOS NFET and PFET Transistors

  


- N channel device: built directly in the P substrate with N-doped source and drain junctions and normally N-doped gate conductor
  - Requires positive voltage applied to gate and drain (with respect to source) for electrons to flow from source to drain (thought of as positive drain current)
- P channel device: built in an N-well (a deep N-type junction diffused into the P substrate) with P-doped source and drain junctions and N or P-doped gate
  - Requires negative voltage applied to gate and drain (with respect to source) for electrons to flow from drain to source (thought of as negative drain current)

# N-FET and P-FET Devices as Switches

 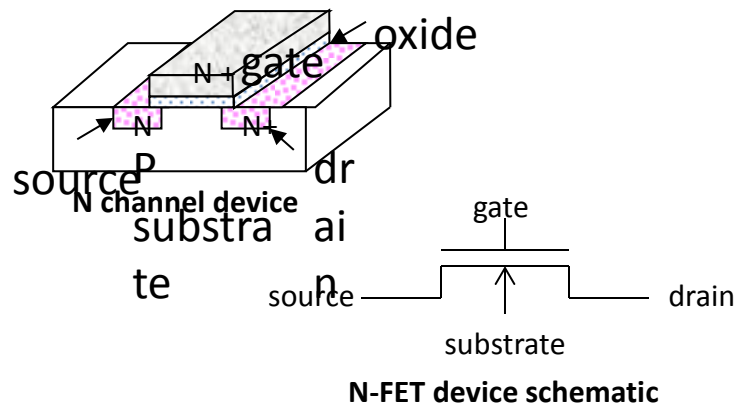

- NFET Device:
  - positive voltage (“1” or high) on gate relative to source turns device ON and allows positive current to flow from drain to source (switch closed)
  - zero volts on gate (“0” or low) turns device OFF (open circuit)
  - Source (vs drain) is the most negative terminal
- PFET Device:
  - Negative voltage (“0” or low) on gate relative to source turns device ON and allows (negative) current to flow from drain to source (closes switch)
  - Zero volts on gate relative to source (“1” or high) turns device OFF (closes switch)
  - source (vs drain) is the most positive terminal

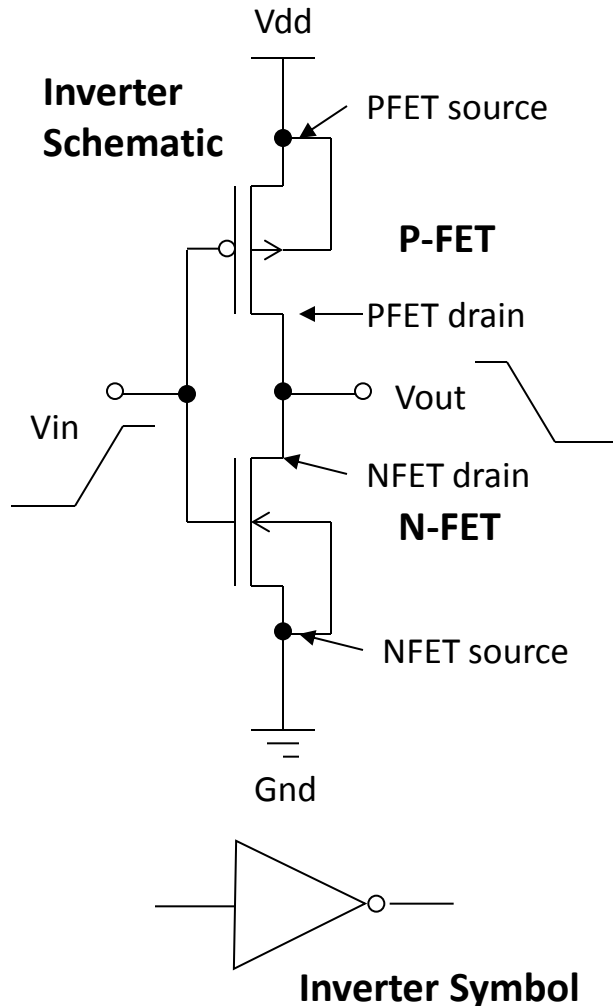
# Simple CMOS Circuits: *The Inverter Gate*




- The simplest complementary MOS (CMOS) circuit is the inverter:
  - NFET & PFET gates are connected together as the input
  - NFET & PFET drains are connected together as the output
  - NFET & PFET sources are connected to Gnd and Vdd, respectively.
  - NFET substrate is normally connected to Gnd for all NFET devices in the circuit
  - PFET well is normally connected to Vdd (most positive voltage in circuit) for all PFET devices
- Operation:
  - If Vin is down (0 volts), NFET is OFF and PFET is ON pulling Vout to Vdd (high = 1)
  - If Vin is up (at Vdd), NFET is ON hard and PFET is OFF pulling Vout low to Gnd ("0")
  - With Vin at 0 or Vdd, no dc current flows in inverter

# Simple CMOS Circuits: *The Transmission Gate*

**X gate  
Schematic**

 


**X-gate  
Symbols**

 


- Circuit topology:
  - N and P devices with sources and drains connected in parallel.
  - $V_g$  is the control signal for the N device;  $V_{gc}$  (complement of  $V_g$ ) is the control signal for the P device.
- Operation:
  - When  $V_g$  is high (at  $V_{dd}$ ) and  $V_{gc}$  is therefore low (at  $Gnd$ ), the NFET and PFET are both ON. (Depending upon the devices' source potentials, one may be ON more strongly than the other.) The switch is therefore CLOSED and  $V_{out}$  will be the same logic level as  $V_{in}$ .
  - When  $V_g$  is low (at  $Gnd$ ) and  $V_{gc}$  is high (at  $V_{dd}$ ), both devices are OFF. The switch is therefore OPEN and  $V_{out}$  will be independent of  $V_{in}$  (high Z connection).

# Simple CMOS Circuits: **2-way NAND**


 

 
$$V_{out} = \overline{A \cdot B} = \overline{A} + \overline{B}$$



- Circuit Topology:
  - T1 and T2 are N-FET devices connected in series; T3 and T4 are P-FET devices connected in parallel with their sources at Vdd and their drains at Vout.
  - Inputs A and B are connected to the gates of T1 & T3 and T2 & T4, respectively.
  - T2, T3, & T4 operate as “grounded source” devices, but T1 has its source generally above Gnd potential.
- Operation:
  - If both A and B are high (at Vdd), both T1 and T2 are ON hard, therefore pulling Vout low (to zero volts). Both T3 and T4 are OFF due to their gate-to-source voltages (Vgs) being at 0 volts, thus preventing any dc current.
  - If either A or B (or both) are low (at 0 volts), either T1 or T2 (or both) are OFF; T3 or T4 (or both) are ON hard, thus pulling Vout high to Vdd (a “1” output).


# Simple CMOS Circuits: **2-way NOR**

  


- Circuit Topology:
  - T1 and T2 are N-FET devices connected in parallel with their sources at Gnd and drains at Vout; T3 and T4 are P-FET devices connected in series.
  - Inputs A and B are connected to the gates of T1 & T3 and T2 & T4, respectively.
- Operation:
  - If either A or B is high, T1 and/or T2 are ON hard and either T3 or T4 (or both) are OFF, pulling Vout to gnd. No dc current flows.
  - If both A and B are low (at gnd), both T1 and T2 are OFF and both T3 and T4 are ON hard, thus pulling Vout to Vdd (a “1” output).
  - T1, T2, and T3 operate as common source, but T4’s source potential will drop below Vdd.



# Simple CMOS Circuits: **3-way NAND**

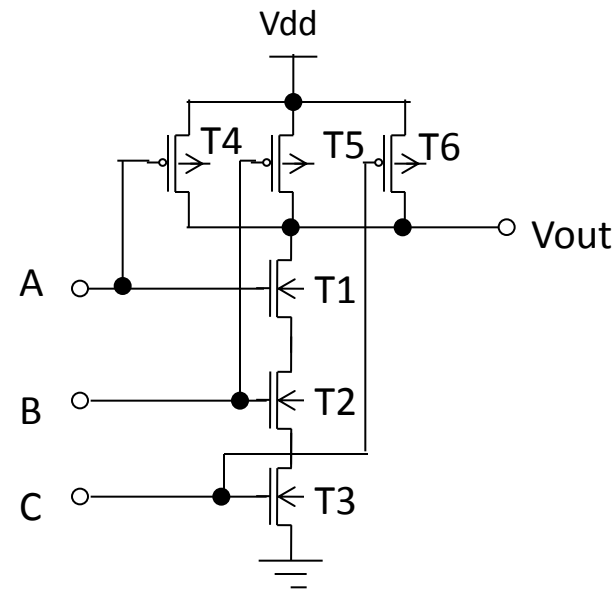

 
$$V_{out} = \overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$




- Circuit Topology:
  - T1,T2,T3 are N-FET devices in series; T4,T5,T6 are P-FET devices in parallel with sources to Vdd.
  - T3, T4, T5, & T6 all operate as grounded source mode; T1 & T2 will have their source potentials above gnd over portions of the switching transient, or if T3 is OFF
- Circuit Operation:
  - If all of T1, T2, & T3 are ON (A, B, & C all high), Vout is pulled low; T4, T5, & T6 are all OFF thus preventing any dc current flow.
  - If one (or more) of A, B, or C are low, then the corresponding P device T4, T5, and/or T6 is ON hard and Vout is pulled high; at the same time one or more of T1, T2, and/or T3 is OFF preventing any dc current flow.

# Simple CMOS Circuits: *Compound Logic*

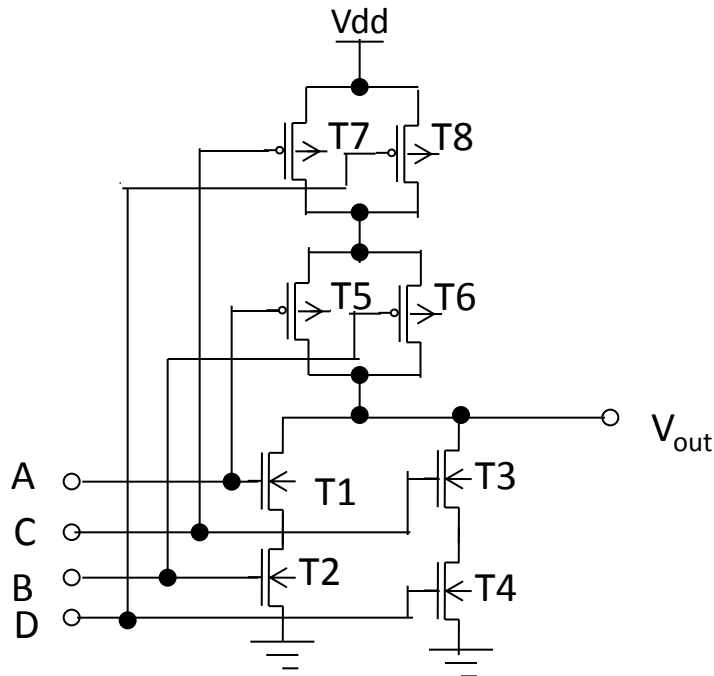
 
$$V_{out} = (A \text{ AND } B) + (C \text{ AND } D)$$




- Circuit Schematic:
  - T1–T4 form a parallel combination of series-connected NFET's; T5-T8 are a series combination of parallel-connected PFET's.
  - T2, T4, T7 & T8 operate as grounded-source devices; T1, T3, T5 & T6 all have their drain's tied together as  $V_{out}$ .
  - Note that the P device combination is arranged complementary to the N device combination!
- Operation:
  - If either A and B or C and D are high, NFET devices T1 and T2 or T3 and T4 are ON and pull  $V_{out}$  down to ground potential (0 volts). No dc current flows.
  - If either A and C, or A and D, or B and C, or B and D are low, PFET devices T5 and T7, or T5 and T8, or T6 and T7, or T6 and T8 will be ON and pull  $V_{out}$  high to Vdd. No dc current flows.

## Simple CMOS Logic Circuits: *Construction Algorithm*

- Design the N-FET logic combination to pull the output down to zero, i.e. for all the min-terms in truth table with “0”s in the output column.
  - N devices are ON when the truth table inputs corresponding to their respective gate electrodes are “1”s; conversely, any truth table inputs that are zero imply that the corresponding N devices for those inputs are OFF.
- Design the P-FET logic combination to pull output high to VDD, i.e. to cover all min-terms in truth table with “1”s in the output column.
  - P devices are ON when the truth table inputs corresponding to their respective gates are “0”s; conversely, P devices are OFF if the voltages on their respective gates are at the “1” level.
- Start with N pull down logic and P pull up logic which are complementary to each other.
- Then, look for ways to simplify the logic combinations by removing devices having redundant paths.

# Simple CMOS Logic Circuits: *XOR*

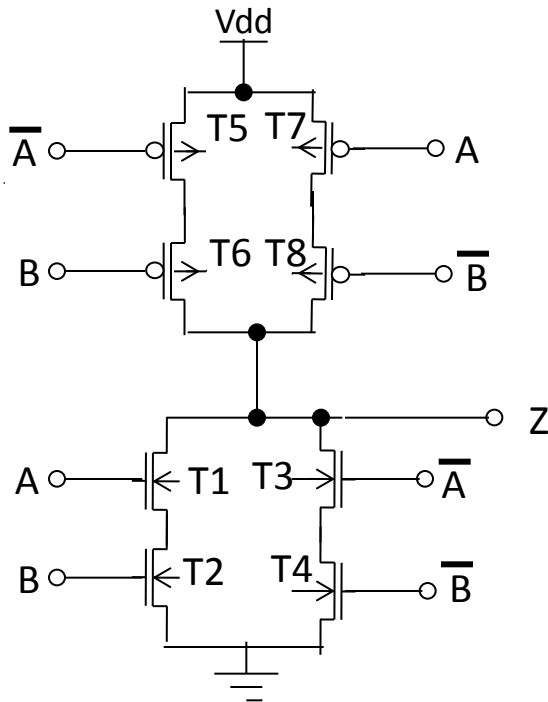

$$Z = (A \quad \overline{B}) + (A \quad \overline{B})$$

$$= \overline{\overline{(A \quad \overline{B})} \quad \overline{(A \quad \overline{B})}}$$

$$= \overline{(\overline{A} + B) \quad (\overline{A} + B)}$$

$$= \overline{(A \quad B) + (A \quad \overline{B})}$$

- Circuit Schematic:

- 4 NFET's (T1-T4) and 4 PFET's (T5-T8) are constructed as four parallel sections of two series devices each.
- Each series connection implements a min-term in the truth table – two for Z=1 and two for Z=0.
- Could implement either tree first and then apply complement procedure, or use DeMorgan's theorem to implement each min-term of truth table directly.

- Operation:

- Output is pulled high to VDD by either A=1 and B=0 (turning on T5 and T6), or by A=0 and B=1 (turning on T7 and T8).
  - Implements the "1" min-terms
- Output is pulled low to ground by either A=1 and B=1 (turning on T1 and T2), or by A=0 and B=0 (turning on T3 and T4).
  - Implements the "0" min-terms

# Simple CMOS Logic Circuits: *Examples from 1.5.5*

In Class Exercise: Work out the following examples from the text.

Design CMOS logic functions for the following gates:

$$(1-c) \quad Z = \overline{(A \cdot B \cdot C) + D}$$

$$(1-d) \quad Z = \overline{((A \cdot B) + C) \cdot D}$$

$$(1-e) \quad Z = \overline{(A \cdot B) + C \cdot (A + B)}$$

Use a combination of CMOS gates to generate the following functions:


$$(2-a) \quad Z = A \text{ (this is a buffer)}$$

$$(2-b) \quad Z = A \cdot \overline{B} + \overline{A} \cdot B \text{ (XOR)}$$

$$(2-c) \quad Z = A \cdot B + \overline{A} \cdot \overline{B} \text{ (XNOR)}$$

$$(2-d) \quad Z = A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot C + A \cdot B \cdot \overline{C} + \overline{A} \cdot B \cdot C \text{ which is the sum function in the binary adder.}$$
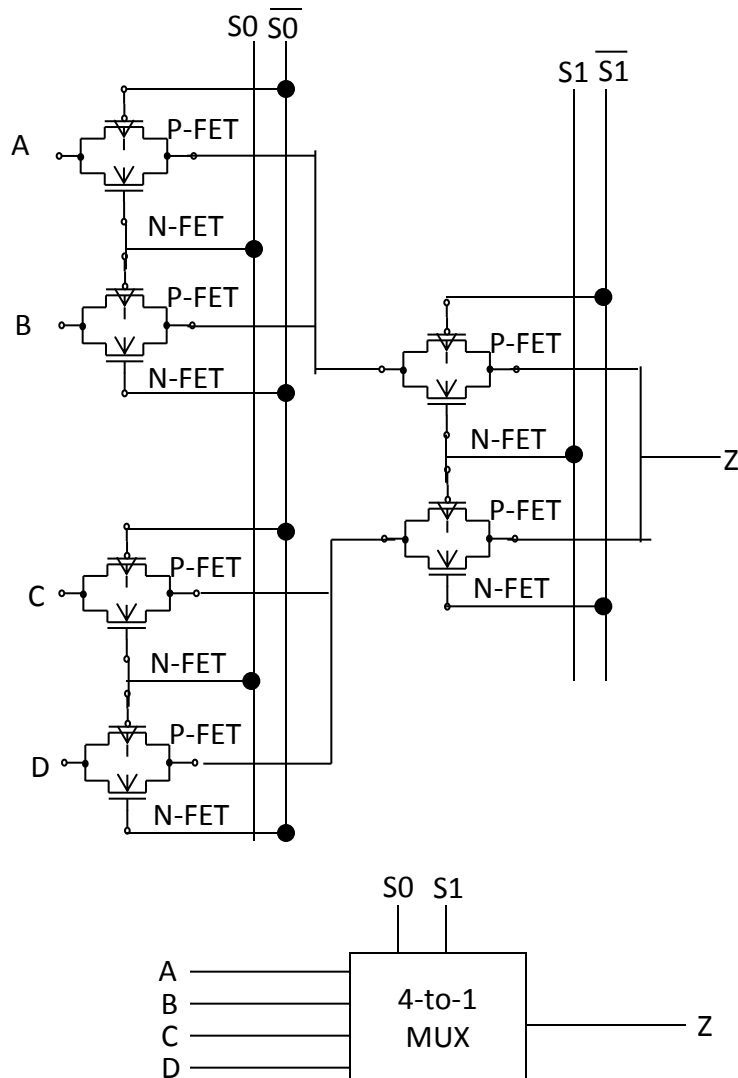
# Simple CMOS Logic Circuits: *The Multiplexer*



- Multiplexers can be implemented with standard CMOS logic gates or with CMOS transmission gates or with a combination of both!
  - With CMOS gates, a 2-to-1 multiplexer requires 3 gates (2 AND's & 1 OR) having 12 Tx's (plus inverter for select)
  - With Xmission gates, a 2-to-1 multiplexer requires only 4 Tx's (plus inverter for the select)
- 4-to-1 multiplexer shown at right:
  - Using Xmission gates, 12 Tx's (plus 2 inverters for selects)
  - Using CMOS logic, it requires four 3-input AND gates plus one 4-input OR gate for a total of 32 Tx's (plus 2 inverters for the selects)

# VLSI Circuit/System Representations

- Design of a digital system may be represented by several different design domains (Behavioral, Structural, and Physical) and within each domain various levels of abstraction (Architectural, Logic, Circuit, Transistor)
  - Behavioral Domain: specifies what the system does
    - Ex: Applications ... Operating System ... Program ... Subroutine ... Instruction
  - Structural Domain: specifies how the entities are connected & organized
    - Ex: PC ... Processor ... Gates & Registers ... Transistors
  - Physical Domain: specifies how to build the structure
    - Ex: Box .... Board/Card ... Modules ... Chips .... Cells ... Transistors ... Process/Masks

# VLSI Circuit/System Representations: *Behavioral*

- Describes how the particular system, chip, or macro should respond to a set of inputs
- May be specified by:
  - Boolean equations
  - Truth tables
  - Algorithms written in standard high level computer languages (e.g. RTL)
  - Special HDL's (Hardware Description Language) such as VHDL and Verilog
- Example in text from adder implementation
  - Sum and carry functions



# VLSI Circuit/System Representations: *Structural*

- Specifies how components are organized and interconnected to perform the given function
- Levels of specification: (use adder example)
  - Functional block: build a 4 bit adder out of 1 bit adders
  - Module add: specify a 1 bit adder with sum and carry functions
  - Logic level: specify the adder or carry as logic functions
  - Circuit level: specify the circuit as interconnected NMOS and PMOS transistors (CMOS circuit)
    - A full description at the circuit level would be a **SPICE** representation which lists the transistor types, transistor interconnections, transistor sizes, junction capacitances, wire capacitances, resistances, etc. for a full circuit performance simulation

# VLSI Circuit/System Representations: *Physical*


- Specifies how to construct (fabricate) the particular chip or system
- Levels of specification:
  - Process description
  - Photo mask image information for building transistors
  - Recipes for building modules, cards, boards, etc.

# Complex Logic Circuits

## Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN:  $G = A B \Rightarrow$  Conduction to GND


PUN:  $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$  Conduction to  $V_{DD}$

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


# Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of a 2 input NOR gate

 

# Example Gate: COMPLEX CMOS GATE

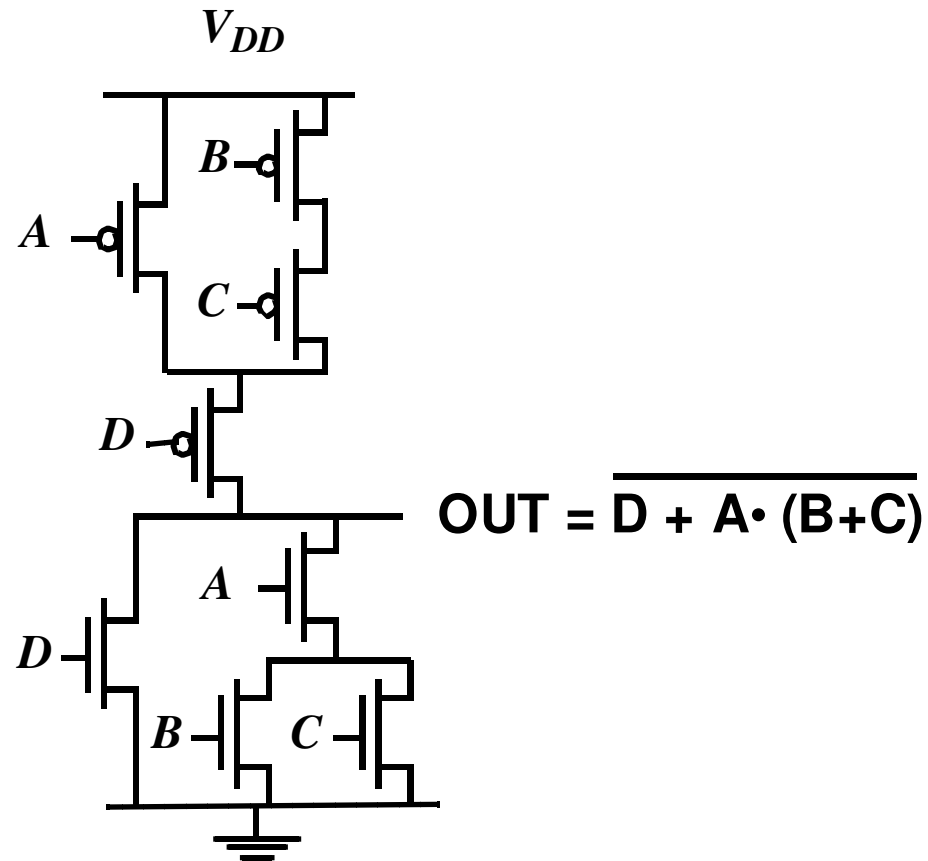

# Properties of Complementary CMOS Gates

***High noise margins:***

**$V_{OH}$  and  $V_{OL}$  are at  $V_{DD}$  and  $GND$ , respectively.**

***No static power consumption:***

**There never exists a direct path between  $V_{DD}$  and  $V_{SS}$  ( $GND$ ) in steady-state mode.**

***Comparable rise and fall times:***

**(under the appropriate scaling conditions)**

# Properties of Complementary CMOS Gates

*High noise margins:*

$V_{OH}$  and  $V_{OL}$  are at  $V_{DD}$  and  $GND$ , respectively.

*No static power consumption:*


There never exists a direct path between  $V_{DD}$  and  $V_{SS}$  ( $GND$ ) in steady-state mode.

*Comparable rise and fall times:*

(under the appropriate scaling conditions)
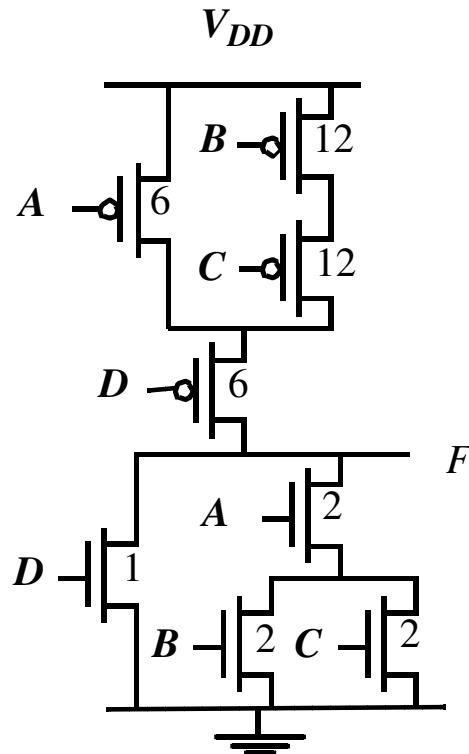
# Transistor Sizing

- for symmetrical response (dc, ac)
- for performance




**Input Dependent**


**Focus on worst-case**



 
# Propagation Delay Analysis - The Switch Model



(a) Inverter

 

(b) 2-input NAND

 

(c) 2-input NOR

$$t_p = 0.69 R_{on} C_L$$


(assuming that  $C_L$  dominates!)

# Fast Complex Gate - Design Techniques

- **Transistor Sizing:**

As long as Fan-out Capacitance dominates

- **Progressive Sizing:**

 



$$M1 > M2 > M3 > MN$$

**Distributed RC-line**

**Can Reduce Delay with more than 30%!**


# Fast Complex Gate - Design Techniques (2)

- **Transistor Ordering**

  


# Fast Complex Gate - Design Techniques (3)

- **Improved Logic Design**

 

 
# Fast Complex Gate - Design Techniques (4)

- **Buffering: Isolate Fan-in from Fan-out**




# Example: Full Adder

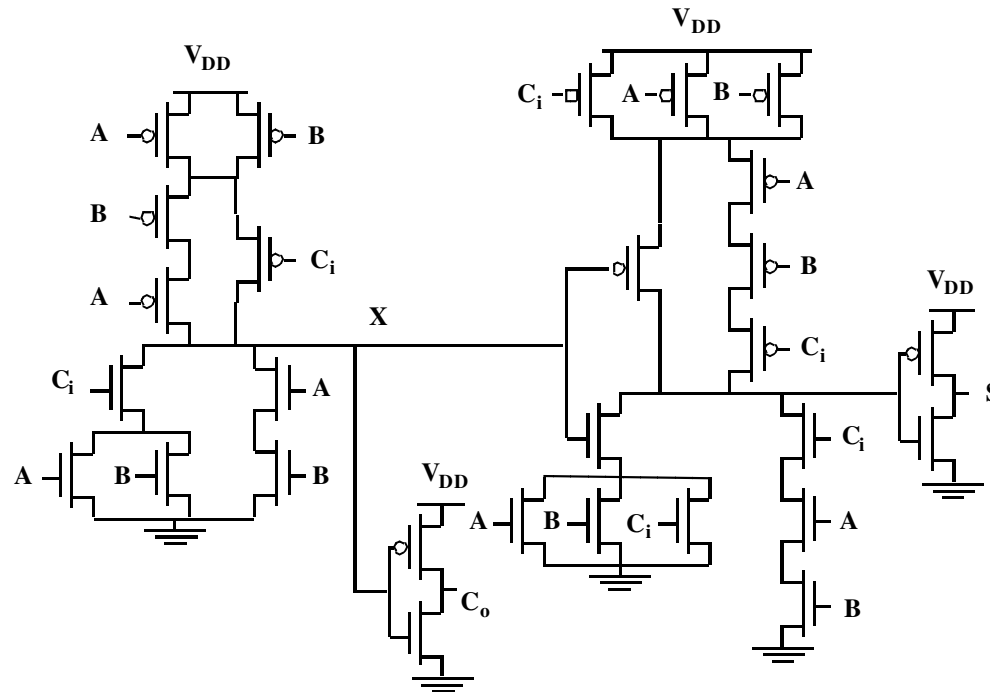

$$C_o = AB + C_i(A+B)$$

28 transistors

# A Revised Adder Circuit

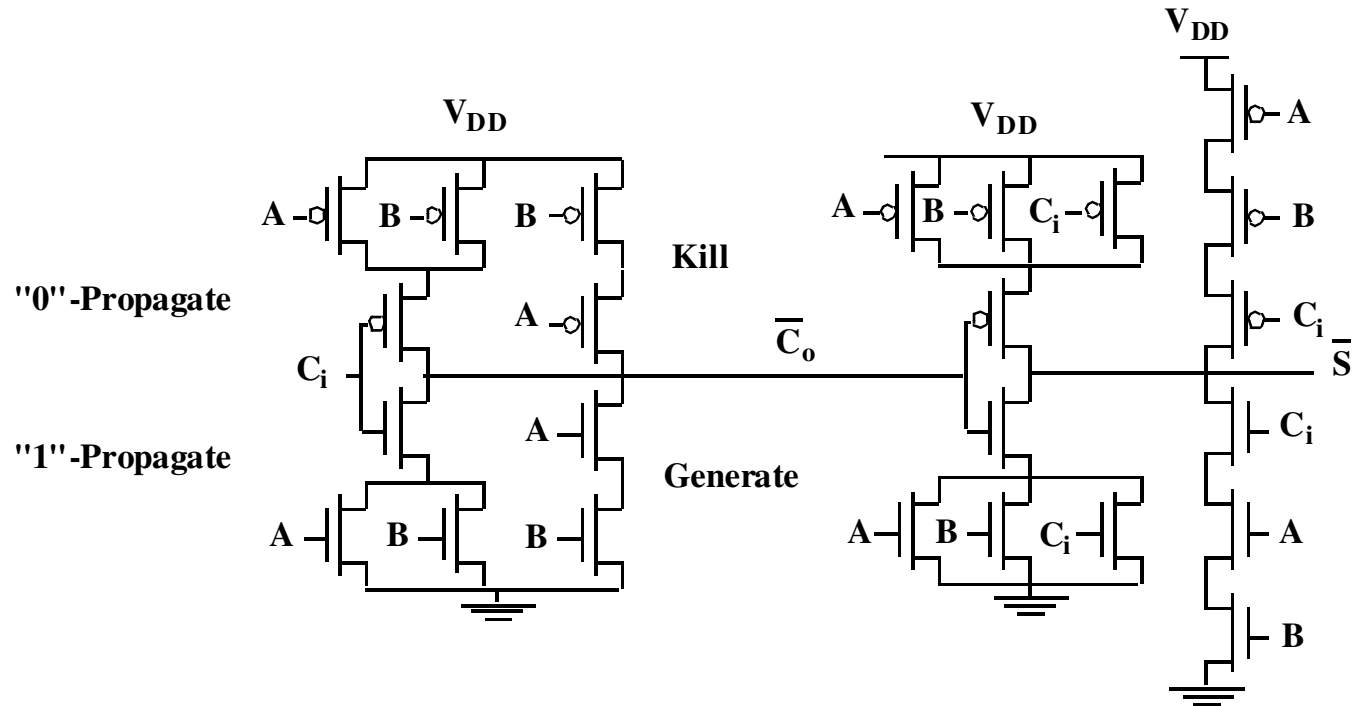

**24 transistors**