

UNIT 5:

Low – Power CMOS Logic Circuits

Controllability and Observability

- The ***controllability*** of a circuit is a measure of the ease (or difficulty) with which the controller (test engineer) can establish a specific signal value at each node by setting values at the circuit input terminals.
- The ***observability*** is a measure of the ease (or difficulty) with which one can determine the signal value at any logic node in the circuit by controlling its primary input and observing the primary output.

- The term *primary* refers to the I/O boundary of the circuit under test.
- The degree of controllability and observability and, thus, the degree of testability of a circuit, can be measured with respect to whether test vectors are generated deterministically or randomly.
- For example, if a logic node can be set to either logic 1 or 0 only through a very long sequence of random test vectors, the node is said to have a very *low random controllability since the* probability of generating such a vector in random test generation is very low.

- There exist time constraints in practice, and in such cases the circuit may not be considered testable.
- There are deterministic procedures for test generation for combinational circuits, such as the D-algorithm which uses a recursive search procedure advancing one gate at a time and backtracking, if necessary, until all the faults are detected.
- The D-algorithm requires a large amount of computer time. To overcome such shortcomings, many improved algorithms such as Path-Oriented DEcision Making (PODEM) and FAN-out-oriented test generation (FAN) have been introduced, Sequential circuit test generation is several orders of magnitude more difficult than these algorithms.
- To ease the task of ATG, design-for-test (DFT) techniques are routinely employed.

 


Fig. A simple circuit consisting of four gates with four primary inputs and one primary output.

- To detect any defect on line 8, the primary inputs A and B must be set to logic 1.
- However, such a setting forces line 7 to logic 1. Thus, any stuck-at- (s-a- 1) fault on line 7 *cannot be tested at the primary output, although in the absence of such a fault, the logic* value on line 7 can be fully controllable through primary inputs B, C, and D.
- Therefore, this circuit is *not fully testable. The main cause of this difficulty in this circuit is the fact* that input B fans out to lines 5 and 6, and then after the OR3 gate, both line signals are combined in the AND3 gate.
- Such a fanout is called ***reconvergent fanout***.
- *Reconvergent* fanouts make the testing of the circuit much more difficult.

- If a large number of input vectors are required to set a particular node value to 1 or 0 (fault excitation) and to propagate an error at the node to an output (fault effect propagation), then the testability is low.
- The circuits with poor controllability include those with feedbacks, decoders, and clock generators.
- The circuits with poor observability include sequential circuits with long feedback loops and circuits with reconvergent fanouts, redundant nodes, and embedded memories such as RAM, ROM, and PLA.