

LECTURE 1 OP-AMP

Introduction of Operation Amplifier (Op-Amp)

Analysis of ideal Op-Amp applications

Comparison of ideal and non-ideal Op-Amp

Non-ideal Op-Amp consideration



OPERATIONAL AMPLIFIER (OP-AMP)

Very high differential gain


High input impedance

Low output impedance

**Provide voltage changes
(amplitude and polarity)**

**Used in oscillator, filter
and instrumentation**

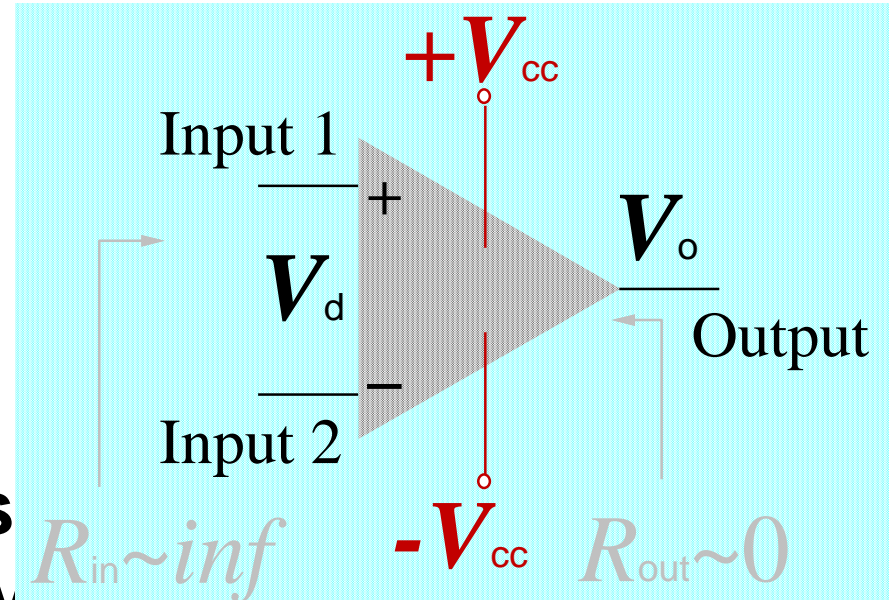
**Accumulate a very high
gain by multiple stages**




$$V_o = G_d V_d$$

G_d : differential gain normally
very large, say 10^5

IC PRODUCT

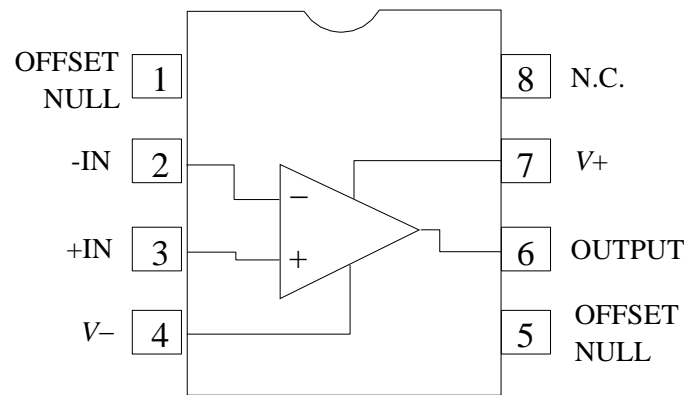


DIP-741

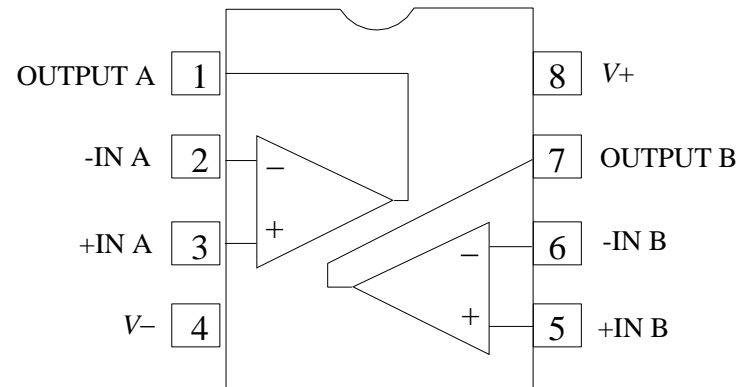


Dual op-amp 1458 device

SINGLE-ENDED INPUT

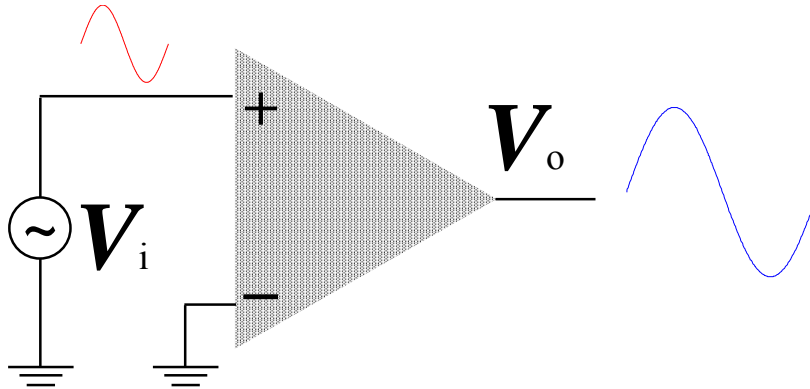


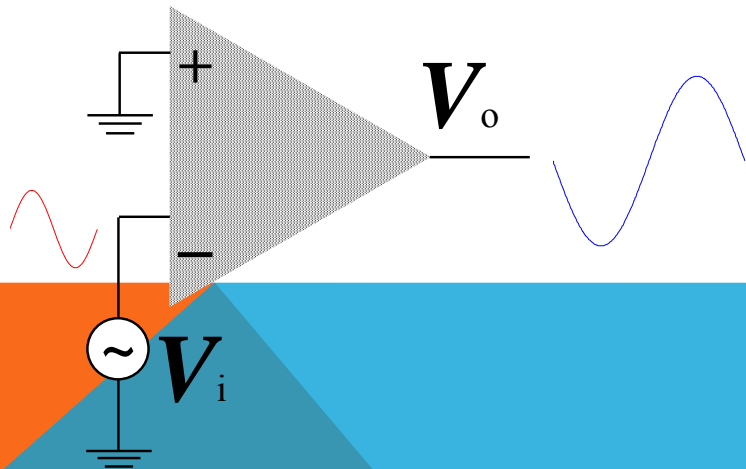- + terminal : Source
- - terminal : Ground
- 0° phase change




- + terminal : Ground
- - terminal : Source
- 180° phase change


DOUBLE-ENDED INPUT

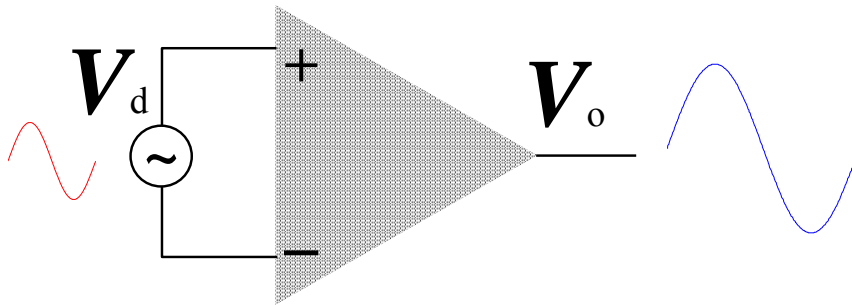

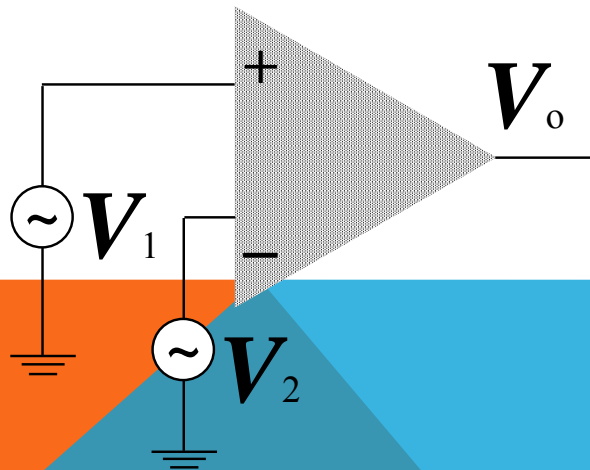
- Differential input
- $V_d = V_+ - V_-$
- 0° phase shift change between V_o and V_d



Qu: What V_o should be if,

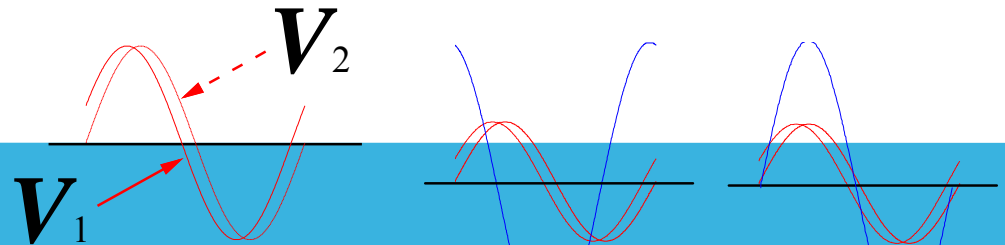


Ans: (A or B) ?

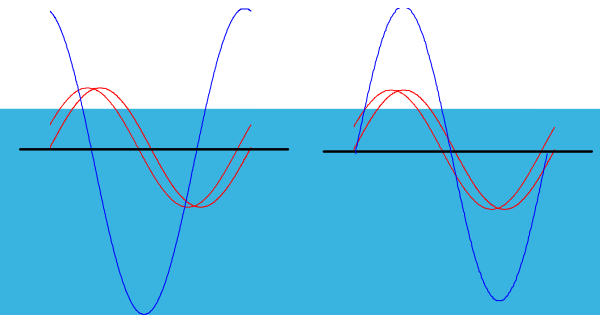

(A)

(B)


DISTORTION

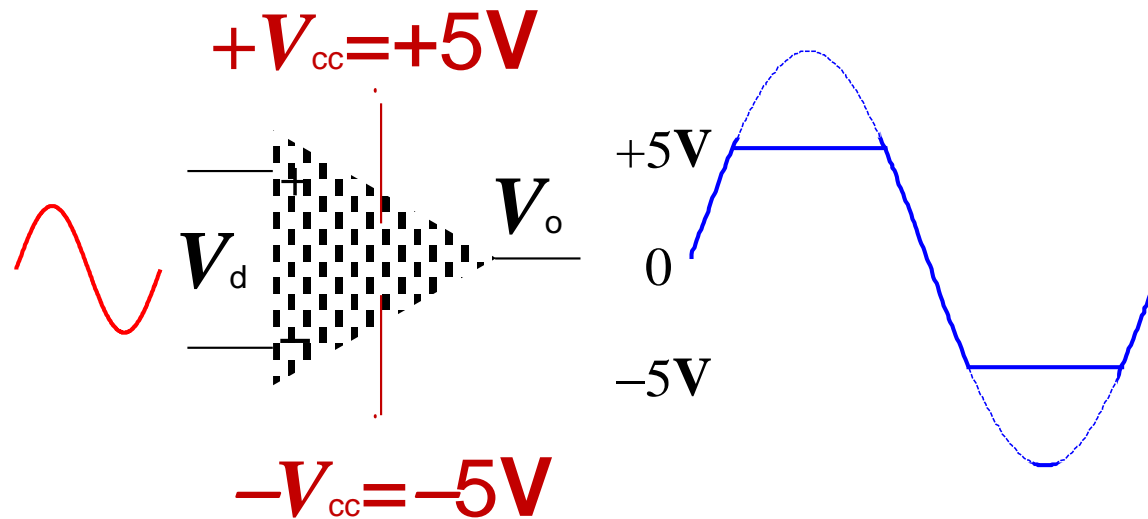

The output voltage never exceeds the DC voltage supply of the Op-Amp

COMMON-MODE OPERATION

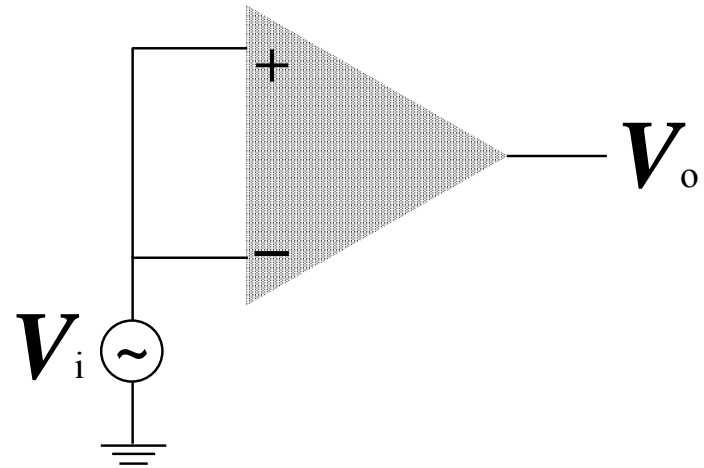- Same voltage source is applied at both terminals
- Ideally, two input are equally amplified
- Output voltage is ideally zero due to differential voltage is zero
- **Practically**, a small output signal can still be measured



Note for differential circuits:
Opposite inputs : highly amplified
Common inputs : slightly amplified
 \Rightarrow Common-Mode Rejection

COMMON-MODE REJECTION RATIO (CMRR)

Differential voltage input :

$$V_d = V_+ - V_-$$

Common voltage input :


$$V_c = \frac{1}{2}(V_+ + V_-)$$

Output voltage :

$$V_o = G_d V_d + G_c V_c$$

G_d : Differential gain

G_c : Common mode gain

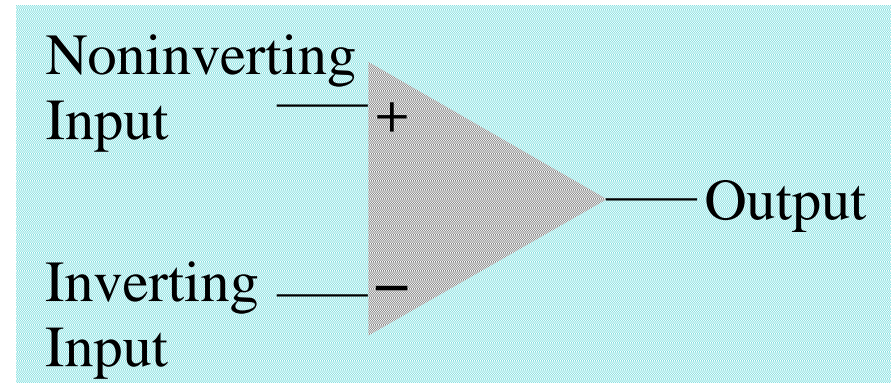

Common-mode rejection ratio:

$$\text{CMRR} = \frac{G_d}{G_c} = 20 \log_{10} \frac{G_d}{G_c} (\text{dB})$$

Note:

When $G_d \gg G_c$ or $\text{CMRR} \rightarrow \infty$
 $\Rightarrow V_o = G_d V_d$