

# LECTURE 2 OP-AMP



**Comparison of ideal and non-ideal Op-Amp**

**Non-ideal Op-Amp consideration**



# CMRR EXAMPLE

What is the CMRR?

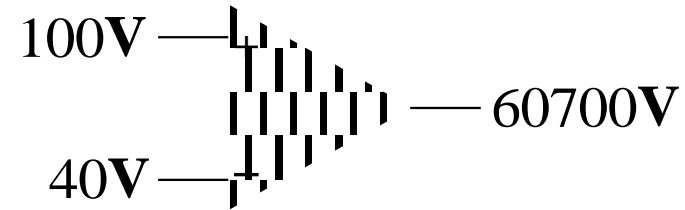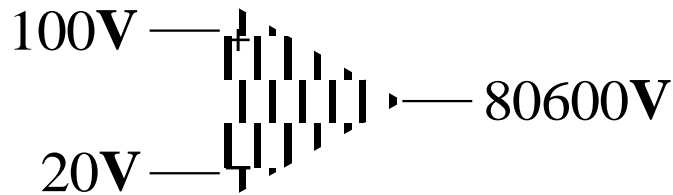

Solution :

$$\left. \begin{aligned} V_{d1} &= 100 - 20 = 80\text{V} \\ V_{c1} &= \frac{100 + 20}{2} = 60\text{V} \end{aligned} \right\} (1)$$

$$\left. \begin{aligned} V_{d2} &= 100 - 40 = 60\text{V} \\ V_{c2} &= \frac{100 + 40}{2} = 70\text{V} \end{aligned} \right\} (2)$$

**From (1)**  $V_o = 80G_d + 60G_c = 80600\text{V}$

**From (2)**  $V_o = 60G_d + 70G_c = 60700\text{V}$


$G_d = 1000$  and  $G_c = 10 \Rightarrow \text{CMRR} = 20\log(1000/10) = 40\text{dB}$

NB: This method is Not work! Why?

# OP-AMP PROPERTIES

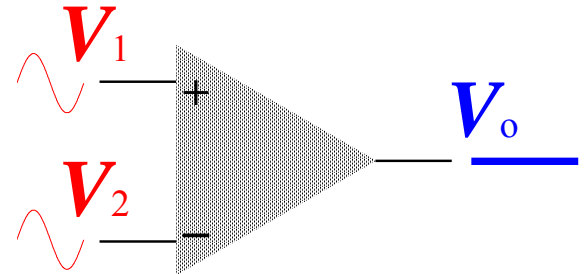
## (1) Infinite Open Loop gain

- The gain without feedback
- Equal to differential gain
- Zero common-mode gain
- Practically,  $G_d = 20,000$  to  $200,000$



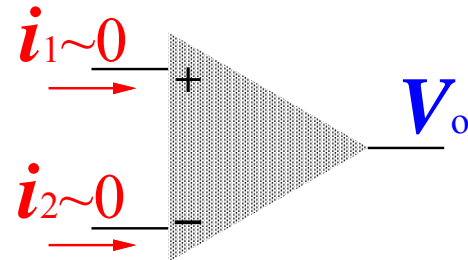
## (2) Infinite Input impedance

- Input current  $i_i \sim 0A$
- T- $\Omega$  in high-grade op-amp
- m-A input current in low-grade op-amp



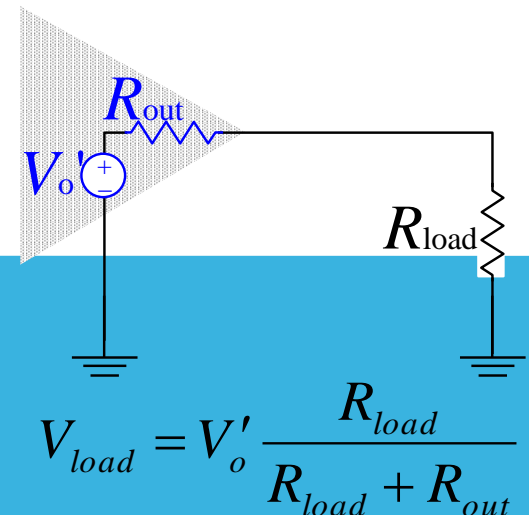
## (3) Zero Output Impedance

- act as perfect internal voltage source
- No internal resistance
- Output impedance in series with load
- Reducing output voltage to the load
- Practically,  $R_{out} \sim 20-100 \Omega$


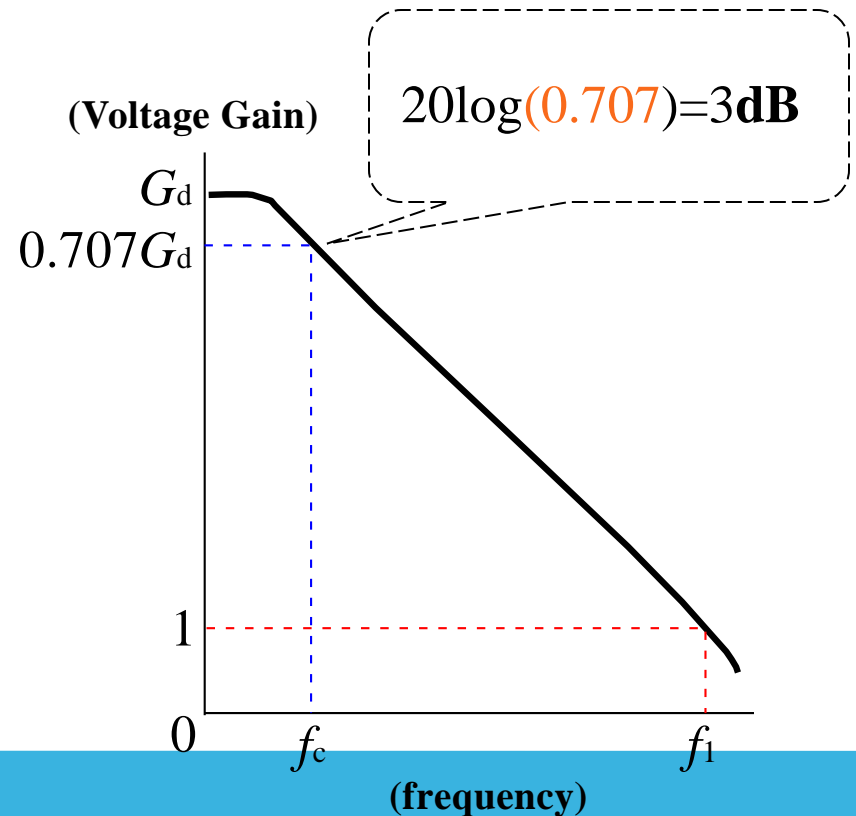
# FREQUENCY-GAIN RELATION

- Ideally, signals are amplified from DC to the highest AC frequency
- Practically, bandwidth is limited
- 741 family op-amp have a limit bandwidth of few KHz.
- Unity Gain frequency  $f_1$ : the gain at unity
- Cutoff frequency  $f_c$ : the gain drop by 3dB from dc gain  $G_d$



$$\text{GB Product : } f_1 = G_d f_c$$

# GB PRODUCT

Example: Determine the cutoff frequency of an op-amp having a unit gain frequency  $f_1 = 10 \text{ MHz}$  and voltage differential gain  $G_d = 20 \text{ V/mV}$

Sol:

Since  $f_1 = 10 \text{ MHz}$


By using GB production equation

$$f_1 = G_d f_c$$

$$f_c = f_1 / G_d = 10 \text{ MHz} / 20 \text{ V/mV}$$



$$= 10 \times 10^6 / 20 \times 10^3$$

$$= 500 \text{ Hz}$$

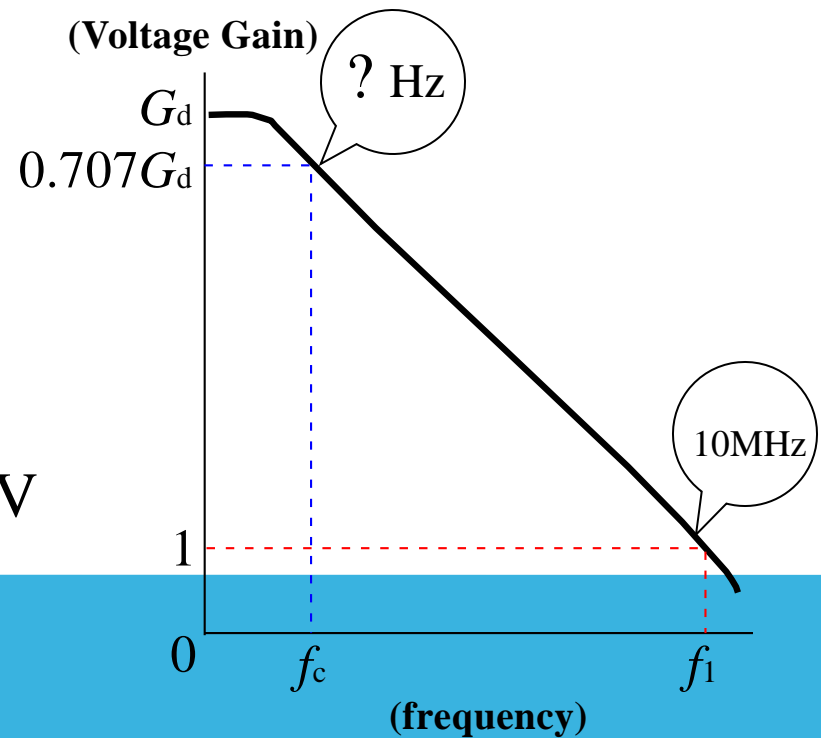

# IDEAL VS PRACTICAL OP-AMP

	Ideal	Practical
Open Loop gain $A$	$\infty$	$10^5$
Bandwidth $BW$	$\infty$	10-100Hz
Input Impedance $Z_{in}$	$\infty$	$>1\text{M}\Omega$
Output Impedance $Z_{out}$	$0\ \Omega$	10-100 $\Omega$
Output Voltage $V_{out}$	Depends only on $V_d = (V_+ - V_-)$ Differential mode signal	Depends slightly on average input $V_c = (V_+ + V_-)/2$ Common-Mode signal
CMRR	$\infty$	10-100dB

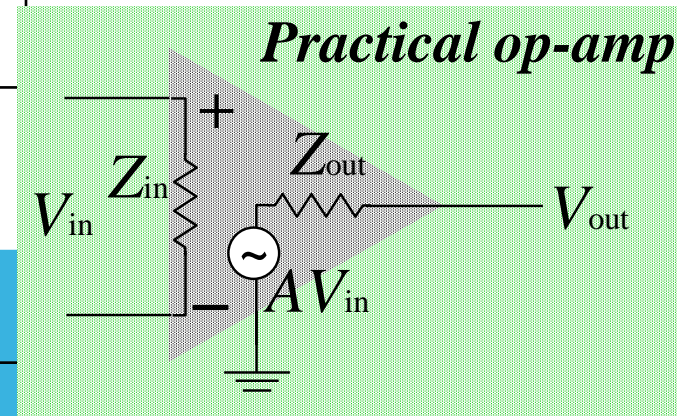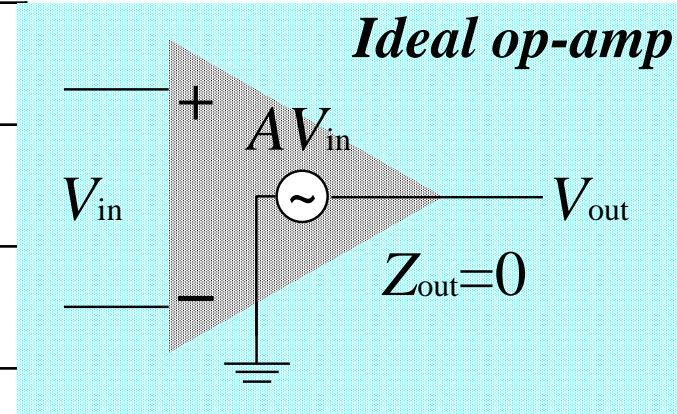

# IDEAL OP-AMP APPLICATIONS

## *Analysis Method :*

**Two ideal Op-Amp Properties:**


- (1) The voltage between  $V_+$  and  $V_-$  is zero  $V_+ = V_-$**
- (2) The current into both  $V_+$  and  $V_-$  terminals is zero**

**For ideal Op-Amp circuit:**

- (1) Write the kirchhoff node equation at the noninverting terminal  $V_+$**
- (2) Write the kirchhoff node equation at the inverting terminal  $V_-$**
- (3) Set  $V_+ = V_-$  and solve for the desired closed-loop gain**

# Noninverting Amplifier

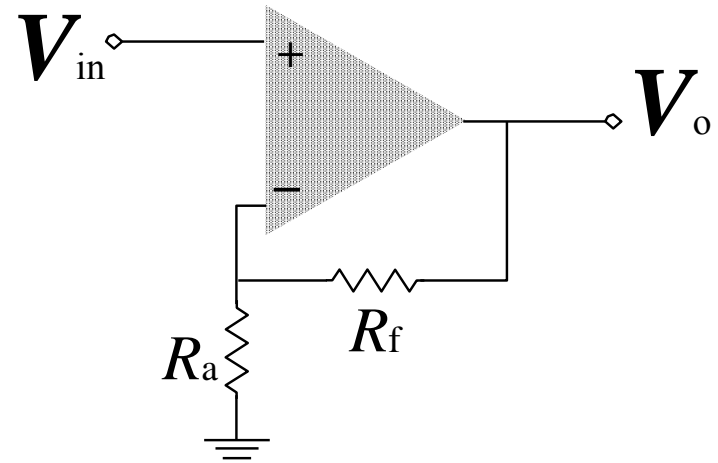(1) Kirchhoff node equation at  $V_+$  yields,  $V_+ = V_i$




(2) Kirchhoff node equation at  $V_-$  yields,  $\frac{V_- - 0}{R_a} + \frac{V_- - V_o}{R_f} = 0$

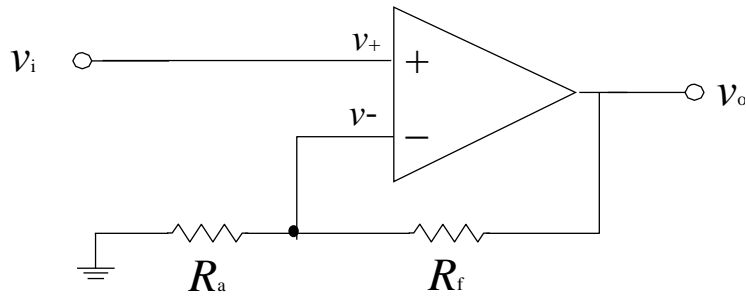(3) Setting  $V_+ = V_-$  yields


$$\frac{V_i}{R_a} + \frac{V_i - V_o}{R_f} = 0 \quad \text{or} \quad \frac{V_o}{V_i} = 1 + \frac{R_f}{R_a}$$






Noninverting amplifier
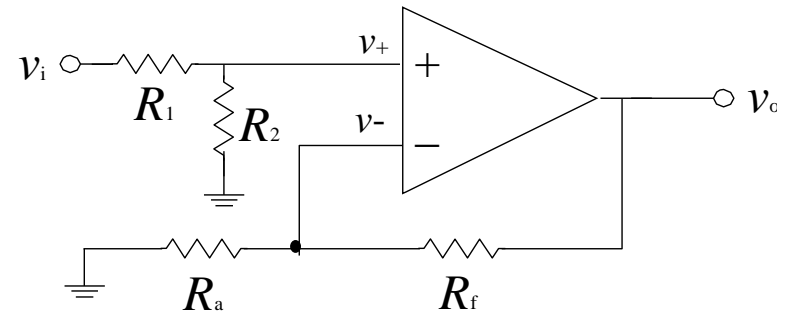
$$v_o = \left(1 + \frac{R_f}{R_a}\right)v_i$$




Noninverting input with voltage divider
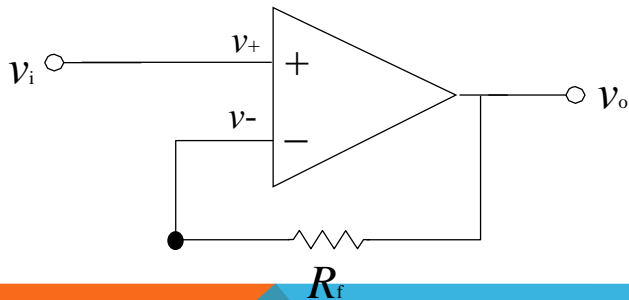
$$v_o = \left(1 + \frac{R_f}{R_a}\right)\left(\frac{R_2}{R_1 + R_2}\right)v_i$$



Voltage follower

$$v_o = v_i$$

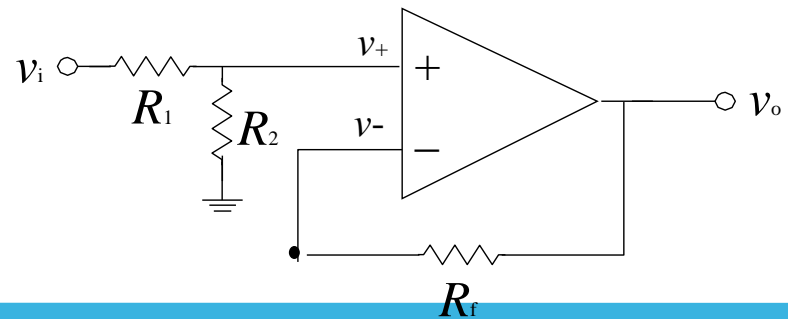

Less than unity gain

$$v_o = \frac{R_2}{R_1 + R_2}v_i$$