

LECTURE 1 OP-AMP

Introduction of Operation Amplifier (Op-Amp)

Analysis of ideal Op-Amp applications

Comparison of ideal and non-ideal Op-Amp

Non-ideal Op-Amp consideration



OPERATIONAL AMPLIFIER (OP-AMP)

Very high differential gain


High input impedance

Low output impedance

**Provide voltage changes
(amplitude and polarity),**

**Used in oscillator, filter
and instrumentation**

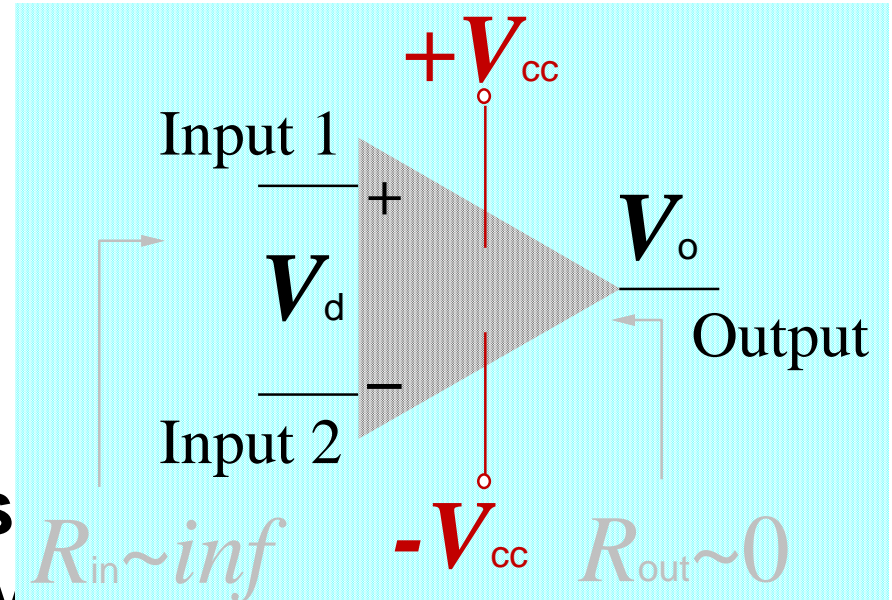
**Accumulate a very high
gain by multiple stages**




$$V_o = G_d V_d$$

G_d : differential gain normally
very large, say 10^5

IC PRODUCT

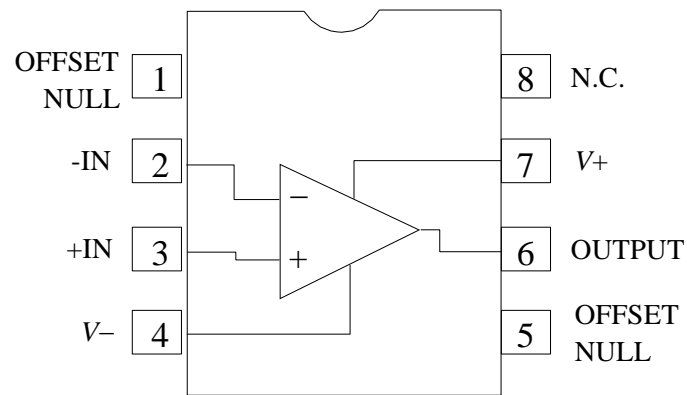


DIP-741

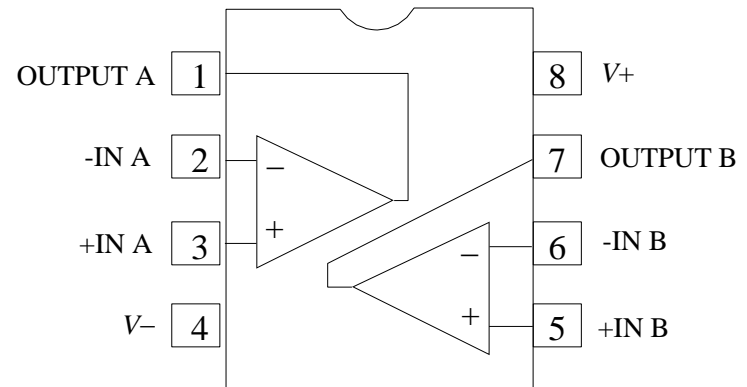


Dual op-amp 1458 device

SINGLE-ENDED INPUT

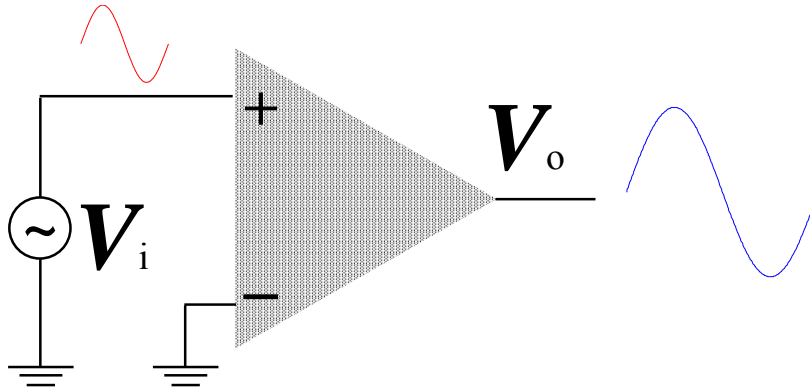


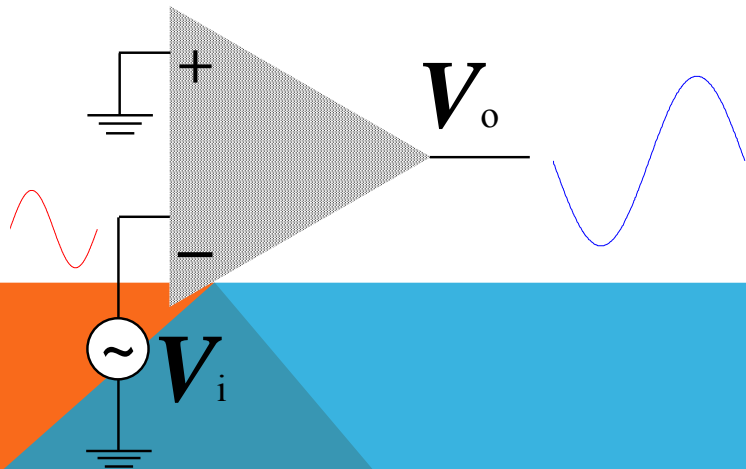- + terminal : Source
- - terminal : Ground
- 0° phase change




- + terminal : Ground
- - terminal : Source
- 180° phase change


DOUBLE-ENDED INPUT

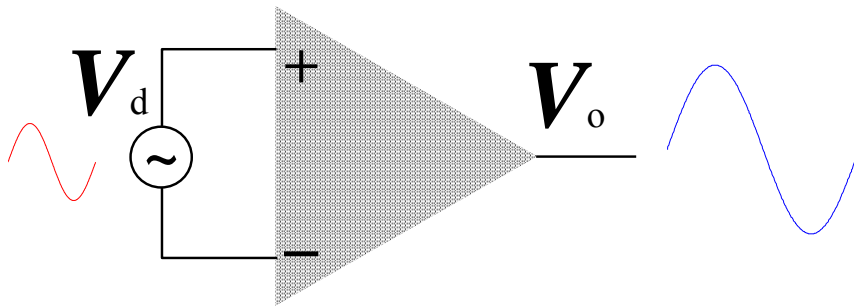

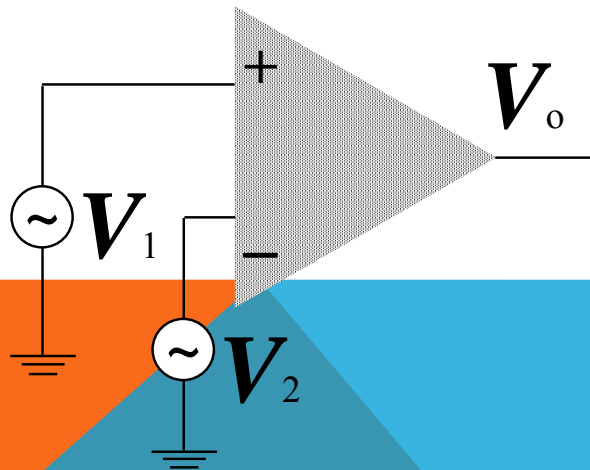- Differential input
- $V_d = V_+ - V_-$
- 0° phase shift change between V_o and V_d



Qu: What V_o should be if,

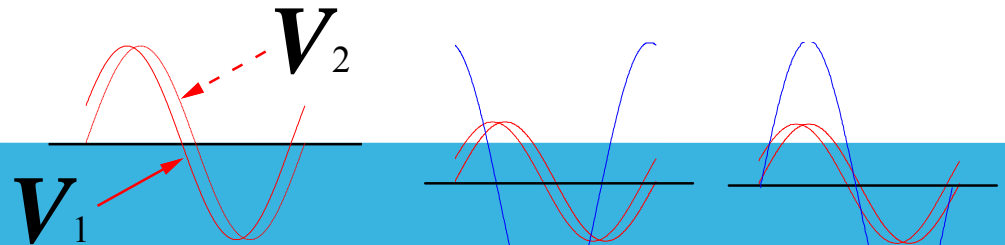


Ans: (A or B) ?

(A)

(B)


DISTORTION

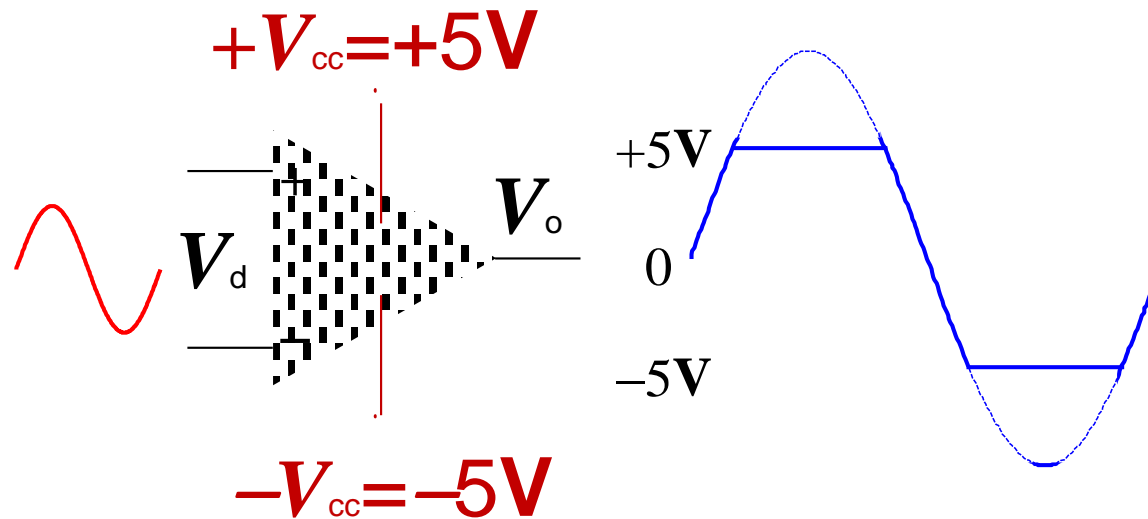

The output voltage never exceeds the DC voltage supply of the Op-Amp

COMMON-MODE OPERATION

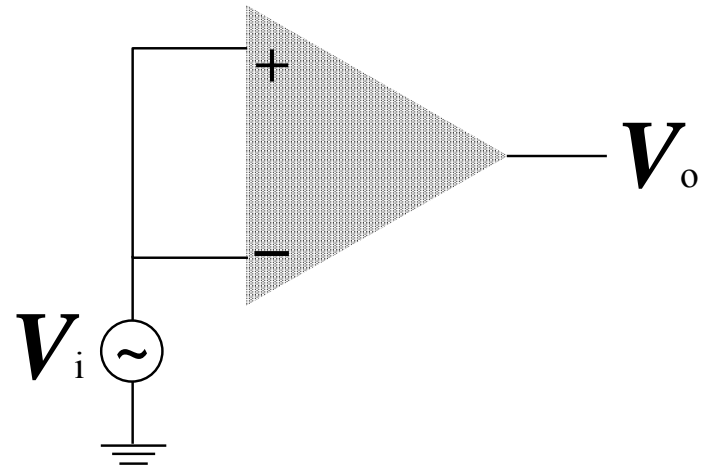- Same voltage source is applied at both terminals
- Ideally, two input are equally amplified
- Output voltage is ideally zero due to differential voltage is zero
- Practically, a small output signal can still be measured



Note for differential circuits:
Opposite inputs : highly amplified
Common inputs : slightly amplified
 \Rightarrow Common-Mode Rejection

COMMON-MODE REJECTION RATIO (CMRR)

Differential voltage input :

$$V_d = V_+ - V_-$$

Common voltage input :


$$V_c = \frac{1}{2}(V_+ + V_-)$$

Output voltage :

$$V_o = G_d V_d + G_c V_c$$

G_d : Differential gain

G_c : Common mode gain

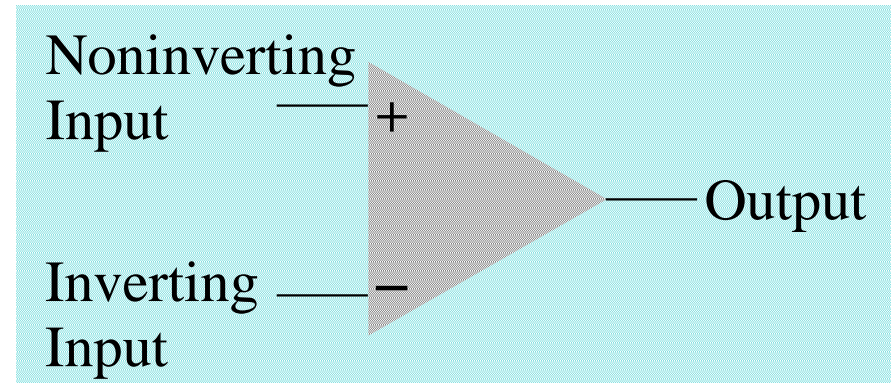

Common-mode rejection ratio:



$$\text{CMRR} = \frac{G_d}{G_c} = 20 \log_{10} \frac{G_d}{G_c} (\text{dB})$$

Note:

When $G_d \gg G_c$ or $\text{CMRR} \rightarrow \infty$
 $\Rightarrow V_o = G_d V_d$

CMRR EXAMPLE

What is the CMRR?

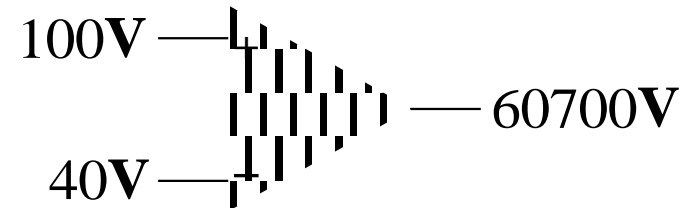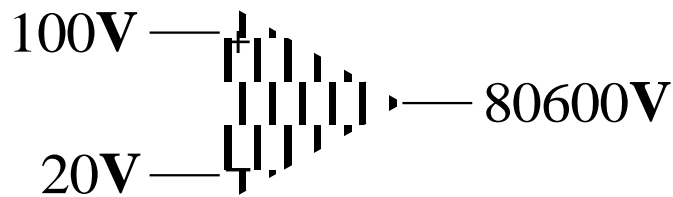

Solution :

$$\left. \begin{aligned} V_{d1} &= 100 - 20 = 80\text{V} \\ V_{c1} &= \frac{100 + 20}{2} = 60\text{V} \end{aligned} \right\} (1)$$

$$\left. \begin{aligned} V_{d2} &= 100 - 40 = 60\text{V} \\ V_{c2} &= \frac{100 + 40}{2} = 70\text{V} \end{aligned} \right\} (2)$$

From (1) $V_o = 80G_d + 60G_c = 80600\text{V}$

From (2) $V_o = 60G_d + 70G_c = 60700\text{V}$


$G_d = 1000$ and $G_c = 10 \Rightarrow \text{CMRR} = 20\log(1000/10) = 40\text{dB}$

NB: This method is Not work! Why?

OP-AMP PROPERTIES

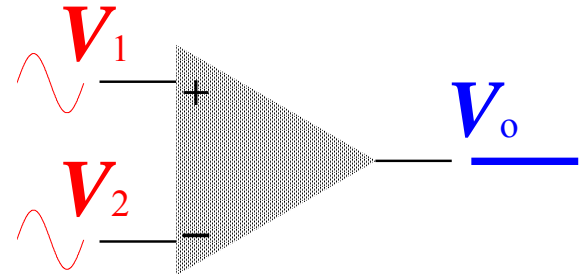
(1) Infinite Open Loop gain

- The gain without feedback
- Equal to differential gain
- Zero common-mode gain
- Practically, $G_d = 20,000$ to $200,000$



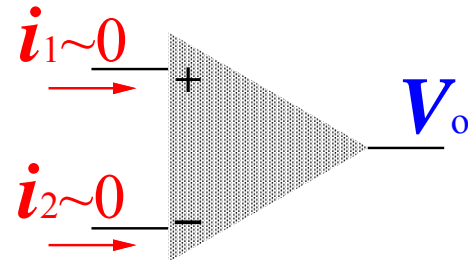
(2) Infinite Input impedance

- Input current $i_i \sim 0A$
- T- Ω in high-grade op-amp
- m-A input current in low-grade op-amp



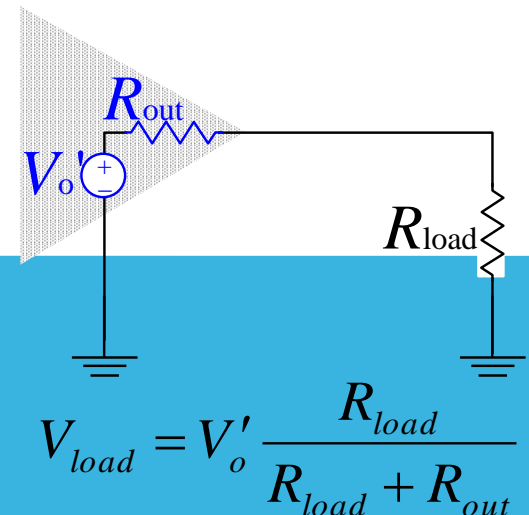
(3) Zero Output Impedance

- act as perfect internal voltage source
- No internal resistance
- Output impedance in series with load
- Reducing output voltage to the load
- Practically, $R_{out} \sim 20-100 \Omega$



FREQUENCY-GAIN RELATION

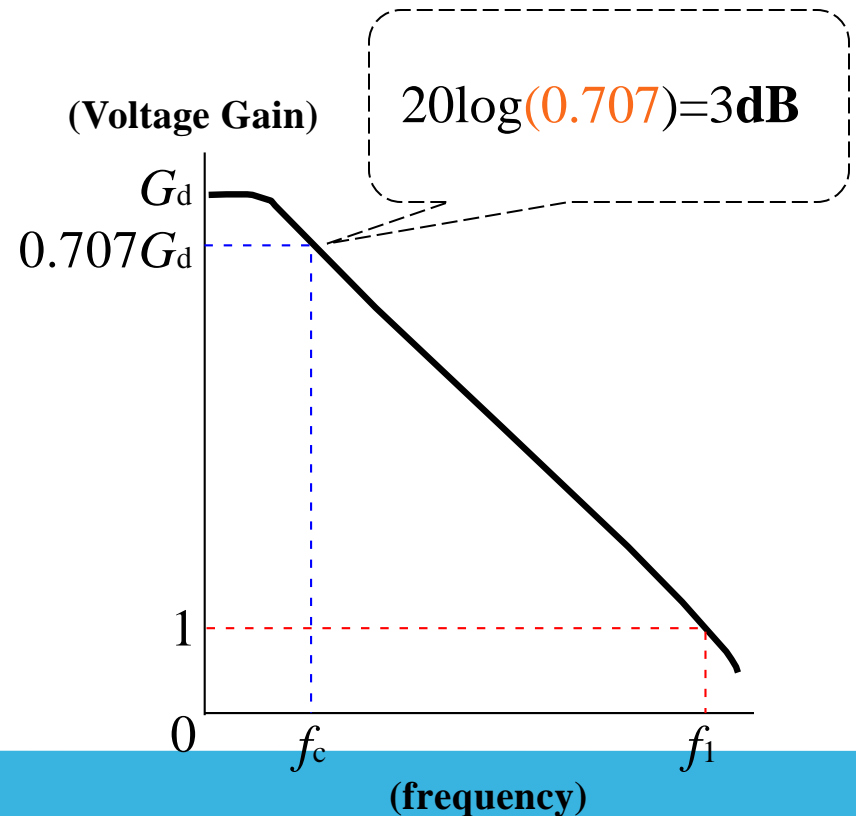- Ideally, signals are amplified from DC to the highest AC frequency
- Practically, bandwidth is limited
- 741 family op-amp have an limit bandwidth of few KHz.
- Unity Gain frequency f_1 : the gain at unity
- Cutoff frequency f_c : the gain drop by 3dB from dc gain G_d



$$\text{GB Product : } f_1 = G_d f_c$$

GB PRODUCT

Example: Determine the cutoff frequency of an op-amp having a unit gain frequency $f_1 = 10 \text{ MHz}$ and voltage differential gain $G_d = 20 \text{ V/mV}$

Sol:

Since $f_1 = 10 \text{ MHz}$


By using GB production equation

$$f_1 = G_d f_c$$

$$f_c = f_1 / G_d = 10 \text{ MHz} / 20 \text{ V/mV}$$



$$= 10 \times 10^6 / 20 \times 10^3$$

$$= 500 \text{ Hz}$$

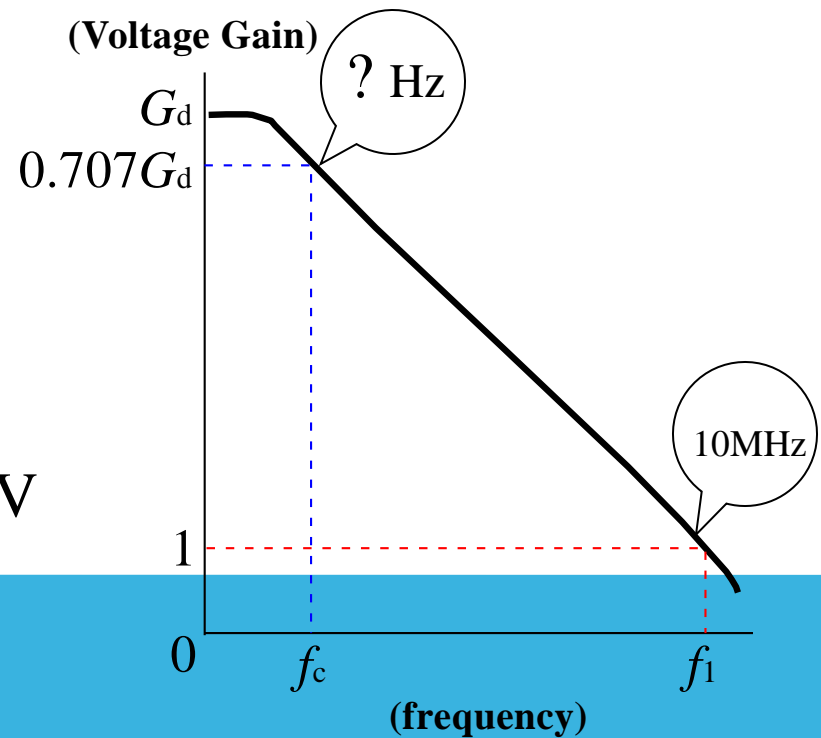

IDEAL VS PRACTICAL OP-AMP

	Ideal	Practical
Open Loop gain A	∞	10^5
Bandwidth BW	∞	10-100Hz
Input Impedance Z_{in}	∞	$>1\text{M}\Omega$
Output Impedance Z_{out}	$0\ \Omega$	10-100 Ω
Output Voltage V_{out}	Depends only on $V_d = (V_+ - V_-)$ Differential mode signal	Depends slightly on average input $V_c = (V_+ + V_-)/2$ Common-Mode signal
CMRR	∞	10-100dB

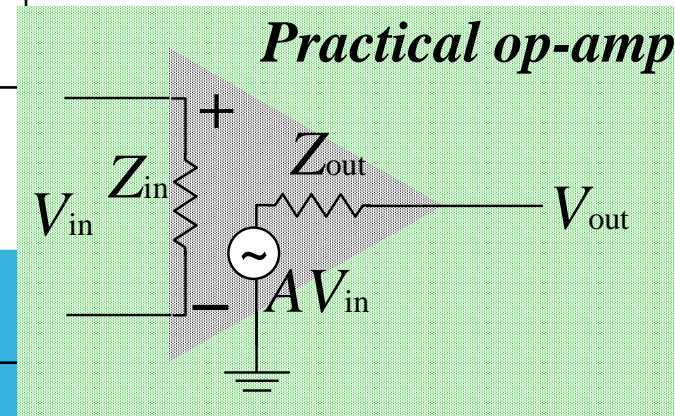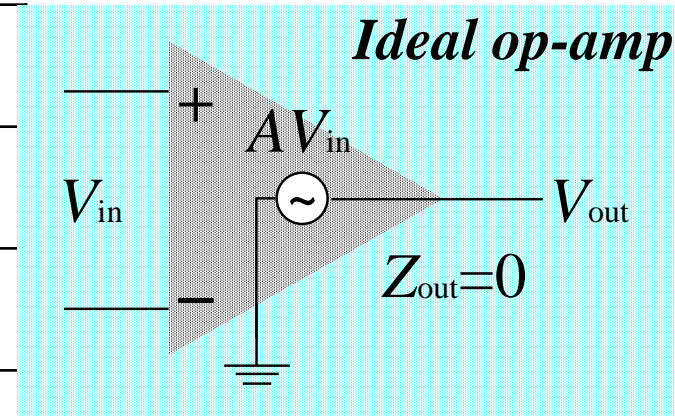

IDEAL OP-AMP APPLICATIONS

Analysis Method :

Two ideal Op-Amp Properties:


- (1) The voltage between V_+ and V_- is zero $V_+ = V_-$**
- (2) The current into both V_+ and V_- terminals is zero**

For ideal Op-Amp circuit:

- (1) Write the kirchhoff node equation at the noninverting terminal V_+**
- (2) Write the kirchhoff node equation at the inverting terminal V_-**
- (3) Set $V_+ = V_-$ and solve for the desired closed-loop gain**

Noninverting Amplifier

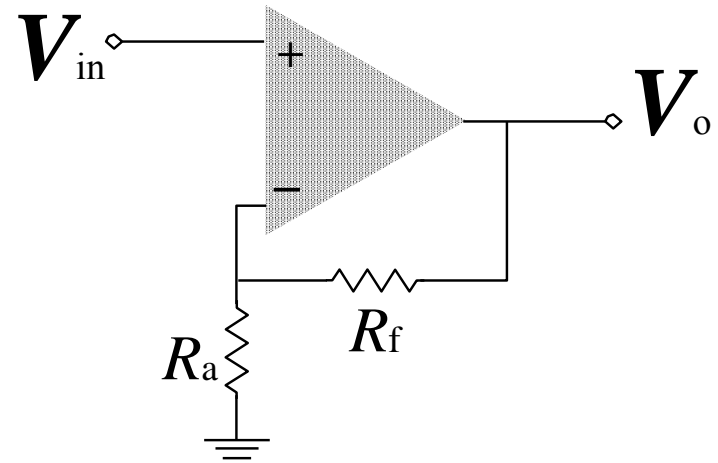
(1) Kirchhoff node equation at V_+ yields, $V_+ = V_i$



(2) Kirchhoff node equation at V_- yields, $\frac{V_- - 0}{R_a} + \frac{V_- - V_o}{R_f} = 0$

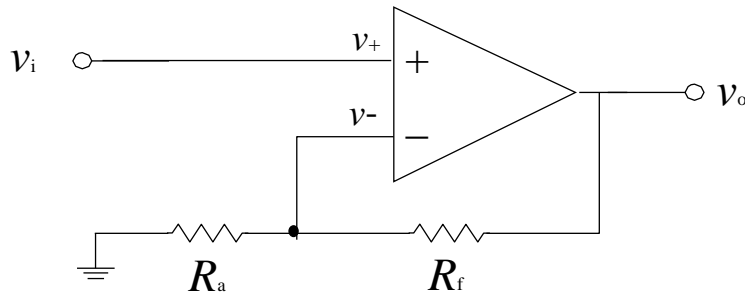
(3) Setting $V_+ = V_-$ yields

$$\frac{V_i}{R_a} + \frac{V_i - V_o}{R_f} = 0 \quad \text{or} \quad \frac{V_o}{V_i} = 1 + \frac{R_f}{R_a}$$




Noninverting amplifier
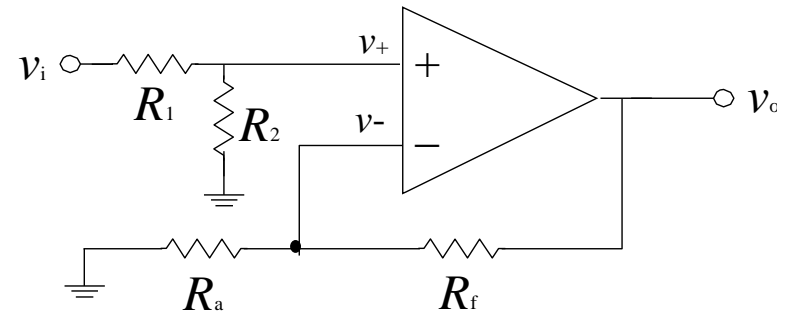
$$v_o = \left(1 + \frac{R_f}{R_a}\right) v_i$$




Noninverting input with voltage divider
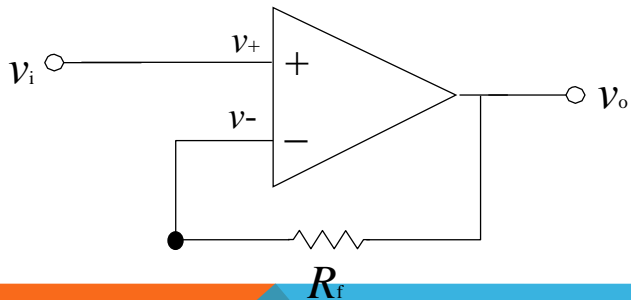
$$v_o = \left(1 + \frac{R_f}{R_a}\right) \left(\frac{R_2}{R_1 + R_2}\right) v_i$$



Voltage follower

$$v_o = v_i$$

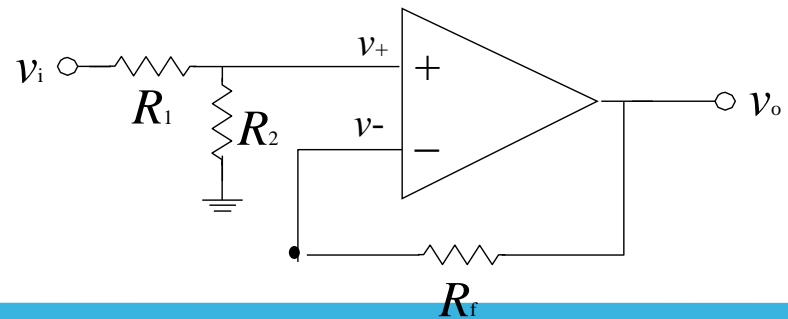


Less than unity gain

$$v_o = \frac{R_2}{R_1 + R_2} v_i$$

INVERTING AMPLIFIER

(1) Kirchhoff node equation at V_+ yields, $V_+ = 0$

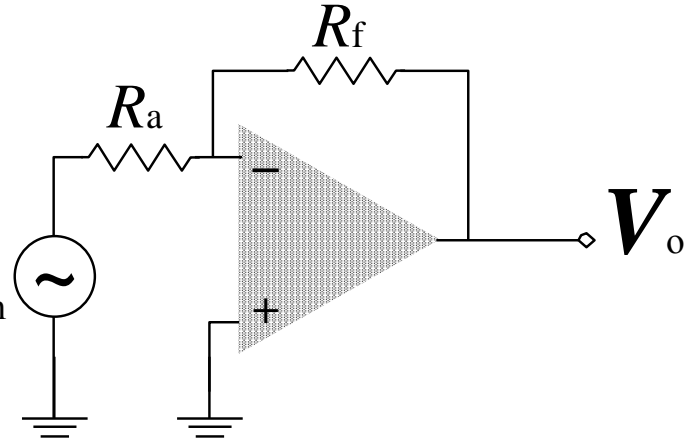(2) Kirchhoff node equation at V_- yields, $\frac{V_{in} - V_-}{R_a} + \frac{V_o - V_-}{R_f} = 0$



(3) Setting $V_+ = V_-$ yields

$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_a}$$


Notice: The **closed-loop gain** V_o/V_{in} is dependent upon the ratio of two resistors, and is independent of the open-loop gain. This is caused by the use of feedback output voltage to subtract from the input voltage.

MULTIPLE INPUTS

(1) Kirchhoff node equation at V_+ yields, $V_+ = 0$

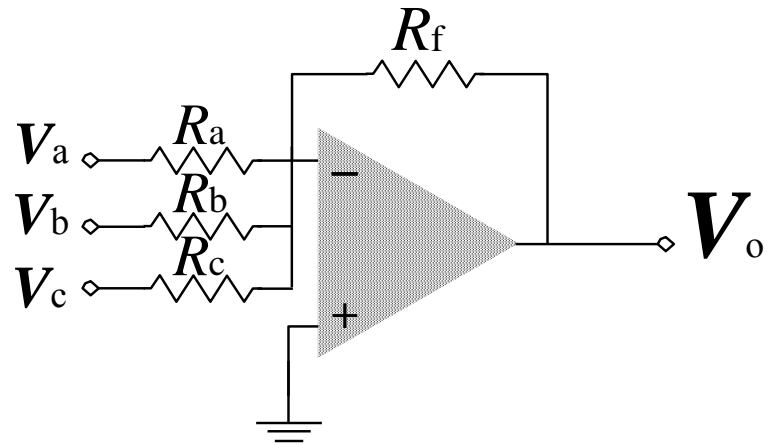(2) Kirchhoff node equation at V_- yields,

$$\frac{V_- - V_o}{R_f} + \frac{V_- - V_a}{R_a} + \frac{V_- - V_b}{R_b} + \frac{V_- - V_c}{R_c} = 0$$



(3) Setting $V_+ = V_-$ yields

$$V_o = -R_f \left(\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right) = -R_f \sum_{j=a}^c \frac{V_j}{R_j}$$

INVERTING INTEGRATOR

Now replace resistors R_a and R_f by complex components Z_a and Z_f , respectively, therefore

Supposing
$$V_o = \frac{-Z_f}{Z_a} V_{in}$$

(i) The feedback component is a capacitor C ,
i.e.,

$$Z_f = \frac{1}{j\omega C}$$

(ii) The input component is a resistor R , $Z_a = R$

Therefore, the closed-loop gain (V_o/V_{in}) become:



$$v_o(t) = \frac{-1}{RC} \int v_i(t) dt$$

where

$$v_i(t) = V_i e^{j\omega t}$$

What happens if $Z_a = 1/j\omega C$ whereas, $Z_f = R$?

Inverting differentiator

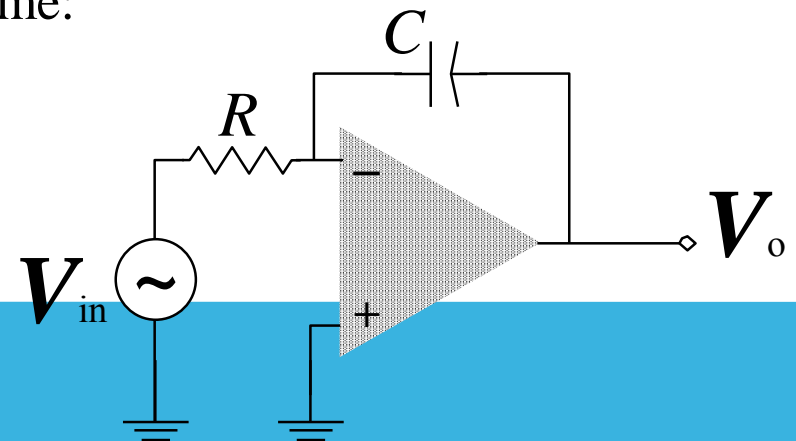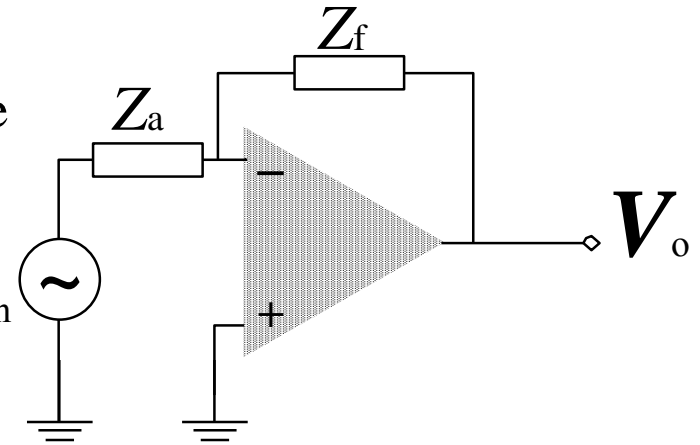

OP-AMP INTEGRATOR

Example:

- (a) Determine the rate of change of the output voltage.

- (b) Draw the output waveform.

Solution:



- (a) Rate of change of the output voltage

$$\frac{\Delta V_o}{\Delta t} = -\frac{V_i}{RC} = \frac{5 \text{ V}}{(10 \text{ k}\Omega)(0.01 \mu\text{F})}$$


$$= -50 \text{ mV}/\mu\text{s}$$

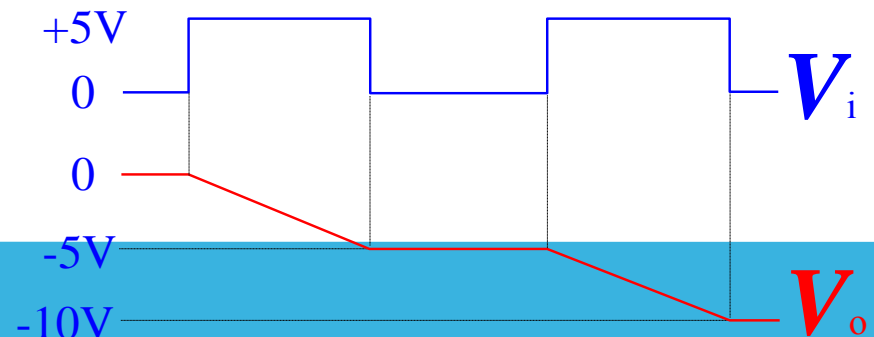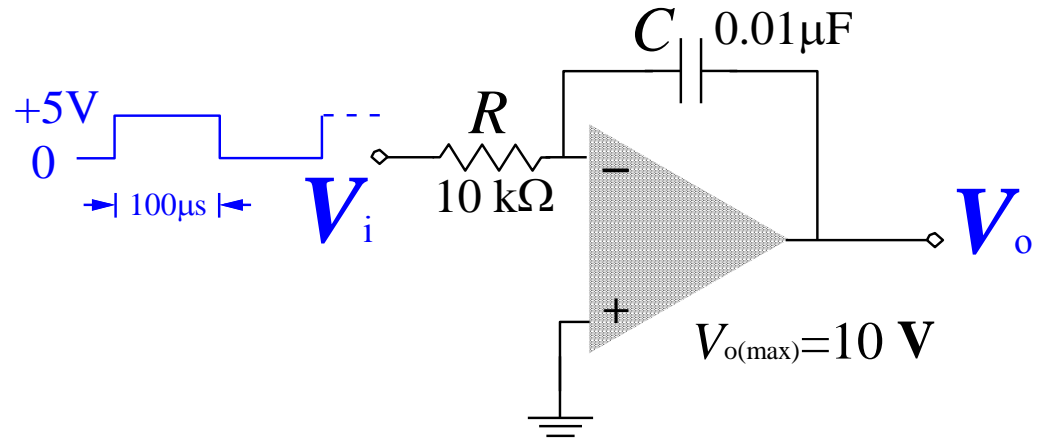- (b) In $100 \mu\text{s}$, the voltage decrease

$$\Delta V_o = (-50 \text{ mV}/\mu\text{s})(100 \mu\text{s}) = -5 \text{ V}$$





OP-AMP DIFFERENTIATOR

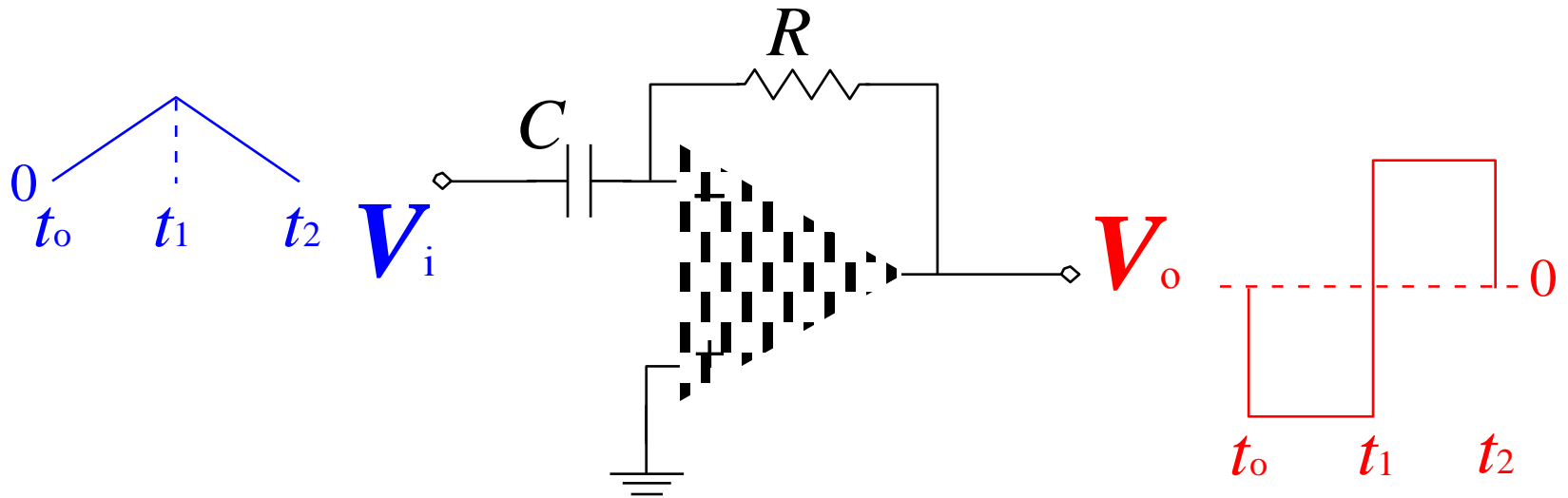


$$v_o = -\left(\frac{dV_i}{dt}\right)RC$$

NON-IDEAL CASE (INVERTING AMPLIFIER)

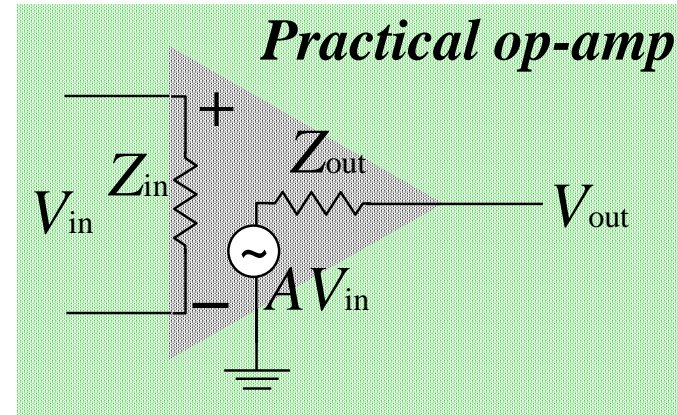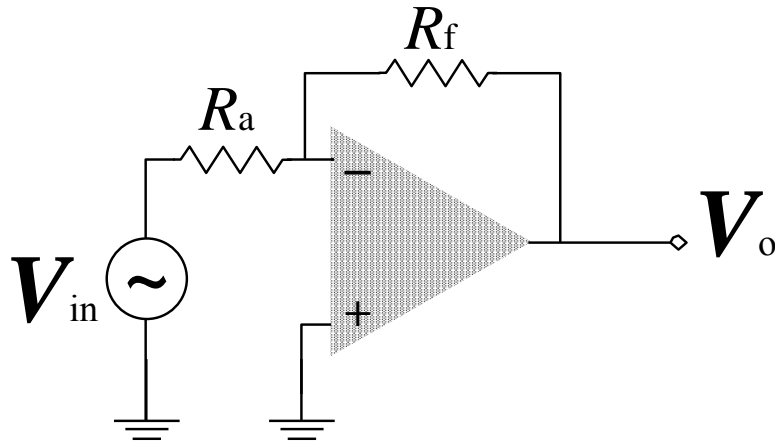

⇓ Equivalent Circuit

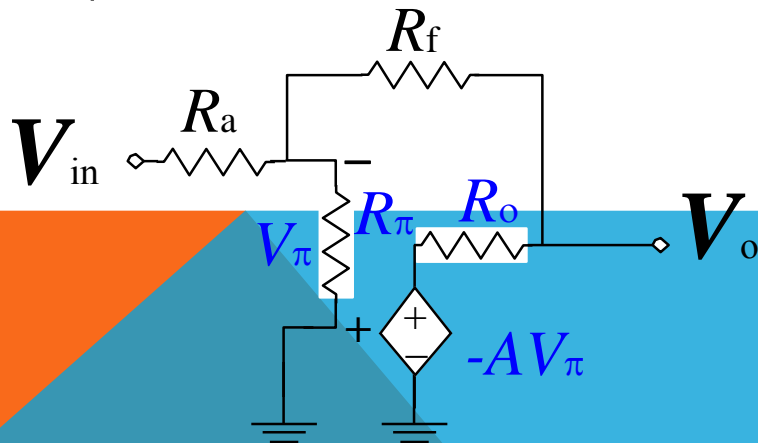

3 categories are considering

- ☐ Close-Loop Voltage Gain
- ☐ Input impedance
- ☐ Output impedance

CLOSE-LOOP GAIN

Applied KCL at V₋ terminal,


$$\frac{V_{in} - V_{\pi}}{R_a} + \frac{-V_{\pi}}{R_{\pi}} + \frac{V_o - V_{\pi}}{R_f} = 0$$

By using the open loop gain,

$$V_o = -AV_{\pi}$$

$$\Rightarrow \frac{V_{in}}{R_a} + \frac{V_o}{AR_a} + \frac{V_o}{AR_{\pi}} + \frac{V_o}{R_f} + \frac{V_o}{AR_f} = 0$$
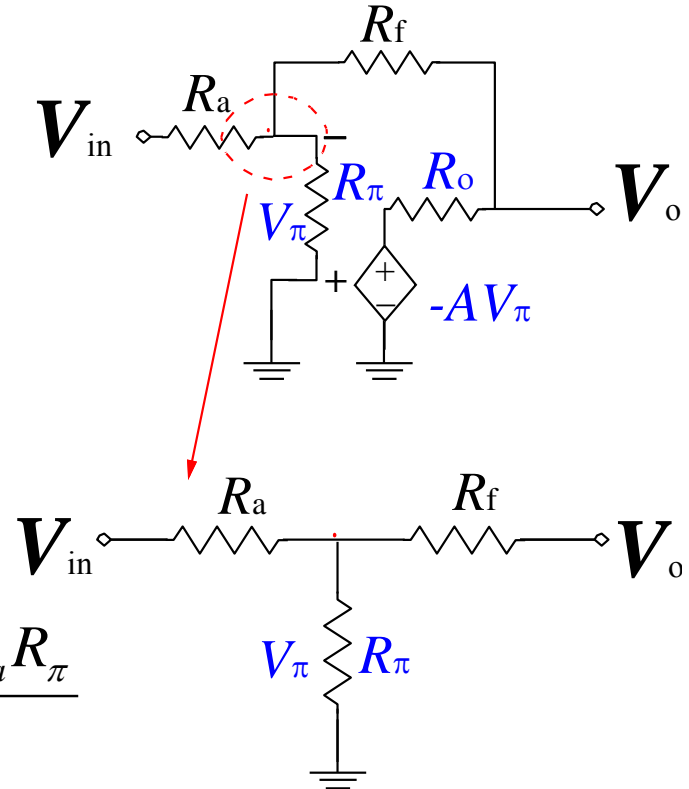
$$\Rightarrow \frac{V_{in}}{R_a} = -V_o \frac{R_{\pi}R_f + R_aR_f + R_aR_{\pi} + AR_aR_{\pi}}{AR_aR_{\pi}R_f}$$



The Close-Loop Gain, A_v

$$A_v = \frac{V_o}{V_{in}} = \frac{-AR_{\pi}R_f}{R_{\pi}R_f + R_aR_f + R_aR_{\pi} + AR_aR_{\pi}}$$

CLOSE-LOOP GAIN

When the open loop gain is very large, the above equation become,

$$A_v \sim \frac{-R_f}{R_a}$$

Note : The close-loop gain now reduce to the same form as an ideal case

INPUT IMPEDANCE

Input Impedance can be regarded as,

$$R_{in} = R_a + R_\pi // R'$$


where R' is the equivalent impedance of the red box circuit, that is

$$R' = \frac{V_\pi}{i_f}$$


However, with the below circuit,

$$V_\pi - (-AV_\pi) = i_f (R_f + R_o)$$
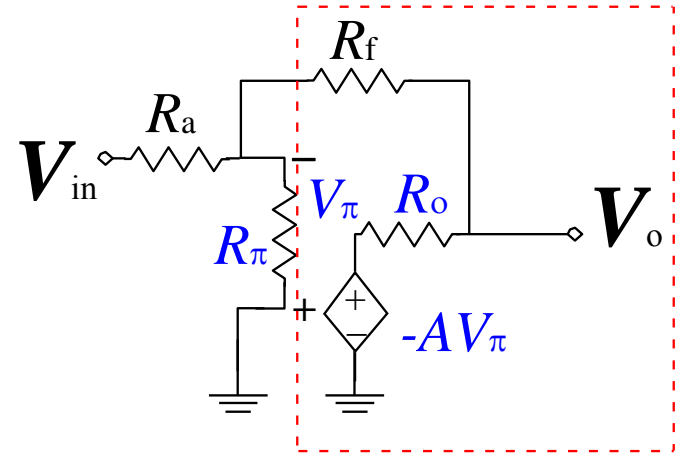
$$\Rightarrow R' = \frac{V_\pi}{i_f} = \frac{R_f + R_o}{1 + A}$$



R'

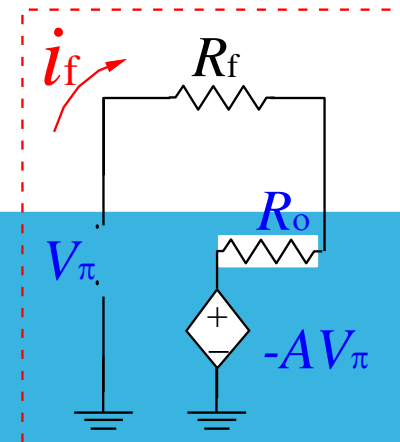

INPUT IMPEDANCE

Finally, we find the input impedance as,

$$R_{in} = R_a + \left[\frac{1}{R_\pi} + \frac{1+A}{R_f + R_o} \right]^{-1} \Rightarrow R_{in} = R_a + \frac{R_\pi (R_f + R_o)}{R_f + R_o + (1+A)R_\pi}$$

Since, $R_f + R_o \ll (1+A)R_\pi$, R_{in} become,

$$R_{in} \sim R_a + \frac{(R_f + R_o)}{(1+A)}$$

Again with $R_f + R_o \ll (1+A)$

$$R_{in} \sim R_a$$

Note: The op-amp can provide an impedance isolated from input to output

OUTPUT IMPEDANCE

Only source-free output impedance would be considered,
i.e. V_i is assumed to be 0

Firstly, with figure (a),

$$V_\pi = \frac{R_a \parallel R_\pi}{R_f + R_a \parallel R_\pi} V_o \Rightarrow V_\pi = \frac{R_a R_\pi}{R_a R_f + R_a R_\pi + R_f R_\pi} V_o$$

By using KCL, $i_o = i_1 + i_2$

$$i_o = \frac{V_o}{R_f + R_a \parallel R_\pi} + \frac{V_o - (-AV_\pi)}{R_o}$$

By substitute the equation from Fig. (a),

The output impedance, R_{out} is

$$\frac{V_o}{i_o} = \frac{R_o (R_a R_f + R_a R_\pi + R_f R_\pi)}{(1 + R_o)(R_a R_f + R_a R_\pi + R_f R_\pi) + (1 + A)R_a R_\pi}$$

$\therefore R_\pi$ and A comparably large,

$$R_{out} \sim \frac{R_o (R_a + R_f)}{AR_a}$$

