

Feedback and its Applications


CONTENTS

- ✖ Introduction
- ✖ Types of feedback
- ✖ Negative feedback applications
- ✖ Positive feedback applications
- ✖ Criterion for oscillations
- ✖ Classification of oscillator
- ✖ Wein bridge oscillator
- ✖ Crystal oscillator
- ✖ Comparison of amplifier and oscillator

crystal oscillator

- ✗ A crystal oscillator is an electronic circuit that uses the mechanical resonance of a vibrating crystal of piezoelectric material (ex. –quartz, rochellesalt) to create an electrical signal with a very precise frequency.
- ✗ This frequency is commonly used to keep track of time (as in quartz wristwatches), to provide a stable clock signal for digital integrated circuits, and to stabilize frequencies for radio transmitters.

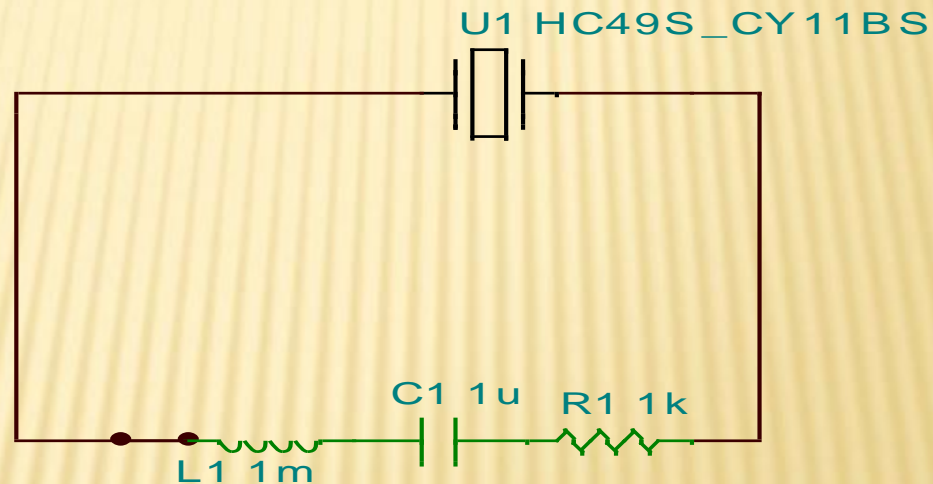Basic circuit diagram for Crystal Oscillator



Relaxation Oscillator

- ✗ A **Relaxation Oscillator** is an oscillator in which a capacitor is charged gradually and then discharged rapidly. It's usually implemented with a resistor, a capacitor, and some sort of "threshold" device such as a neon lamp, diac, uni junction transistor, or Gunn diode .

MERITS OF OSCILLATOR

- ✖ Portable and cheap in cost.
- ✖ An oscillator is a non-rotating device. Consequently, there is no wear & tear & hence longer life.
- ✖ Frequency of oscillation may be conveniently varied.
- ✖ Frequency once set remain constant for a considerable period of time.
- ✖ It operates at a very high efficiency since there is no wastage of energy due to friction.