

Feedback and its Applications

LECTURE 6 OSCILLATOR

- ✖ Introduction of Oscillator
- ✖ Linear Oscillator
 - + Wien Bridge Oscillator
 - + RC Phase-Shift Oscillator
 - + LC Oscillator
- ✖ Stability


APPLICATION OF OSCILLATORS

- ✖ Oscillators are used to generate signals, e.g.
 - + Used as a local oscillator to transform the RF signals to IF signals in a receiver;
 - + Used to generate RF carrier in a transmitter
 - + Used to generate clocks in digital systems;
 - + Used as sweep circuits in TV sets and CRO.

LINEAR OSCILLATORS

1. Wien Bridge Oscillators
2. RC Phase-Shift Oscillators
3. LC Oscillators
4. Stability

INTEGRANT OF LINEAR OSCILLATORS

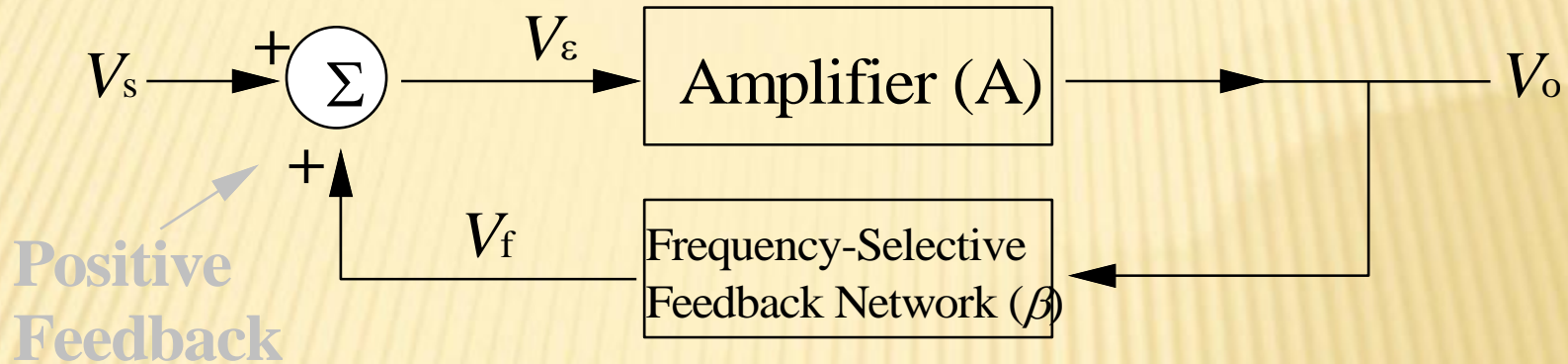


For sinusoidal input is connected

“**Linear**” because the output is approximately sinusoidal

A linear oscillator contains:

- a frequency selection feedback network
- an amplifier to maintain the loop gain at **unity**

BASIC LINEAR OSCILLATOR

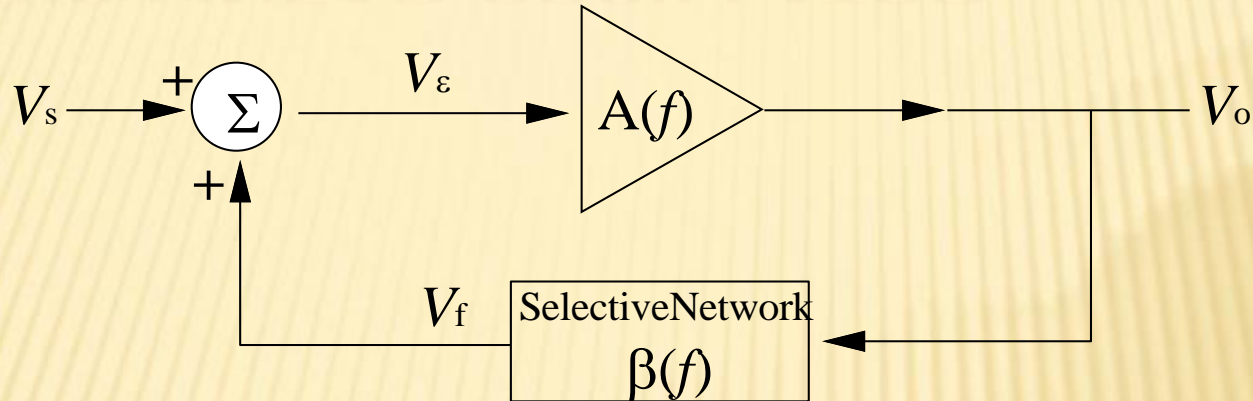

$$V_o = AV_\varepsilon = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

If $V_s = 0$, the only way that V_o can be nonzero is that **loop gain $A\beta=1$** which implies that

$$|A\beta| = 1 \quad (\text{Barkhausen Criterion})$$

$$\angle A\beta = 0$$

WIEN BRIDGE OSCILLATOR

Let $X_{C1} = \frac{1}{\omega C_1}$ and $X_{C2} = \frac{1}{\omega C_2}$

$$Z_1 = R_1 - jX_{C1}$$


$$Z_2 = \left[\frac{1}{R_2} + \frac{1}{-jX_{C2}} \right]^{-1} = \frac{-jR_2 X_{C2}}{R_2 - jX_{C2}}$$

Therefore, the feedback factor,

$$\beta = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{(-jR_2 X_{C2} / R_2 - jX_{C2})}{(R_1 - jX_{C1}) + (-jR_2 X_{C2} / R_2 - jX_{C2})}$$

$$\beta = \frac{-jR_2 X_{C2}}{(R_1 - jX_{C1})(R_2 - jX_{C2}) - jR_2 X_{C2}}$$

Frequency Selection Network

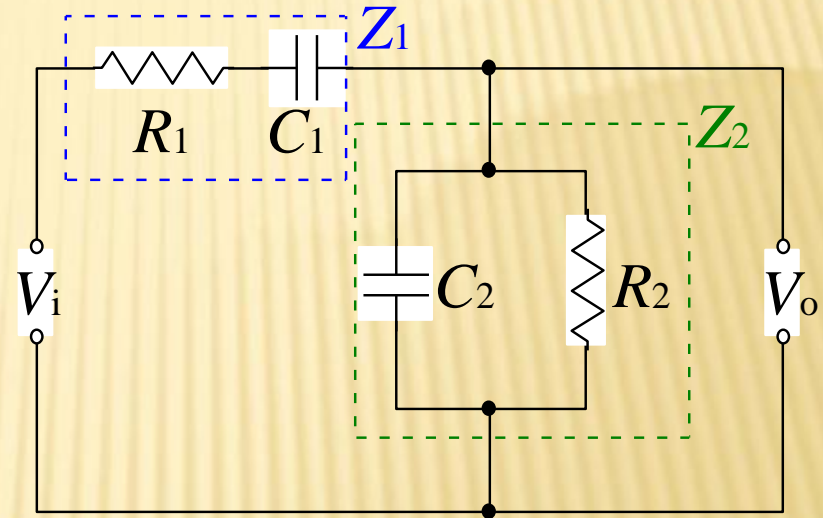

β can be rewritten as:

$$\beta = \frac{R_2 X_{C2}}{R_1 X_{C2} + R_2 X_{C1} + R_2 X_{C2} + j(R_1 R_2 - X_{C1} X_{C2})}$$

For **Barkhausen Criterion**, imaginary part = 0, i.e.,

$$R_1 R_2 - X_{C1} X_{C2} = 0$$

$$\text{or } R_1 R_2 = \frac{1}{\omega C_1} \frac{1}{\omega C_2}$$

$$\Rightarrow \omega = 1 / \sqrt{R_1 R_2 C_1 C_2}$$

Supposing,

$$R_1 = R_2 = R \text{ and } X_{C1} = X_{C2} = X_C,$$

$$\beta = \frac{R X_C}{3 R X_C + j(R^2 - X_C^2)}$$

