UNIT-1 (Lecture-3)

Realization of Digital Systems:
Direct form realization of IIR systems

Basic IIR Digital Filter Structures

- The causal IIR digital filters we are concerned with in this course are characterized by a real rational transfer function of z^{-1} or, equivalently by a constant coefficient difference equation
- From the difference equation, it can be seen that the realization of the causal IIR digital filters requires some form of feedback

Basic IIR Digital Filter Structures

• An *N*-th order IIR digital transfer function is characterized by 2*N*+1 unique coefficients, and in general, requires 2*N*+1 multipliers and 2*N* two-input adders for implementation

Direct form IIR filters:

Filter structures in which the multiplier coefficients are precisely the coefficients of the transfer function

 Consider for simplicity a 3rd-order IIR filter with a transfer function

$$H(z) = \frac{P(z)}{D(z)} = \frac{p_0 + p_1 z^{-1} + p_2 z^{-2} + p_3 z^{-3}}{1 + d_1 z^{-1} + d_2 z^{-2} + d_3 z^{-3}}$$

• We can implement H(z) as a cascade of two filter sections as shown on the next slide

$$X(z) \longrightarrow H_1(z) \xrightarrow{W(z)} H_2(z) \longrightarrow Y(z)$$


where

$$H_1(z) = \frac{W(z)}{X(z)} = P(z) = p_0 + p_1 z^{-1} + p_2 z^{-2} + p_3 z^{-3}$$

$$H_2(z) = \frac{Y(z)}{W(z)} = \frac{1}{D(z)} = \frac{1}{1 + d_1 z^{-1} + d_2 z^{-2} + d_3 z^{-3}}$$

• The filter section $H_1(z)$ can be seen to be an FIR filter and can be realized as shown

below

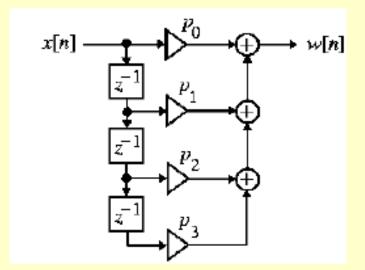


$$w[n] = p_0x[n] + p_1x[n-1] + p_2x[n-2] + p_3x[n-3]$$


• The time-domain representation of $H_2(z)$ is given by

$$y[n] = w[n] - d_1y[n-1] - d_2y[n-2] - d_3y[n-3]$$

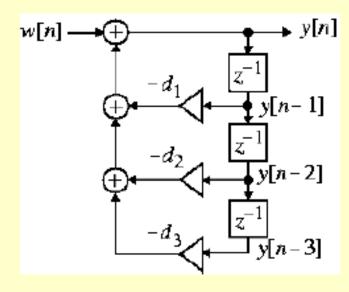
• The realization of $H_2(z)$ follows from the above equation and is shown in the figure



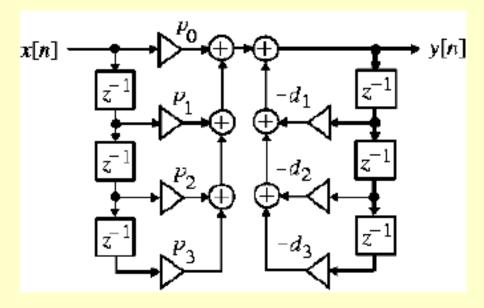
A cascade of the two structures realizing
 H₁(z) and H₂(z) leads to the realization
 of H(z) shown below and is known as the
 direct form I structure




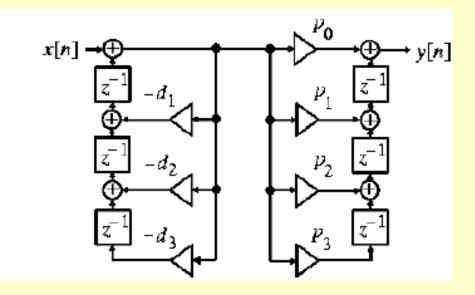- The direct form I structure is noncanonic as it employs 6 delays to realize a 3rd-order transfer function
- The transpose of the direct form I structure is shown in the figure and it is called the direct form I_t structure



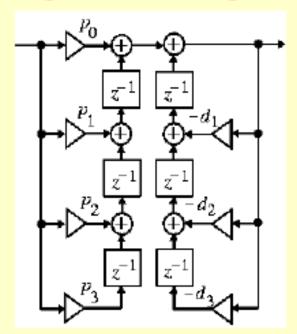
 Various other noncanonic direct form structures can be derived by simple block diagram manipulations as shown below



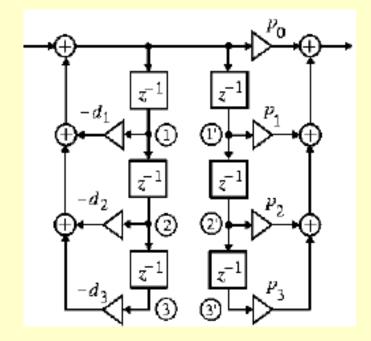



Observe in the direct form structure shown right, the signal variable at nodes

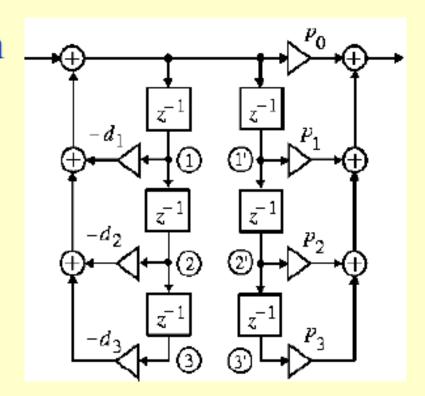and Tare
and hence the two top delays can be shared



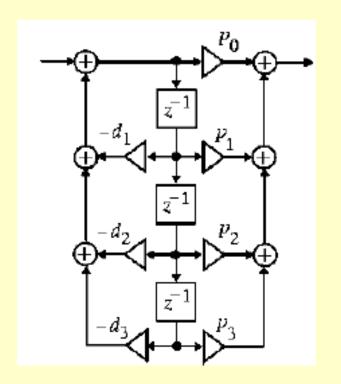- Likewise, the signal variables at nodes 2 and 2 are the same, permitting the sharing of the middle two delays
- Following the same argument, we can share the bottom two delays leading to the final canonic structure, which is called the **direct** form II structure
- The direct form II and the **direct form II**_t structure are shown on the next slide



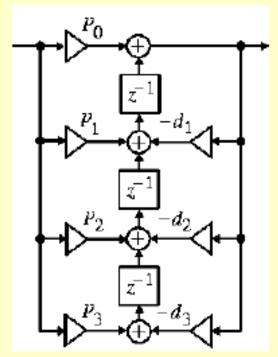

• Direct form realizations of an *N*-th order IIR transfer function should be evident