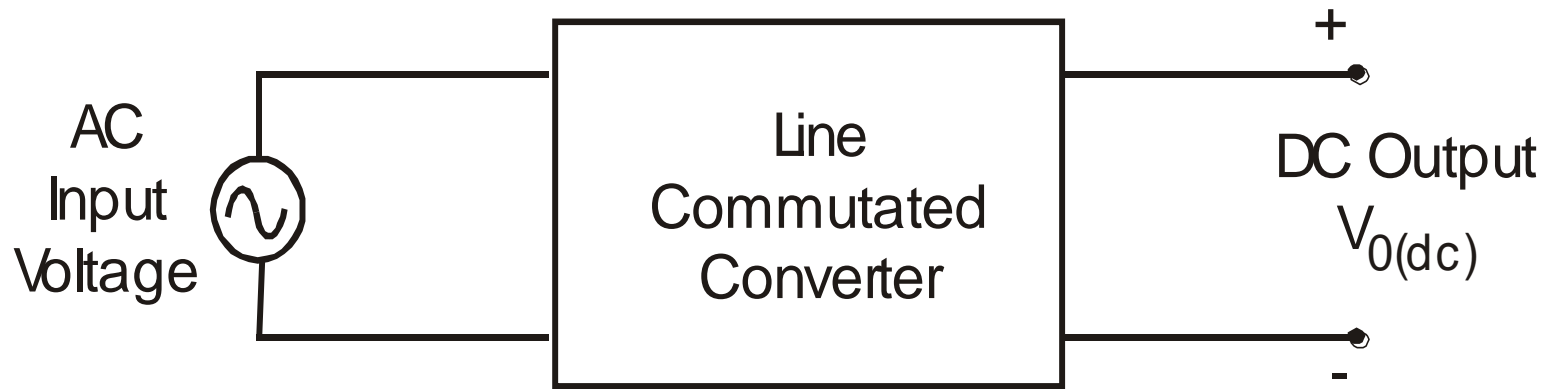


Controlled Rectifiers

(Line Commutated AC to DC converters)



- Type of input: Fixed voltage, fixed frequency ac power supply.
- Type of output: Variable dc output voltage
- Type of commutation: Natural / AC line commutation.

Different types of Line Commutated Converters

- AC to DC Converters (Phase controlled rectifiers)
- AC to AC converters (AC voltage controllers)
- AC to AC converters (Cyclo converters) at low output frequency.

Differences Between Diode Rectifiers & Phase Controlled Rectifiers

- The diode rectifiers are referred to as uncontrolled rectifiers .
- The diode rectifiers give a fixed dc output voltage .
- Each diode conducts for one half cycle.
- Diode conduction angle = 180^0 or π radians.
- We can not control the dc output voltage or the average dc load current in a diode rectifier circuit.

Single phase half wave diode rectifier gives an

Average dc output voltage $V_{O(dc)} = \frac{V_m}{\pi}$

Single phase full wave diode rectifier gives an

Average dc output voltage $V_{O(dc)} = \frac{2V_m}{\pi}$

Applications of Phase Controlled Rectifiers

- DC motor control in steel mills, paper and textile mills employing dc motor drives.
- AC fed traction system using dc traction motor.
- Electro-chemical and electro-metallurgical processes.
- Magnet power supplies.
- Portable hand tool drives.

Classification of Phase Controlled Rectifiers

- Single Phase Controlled Rectifiers.
- Three Phase Controlled Rectifiers.


Different types of Single Phase Controlled Rectifiers.


- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
 - Using a center tapped transformer.
 - Full wave bridge circuit.
 - Semi converter.
 - Full converter.

Different Types of Three Phase Controlled Rectifiers

- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
 - Semi converter (half controlled bridge converter).
 - Full converter (fully controlled bridge converter).

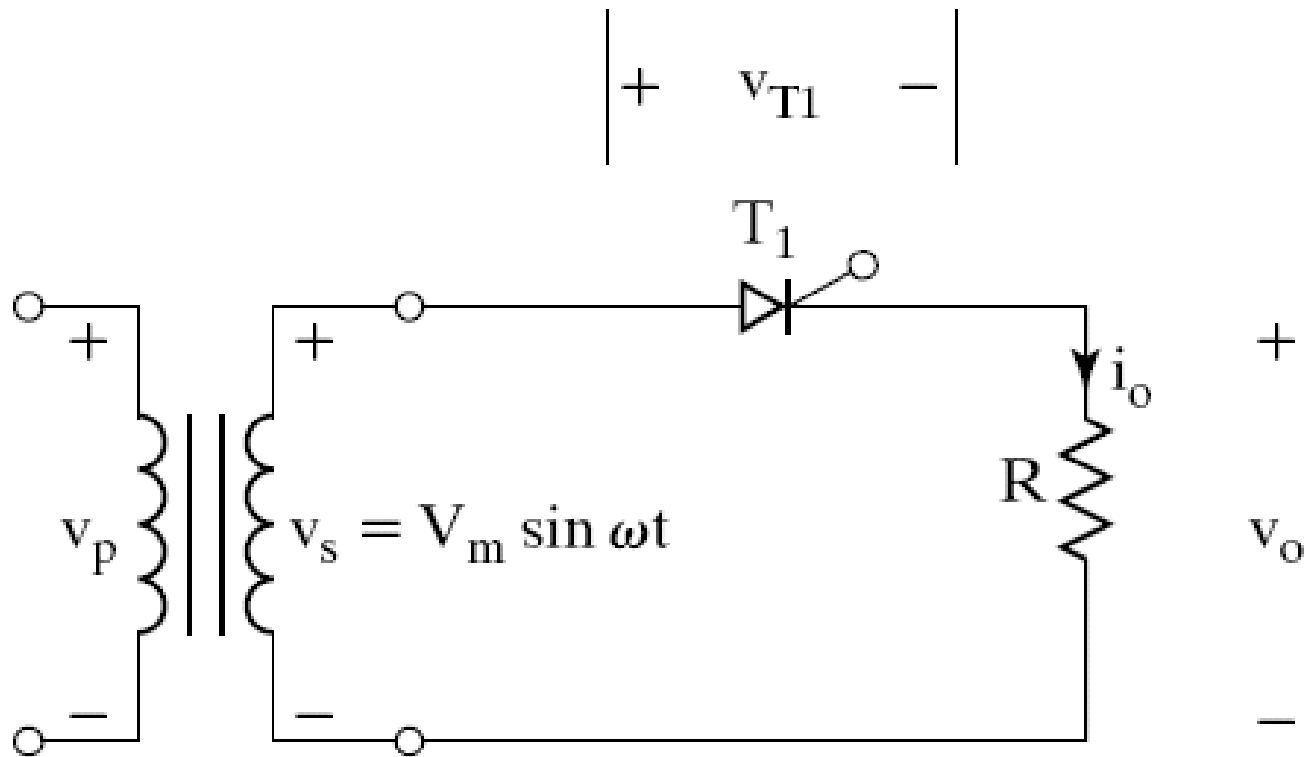Single Phase Half-Wave Thyristor Converter with a Resistive Load




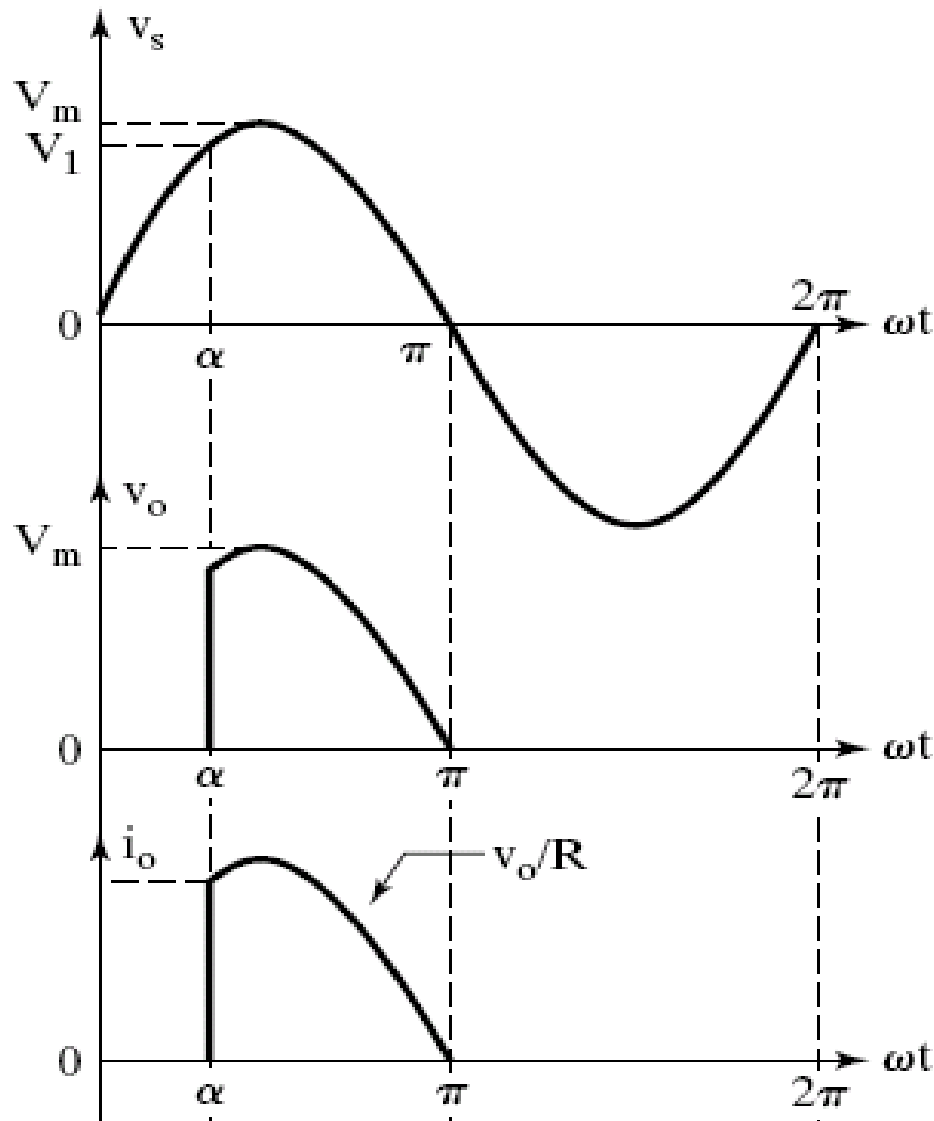


Supply Voltage

Output Voltage

Output (load)
Current

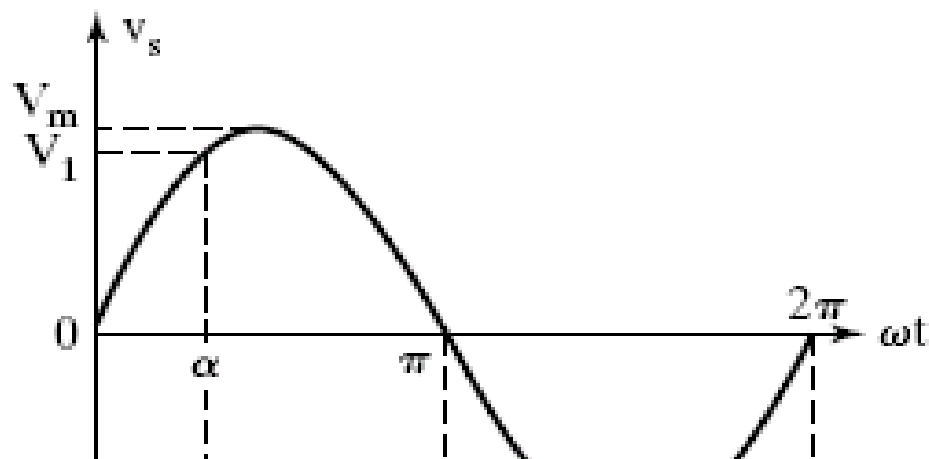

Supply Voltage

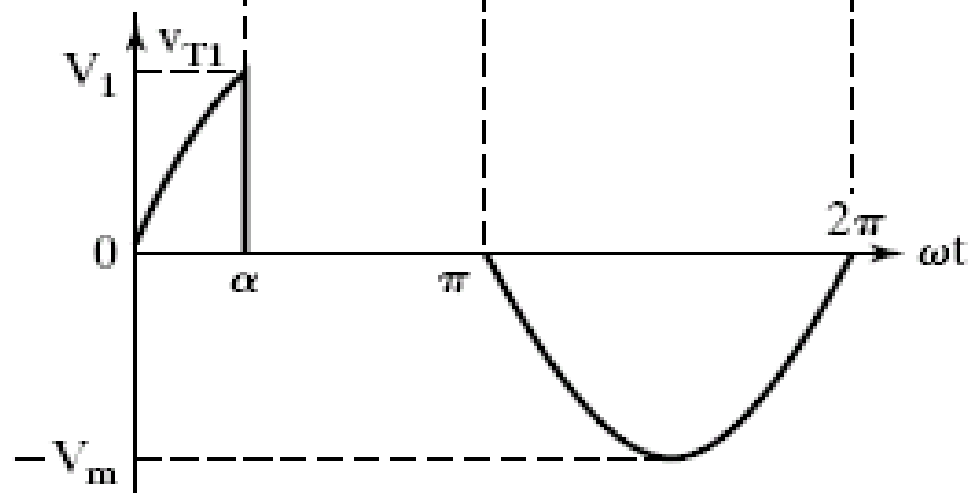

Thyristor Voltage

Equations

$$v_s = V_m \sin \omega t = \text{i/p ac supply voltage}$$

$$V_m = \text{max. value of i/p ac supply voltage}$$

$$V_s = \frac{V_m}{\sqrt{2}} = \text{RMS value of i/p ac supply voltage}$$

$$v_o = v_L = \text{output voltage across the load}$$

When the thyristor is triggered at $\omega t = \alpha$

$$v_O = v_L = V_m \sin \omega t; \quad \omega t = \alpha \text{ to } \pi$$

$$i_O = i_L = \frac{v_O}{R} = \text{Load current}; \quad \omega t = \alpha \text{ to } \pi$$

$$i_O = i_L = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t; \quad \omega t = \alpha \text{ to } \pi$$

$$\text{Where } I_m = \frac{V_m}{R} = \text{max. value of load current}$$

To Derive an Expression for the
Average (DC)
Output Voltage Across The
Load

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_o \cdot d(\omega t);$$

$$v_o = V_m \sin \omega t \text{ for } \omega t = \alpha \text{ to } \pi$$

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t . d(\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[-\cos \omega t \right]_{\alpha}^{\pi}$$

$$V_{O(dc)} = \frac{V_m}{2\pi} [-\cos \pi + \cos \alpha]; \quad \cos \pi = -1$$

$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha] ; \quad V_m = \sqrt{2} V_s$$

Maximum average (dc) o/p
voltage is obtained when $\alpha = 0$
and the maximum dc output voltage

$$V_{dc(\max)} = V_{dm} = \frac{V_m}{2\pi} (1 + \cos 0); \quad \cos(0) = 1$$

$$\therefore V_{dc(\max)} = V_{dm} = \frac{V_m}{\pi}$$

$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha] ; V_m = \sqrt{2}V_s$$

The average dc output voltage can be varied by varying the trigger angle α from 0 to a maximum of 180° (π radians)

We can plot the control characteristic ($V_{O(dc)}$ vs α) by using the equation for $V_{O(dc)}$

Control Characteristic
of
Single Phase Half Wave Phase
Controlled Rectifier
with
Resistive Load

The average dc output voltage is given by the expression


$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

We can obtain the control characteristic by plotting the expression for the dc output voltage as a function of trigger angle α

Trigger angle α in degrees	$V_{O(dc)}$	%
0	$V_{dm} = \frac{V_m}{\pi}$	100% V_{dm}
30°	$0.933 V_{dm}$	93.3 % V_{dm}
60°	$0.75 V_{dm}$	75 % V_{dm}
90°	$0.5 V_{dm}$	50 % V_{dm}
120°	$0.25 V_{dm}$	25 % V_{dm}
150°	$0.06698 V_{dm}$	6.69 % V_{dm}
180°	0	0

$$V_{dm} = \frac{V_m}{\pi} = V_{dc(max)}$$

Control Characteristic

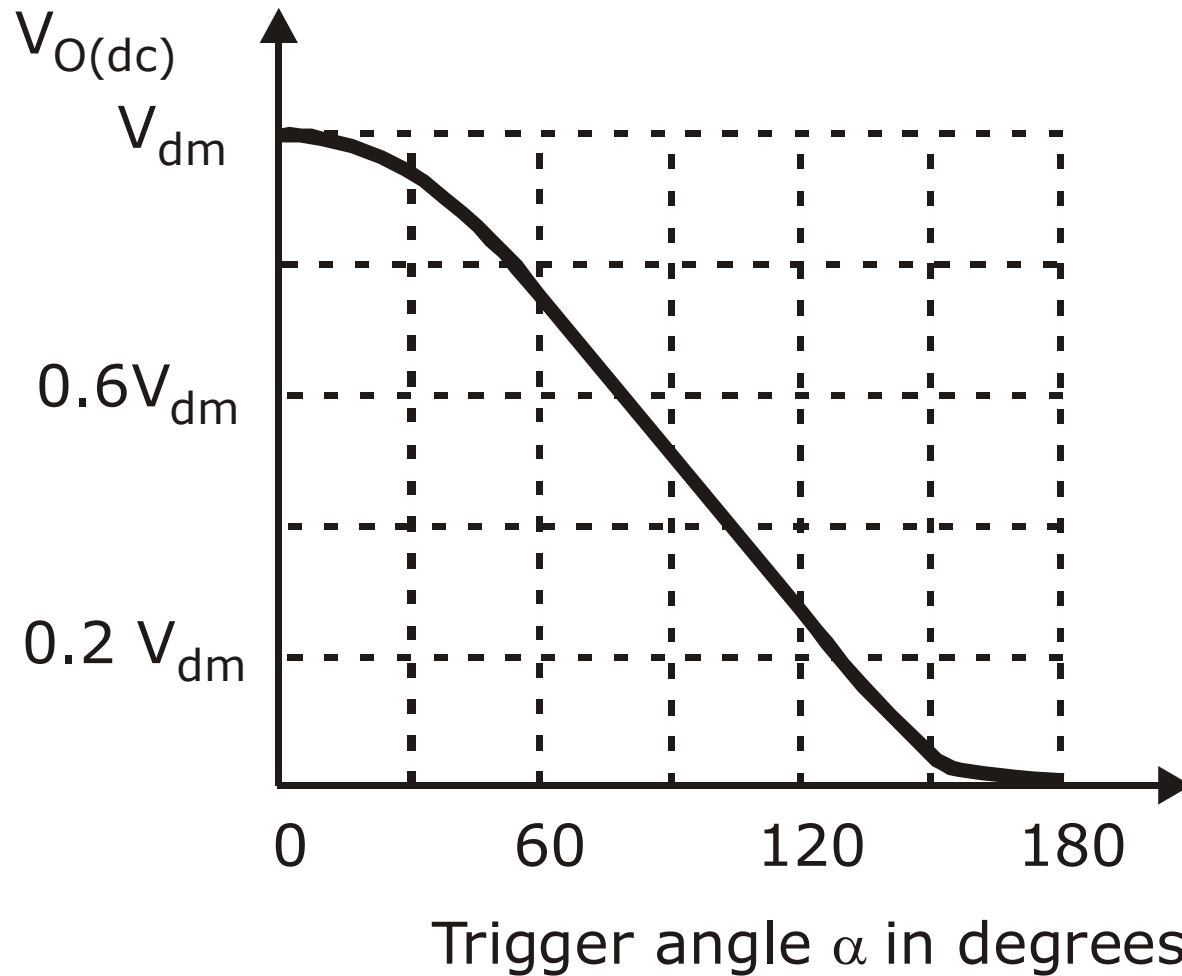

Normalizing the dc output
voltage with respect to V_{dm} , the
Normalized output voltage

$$V_n = \frac{V_{dc}}{V_{dm}} = \frac{\frac{V_m}{2\pi} (1 + \cos \alpha)}{\frac{V_m}{\pi}}$$

$$V_n = \frac{V_{dc}}{V_{dm}} = \frac{1}{2} (1 + \cos \alpha) = V_{dcn}$$

To Derive An
Expression for the
RMS Value of Output Voltage
of a
Single Phase Half Wave Controlled Rectifier With
Resistive Load

The RMS output voltage is given by

$$V_{O(RMS)} = \left[\frac{1}{2\pi} \int_0^{2\pi} v_o^2 . d(\omega t) \right]$$

Output voltage $v_o = V_m \sin \omega t$; for $\omega t = \alpha$ to π

$$V_{O(RMS)} = \left[\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t . d(\omega t) \right]^{\frac{1}{2}}$$

By substituting $\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2}$, we get

$$V_{O(RMS)} = \left[\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \frac{(1 - \cos 2\omega t)}{2} d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[\frac{V_m^2}{4\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[\frac{V_m^2}{4\pi} \left\{ \int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t d(\omega t) \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[\frac{1}{\pi} \left\{ (\omega t) \Big/_{\alpha}^{\pi} - \left(\frac{\sin 2\omega t}{2} \right) \Big/_{\alpha}^{\pi} \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[\frac{1}{\pi} \left((\pi - \alpha) - \frac{(\sin 2\pi - \sin 2\alpha)}{2} \right) \right]^{\frac{1}{2}} ; \sin 2\pi = 0$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[\frac{1}{\pi} \left((\pi - \alpha) + \frac{\sin 2\alpha}{2} \right) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \left((\pi - \alpha) + \frac{\sin 2\alpha}{2} \right)^{\frac{1}{2}}$$