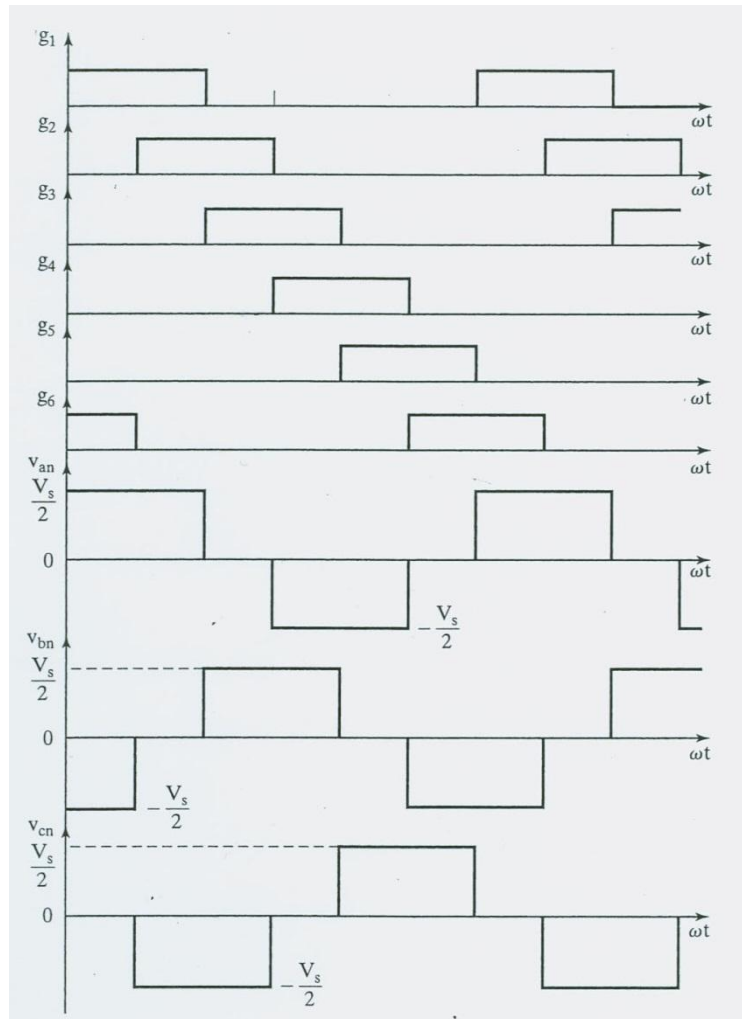


SELF-COMMUTATION INVERTERS

- For 120 degrees operation, each transistor conducts for 120 degrees
- The sequence of firing is: 61, 12, 23, 34, 45, 56, 61





SELF-COMMUTATION INVERTERS



SELF-COMMUTATION INVERTERS

- Current source inverters and voltage source inverters are different from PWM inverters and have been used for a long time
- PWM inverters require more complex control circuitry and faster switching components than CSI and VSI

SELF-COMMUTATION INVERTERS

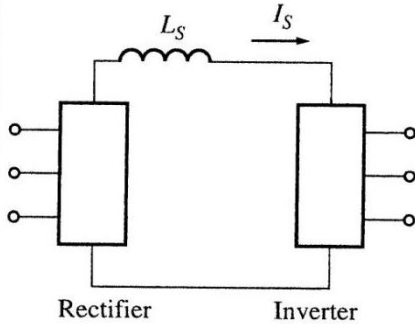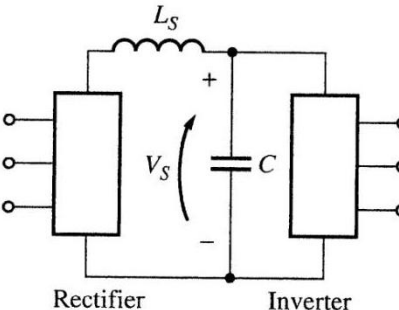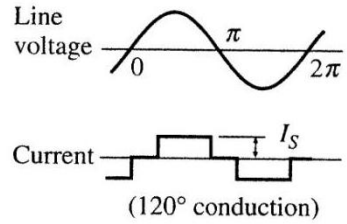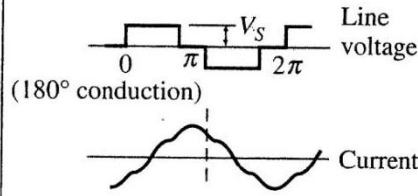	Current source inverter	Voltage source inverter
Main circuit configuration	 <p>Rectifier Inverter</p>	 <p>Rectifier Inverter</p>
Type of source	Current source $-I_S$ almost constant	Voltage source $-V_S$ almost constant
Output impedance	High	Low
Output waveform	 <p>(120° conduction)</p>	 <p>(180° conduction)</p>
Characteristics	<ol style="list-style-type: none"> 1. Easy to control overcurrent conditions with this design 2. Output voltage varies widely with changes in load 	<ol style="list-style-type: none"> 1. Difficult to limit current because of capacitor 2. Output voltage variations small because of capacitor

SELF-COMMUTATION INVERTERS


- In the **current source inverter**, a rectifier is connected to an inverter through a large series **inductor L_s**
- The inductance of **L_s** is sufficiently large that the dc current **I** constrained to be **almost constant**

SELF-COMMUTATION INVERTERS

- The SCR **current** output waveform will be roughly a **square wave** since I_S is constrained to be nearly constant
- The line-to-line **voltage** will be **triangular**
- It is easy to limit overcurrent conditions in this design, but the output voltage can swing widely in response to changes in load

SINGLE-PHASE CURRENT SOURCE INVERTER

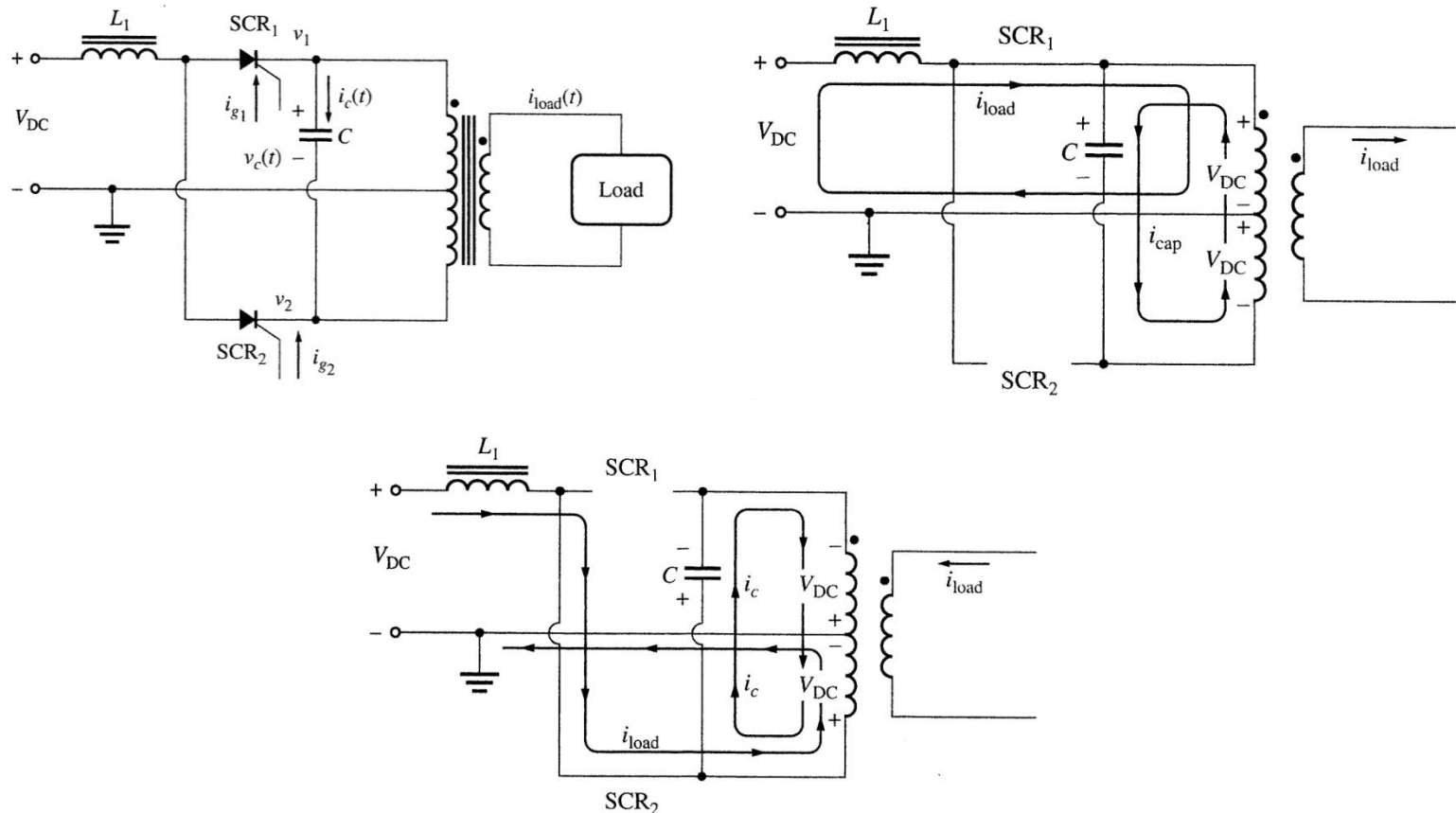- A single-phase **CSI** circuit with **capacitor** commutation is shown below



SINGLE-PHASE VOLTAGE SOURCE INVERTER

- In the **voltage source inverter**, a rectifier is connected to an inverter through a series inductor L_S and a parallel **capacitor C**
- The capacitance of **C** is sufficiently large that the **voltage is constrained to be almost constant**

SINGLE-PHASE VOLTAGE SOURCE INVERTER

- The SCR line-to-line **voltage** output waveform will be roughly a **square wave**, since the voltage V_c is constrained to be nearly constant
- The output **current** flow will be approximately **triangular**

SINGLE-PHASE VOLTAGE SOURCE INVERTER

- Voltage variations are small in this circuit, but currents can vary wildly with variations in load, and overcurrent protection is difficult to implement
- The frequency of both current and voltage source inverters can be easily changed by changing the firing pulses on the gates of the SCRs, so both inverters can be used to drive ac motors at variable speeds