

Performance Parameters Of Phase Controlled Rectifiers

Output dc power (avg. or dc o/p power delivered to the load)

$$P_{O(dc)} = V_{O(dc)} \times I_{O(dc)} \ ; \ i.e., \ P_{dc} = V_{dc} \times I_{dc}$$

Where

$V_{O(dc)} = V_{dc}$ = avg./ dc value of o/p voltage.

$I_{O(dc)} = I_{dc}$ = avg./dc value of o/p current

Output ac power

$$P_{O(ac)} = V_{O(RMS)} \times I_{O(RMS)}$$

Efficiency of Rectification (Rectification Ratio)

$$\text{Efficiency } \eta = \frac{P_{O(dc)}}{P_{O(ac)}}; \quad \% \text{ Efficiency } \eta = \frac{P_{O(dc)}}{P_{O(ac)}} \times 100$$

The o/p voltage consists of two components

The dc component $V_{O(dc)}$

The ac /ripple component $V_{ac} = V_{r(rms)}$

The total RMS value of output voltage is given by

$$V_{O(RMS)} = \sqrt{V_{O(dc)}^2 + V_{r(rms)}^2}$$

$$\therefore V_{ac} = V_{r(rms)} = \sqrt{V_{O(RMS)}^2 - V_{O(dc)}^2}$$

Form Factor (FF) which is a measure of the shape of the output voltage is given by

$$FF = \frac{V_{O(RMS)}}{V_{O(dc)}} = \frac{\text{RMS output (load) voltage}}{\text{DC load output (load) voltage}}$$

The Ripple Factor (RF) w.r.t. o/p voltage w/f

$$r_v = RF = \frac{V_{r(rms)}}{V_{O(dc)}} = \frac{V_{ac}}{V_{dc}}$$

$$r_v = \frac{\sqrt{V_{O(RMS)}^2 - V_{O(dc)}^2}}{V_{O(dc)}} = \sqrt{\left[\frac{V_{O(RMS)}}{V_{O(dc)}} \right]^2 - 1}$$

$$\therefore r_v = \sqrt{FF^2 - 1}$$

Current Ripple Factor $r_i = \frac{I_{r(rms)}}{I_{O(dc)}} = \frac{I_{ac}}{I_{dc}}$

Where $I_{r(rms)} = I_{ac} = \sqrt{I_{O(RMS)}^2 - I_{O(dc)}^2}$

$V_{r(pp)}$ = peak to peak ac ripple output voltage

$$V_{r(pp)} = V_{O(max)} - V_{O(min)}$$

$I_{r(pp)}$ = peak to peak ac ripple load current

$$I_{r(pp)} = I_{O(max)} - I_{O(min)}$$


Transformer Utilization Factor (TUF)

$$TUF = \frac{P_{O(dc)}}{V_S \times I_S}$$

Where

V_S = RMS supply (secondary) voltage

I_S = RMS supply (secondary) current

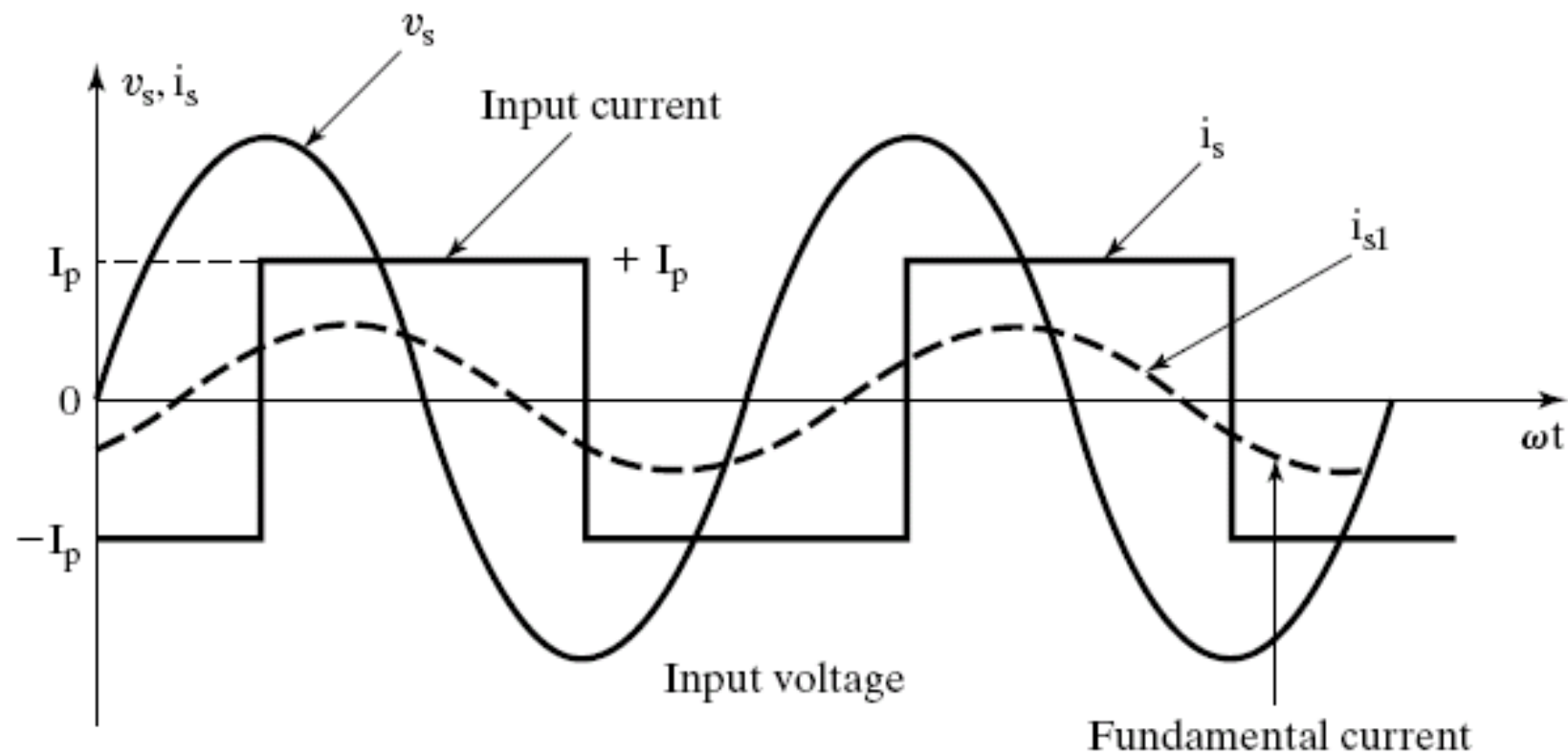

Where

v_s = Supply voltage at the transformer secondary side

i_s = i/p supply current

(transformer secondary winding current)

i_{s1} = Fundamental component of the i/p supply current

I_p = Peak value of the input supply current

ϕ = Phase angle difference between (sine wave components) the fundamental components of i/p supply current & the input supply voltage.

ϕ = Displacement angle (phase angle)

For an RL load

ϕ = Displacement angle = Load impedance angle

$$\therefore \phi = \tan^{-1} \left(\frac{\omega L}{R} \right) \text{ for an RL load}$$

Displacement Factor (DF) or

Fundamental Power Factor

$$DF = \cos \phi$$

Harmonic Factor (HF) or
Total Harmonic Distortion Factor ; THD

$$HF = \left[\frac{I_S^2 - I_{S1}^2}{I_{S1}^2} \right]^{\frac{1}{2}} = \left[\left(\frac{I_S}{I_{S1}} \right)^2 - 1 \right]^{\frac{1}{2}}$$

Where

I_S = RMS value of input supply current.

I_{S1} = RMS value of fundamental component of
the i/p supply current.

Input Power Factor (PF)

$$PF = \frac{V_S I_{S1}}{V_S I_S} \cos \phi = \frac{I_{S1}}{I_S} \cos \phi$$

The Crest Factor (CF)


$$CF = \frac{I_{S(\text{peak})}}{I_S} = \frac{\text{Peak input supply current}}{\text{RMS input supply current}}$$

For an Ideal Controlled Rectifier


$$FF = 1; \quad \eta = 100\% ; \quad V_{ac} = V_{r(rms)} = 0 ; \quad TUF = 1;$$

$$RF = r_v = 0 ; \quad HF = THD = 0; \quad PF = DPF = 1$$

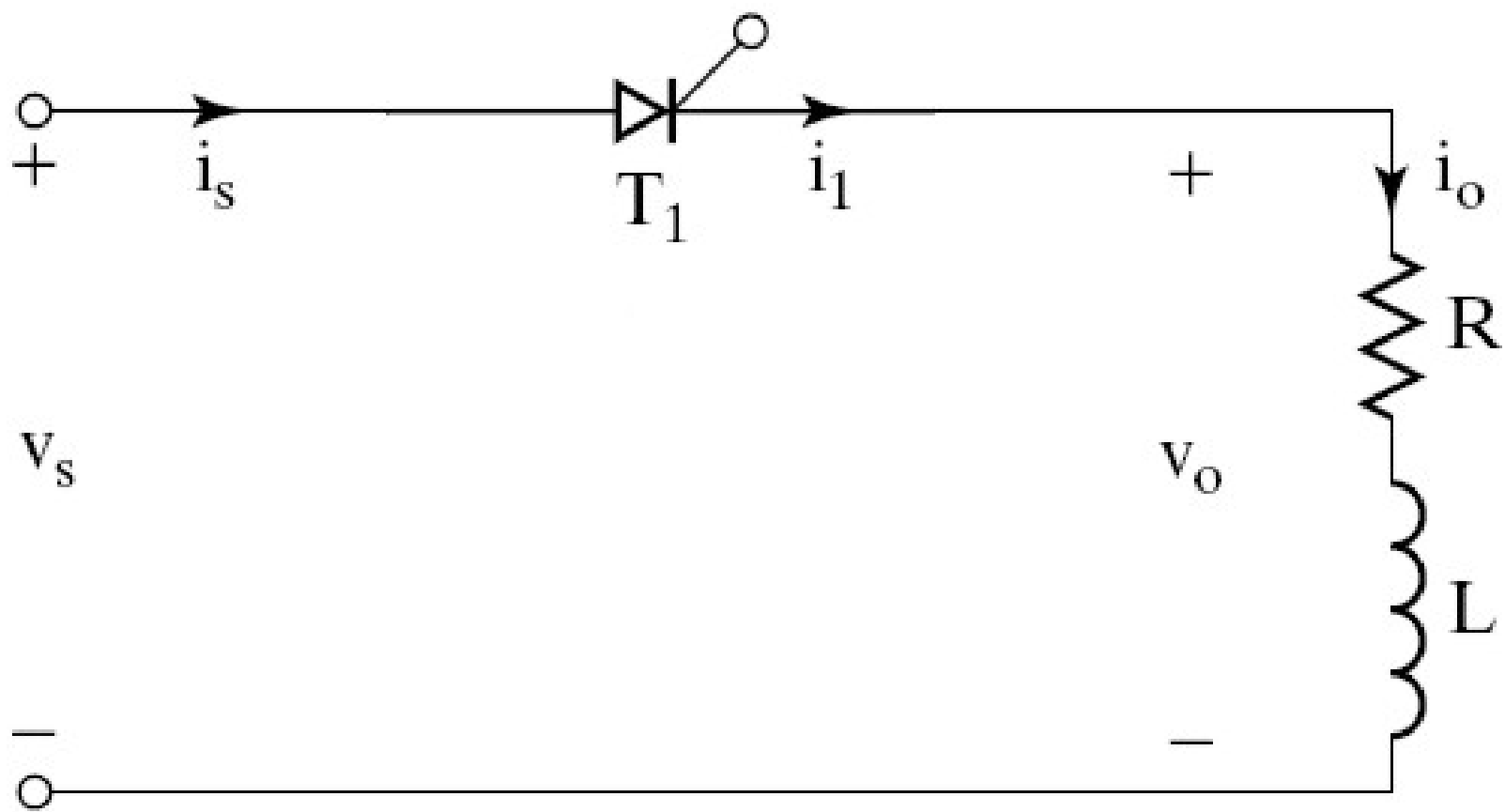
Single Phase Half Wave
Controlled Rectifier
With
An
RL Load



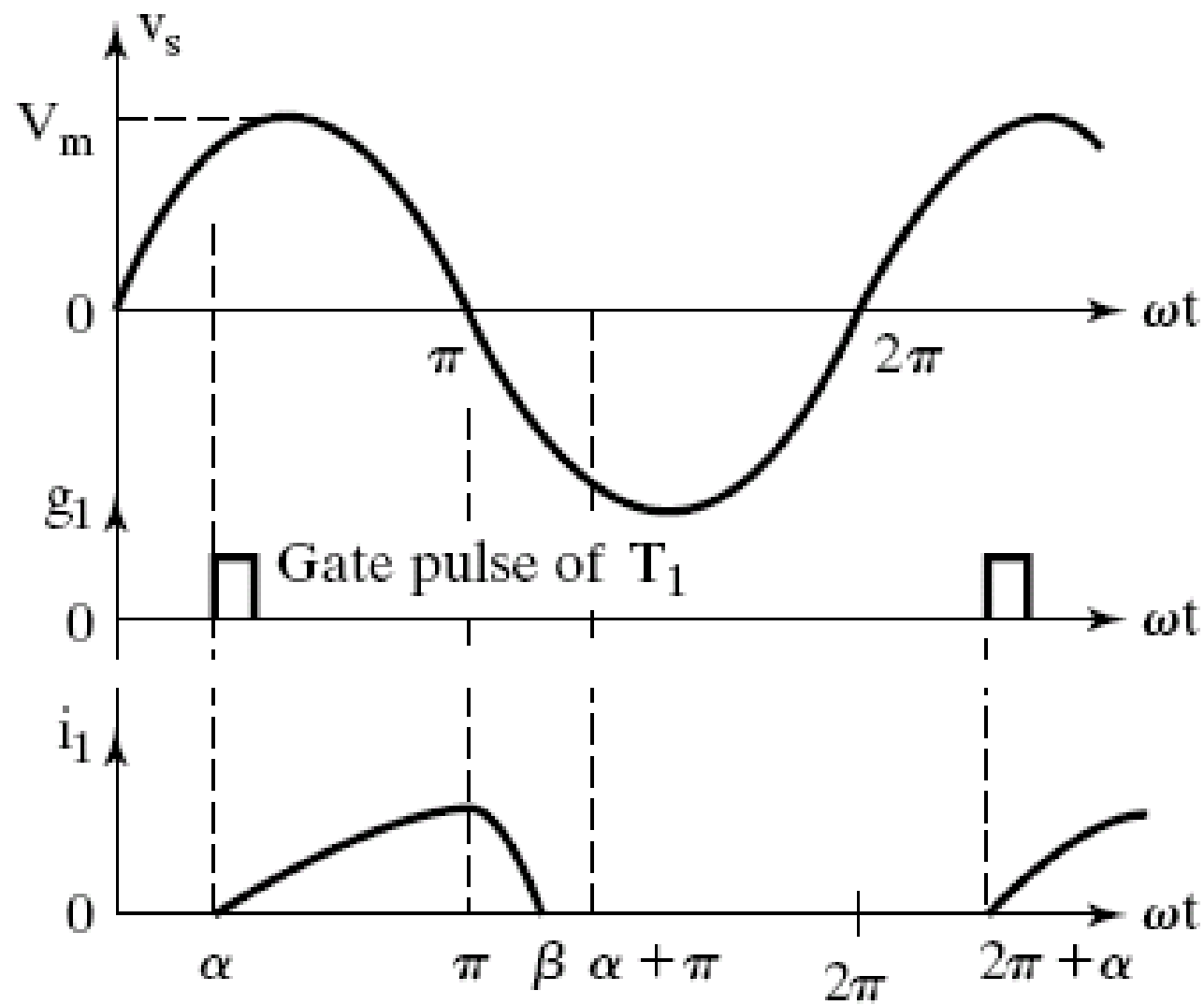Input Supply Voltage (V_s)
&
Thyristor (Output) Current
Waveforms



Output (Load) Voltage Waveform

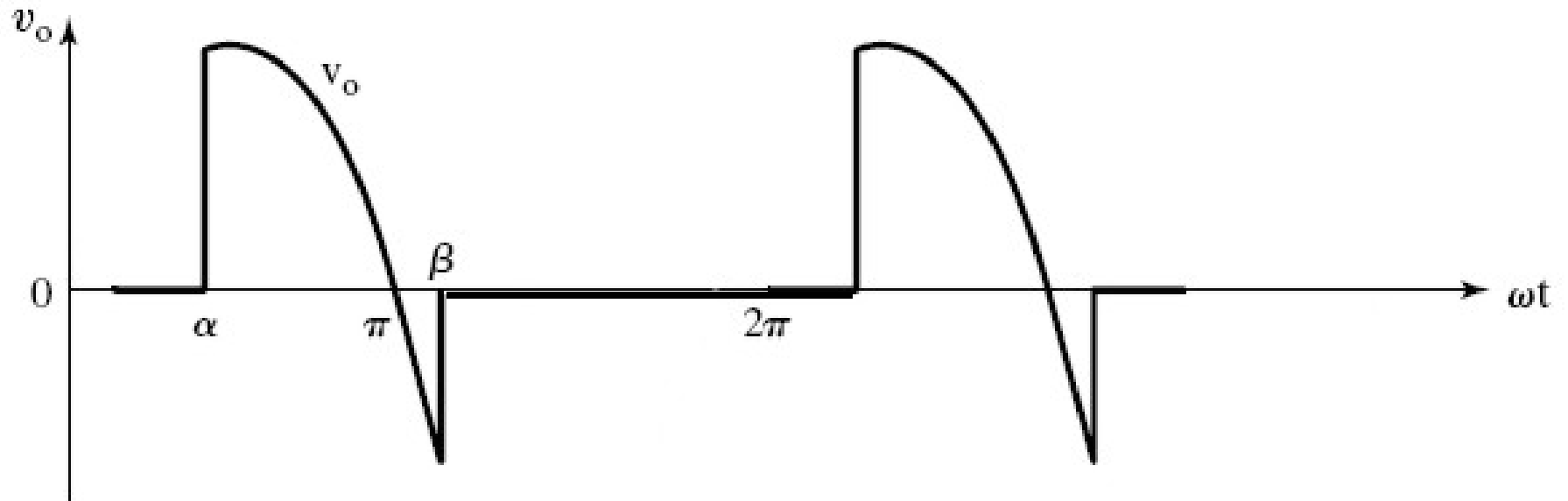

To Derive An Expression For
The Output
(Load) Current, During $\omega t = \alpha$ to β
When Thyristor T_1 Conducts

Assuming T_1 is triggered $\omega t = \alpha$,
we can write the equation,

$$L \left(\frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ; \alpha \leq \omega t \leq \beta$$

General expression for the output current,

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}}$$

$$V_m = \sqrt{2}V_s = \text{maximum supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

\therefore general expression for the output load current

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t}$$

Constant A_1 is calculated from

initial condition $i_o = 0$ at $\omega t = \alpha$; $t = \left(\frac{\alpha}{\omega} \right)$

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

$$\therefore A_1 e^{\frac{-R}{L} t} = \frac{-V_m}{Z} \sin(\alpha - \phi)$$

We get the value of constant A_1 as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[\frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

Substituting the value of constant A_1 in the general expression for i_o

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{\omega L}(\omega t - \alpha)} \left[\frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

\therefore we obtain the final expression for the inductive load current

$$i_o = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right];$$

Where $\alpha \leq \omega t \leq \beta$

Extinction angle β can be calculated by using the condition that $i_o = 0$ at $\omega t = \beta$

$$i_o = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] = 0$$

$$\therefore \sin(\beta - \phi) = e^{\frac{-R}{\omega L}(\beta - \alpha)} \times \sin(\alpha - \phi)$$

β can be calculated by solving the above eqn.

To Derive An Expression
For
Average (DC) Load Voltage of a Single
Half Wave Controlled Rectifier with
RL Load

$$V_{O(dc)} = V_L = \frac{1}{2\pi} \int_0^{2\pi} v_o \cdot d(\omega t)$$

$$V_{O(dc)} = V_L = \frac{1}{2\pi} \left[\int_0^{\alpha} v_o \cdot d(\omega t) + \int_{\alpha}^{\beta} v_o \cdot d(\omega t) + \int_{\beta}^{2\pi} v_o \cdot d(\omega t) \right]$$

$$v_o = 0 \text{ for } \omega t = 0 \text{ to } \alpha \text{ \& for } \omega t = \beta \text{ to } 2\pi$$

$$\therefore V_{O(dc)} = V_L = \frac{1}{2\pi} \left[\int_{\alpha}^{\beta} v_o \cdot d(\omega t) \right];$$

$$v_o = V_m \sin \omega t \text{ for } \omega t = \alpha \text{ to } \beta$$

$$V_{O(dc)} = V_L = \frac{1}{2\pi} \left[\int_{\alpha}^{\beta} V_m \sin \omega t . d(\omega t) \right]$$

$$V_{O(dc)} = V_L = \frac{V_m}{2\pi} \left[-\cos \omega t \Big/_{\alpha}^{\beta} \right]$$

$$V_{O(dc)} = V_L = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$\therefore V_{O(dc)} = V_L = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

Effect of Load


Inductance on the Output


During the period $\omega t = \pi$ to β the instantaneous o/p voltage is negative and this reduces the average or the dc output voltage when compared to a purely resistive load.

Average DC Load Current

$$I_{O(dc)} = I_{L(Avg)} = \frac{V_{O(dc)}}{R_L} = \frac{V_m}{2\pi R_L} (\cos \alpha - \cos \beta)$$

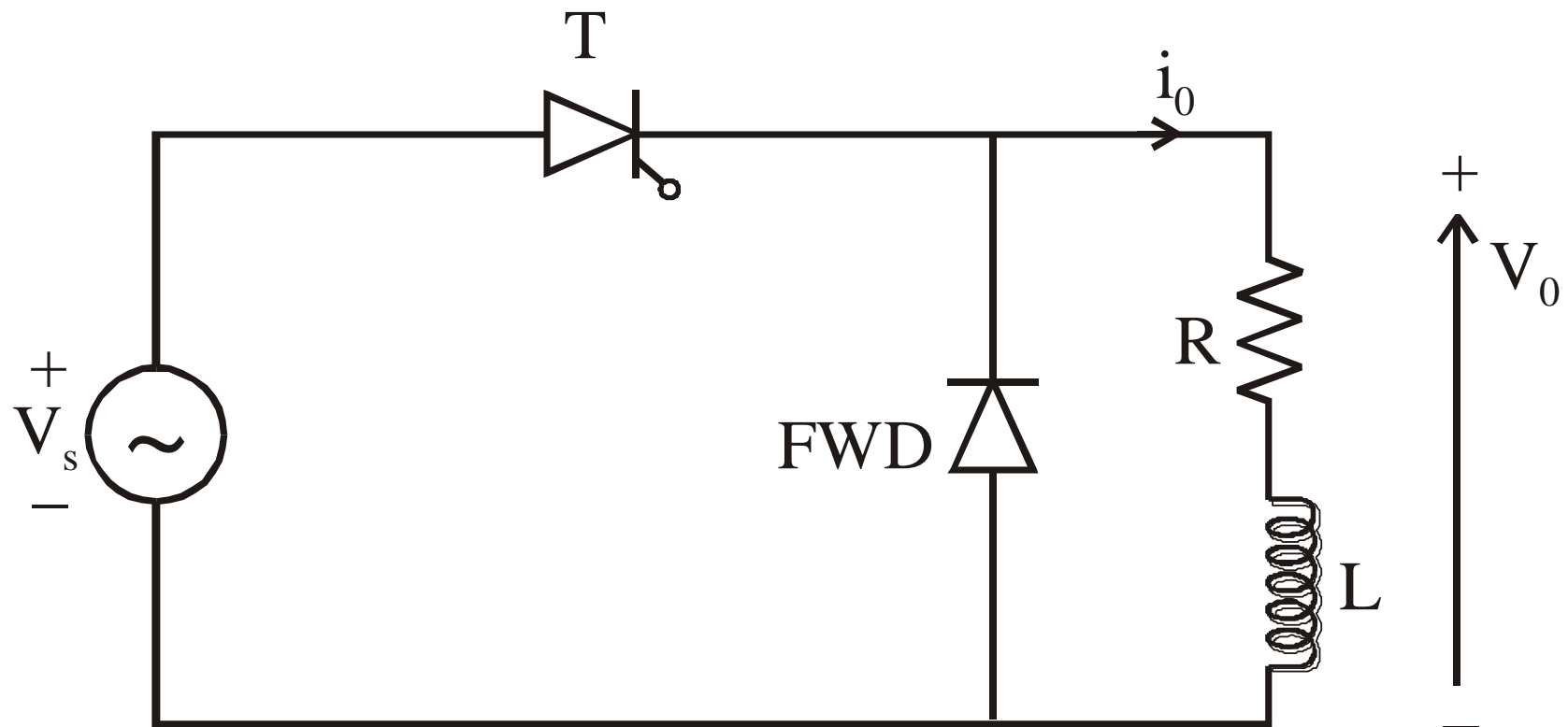Single Phase Half Wave
Controlled Rectifier
With RL Load
&
Free Wheeling Diode



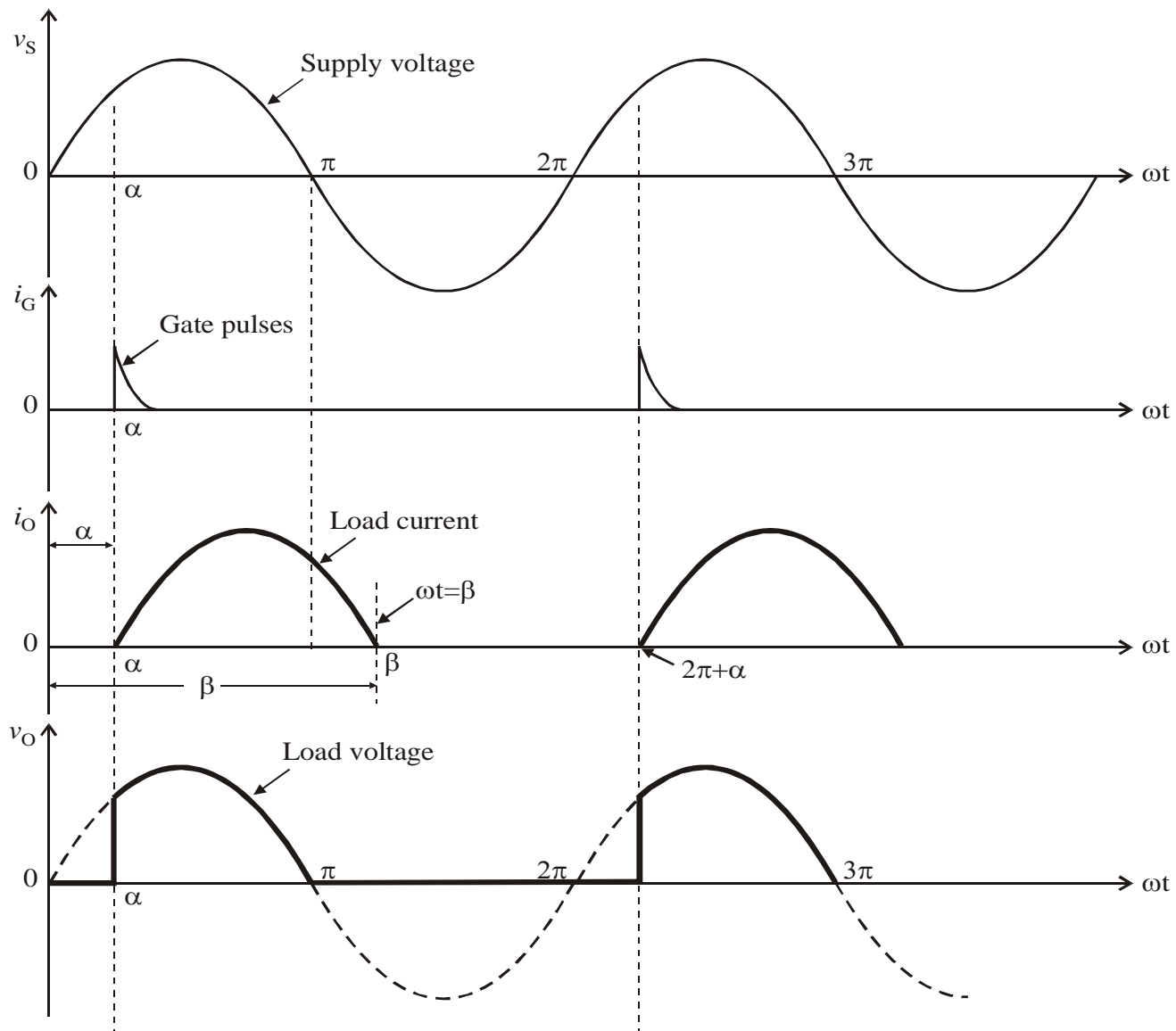

The average output voltage

$V_{dc} = \frac{V_m}{2\pi} [1 + \cos \alpha]$ which is the same as that of a purely resistive load.

The following points are to be noted

For low value of inductance, the load current tends to become discontinuous.

During the period α to π

the load current is carried by the SCR.

During the period π to β load current is carried by the free wheeling diode.

The value of β depends on the value of R and L and the forward resistance of the FWD.

For Large Load Inductance
the load current does not reach zero, & we
obtain continuous load current

