
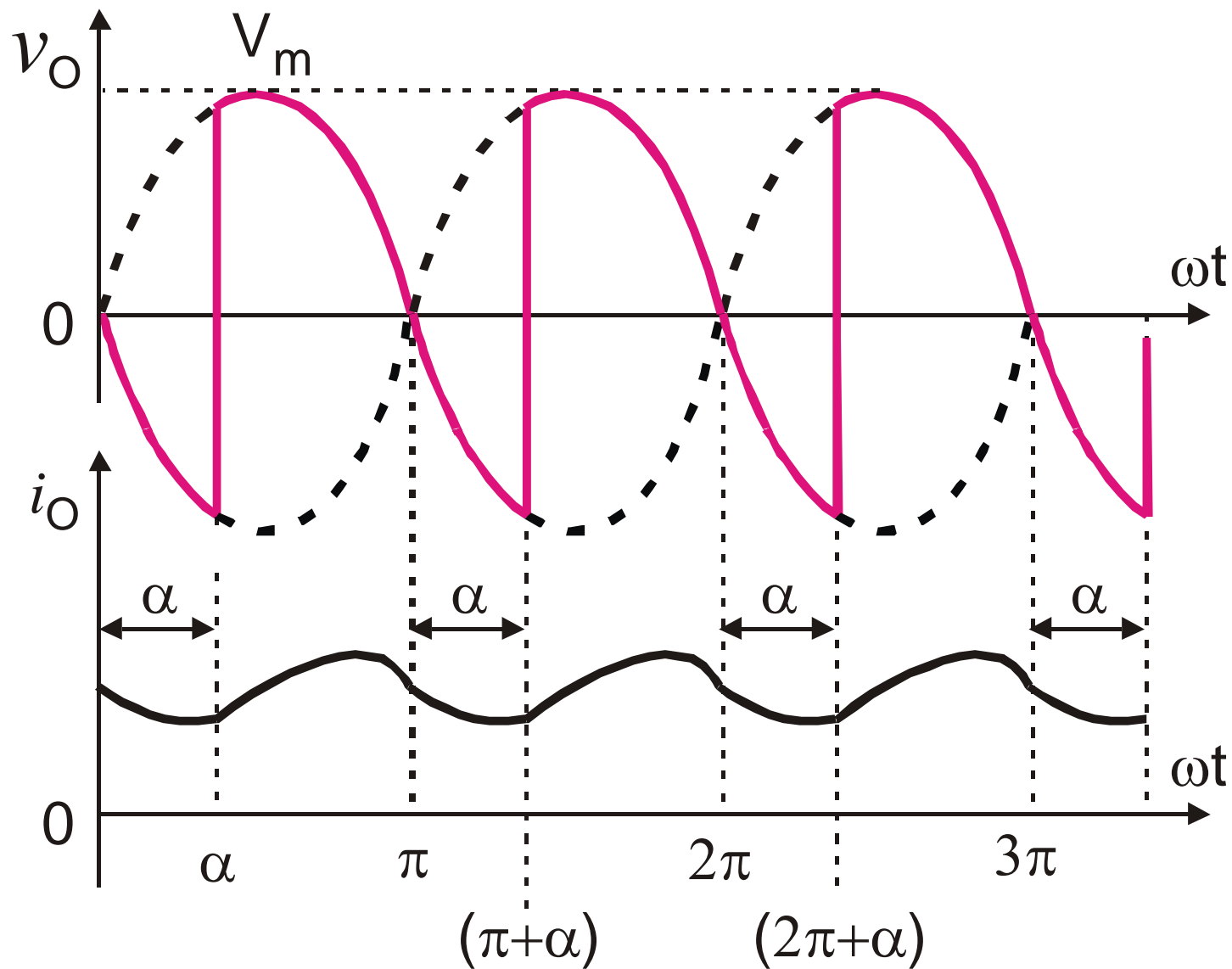

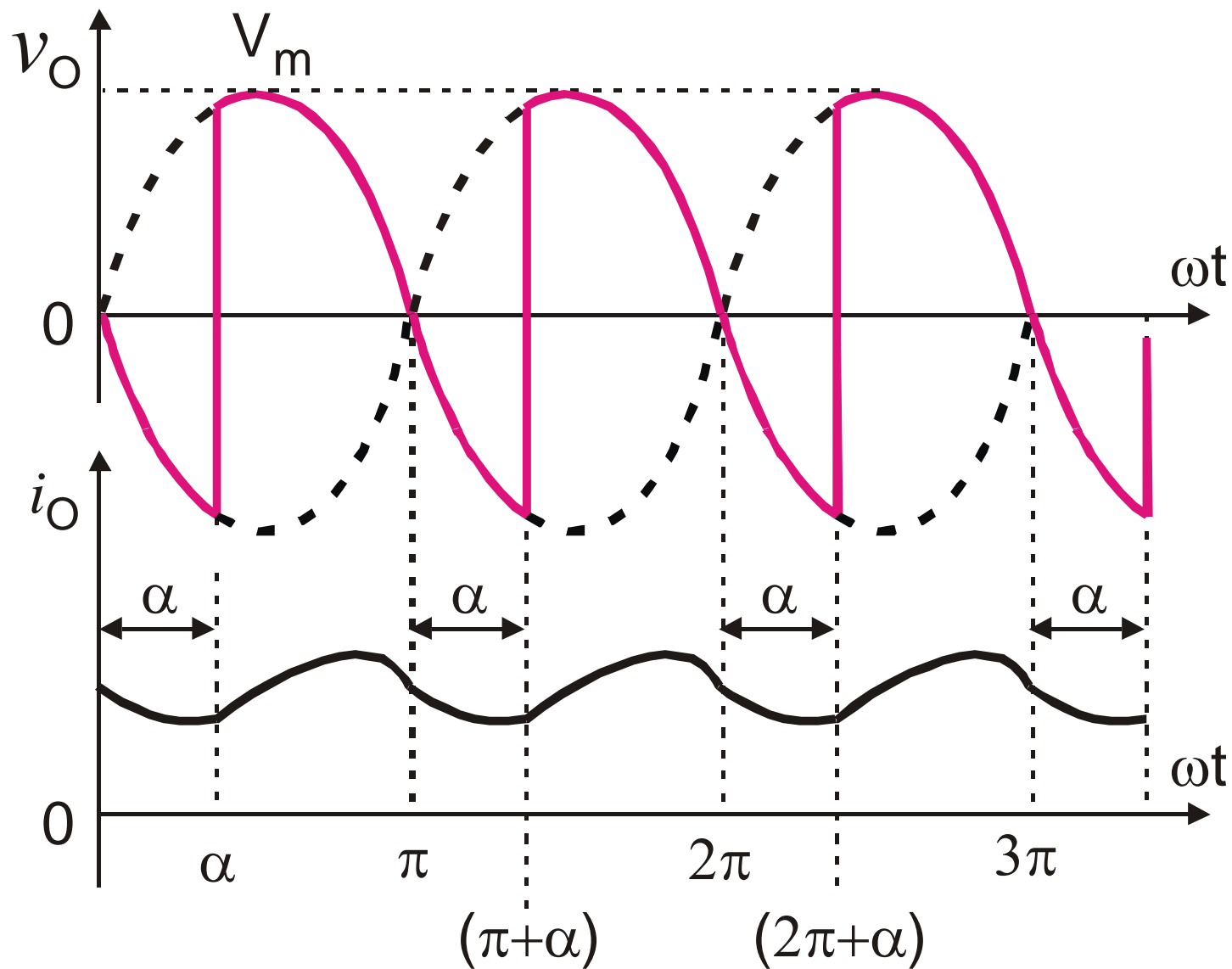
# Continuous Load Current Operation (Without FWD)



To Derive  
An Expression For  
Average / DC Output Voltage  
Of

Single Phase Full Wave Controlled Rectifier For  
Continuous Current Operation without FWD



$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t = \alpha}^{(\pi + \alpha)} v_o . d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \left[ \int_{\alpha}^{(\pi + \alpha)} V_m \sin \omega t . d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big/_{\alpha}^{(\pi + \alpha)} \right]$$

$$V_{O(dc)} = V_{dc}$$

$$= \frac{V_m}{\pi} \left[ \cos \alpha - \cos (\pi + \alpha) \right] ;$$

$$\cos (\pi + \alpha) = -\cos \alpha$$


$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ \cos \alpha + \cos \alpha \right]$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$

- By plotting  $V_{O(dc)}$  *versus*  $\alpha$ ,  
we obtain the control characteristic of a  
single phase full wave controlled rectifier with  
RL load for continuous load current operation  
without FWD

Trigger angle $\alpha$ in degrees	$V_{O(dc)}$	Remarks
0	$V_{dm} = \left( \frac{2V_m}{\pi} \right)$	Maximum dc output voltage $V_{dc(max)} = V_{dm} = \left( \frac{2V_m}{\pi} \right)$
$30^0$	$0.866 V_{dm}$	$V_{dc} = V_{dm} \times \cos \alpha$
$60^0$	$0.5 V_{dm}$	
$90^0$	$0 V_{dm}$	
$120^0$	$-0.5 V_{dm}$	
$150^0$	$-0.866 V_{dm}$	
$180^0$	$-V_{dm} = -\left( \frac{2V_m}{\pi} \right)$	



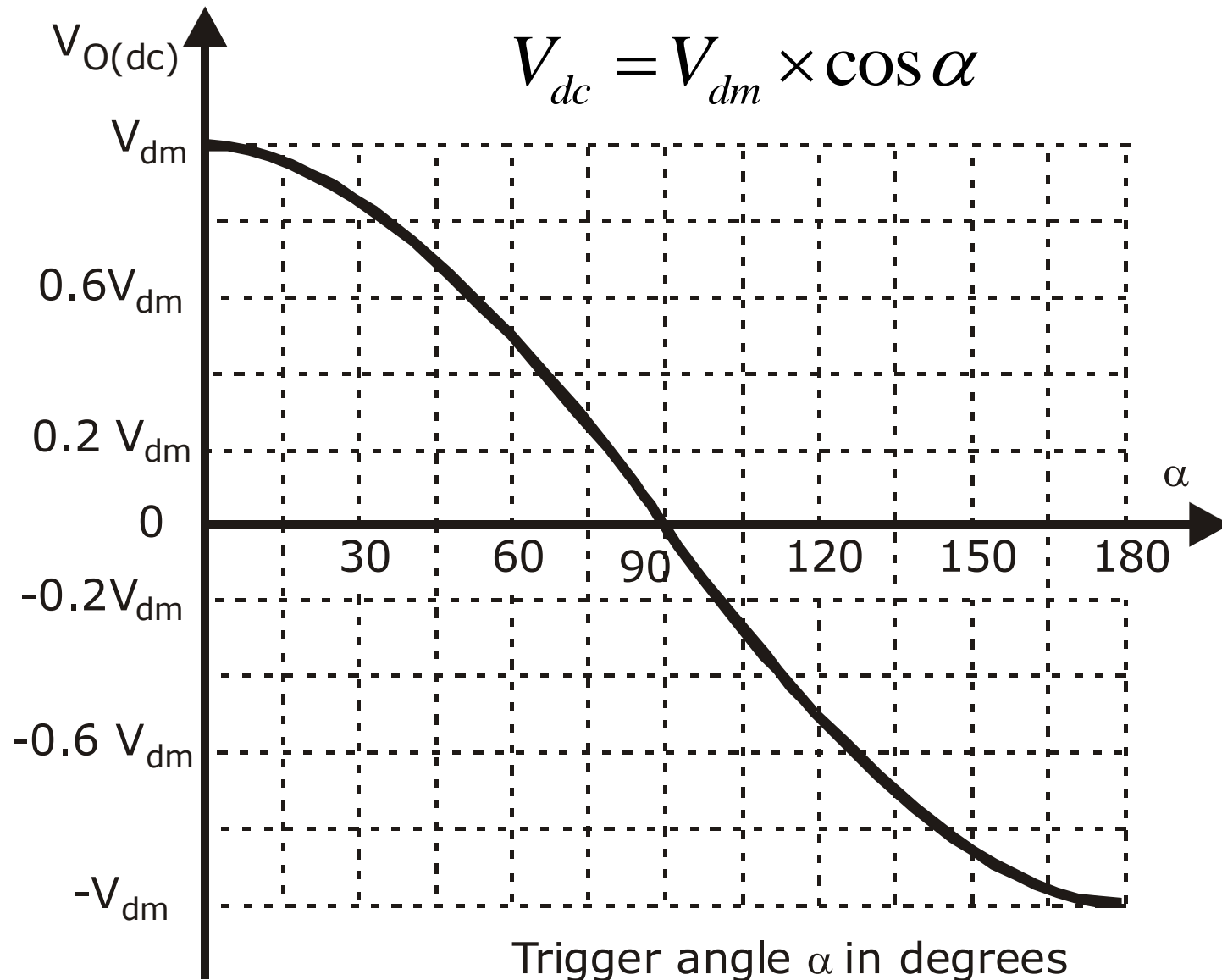

By varying the trigger angle we can vary the output dc voltage across the load. Hence we can control the dc output power flow to the load.

For trigger angle  $\alpha$ , 0 to  $90^\circ$  (*i.e.*,  $0 \leq \alpha \leq 90^\circ$ );

$\cos \alpha$  is positive and hence  $V_{dc}$  is positive

$V_{dc}$  &  $I_{dc}$  are positive ;  $P_{dc} = (V_{dc} \times I_{dc})$  is positive

Converter operates as a **Controlled Rectifier**.

Power flow is from the ac source to the load.

For trigger angle  $\alpha$ ,  $90^\circ$  to  $180^\circ$

$$(i.e., 90^\circ \leq \alpha \leq 180^\circ),$$

$\cos \alpha$  is negative and hence

$V_{dc}$  is negative;  $I_{dc}$  is positive ;

$$P_{dc} = (V_{dc} \times I_{dc}) \text{ is negative.}$$

In this case the converter operates

as a **Line Commutated Inverter**.

Power flows from the load ckt. to the i/p ac source.

The inductive load energy is fed back to the i/p source.

## Drawbacks Of Full Wave Controlled Rectifier With Centre Tapped Transformer

- We require a centre tapped transformer which is quite heavier and bulky.
- Cost of the transformer is higher for the required dc output voltage & output power.
- Hence full wave bridge converters are preferred.

# Single Phase


## Full Wave Bridge Controlled Rectifier

2 types of FW Bridge Controlled Rectifiers are

- Half Controlled Bridge Converter  
(Semi-Converter)
- Fully Controlled Bridge Converter  
(Full Converter)

*The bridge full wave controlled rectifier does not require a centre tapped transformer*

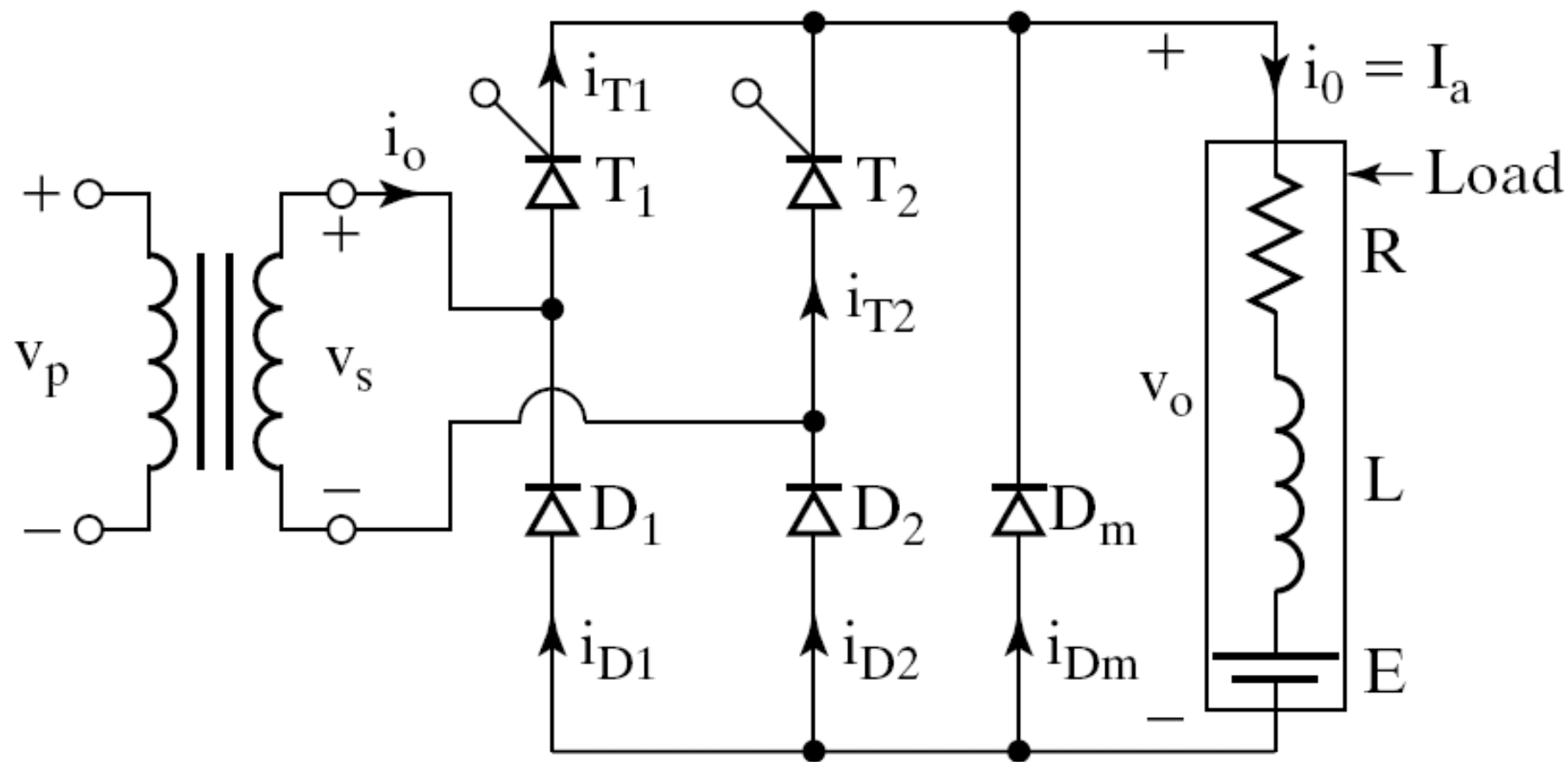Single Phase  
Full Wave Half Controlled Bridge  
Converter  
(Single Phase Semi Converter)



# Trigger Pattern of Thyristors

*Thyristor  $T_1$  is triggered at*

$$\omega t = \alpha, \text{ at } \omega t = (2\pi + \alpha), \dots$$

*Thyristor  $T_2$  is triggered at*



$$\omega t = (\pi + \alpha), \text{ at } \omega t = (3\pi + \alpha), \dots$$

*The time delay between the gating*


*signals of  $T_1$  &  $T_2 = \pi$  radians or  $180^\circ$*




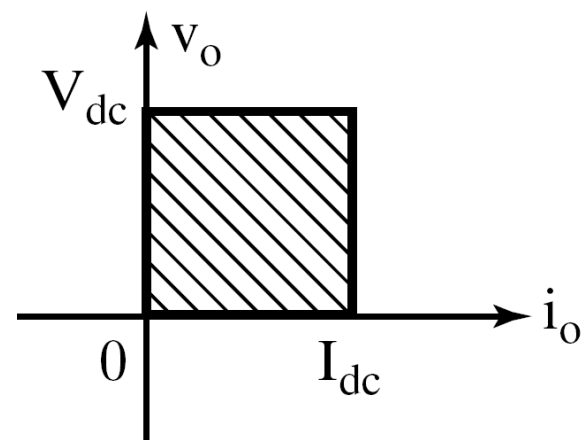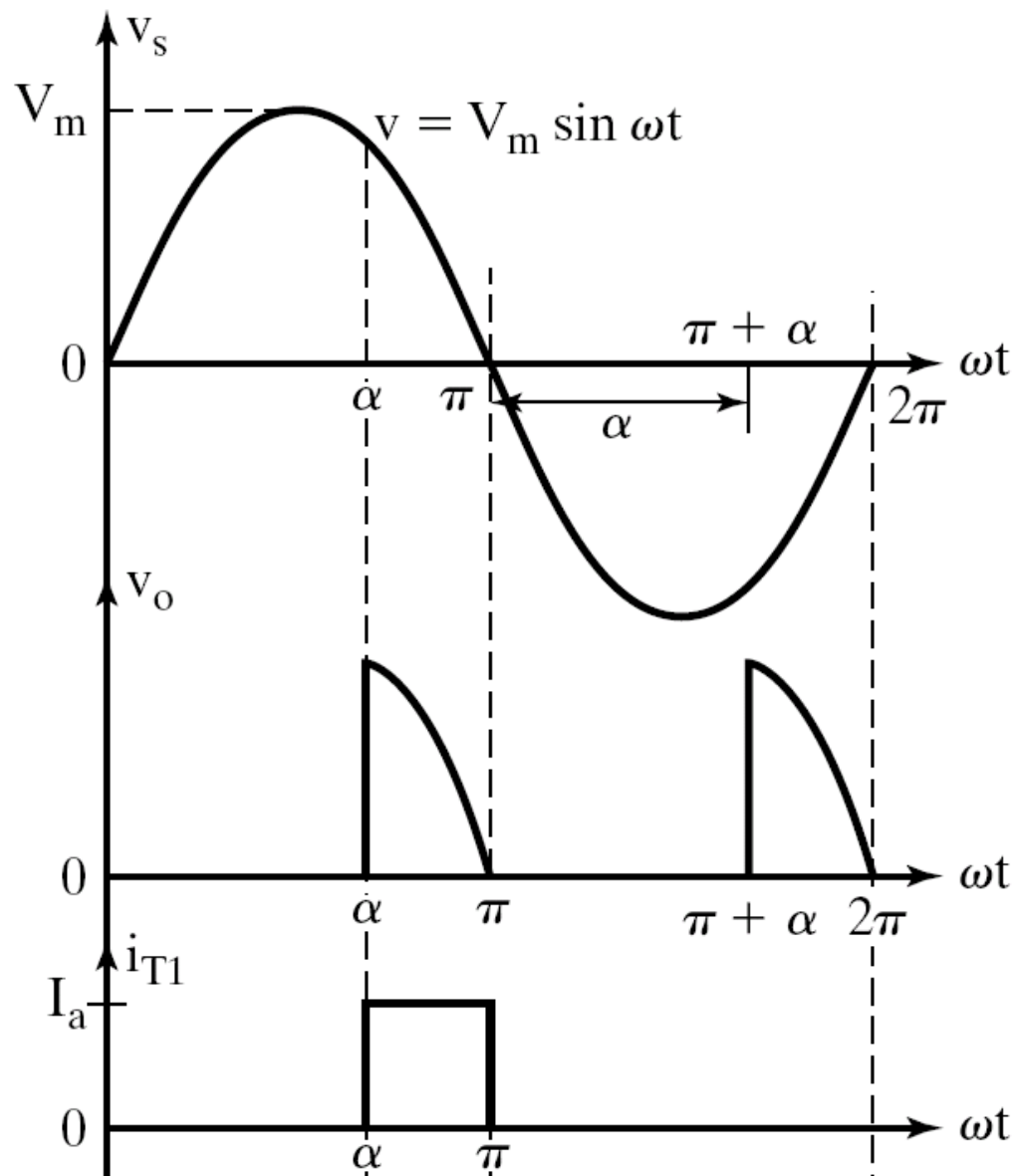Waveforms of  
single phase semi-converter  
with general load & FWD  
for  $\alpha > 90^\circ$



Single Quadrant  
Operation

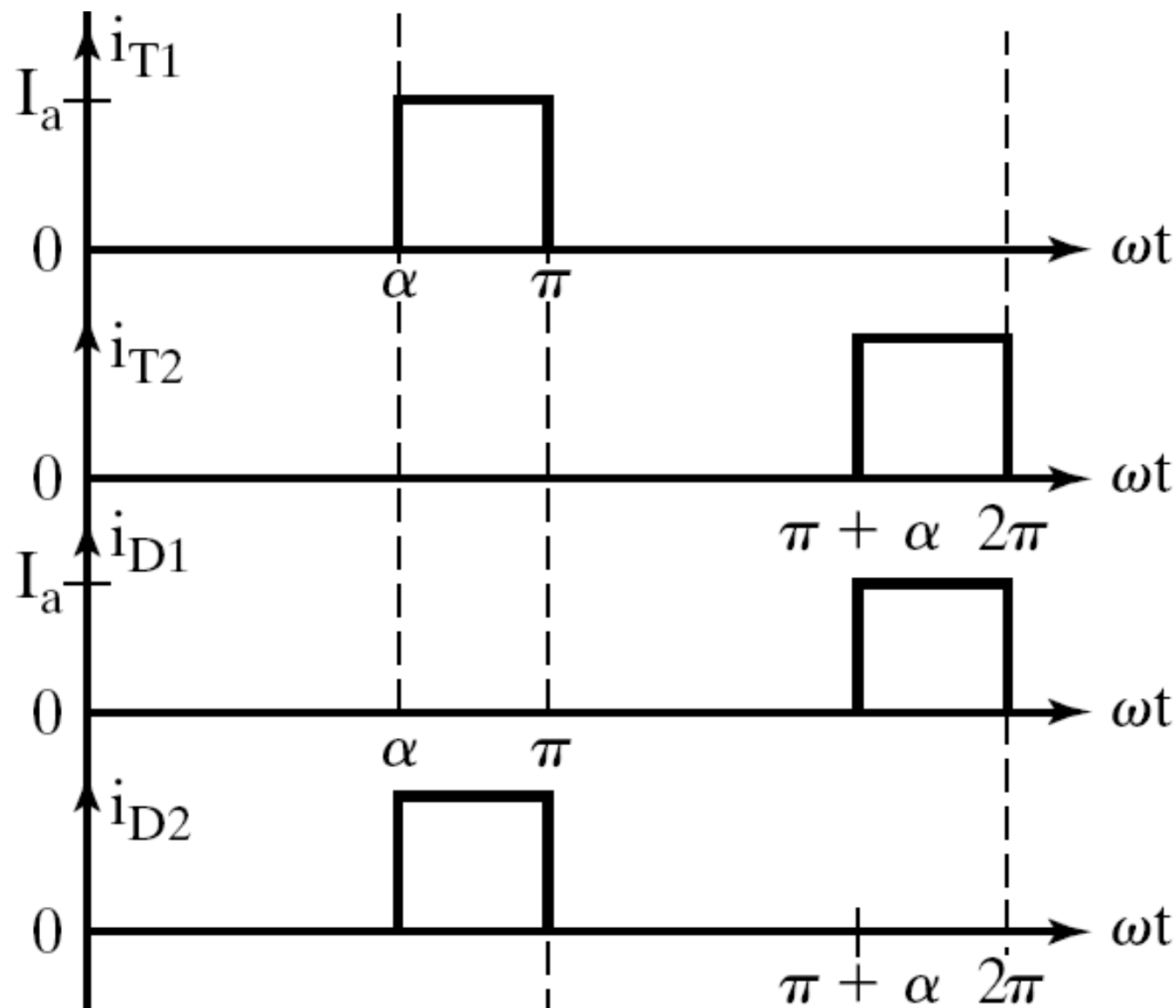

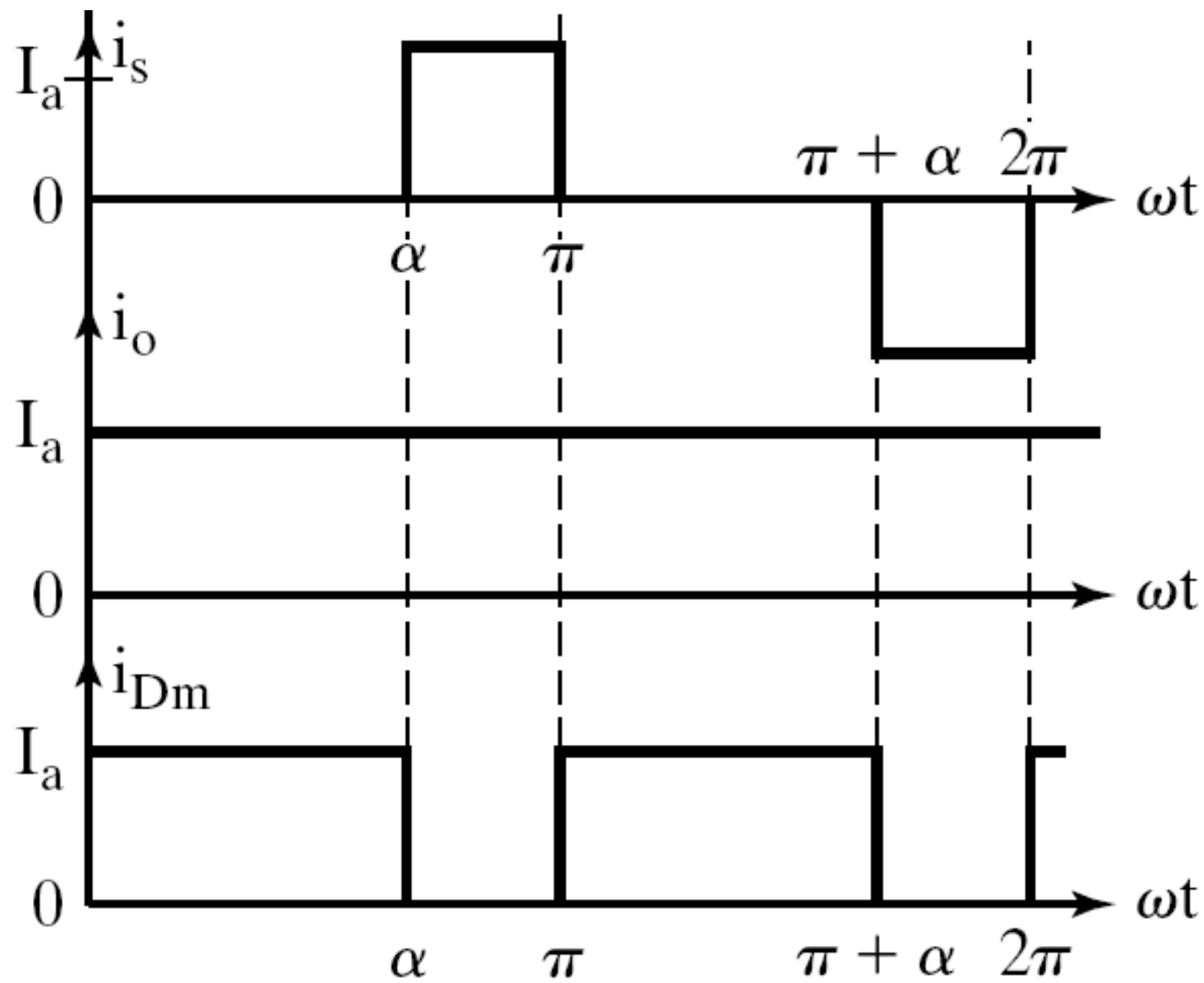

Thyristor  $T_1$  &  $D_1$  conduct

from  $\omega t = \alpha$  to  $\pi$


Thyristor  $T_2$  &  $D_2$  conduct

from  $\omega t = (\pi + \alpha)$  to  $2\pi$

FWD conducts during

$\omega t = 0$  to  $\alpha$ ,  $\pi$  to  $(\pi + \alpha), \dots$

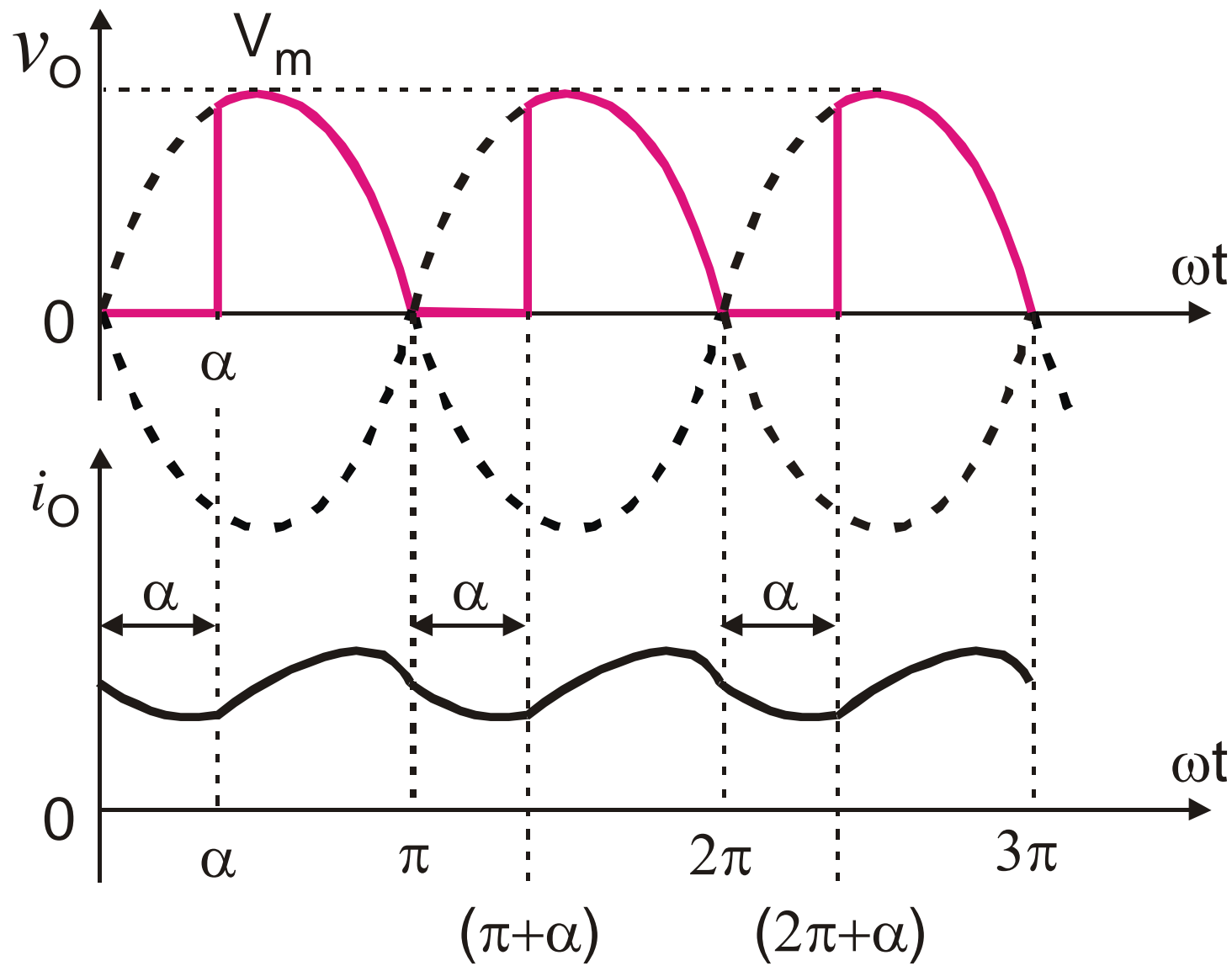Load Voltage & Load Current Waveform of  
Single Phase Semi Converter for  
 $\alpha < 90^\circ$   
& Continuous load current operation



To Derive an Expression  
For The  
DC Output Voltage of  
A  
Single Phase Semi-Converter With R,L,  
& E Load & FWD  
For Continuous, Ripple Free Load  
Current Operation



$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t=0}^{\pi} v_o \cdot d(\omega t)$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi}$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} [-\cos \pi + \cos \alpha] \quad ; \quad \cos \pi = -1$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$V_{dc}$  can be varied from a max.

value of  $\frac{2V_m}{\pi}$  to 0 by varying  $\alpha$  from 0 to  $\pi$ .

For  $\alpha = 0$ , The max. dc o/p voltage obtained is

$$V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi}$$

Normalized dc o/p voltage is

$$V_{dcn} = V_n = \frac{V_{dc}}{V_{dn}} = \frac{\frac{V_m}{\pi} (1 + \cos \alpha)}{\left( \frac{2V_m}{\pi} \right)} = \frac{1}{2} (1 + \cos \alpha)$$


# RMS O/P Voltage $V_{O(RMS)}$

$$V_{O(RMS)} = \left[ \frac{2}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$


$$V_{O(RMS)} = \left[ \frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \cdot d(\omega t) \right]^{\frac{1}{2}}$$


$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \left[ \frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{\frac{1}{2}}$$

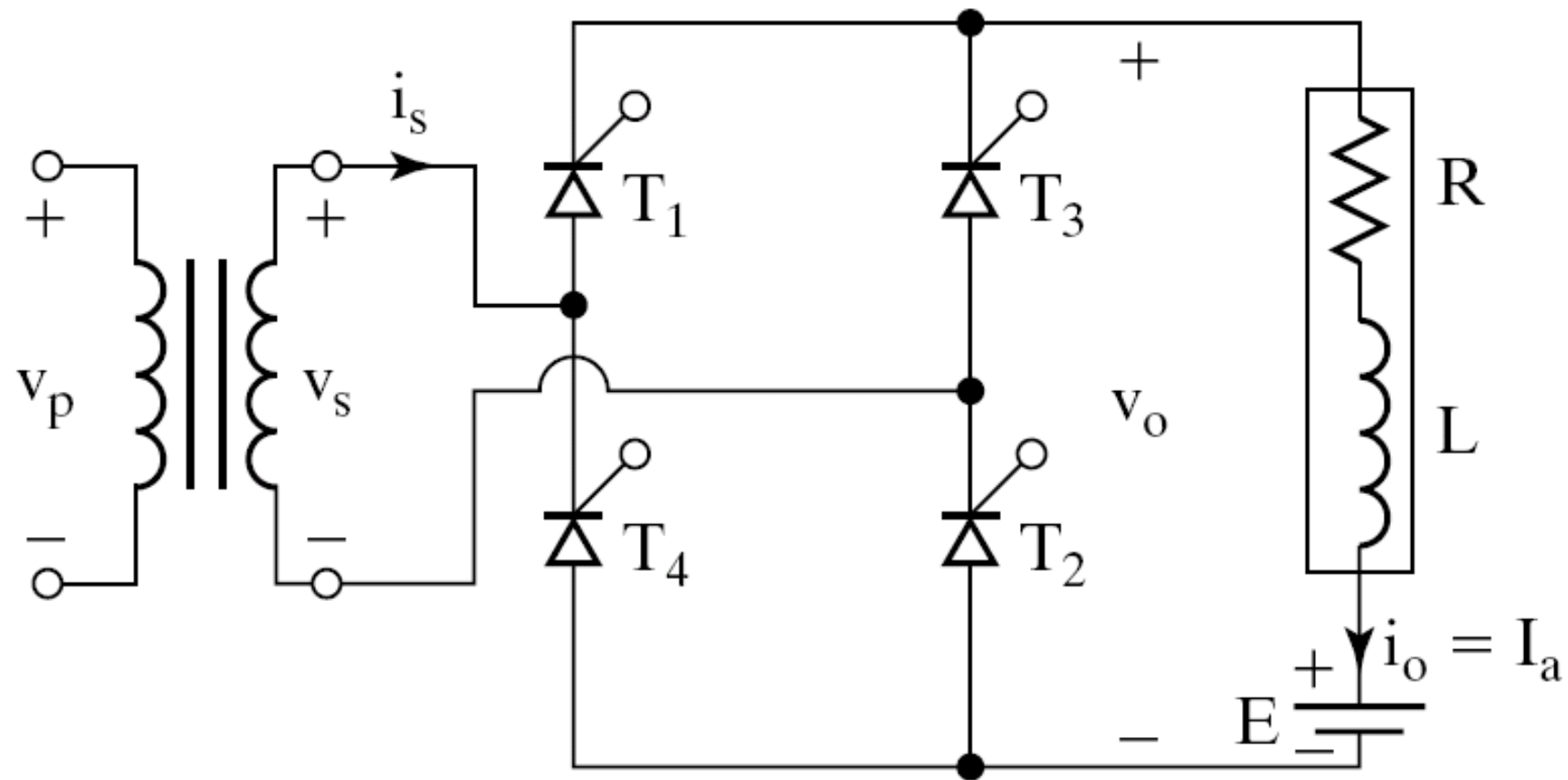Single Phase Full Wave  
Full Converter  
(Fully Controlled Bridge Converter)  
With R,L, & E Load




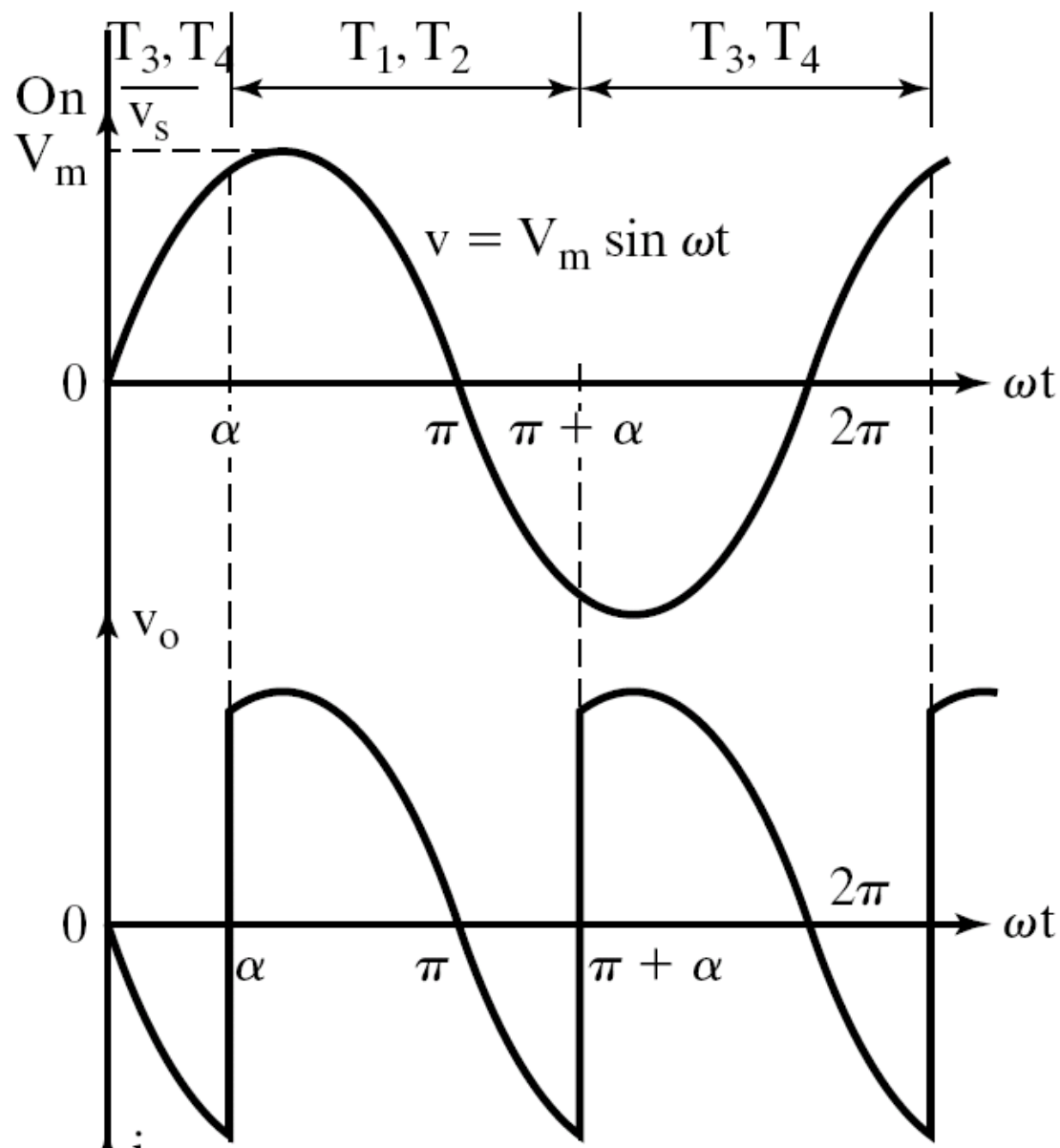Waveforms of  
Single Phase Full Converter  
Assuming Continuous (Constant Load  
Current)  
&  
Ripple Free Load Current



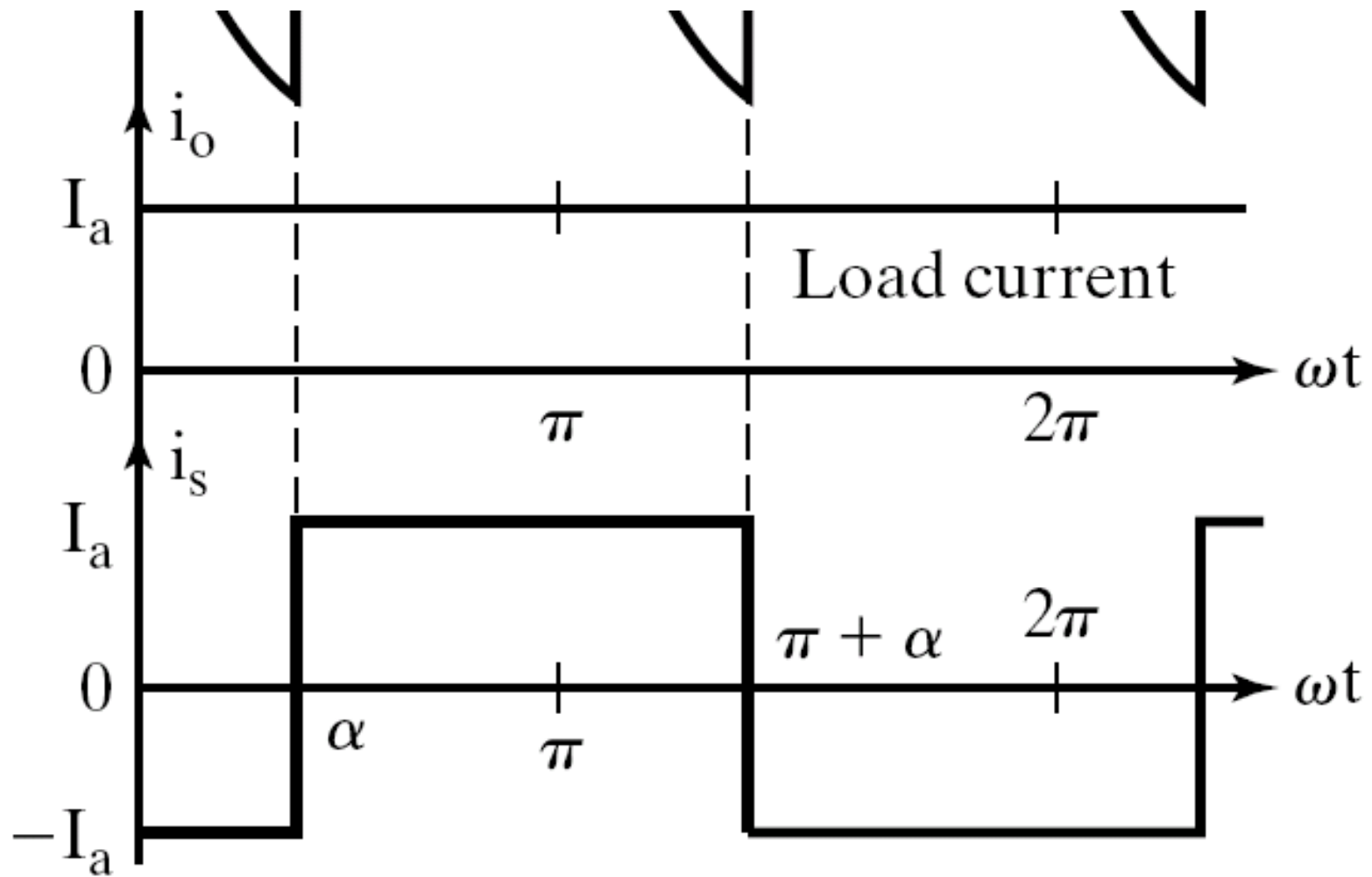



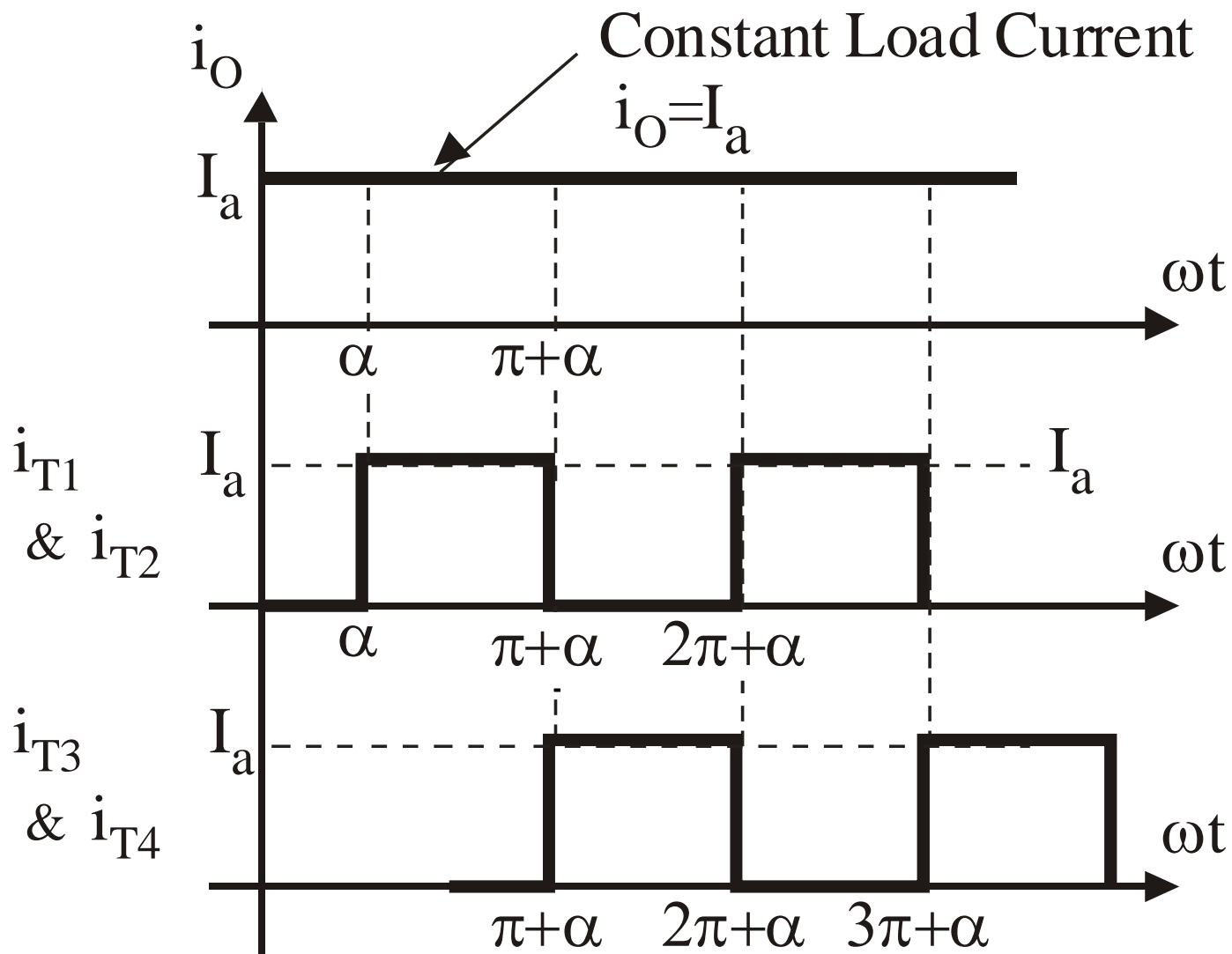

To Derive  
An Expression For  
The Average DC Output Voltage of a Single  
Phase Full Converter  
assuming  
Continuous & Constant Load Current

The average dc output voltage can be determined by using the expression

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \left[ \int_0^{2\pi} v_o \cdot d(\omega t) \right];$$

The o/p voltage waveform consists of two o/p pulses during the input supply time period of 0 to  $2\pi$  radians. Hence the Average or dc o/p voltage can be calculated as

$$V_{O(dc)} = V_{dc} = \frac{2}{2\pi} \left[ \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t . d (\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi+\alpha}$$

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$

Maximum average dc output voltage is calculated for a trigger angle  $\alpha = 0^\circ$  and is obtained as

$$V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi} \times \cos(0) = \frac{2V_m}{\pi}$$

$$\therefore V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi}$$

The normalized average output voltage is given by

$$V_{dcn} = V_n = \frac{V_{O(dc)}}{V_{dc(\max)}} = \frac{V_{dc}}{V_{dm}}$$
$$\therefore V_{dcn} = V_n = \frac{\frac{2V_m}{\pi} \cos \alpha}{\frac{2V_m}{\pi}} = \cos \alpha$$

By plotting  $V_{O(dc)}$  *versus*  $\alpha$ ,  
we obtain the control characteristic of a  
single phase full wave fully controlled bridge  
converter  
(single phase full converter)  
for constant & continuous  
load current operation.

To plot the control characteristic of a Single Phase Full Converter for constant & continuous load current operation.

We use the equation for the average/ dc output voltage

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$



Trigger angle $\alpha$ in degrees	$V_{O(dc)}$	Remarks
0	$V_{dm} = \left( \frac{2V_m}{\pi} \right)$	Maximum dc output voltage $V_{dc(max)} = V_{dm} = \left( \frac{2V_m}{\pi} \right)$
$30^\circ$	$0.866 V_{dm}$	
$60^\circ$	$0.5 V_{dm}$	
$90^\circ$	$0 V_{dm}$	
$120^\circ$	$-0.5 V_{dm}$	
$150^\circ$	$-0.866 V_{dm}$	
$180^\circ$	$-V_{dm} = -\left( \frac{2V_m}{\pi} \right)$	