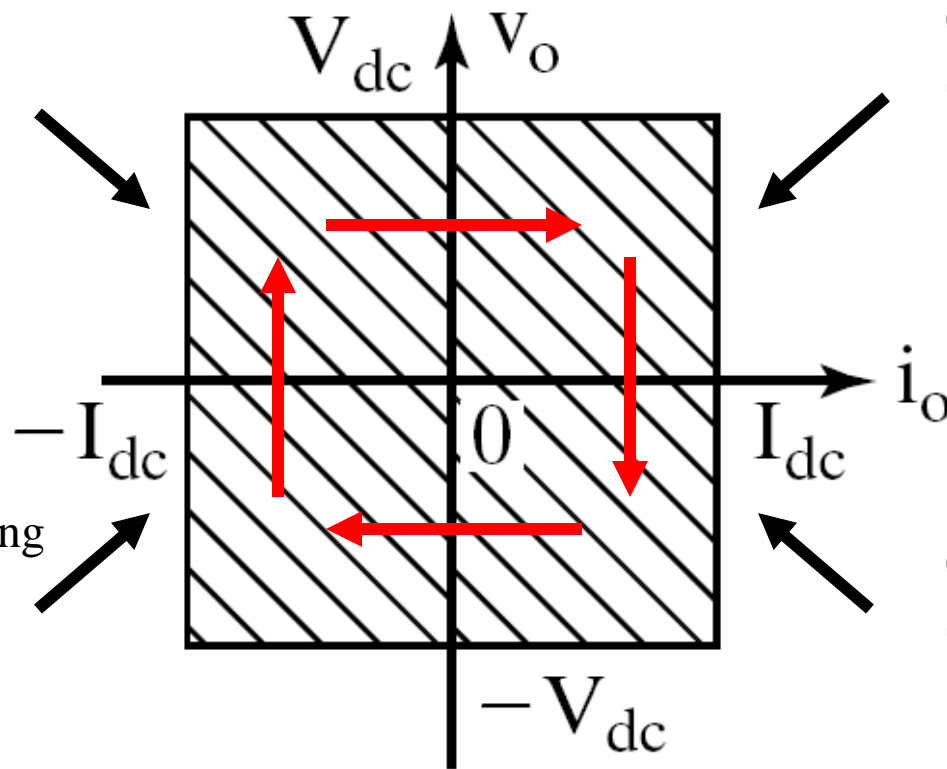


# Four Quadrant Operation

Conv. 2  
Inverting  
 $\alpha_2 > 90^\circ$


Conv. 2 Rectifying  
 $\alpha_2 < 90^\circ$



Conv. 1 Rectifying  
 $\alpha_1 < 90^\circ$

Conv. 1 Inverting  
 $\alpha_1 > 90^\circ$

## 3-Phase Thyristor Converters

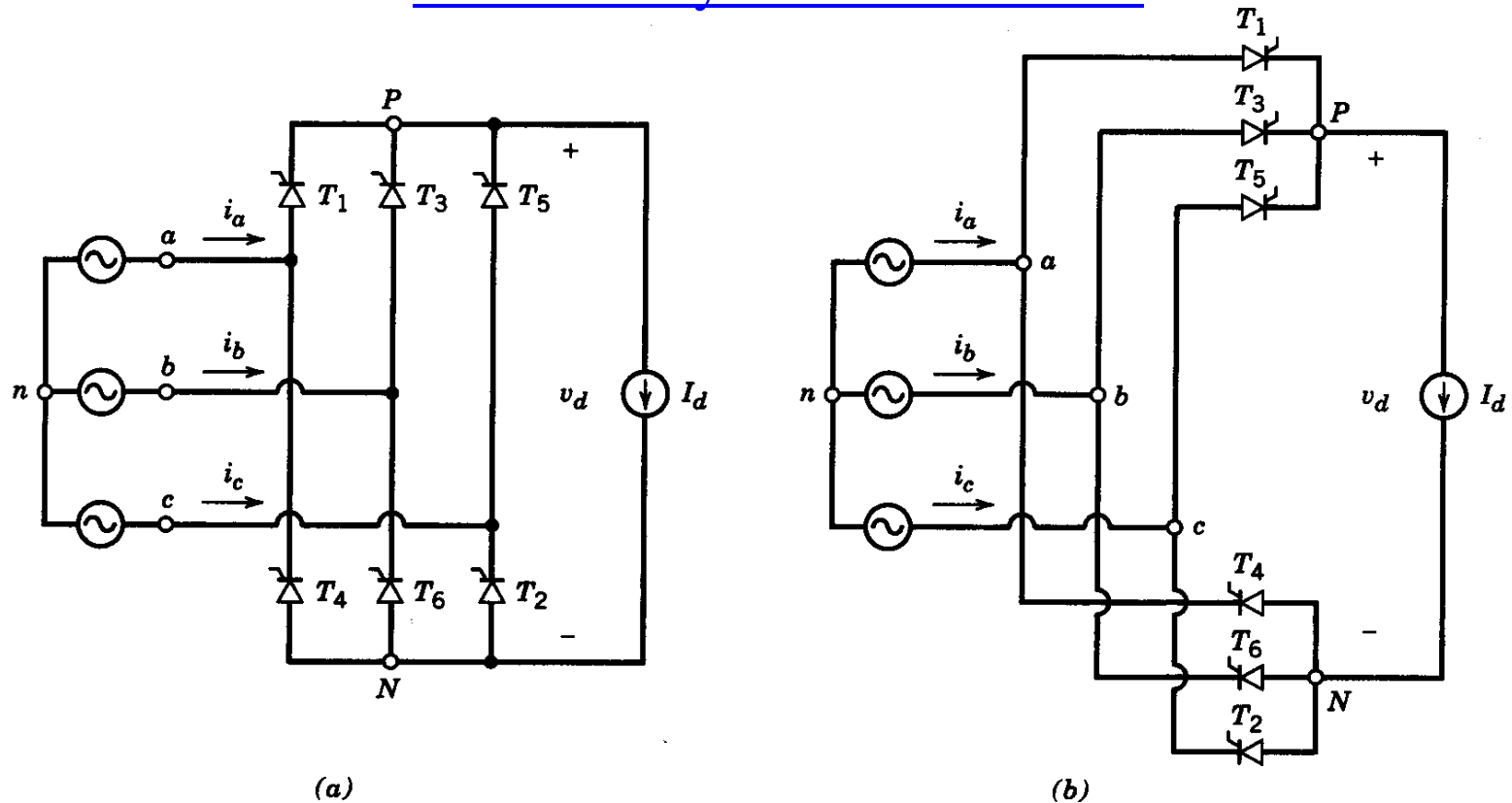


**Figure 6-19** Three-phase thyristor converter with  $L_s = 0$  and a constant dc current.

- Current  $I_d$  flows through the one thyristor of the top group and one of the bottom group
- If a continuous gate pulse is applied then this circuit will act like a three-phase full bridge diode rectifier and, as a result,

$$V_{d0} = 1.35 V_{LL}$$

# 3-Phase Thyristor Converter Waveforms

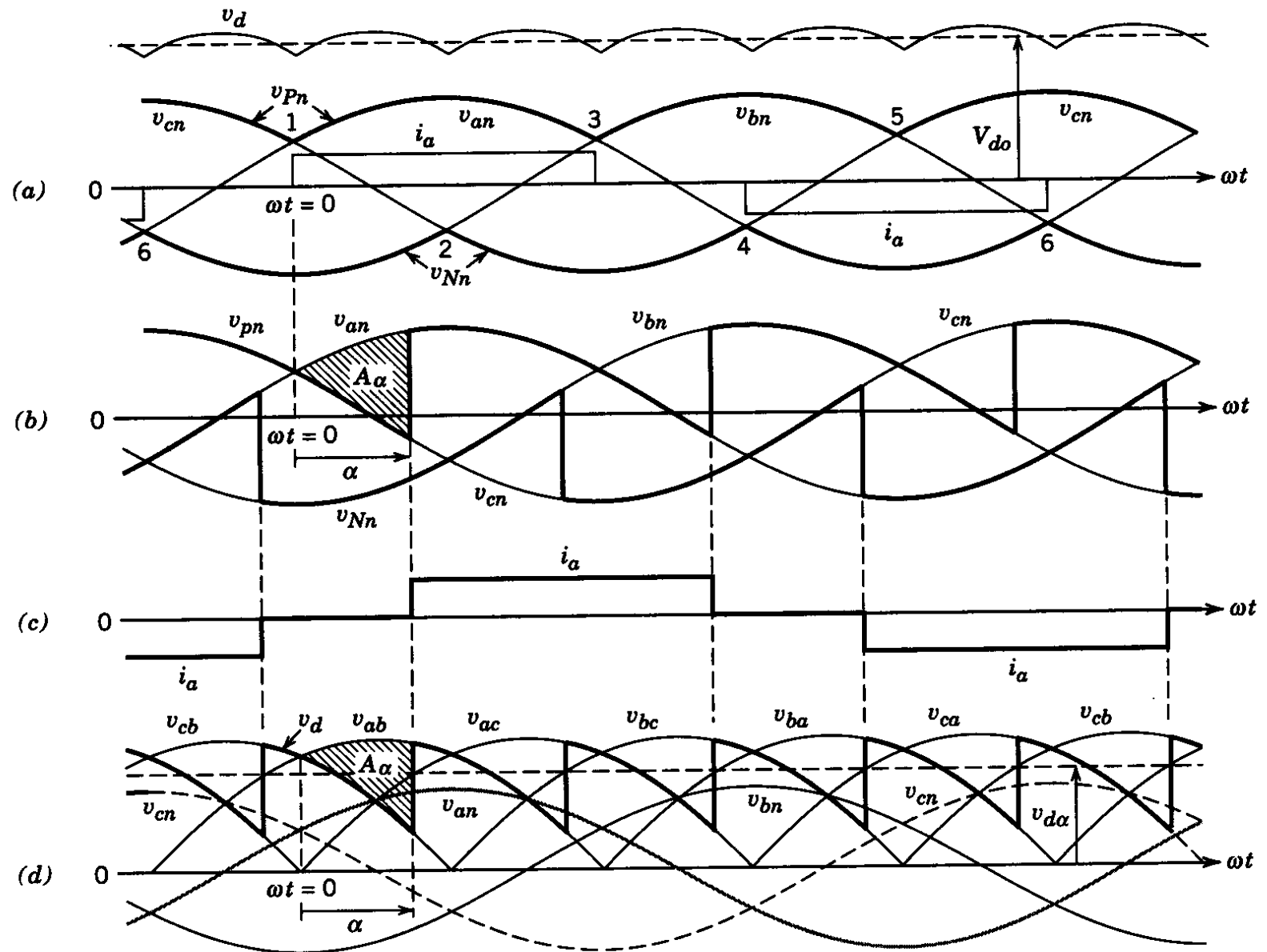

**Figure 6-20** Waveforms in the converter of Fig. 6-19.

## Average Output DC Voltage

$$V_{d\alpha} = V_{d0} - \frac{A_{\mu}}{\pi/3}$$

$$V_{ac} = \sqrt{2}V_{LL} \sin(\omega t)$$

*The reduction in the average dc voltage due to the delay angle  $\alpha$*

$$A_{\mu} = \int_0^{\alpha} \sqrt{2}V_{LL} \sin(\omega t) d(\omega t) = \sqrt{2}V_{LL} (1 - \cos \alpha)$$


$$\begin{aligned} \therefore V_{d\alpha} &= V_{d0} - \frac{A_{\mu}}{\pi/3} = 1.35V_{LL} - \frac{\sqrt{2}V_{LL} (1 - \cos \alpha)}{\pi/3} \\ &= 1.35V_{LL} \cos \alpha = 1.35V_{d0} \end{aligned}$$

*Average Power*

$$P_{d\alpha} = V_{d\alpha} I_d = 1.35V_{LL} I_d \cos \alpha$$

❖ dc-side voltage waveforms as a function of  $\alpha$

❖  $V_d$  repeats at six times the line frequency

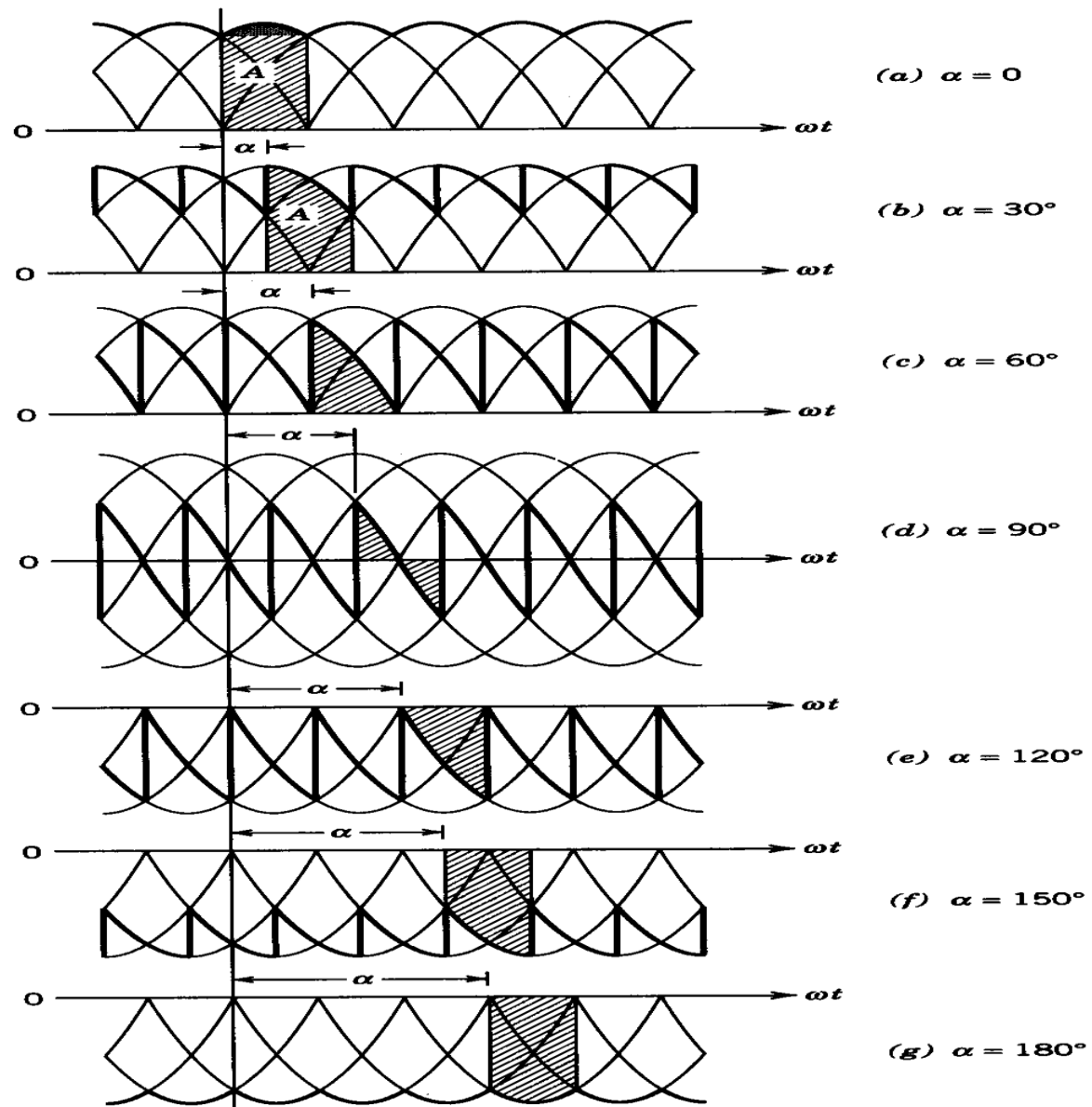

**Figure 6-21** The dc-side voltage waveforms as a function of  $\alpha$  where  $V_{d\alpha} = A/(\pi/3)$ . (From ref. 2 with permission.)

## **Conclusions**

- Thyristor converters provides controlled transfer of power between the line frequency ac and adjustable-magnitude dc
- By controlling  $\alpha$ , transition from rectifier to inverter mode of operation can be made and vice versa
- Thyristor converters are mostly used at high-power levels
- Thyristor converters inject large harmonics into the utility system