
INVERTERS

- Inverters are classified into two basic types by the utilized commutation technique:
 - External Commutation
 - Self Commutation

External commutation inverters are inverters in which the energy required to turn off the SCRs is provided by an external motor or power supply

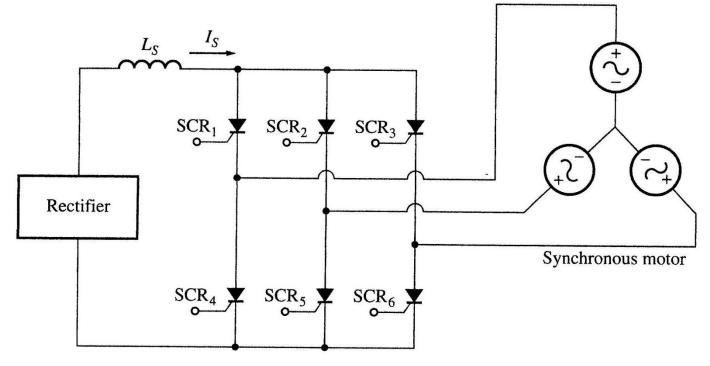An example of an external commutation is shown below



- The inverter is connected to a three-phase synchronous motor, which provides the countervoltage necessary to turn off one SCR when its companion is fired
- The SCRs in this circuit are triggered in the following order:
 - SCR₁, SCR₆, SCR₂, SCR₄, SCR₃, SCR₅

- When SCR₁ fires, the internal generated voltage in the synchronous motor provides the voltage necessary to turn off SCR₃
- Note that if the load is not connected to the inverter, the SCRs would never be tuned off and after ½ cycle a short circuit would develop through SCR₁ and SCR₄
- This inverter is also called a loadcommutated inverter


If it is not possible to guarantee that a load will always provide the proper countervoltage for commutation, then a self-commutation inverter must be used

Self-commutation inverters can be designed using GTOs, IGBTs, or power transistors

- There are three major types of selfcommutation inverters:
 - 1. Current source inverters (SCI)
 - 2. Voltage source inverters (VSI)
 - 3. Pulse-width modulation inverters (PWM)

Pulse-width modulation is the process of modifying the width of the pulses in a pulse train in direct proportion to a small control signal

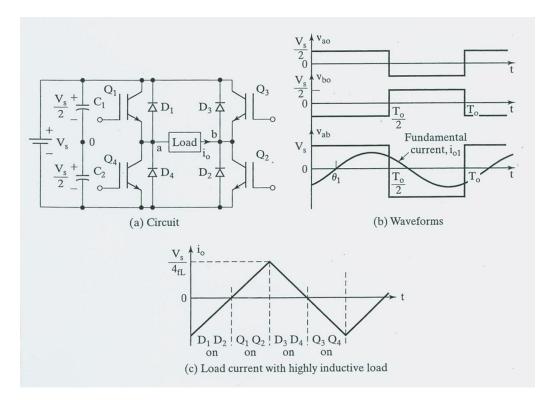 The principle of single-phase inverter operation can be explained with the following figure



The figure shown is a three-phase inverter using power transistors as active devices

