

# D.C. Chopper Drives

A chopper is a static power electronic device that converts fixed dc input voltage to a variable dc output voltage. A Chopper may be considered as dc equivalent of an ac transformer since they behave in an identical manner. As chopper involves one stage conversion, these are more efficient

A chopper is a high speed “on” or “off” semiconductor switch. It connects source to load and load and disconnect the load from source at a fast speed. A constant dc supply of magnitude is given as input voltage and let its output voltage across load be  $V_o$


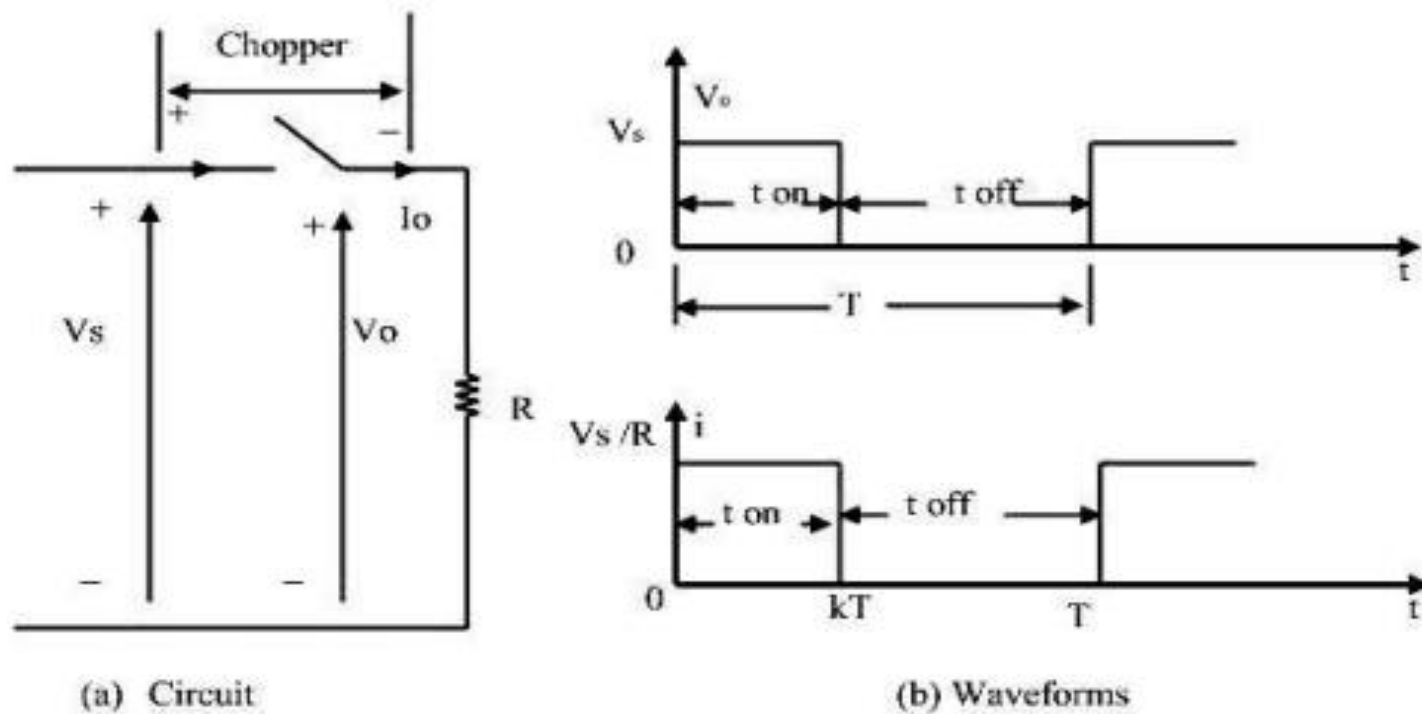


Figure Chopper circuit diagram and its voltage and current waveform

# Chopper fed DC motor Drive

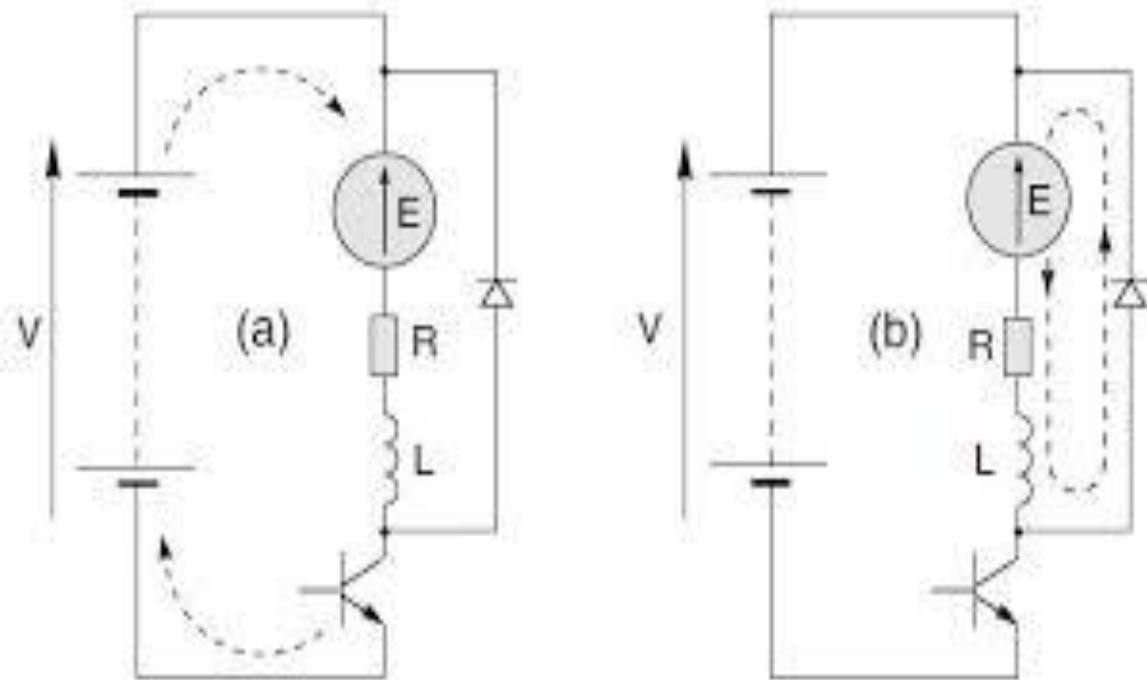

- Chopper fed Dc motor Drives is shown in figure.
- Output voltage of DC chopper can be varied by varying duty cycle of Chopper.
- This varying output voltage is fed to DC motor.
- Speed of DC motor depends upon Voltage across armature.
- So by varying armature voltage of motor using Chopper speed of Dc motor can be controlled.