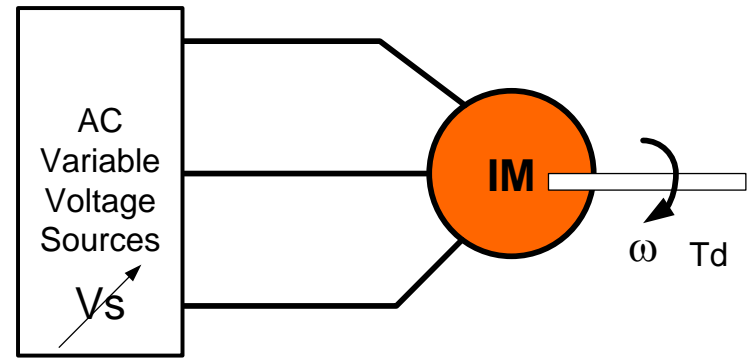


stator



Voltage Control, Variable
Frequency control, Rotor
Resistance Control

Stator Voltage Control

Controlling Induction Motor Speed by
Adjusting The Stator Voltage



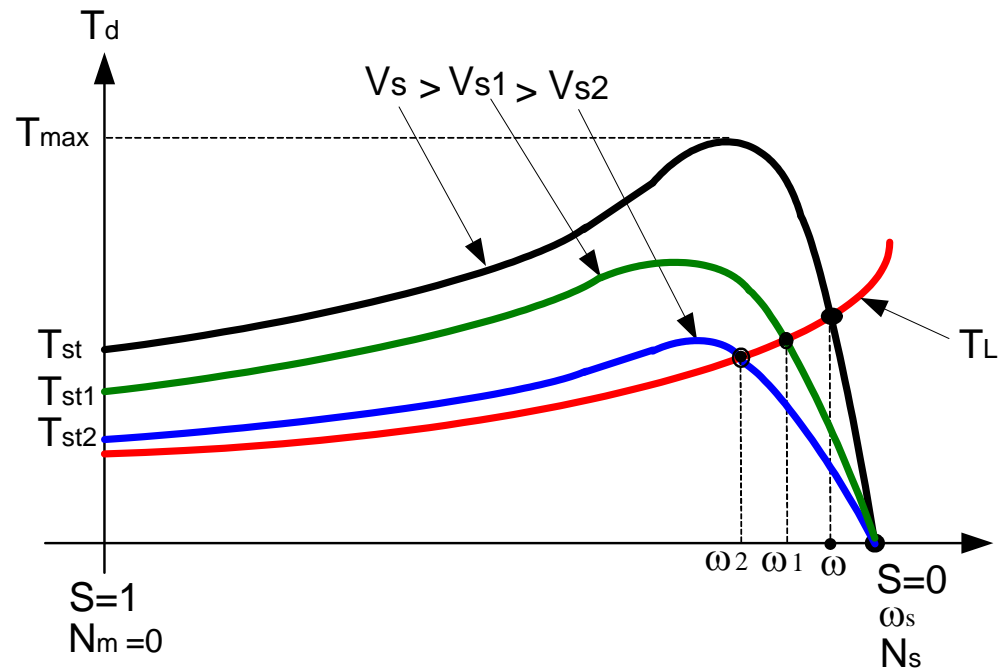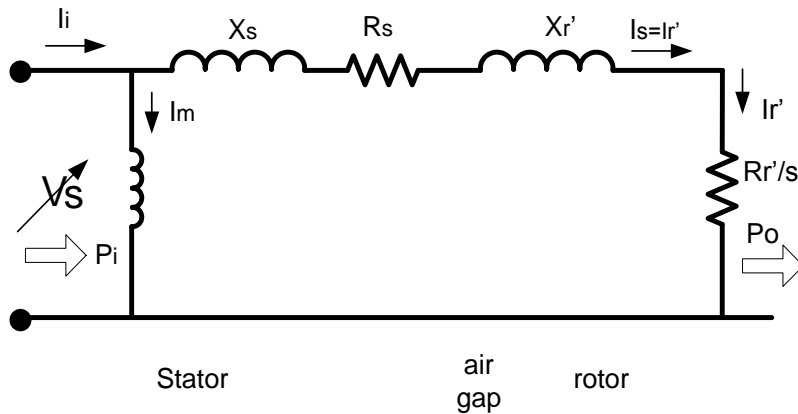
$$T_d = \frac{3 R_r' V_s^2}{S \omega_s \left[\left(R_s + \frac{R_r'}{S} \right)^2 + (X_s + X_r')^2 \right]}$$





Frequency Voltage Control

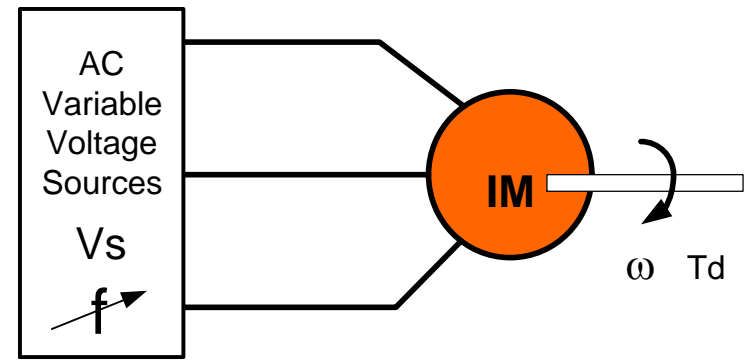Controlling Induction Motor Speed by
Adjusting The Frequency Stator Voltage


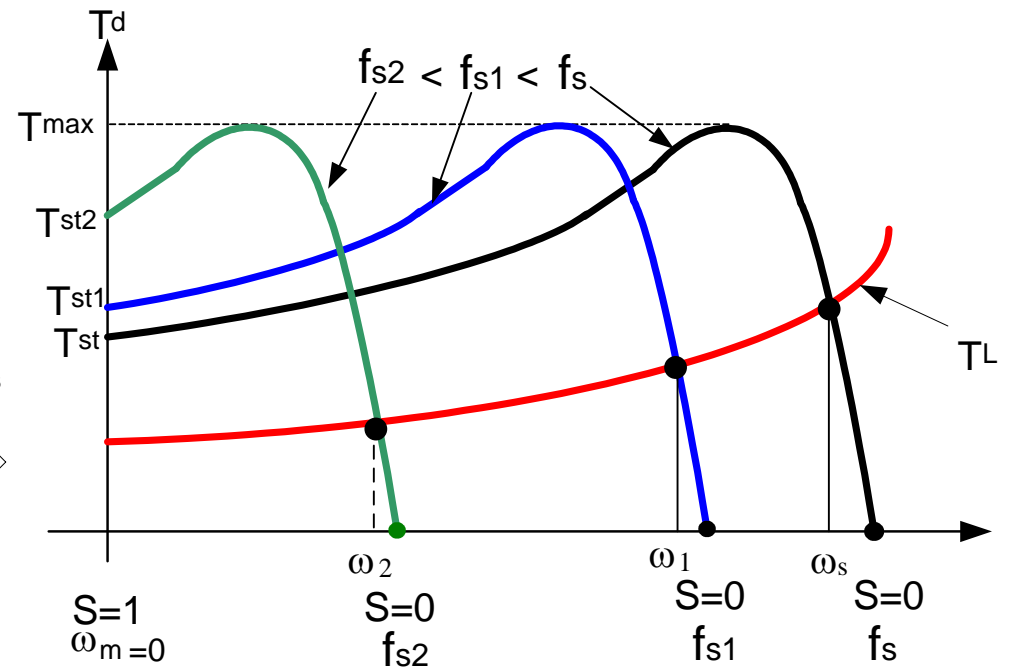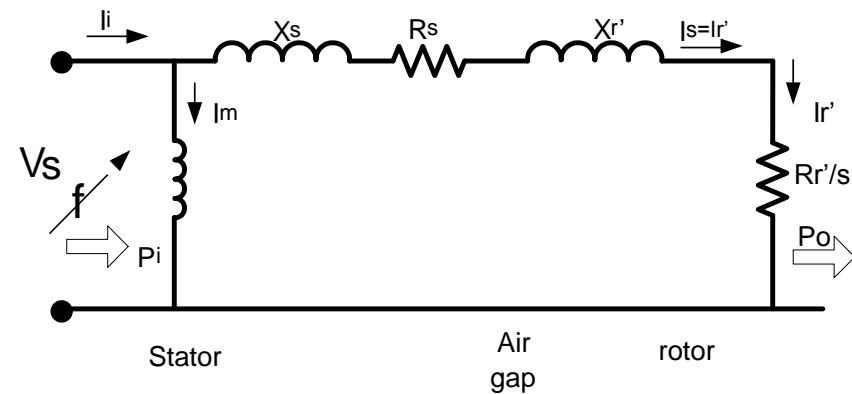
$$T_d = \frac{3 R_r' V_s^2}{S \omega_s \left[\left(R_s + \frac{R_r'}{S} \right)^2 + (X_s + X_r')^2 \right]}$$



If the frequency is increased above its rated value, the flux and torque would decrease. If the synchronous speed corresponding to the rated frequency is call the base speed ω_b , the synchronous speed at any other frequency becomes:

$$\omega_s = \beta \omega_b$$

And :
$$S = \frac{\beta \omega_b - \omega_m}{\beta \omega_b} = 1 - \frac{\omega_m}{\beta \omega_b}$$

The motor torque :

$$T_d = \frac{3 R_r' V_s^2}{S \omega_s \left[\left(R_s + \frac{R_r'}{S} \right)^2 + (X_s + X_r')^2 \right]}$$

$$T_d = \frac{3 R_r' V_s^2}{S \beta \omega_b \left[\left(R_s + \frac{R_r'}{S} \right)^2 + (\beta X_s + \beta X_r')^2 \right]}$$

If R_s is negligible, the maximum torque at the base speed as :

$$T_{mb} = \frac{3 V_s^2}{2S \omega_b (X_s + X_r')}$$

And the maximum torque at any other frequency is :

$$T_m = \frac{3}{2S \omega_b (X_s + X_r')} \frac{V_s^2}{\beta^2}$$

At this maximum torque, slip S is :

$$S_m = \frac{R_r'}{\beta (X_s + X_r')}$$

Normalizing :

$$\frac{T_m = \frac{3}{2S \omega_b (X_s + X_r')} \frac{V_s^2}{\beta^2}}{T_{mb} = \frac{3 V_s^2}{2S \omega_b (X_s + X_r')}} \quad \Rightarrow \quad \boxed{\frac{T_m}{T_{mb}} = \frac{1}{\beta^2}}$$

And

$$T_m \beta^2 = T_{mb}$$

Example :

A three-phase , 11.2 kW, 1750 rpm, 460 V, 60 Hz, four pole, Y-connected induction motor has the following parameters : $R_s = 0.1\Omega$, $R_r' = 0.38\Omega$, $X_s = 1.14\Omega$, $X_r' = 1.71\Omega$, and $X_m = 33.2\Omega$. If the breakdown torque requirement is 35 Nm, Calculate :
a) the frequency of supply voltage, b) speed of motor at the maximum torque

Solution :

Input voltage per-phase : $V_s = \frac{460}{\sqrt{3}} = 265 \text{ volt}$

Base frequency : $\omega_b = 2\pi f = 2 \times 3.14 \times 60 = 377 \text{ rad / s}$

Base Torque : $T_{mb} = \frac{60P_o}{2\pi N_m} = \frac{60 \times 11200}{2 \times 3.14 \times 1750} = 61.11 \text{ Nm}$

Motor Torque : $T_m = 35 \text{ Nm}$

a) the frequency of supply voltage :

$$\boxed{\frac{T_m}{T_{mb}} = \frac{1}{\beta^2}} \Rightarrow \boxed{\beta = \sqrt{\frac{T_{mb}}{T_m}} = \sqrt{\frac{61.11}{35}} = 1.321}$$

Synchronous speed at this frequency is :

$$\omega_s = \beta \omega_b$$

$$\omega_s = 1.321 \times 377 = 498.01 \text{ rad / s} \quad \text{or}$$

$$N_s = \beta N_b = \frac{60 \times 498.01}{2 \times \pi} = 4755.65 \text{ rpm}$$

So, the supply frequency is :

$$f_s = \frac{p N_s}{120} = \frac{4 \times 4755.65}{120} = 158.52 \text{ Hz}$$

b) speed of motor at the maximum torque :

At this maximum torque, slip S_m is :

$$S_m = \frac{R_r'}{\beta(X_s + X_r')}$$

$$R_r' = 0.38 \Omega, X_s = 1.14 \Omega, X_r' = 1.71 \Omega \text{ and } \beta = 1.321$$



So,

$$S_m = \frac{0.38}{1.321(1.14 + 1.71)} = 0.101 \quad \text{or,}$$

$$N_m = N_s (1 - S) = 4755.65 (1 - 0.101) = 4275 \text{ rpm}$$

CONTROLLING INDUCTION MOTOR SPEED USING ROTOR RESISTANCE

(Rotor Voltage Control)

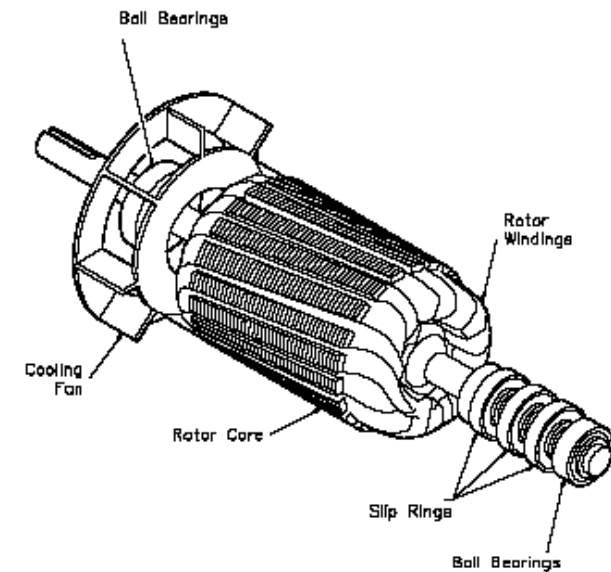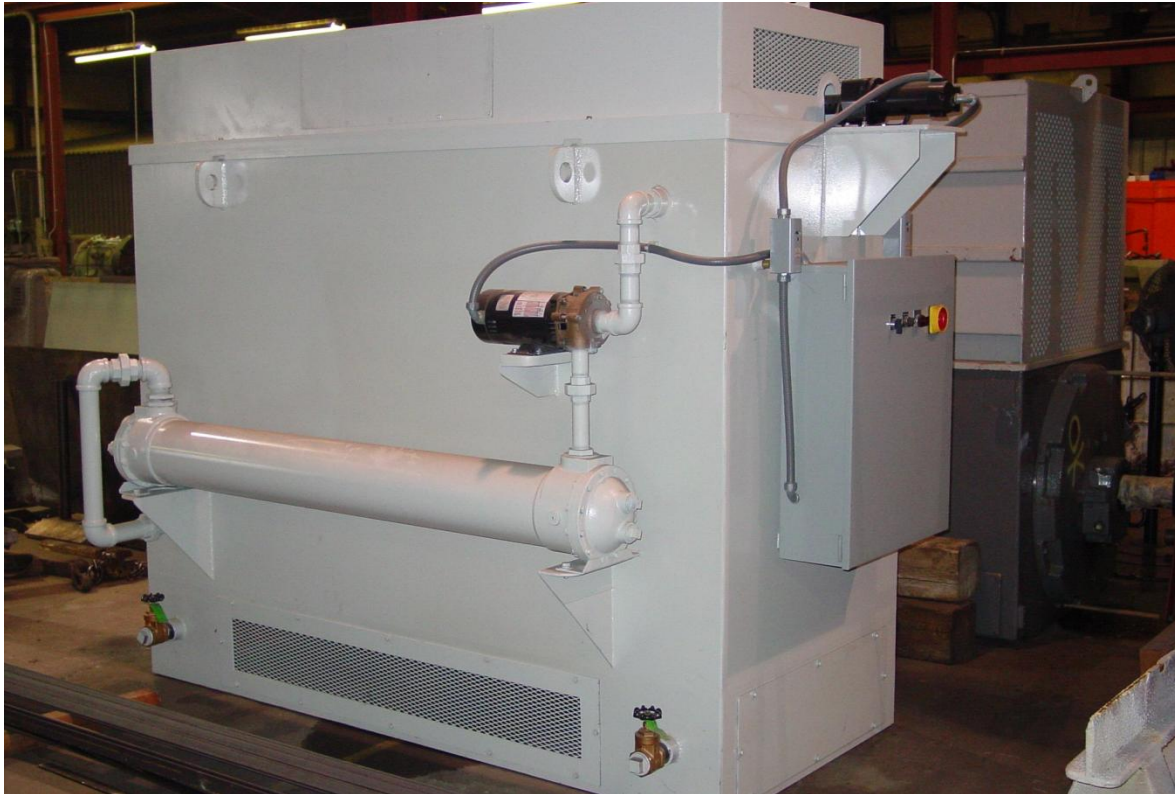

CONTROLLING INDUCTION MOTOR SPEED USING ROTOR RESISTANCE


(Rotor Voltage Control)

Equation of Speed-Torque :

$$T_d = \frac{3 R'_r V_s^2}{S \omega_s \left[\left(R_s + \frac{R'_r}{S} \right)^2 + (X_s + X'_r)^2 \right]}$$

In a wound rotor induction motor, an external three-phase resistor may be connected to its slip rings,
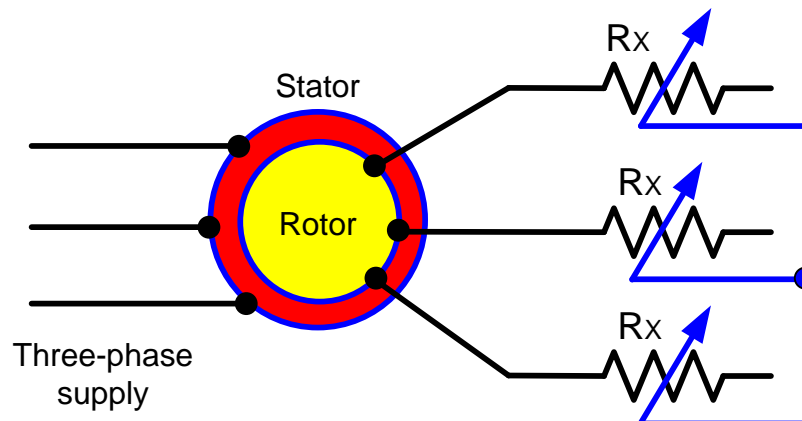
$$T_d = \frac{3 V_s^2 S}{\omega_s R'_r}$$



These resistors Rx are used to control motor starting and stopping anywhere from reduced voltage motors of low horsepower up to large motor applications such as materials handling, mine hoists, cranes etc.

The most common applications are:


AC Wound Rotor Induction Motors – where the resistor is wired into the motor secondary slip rings and provides a soft start as resistance is removed in steps.

AC Squirrel Cage Motors – where the resistor is used as a ballast for soft starting also known as reduced voltage starting.

DC Series Wound Motors – where the current limiting resistor is wired to the field to control motor current, since torque is directly proportional to current, for starting and stopping.

The developed torque may be varying the resistance R_x

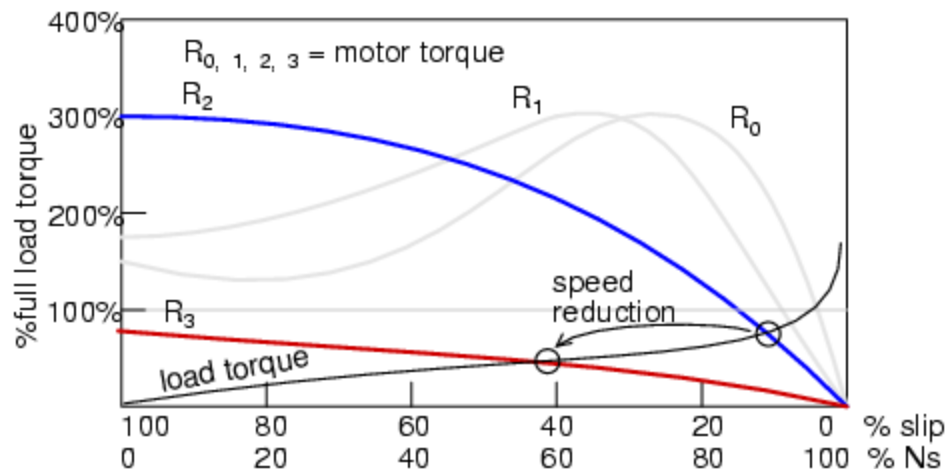The torque-speed characteristic for variations in rotor resistance



This method increases the starting torque while limiting the starting current.


Wound rotor induction motors are widely used in applications requiring frequent starting and braking with large motor torque (crane, hoists, etc).

The three-phase resistor may be replaced by a three-phase diode rectifier and a DC chopper. The inductor L_d acts as a current source I_d and the DC chopper varies the effective resistance:


$$R_e = R(1 - k)$$

Where k is duty cycle of DC chopper

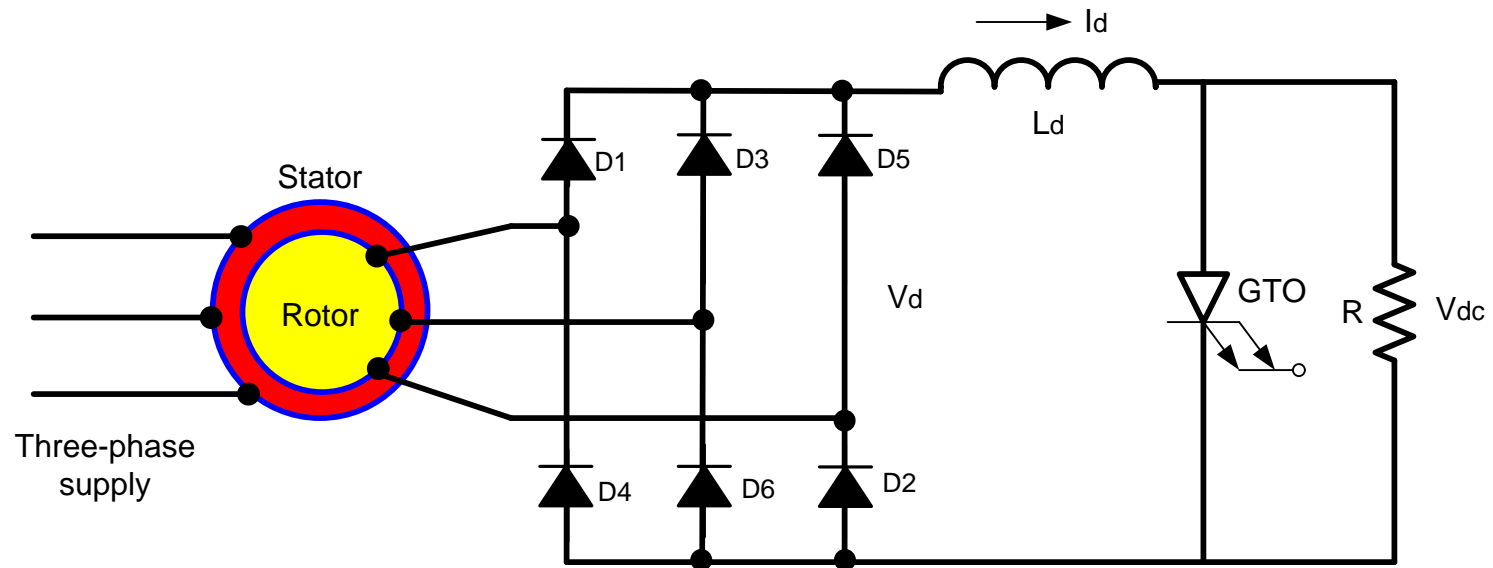The speed can be controlled by varying the duty cycle k , (slip power)



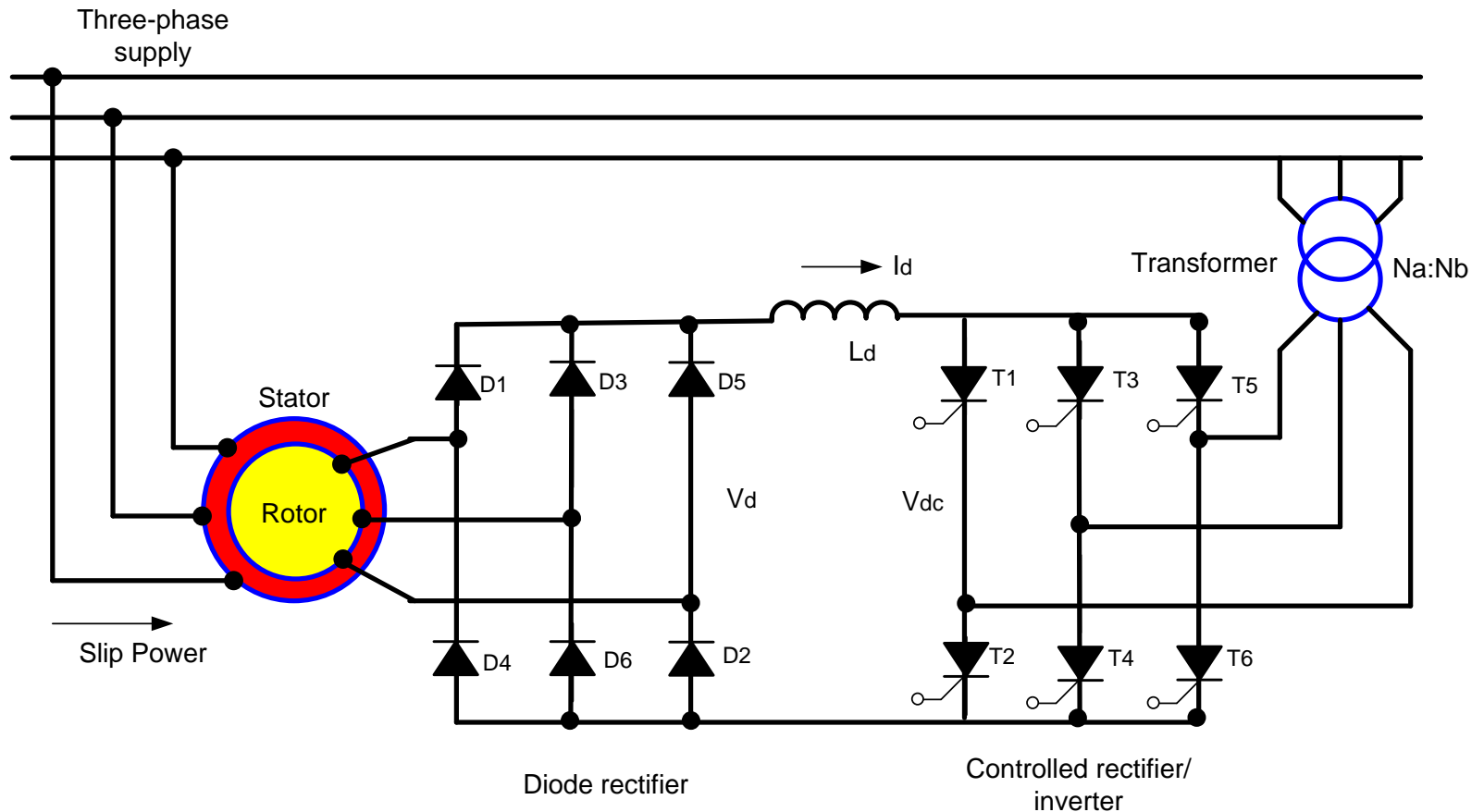The slip power in the rotor circuit may be returned to the supply by replacing the DC converter and resistance R with a three-phase full converter (inverter)



Example:

A three-phase induction motor, 460, 60Hz, six-pole, Y connected, wound rotor that speed is controlled by slip power such as shown in Figure below. The motor parameters are $R_s=0.041\ \Omega$, $R_r'=0.044\ \Omega$, $X_s=0.29\ \Omega$, $X_r'=0.44\ \Omega$ and $X_m=6.1\ \Omega$. The turn ratio of the rotor to stator winding is $n_m=N_r/N_s=0.9$. The inductance L_d is very large and its current I_d has negligible ripple.

The value of R_s , R_r' , X_s and X_r' for equivalent circuit can be considered negligible compared with the effective impedance of L_d . The no-load of motor is negligible. The losses of rectifier and Dc chopper are also negligible.

The load torque, which is proportional to speed square is 750 Nm at 1175 rpm.

- (a) If the motor has to operate with a minimum speed of 800 rpm, determine the resistance R , if the desired speed is 1050 rpm,
- (b) Calculate the inductor current I_d .
- (c) The duty cycle k of the DC chopper.
- (d) The voltage V_d .
- (e) The efficiency.
- (f) The power factor of input line of the motor.

$$V_s = \frac{460}{\sqrt{3}} = 265.58 \text{ volt}$$

$$p = 6$$

$$\omega = 2\pi \times 60 = 377 \text{ rad / s}$$

$$\omega_s = 2 \times 377 / 6 = 125.66 \text{ rad / s}$$

The equivalent circuit :

The dc voltage at the rectifier output is :

$$V_d = I_d R_e = I_d R (1 - k)$$

and

$$E_r = S V_s \frac{N_r}{N_s} = S V_s n_m$$

For a three-phase rectifier, relates E_r and V_d as :

$$V_d = 1.65 \times \sqrt{2} E_r = 2.3394 E_r$$

Using : $E_r = S V_s \frac{N_r}{N_s} = S V_s n_m$

$$V_d = 2.3394 S V_s n_m$$

If P_r is the slip power, air gap power is : $P_g = \frac{P_r}{S}$

Developed power is : $P_d = 3(P_g - P_r) = 3\left(\frac{P_r}{S} - P_r\right) = \frac{3P_r(1 - S)}{S}$

Because the total slip power is $3P_r = V_d I_d$ and $P_d = T_L \omega_m$

So,
$$P_d = \frac{(1-S)V_d I_d}{S} = T_L \omega_m = T_L \omega_m (1-S)$$

Substituting V_d from $V_d = 2.3394 S V_s n_m$ In equation P_d above, so :

Solving for I_d gives :

$$I_d = \frac{T_L \omega_s}{2.3394 V_s n_m}$$

Which indicates that the inductor current is independent of the speed.

From equation : $V_d = I_d R_e = I_d R(1-k)$ and equation : $V_d = 2.3394 S V_s n_m$

So,
$$I_d R(1-k) = 2.3394 S V_s n_m$$

Which gives :
$$S = \frac{I_d R(1-k)}{2.3394 S V_s n_m}$$

The speed can be found from equation : $S = \frac{I_d R(1-k)}{2.3394 S V_s n_m}$ as :

$$\omega_m = \omega_s (1-S) = \omega_s \left[1 - \frac{I_d R(1-k)}{2.3394 V_s n_m} \right]$$

$$\omega_m = \omega_s \left[1 - \frac{T_L \omega_s R(1-k)}{(2.3394 V_s n_m)^2} \right]$$

Which shows that for a fixed duty cycle, the speed decrease with load torque. By varying k from 0 to 1, the speed can be varied from minimum value to ω_s

$$\omega_m = 180 \pi / 30 = 83.77 \text{ rad} / s$$

From torque equation : $T_L = K_v \omega_m^2$

$$= 750 x \left(\frac{800}{1175} \right)^2 = 347.67 \text{ Nm}$$

From equation : $I_d = \frac{T_L \omega_s}{2.3394 V_s n_m}$ The corresponding inductor current is :

$$I_d = \frac{347.67 \times 125.66}{2.3394 \times 265.58 \times 0.9} = 78.13 \text{ A}$$

The speed is minimum when the duty-cycle k is zero and equation :

$$\omega_m = \omega_s (1 - S) = \omega_s \left[1 - \frac{I_d R (1 - k)}{2.3394 V_s n_m} \right]$$

$$83.77 = 125.66 \left(1 - \frac{78.13 R}{2.3394 \times 265.58 \times 0.9} \right)$$

And : $R = 2.3856 \Omega$