

ELECTRICAL MEASUREMENT & MEASURING INSTRUMENTS

UNIT 3

Measurement of Parameters


MEASUREMENT OF MEDIUM RESISTANCES

Volt-Ampere Method

- Here an ammeter and a voltmeter are used respectively in series and in parallel with the resistor under measurement.
- Resistances are obtained for each trial as per ohmic-principle, using equation $R = V/I$.
- The average value of all the trails will give the measured value of resistance.
- This method is also referred as the potential drop method or VA method.
- Here, the meter ranges are to be chosen carefully based on the circuit conditions and the resistance value to be obtained.
- This method suffers from the ***connection errors***.


Wheatstone's bridge

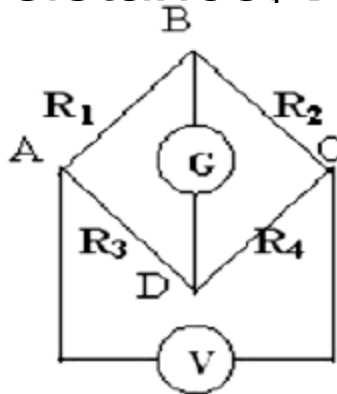- The bridge is said to be balanced when the galvanometer current is
- Solving further, we get, $R_1/R_2 = R_3/ R_4$ and **$R_1R_4 = R_2R_3$**
- ***This is the balance equation of the bridge.***
- Thus, unknown resistance, **$R_3 = R_1R_4/ R_2$**
ohms.zero.




MEASUREMENT OF LOW RESISTANCES

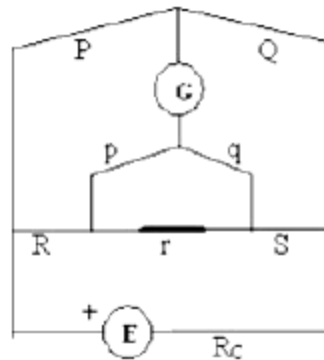
- **Kelvin's Double Bridge**
- Kelvin's Double Bridge (KDB) is the most widely used method



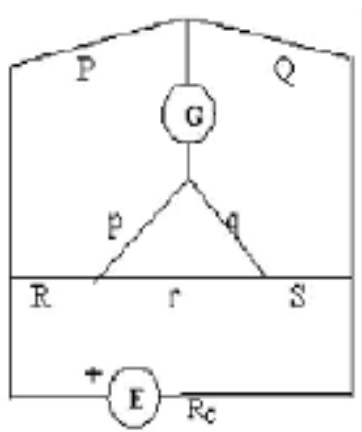
- The balance equation of KDB can be derived as under. Using star-delta conversion principle, the KDB circuit
- $P(S+r_3) = Q(R+r_2)$



(a)

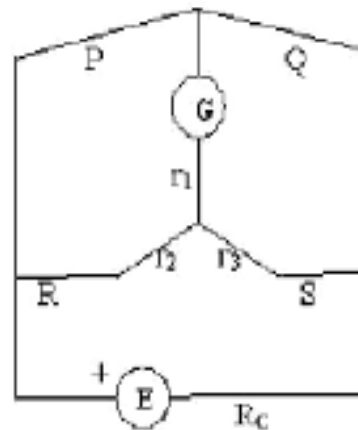

(b)

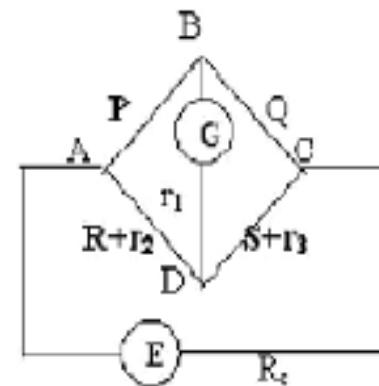

(c)