

ELECTRICAL MEASUREMENT & MEASURING INSTRUMENTS

UNIT 3


Measurement of Parameters

MEASUREMENT OF HIGH RESISTANCES

- Very high resistances of the order of mega-ohms can be measured by using an instrument called MEGGER, also called as the insulation resistance tester.
- It is used as a high resistance measuring meter as also a tester for testing the earth resistances.

Measurement Of Inductance & Capacitance With The Help Of AC Bridges

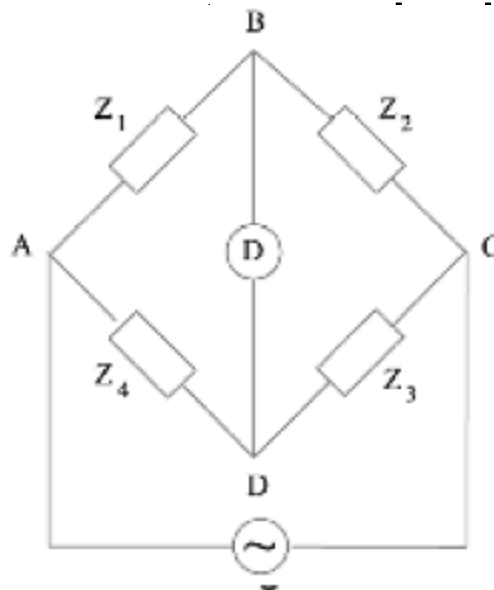- Alternating Current bridges are widely used for measurement of inductance, capacitance, storage factor, loss factor etc.
- A.C bridge circuits also find application in providing phase shift, feedback paths for oscillators and amplifiers, filter circuits, etc. measuring frequency, etc.



- **Balancing Condition**

$$Z_1 / Z_2 = Z_4 / Z_3 \quad \text{or} \quad Z_1 Z_3 = Z_2 Z_4$$

$$Z_1 \angle \phi_1 \cdot Z_3 \angle \phi_3 = Z_2 \angle \phi_2 \cdot Z_4 \angle \phi_4 \quad \text{or} \quad Z_1 Z_3 \angle \phi_1 + \phi_3 = Z_2 Z_4 \angle \phi_2 + \phi_4$$

$$Z_1 Z_3 = Z_2 Z_4$$


$$\phi_1 + \phi_3 = \phi_2 + \phi_4$$


... for magnitude balance

... for phase angle balance

Maxwell Bridge

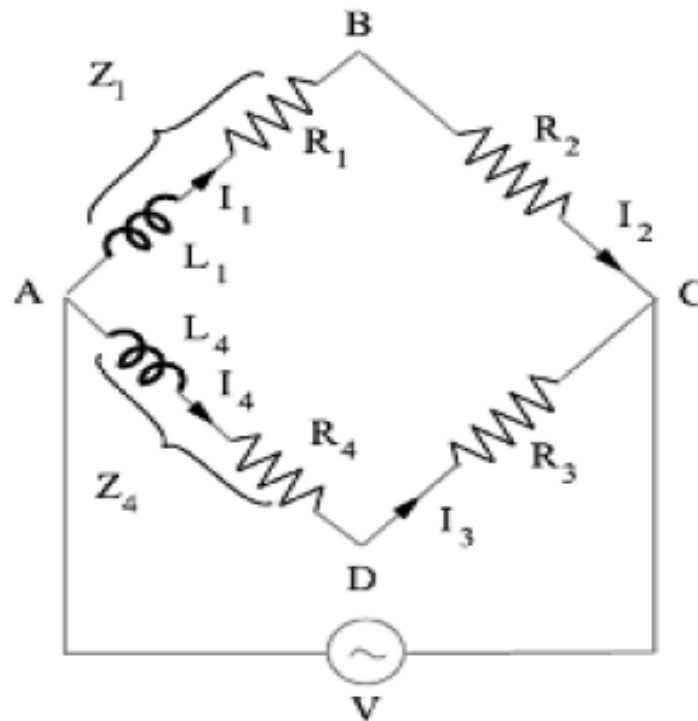- The Maxwell bridge measures an unknown inductance in terms of a known capacitance.
- The maxwell bridge is limited to the measurement of medium- Q coils ($1 < Q < 10$).



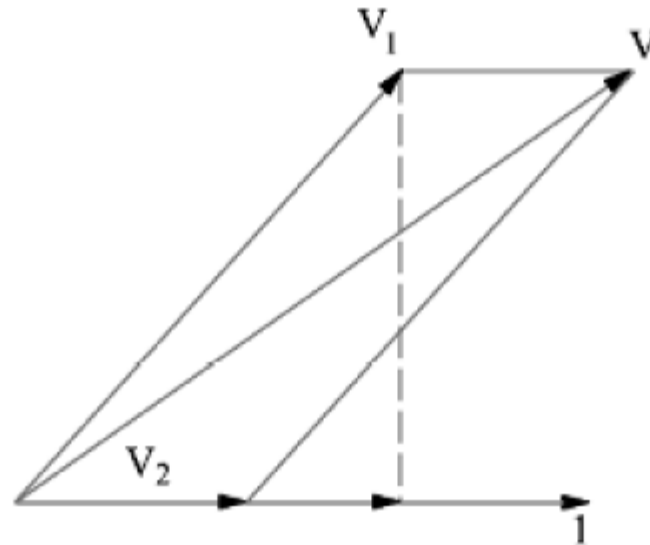

$$I_2 R_2 = I_3 R_3 ; I_1 R_1 = I_4 R_4$$

The balance condition is that $Z_1 Z_3 = Z_2 Z_4$

$$\therefore (R_1 + j\omega L_1)R_3 = (R_4 + j\omega L_4)R_2$$

Equating the real and imaginary parts on both sides, we have

$$R_1 R_3 = R_2 R_4 \text{ or } R_1 / R_4 = R_2 / R_3 *$$

(i.e. products of the resistances of opposite arms are equal).

$$\text{and } \omega L_1 R_3 = \omega L_4 R_2 \text{ or } L_1 = L_4 \frac{R_2}{R_3}$$